

Maximum Power Transfer

Occurs when $R_{th} = R_L$: $P_{L \max} = \frac{V_s^2}{4R_L}$

Inductors

$$V_L(t) = L \frac{di_L(t)}{dt} = L \cdot i_L'(t) \quad i_L(t) = \frac{1}{L} \int_{-\infty}^t V_L(t) dt = i_L(t_0) + \frac{1}{L} \int_{t_0}^t V_L(t) dt \quad W_L(t) = \frac{L}{2} i_L^2(t)$$

Capacitors

$$i_c(t) = C \frac{dV_c(t)}{dt} = CV_c'(t) \quad V_c(t) = \frac{1}{C} \int_{-\infty}^t i_c(t) dt = V_c(t_0) + \frac{1}{C} \int_{t_0}^t i_c(t) dt \quad W_c(t) = \frac{C}{2} V_c^2(t)$$

First Order Circuits

$$x(t) = x(\infty) + [x(0) - x(\infty)] e^{\frac{t-t_0}{-\tau}}$$

Second Order Circuits

$$\omega = \frac{1}{\sqrt{LC}}$$