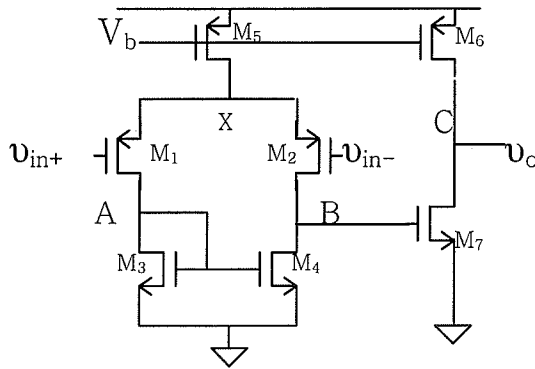


1. [25 points] Consider the differential input / single-ended output amplifier shown below. Assume the signal source has zero source impedance, node X is analog ground, and $C_{gd}=0$ for all transistors. Assume all transistors have finite r_o . Assume $M1=M2$, $M3=M4$, and $M5=M6$.



and $r_o \gg \frac{1}{g_m}$
assume

- (a) [6 points] Derive the expression for the low frequency gain $[V_o/V_{in} = V_o/(V_{in+} - V_{in-})]$.

~~$$\frac{V_o}{V_{in+}} = -g_{m1}(r_{o2} \parallel r_{o4}) g_{m7}(r_{o6} \parallel r_{o7})$$

$$\frac{V_o}{V_{in-}} = g_{m2}(r_{o2} \parallel r_{o4}) g_{m7}(r_{o6} \parallel r_{o7})$$

$$V_o \left(\frac{1}{2V_{in+}} + \frac{1}{2V_{in-}} \right) = -2g_{m1}(r_{o2} \parallel r_{o4}) g_{m7}(r_{o6} \parallel r_{o7})$$

$$V_o \left(\frac{1}{2V_{in}} + \frac{1}{2V_{in}} \right) = \frac{V_o}{V_{in}} 4$$~~

$$i_o = +g_{m1} V_{in+} + g_{m2} V_{in-}$$

$$= +g_{m1} \frac{1}{2} V_{in} + g_{m1} \frac{1}{2} V_{in} = +g_{m1} V_{in}$$

$$V_{oB} = +g_{m1} V_{in} (r_{o2} \parallel r_{o4}) = \underline{i_o (r_{o2} \parallel r_{o4})}$$

$$A_{v1} = g_{m1} (r_{o2} \parallel r_{o4})$$

$$A_{v2} = -g_{m7} (r_{o6} \parallel r_{o7})$$

- (b) [6 points] Derive the expression for the positive-input to the output transfer function, $H_1(s) = V_o/V_{in+}$. [Note: The low frequency gain is slightly different from the one in (a). Include C_{gs} , C_{db} , and C_{sb} in pole analysis. Find "POLES", but you don't need to find zero.]

$$I_o = g_{m1} V_{int} = \frac{1}{2} g_{m1} V_{in}$$

$$V_{oB} = \frac{1}{2} g_{m1} (r_{o2} \parallel r_{o4}) V_{in}$$

$$A_{v1} = \frac{1}{2} g_{m1} (r_{o2} \parallel r_{o4})$$

$$A_{v2} = -g_{m7} (r_{o6} \parallel r_{o8})$$

$$A_{v4} = -\frac{1}{2} g_{m1} (r_{o2} \parallel r_{o4}) g_{m7} (r_{o6} \parallel r_{o8})$$

$$\omega_{pA} = \frac{1}{(\cancel{C_{gd1}} + C_{db1} + C_{db3} + C_{gs3} + C_{gs4}) \left(\frac{1}{g_{m3}}\right)}$$

$$\omega_{pB} = \frac{1}{(C_{db2} + C_{db4} + C_{gs7}) (r_{o2} \parallel r_{o4})}$$

$$\omega_{pC} = \frac{1}{(C_{db6} + C_{db4}) (r_{o6} \parallel r_{o8})}$$

$$H_1(s) = \frac{A_{v4}}{\left(1 + \frac{s}{\omega_{pA}}\right) \left(1 + \frac{s}{\omega_{pB}}\right) \left(1 + \frac{s}{\omega_{pC}}\right)}$$

- (c) [6 points] Derive the expression for the negative-input to the output transfer function, $H_2(s) = v_o/v_{in-}$. [Note: The low frequency gain is slightly different from the one in (a). Include C_{gs} , C_{db} , and C_{sb} in pole analysis. Find "POLES", but you don't need to find zero.]

$$A_{v2} = + \frac{1}{2} g_{m2} (r_{o2} \parallel r_{o4}) g_{m7} (r_{o6} \parallel r_{o8}) = - A_{v1}$$

$$H_2(s) = \frac{A_{v2}}{\left(1 + \frac{s}{\omega_{pb}}\right) \left(1 + \frac{s}{\omega_{pc}}\right)}$$

- (d) [7 points] Using $H_1(s)$ and $H_2(s)$, calculate the differential input to single-ended output transfer function, $H(s) = \mathbf{V}_o / \mathbf{V}_{in}(s) = \mathbf{V}_o / (\mathbf{V}_{in+} - \mathbf{V}_{in-})(s)$ [Note: $\mathbf{V}_{in+} = 0.5\mathbf{V}_{in}$, $\mathbf{V}_{in-} = -0.5\mathbf{V}_{in}$] [Hint: Although $H_1(s)$ and $H_2(s)$ do not have zero, $H(s)$ could have zero.]

$$\begin{aligned}
 H(s) &= \frac{A_1}{(1 + \frac{s}{\omega_{PA}})(1 + \frac{s}{\omega_{PB}})(1 + \frac{s}{\omega_{PC}})} + \frac{A_2}{(1 + \frac{s}{\omega_{PB}})(1 + \frac{s}{\omega_{PC}})} \\
 &= \frac{A_1 \left(\frac{s}{\omega_{PB}} + \frac{s}{\omega_{PC}} \right) + A_2 \left(1 + \frac{s}{\omega_{PA}} \right)}{\left(1 + \frac{s}{\omega_{PA}} \right) \left(1 + \frac{s}{\omega_{PB}} \right) \left(1 + \frac{s}{\omega_{PC}} \right)} \\
 &= \frac{A_1 \frac{s}{\omega_{PB}} + A_1 \frac{s}{\omega_{PC}} + A_2 \left(1 + \frac{s}{\omega_{PA}} \right)}{\left(1 + \frac{s}{\omega_{PA}} \right) \left(1 + \frac{s}{\omega_{PB}} \right) \left(1 + \frac{s}{\omega_{PC}} \right)} \\
 &= \frac{A_1 \frac{s}{\omega_{PB}} + A_1 \frac{s}{\omega_{PC}} + A_2 + A_2 \frac{s}{\omega_{PA}}}{\left(1 + \frac{s}{\omega_{PA}} \right) \left(1 + \frac{s}{\omega_{PB}} \right) \left(1 + \frac{s}{\omega_{PC}} \right)} \\
 &= \frac{A_1 \frac{s}{\omega_{PB}} + A_1 \frac{s}{\omega_{PC}} + A_2 + A_2 \frac{s}{\omega_{PA}}}{\left(1 + \frac{s}{\omega_{PA}} \right) \left(1 + \frac{s}{\omega_{PB}} \right) \left(1 + \frac{s}{\omega_{PC}} \right)} \\
 \end{aligned}$$

$$\begin{aligned}
 \mathbf{V}_{o1} &= H_1(s) \mathbf{V}_{in+} = H_1(s) \frac{\mathbf{V}_{in}}{2} \\
 \mathbf{V}_{o2} &= H_2(s) \mathbf{V}_{in-} = H_2(s) \left(-\frac{\mathbf{V}_{in}}{2} \right)
 \end{aligned}$$


$$\mathbf{V}_o = \frac{\mathbf{V}_{in}}{2} [H_1(s) - H_2(s)]$$

$$= \frac{\mathbf{V}_{in}}{2} \left[\frac{A_1}{\left(1 + \frac{s}{\omega_{PA}} \right) \left(1 + \frac{s}{\omega_{PB}} \right) \left(1 + \frac{s}{\omega_{PC}} \right)} - \frac{-A_1}{\left(1 + \frac{s}{\omega_{PB}} \right) \left(1 + \frac{s}{\omega_{PC}} \right)} \right]$$

$$= \frac{\mathbf{V}_{in}}{2} A_1 \left[\frac{1 + 1 + \frac{s}{\omega_{PA}}}{\left(1 + \frac{s}{\omega_{PA}} \right) \left(1 + \frac{s}{\omega_{PB}} \right) \left(1 + \frac{s}{\omega_{PC}} \right)} \right]$$

$$\frac{\mathbf{V}_o}{\mathbf{V}_{in}} = \frac{A_1}{2} \left[\frac{2 + \frac{s}{\omega_{PA}}}{\left(1 + \frac{s}{\omega_{PA}} \right) \left(1 + \frac{s}{\omega_{PB}} \right) \left(1 + \frac{s}{\omega_{PC}} \right)} \right]$$

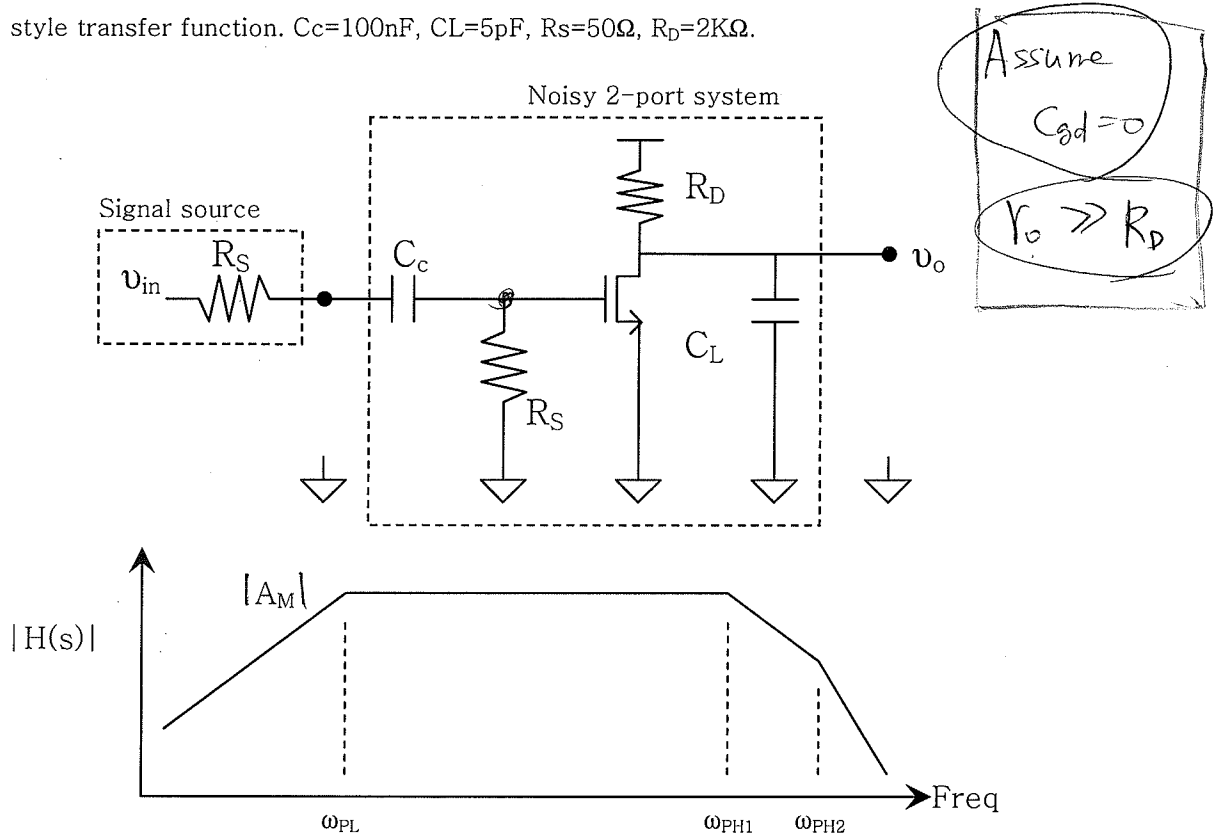2. [25 points] Consider the common source amplifier shown below. It has band pass style transfer function. $C_c=100\text{nF}$, $C_L=5\text{pF}$, $R_s=50\Omega$, $R_D=2\text{K}\Omega$.



- (a) [5 points] Derive the expression for the mid-band gain, A_M .

$$A_M = -\frac{1}{2} g_m R_D$$

v_{in} to the gate

$$\frac{R_s}{R_s + \frac{1}{sC_c} + R_s} = \frac{R_s}{2R_s + \frac{1}{sC_c}} = \frac{R_s}{1 + s2R_sC_c}$$

Zero

Pole


- (b) [10 points] Derive the expressions for ω_{PL} , ω_{PH1} , and ω_{PH2} . [Hint: C_c is much bigger than C_{gs} . You can ignore C_{gs} , C_{gd} , C_L and C_{db} for low frequency analysis, and ignore C_c for high frequency analysis. You don't need to calculate zero.]

$$\omega_{PL} = \frac{1}{C_c (R_S + R_S)}$$

$$\omega_{PH1} = \frac{1}{C_{gs} \left(\frac{1}{2} R_S \right)}$$

$$\omega_{PH2} = \frac{1}{C_L R_D}$$

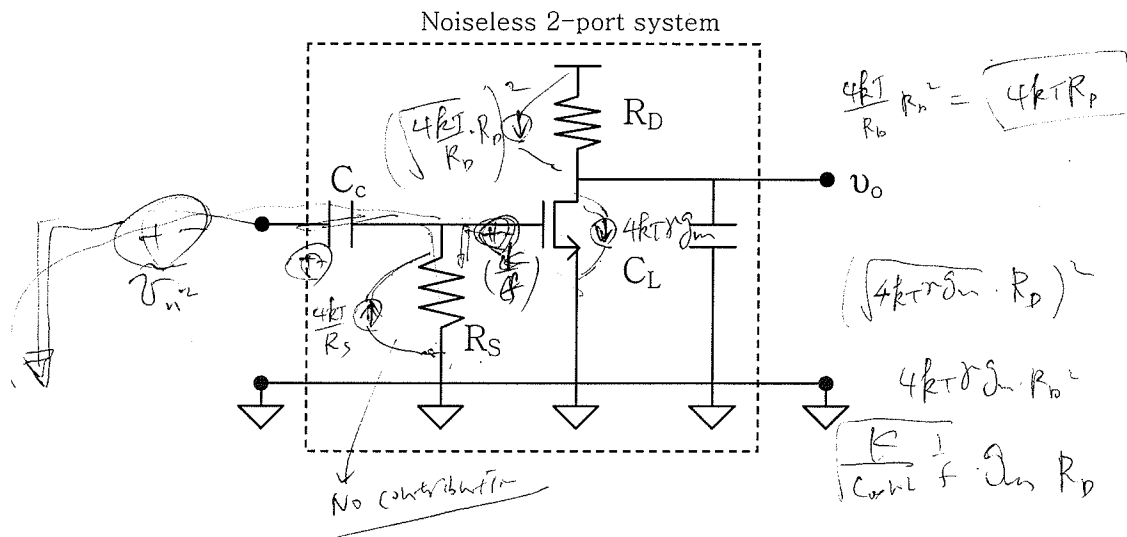- (c) [10 points] Calculate the input-referred noise voltage at mid-band. You don't need to calculate the input-referred noise current. Assume there are drain current noise and flicker noise in the transistor. [Hint: For mid-band analysis, you can ignore C_c , C_{gs} , C_{gd} , C_L and C_{db} .]





$$\begin{cases} \overline{v_{n,out}^2} = 4kTR_D + 4kTR_S g_m^2 R_D^2 + \frac{k}{C_{ox}WL} \frac{1}{f} g_m^2 R_D^2 \\ A_v = -g_m R_D \end{cases}$$

$$\overline{v_{n,in}^2} = \frac{4kTR_D}{g_m^2 R_D^2} + \frac{4kTR_S g_m^2 R_D^2}{g_m^2 R_D^2} + \frac{k}{C_{ox}WL} \frac{1}{f} \frac{g_m^2 R_D^2}{g_m^2 R_D^2}$$

$$= \boxed{\frac{4kT}{g_m^2 R_D} + \frac{4kTR_S}{g_m} + \frac{k}{C_{ox}WL} \frac{1}{f}}$$

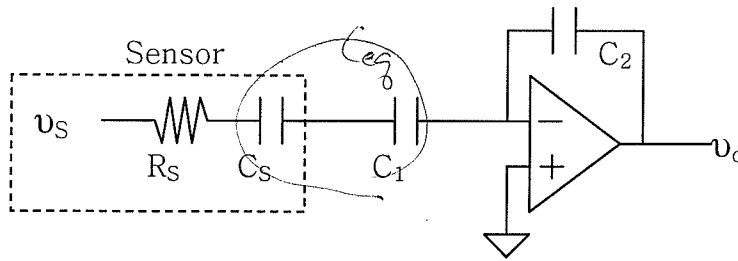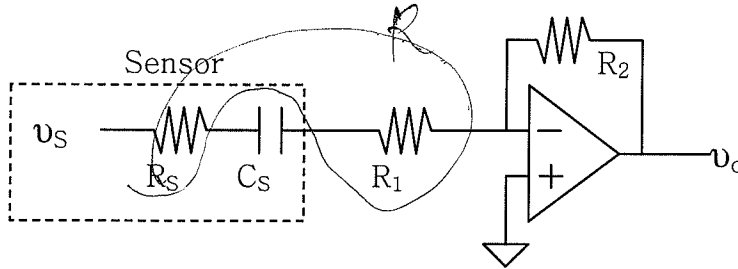4. [25 points] Assume there is a sensor that has resistive and capacitive source impedance. Two different types of amplifiers are used to amplify the sensor signal. Calculate the voltage transfer function, $H(s) = v_o/v_s$, for each case [12.5 points each]. Assume the op-amp is ideal.



~~$R + \frac{1}{sC_s}$~~

$$\frac{v_s}{R + \frac{1}{sC_s}} = \frac{0 - v_o}{R_2}$$

$\frac{-R_2 s C_s}{1 + s C_s R}$

$$\frac{v_o}{v_s} = \frac{-R_2}{R + \frac{1}{sC_s}} \quad (R = R_s + R_1)$$

$$\frac{v_s}{R_s + \frac{1}{sC_1}} = \frac{0 - v_o}{(1/sC_2)}$$

$$\frac{v_o}{v_s} = \frac{(-\frac{1}{sC_2})}{R_s + \frac{1}{sC_1}} = \frac{-1}{sC_2 (R_s + \frac{1}{sC_1})} = \frac{-1}{sC_2 R_s + \frac{C_2}{C_1}}$$

