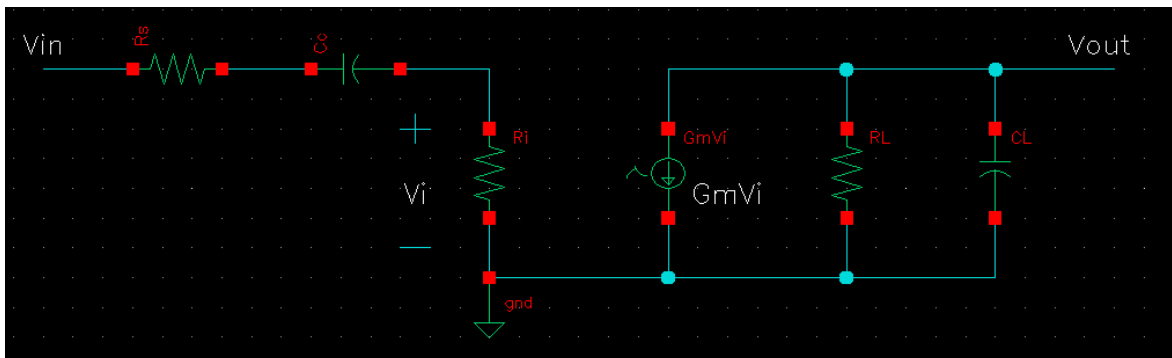



ECE595B HW2

Due: Nov 9, 6:00PM


1. The equivalent circuit of an amplifier is shown below. The input signal source is coupled to the amplifier input via coupling capacitor  $C_c$ . Capacitor  $C_L$  represents a parasitic capacitance appearing across the load resistance  $R_L$ .
  - (a) Derive an expression for the amplifier voltage gain  $A(s)$  – mid-band gain.
  - (b) Noting that  $C_c$  is responsible for the frequency dependence of the gain at low frequencies, and the  $C_L$  causes the gain to fall off at high frequencies, find  $H(s)$ .
  - (c) For  $R_s=20K$ ,  $R_i=100K$ , and  $R_L=10K$ , find the required value of  $G_m$  to obtain a midband gain of 20dB.



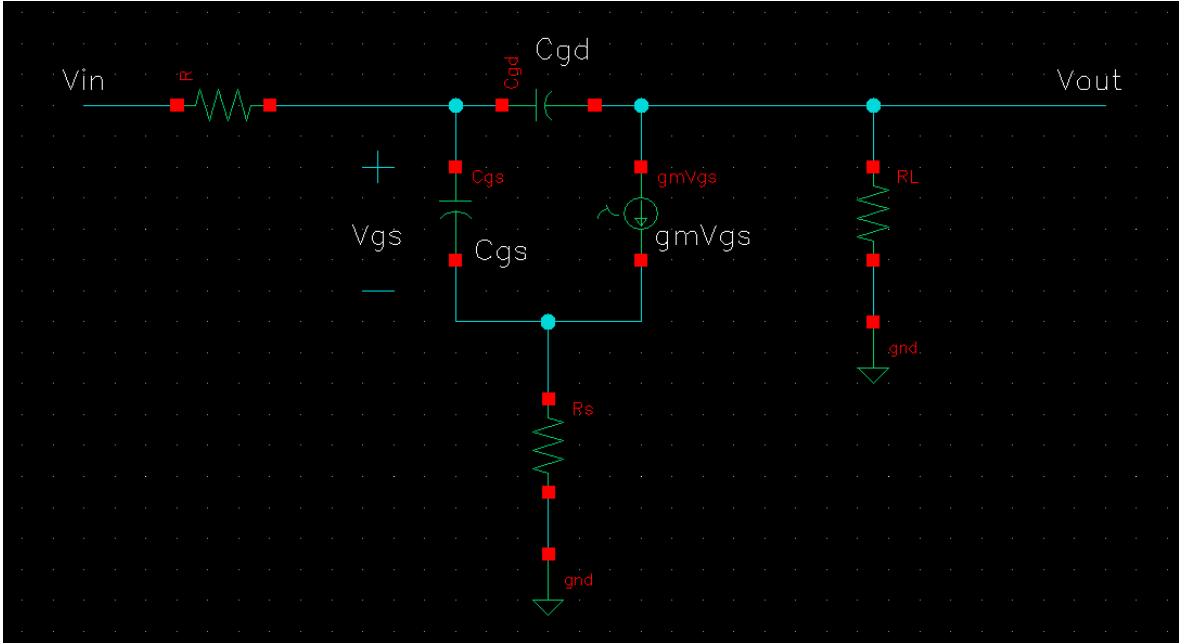
2. The following figure shows the high-frequency equivalent circuit of a FET amplifier with a resistance  $R_s$  connected in the source. The purpose of the problem is to show that the value of  $R_s$  can be used to control the gain and bandwidth of the amplifier, specifically to allow the designer to trade off gain for increased bandwidth.
  - (a) Derive an expression for the low-frequency voltage gain.
  - (b) Derive an expression for the transfer function.
  - (c) Let  $R=100K$ ,  $g_m=4mA/V$ ,  $R_L=5K$ ,  $C_{gs}=100fF$ , and  $C_{gd}=20fF$ . Find the low frequency gain and 3-dB frequency for the cases  $R_s=0$ , 100 and 250ohm. In each case evaluate also the gain-bandwidth product.



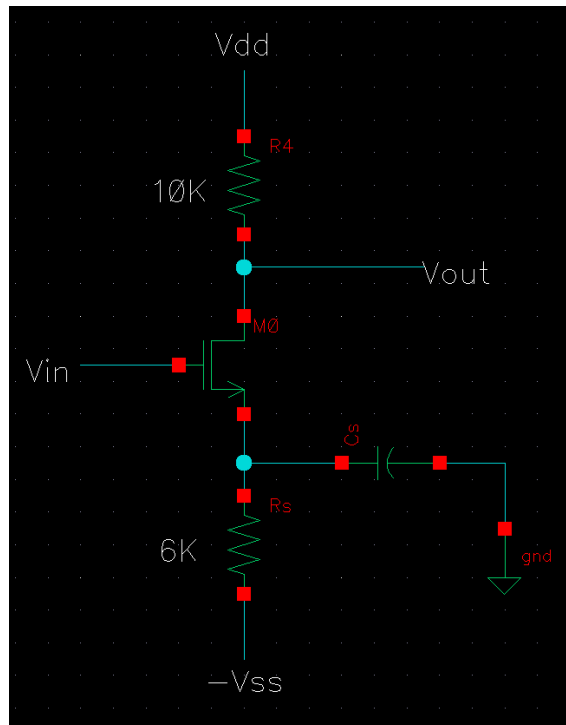
3. The amplifier shown below is biased to operate at  $I_d=1\text{mA}$  and  $g_m=15\text{mA/V}$ . Neglecting  $r_o$ , find the midband gain. Find the value of  $C_s$  that places the corresponding pole at  $10\text{Hz}$ . What is the frequency of transfer-function zero introduced by  $C_s$ ? Give an expression for the gain function.



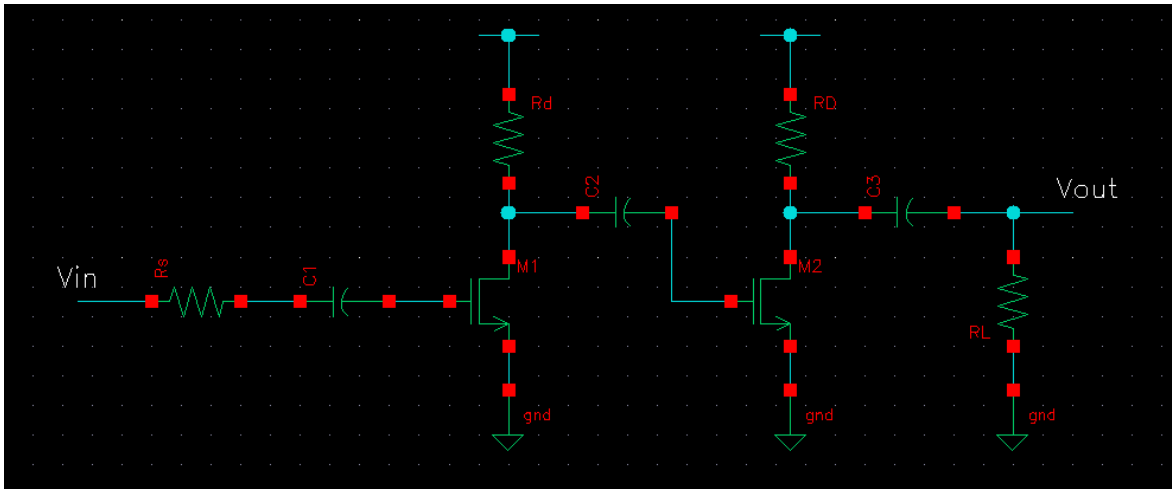
4. The circuit shown below is a basic two-stage capacitor coupled amplifier.  $R_s=R_L=R_d=R_D=1K$ ,  $C_1=C_2=1\mu F$ , and  $C_3=10\mu F$ . Find the voltage transfer function. (Hint: use the Miller method and ignore  $C_1$ ,  $C_2$ , and  $C_3$  at high frequencies.)



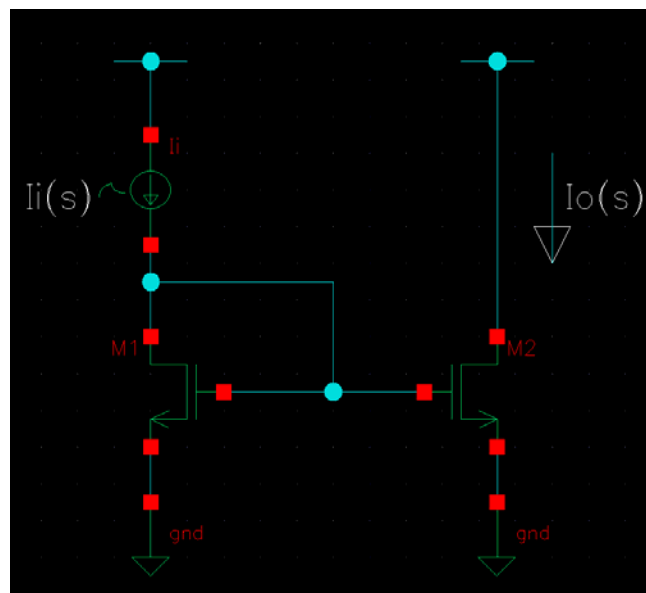
5. For the current mirror shown below, derive an expression for the current transfer function  $I_o(s)/I_i(s)$  taking into account the MOS internal capacitance and neglecting  $r_o$ . Assume the MOSFETs to be identical. Observe that a signal ground appears at the drain of M2.



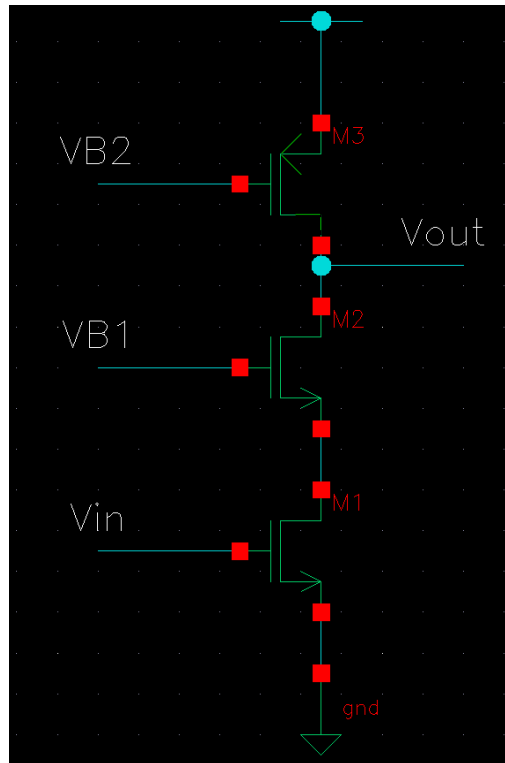6. The following figure shows a cascode CMOS amplifier using three devices.
- (a) Draw the amplifier small signal equivalent circuit. It should include three capacitors:  $C_{gd1}$ ,  $C_1$ , and  $C_2$ , where  $C_1$  is the total capacitance at the drain of  $M_1$ , and  $C_2$  is the total capacitance at the drain of  $M_2$ . Since the resistance between the output node and ground is dominated by  $r_{o3}$  you may neglect the effect of  $r_{o2}$  and omit it from the equivalent circuit. Also neglect body effect in  $M_2$ .
- (b) Derive an expression for the transfer function.



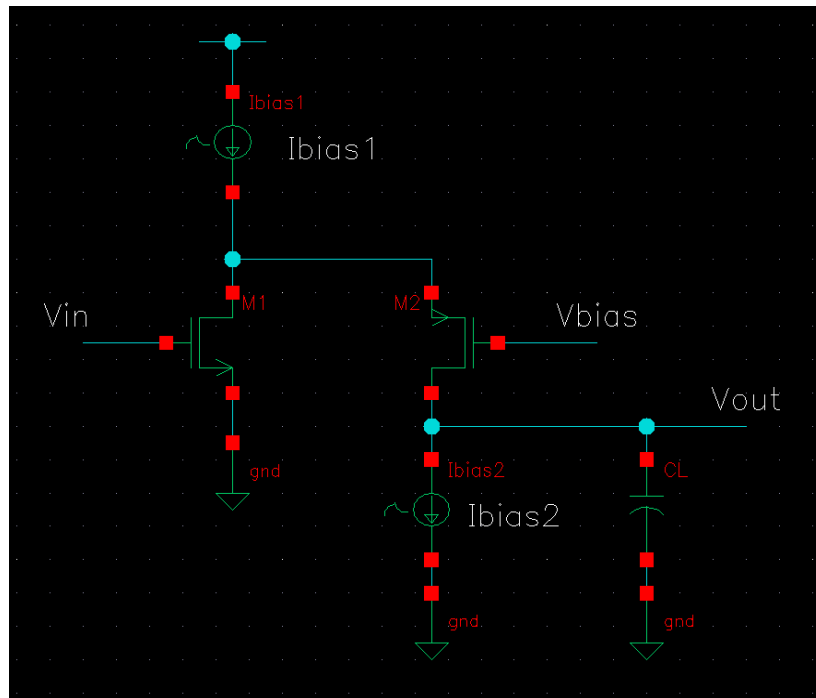7. The following figure shows the circuit of a folded cascode amplifier. The folded cascode is a cascode circuit in which the cascode transistor  $M_2$  is of complementary polarity to  $M_1$ .
- (a) If the bias current are such that  $M_1$  and  $M_2$  have equal  $g_m$  and  $r_o$  values and assuming the current source  $I_{bias2}$  is implemented with a cascode and thus has an output resistance equal to that looking back into the drain of  $M_2$ , show the gain equation.
- (b) The dominant high-frequency pole is usually formed at the output node. Find out the pole frequency.



8. The transistors in the following circuit have  $g_m=10\text{mA/V}$ ,  $r_o=30\text{K}$ ,  $C_{gs}=100\text{fF}$ , and  $C_{gd}=20\text{fF}$ . (Note that the bias details are not shown.)
- Find  $R_{in}$  (input resistance) and the low frequency gain.
  - Find an estimate of the upper 3dB frequency. Which capacitor dominates? Which one is the second most significant?

