

ECE 201, Section 3


Lecture 11

Prof. Peter Bermel


September 14, 2012

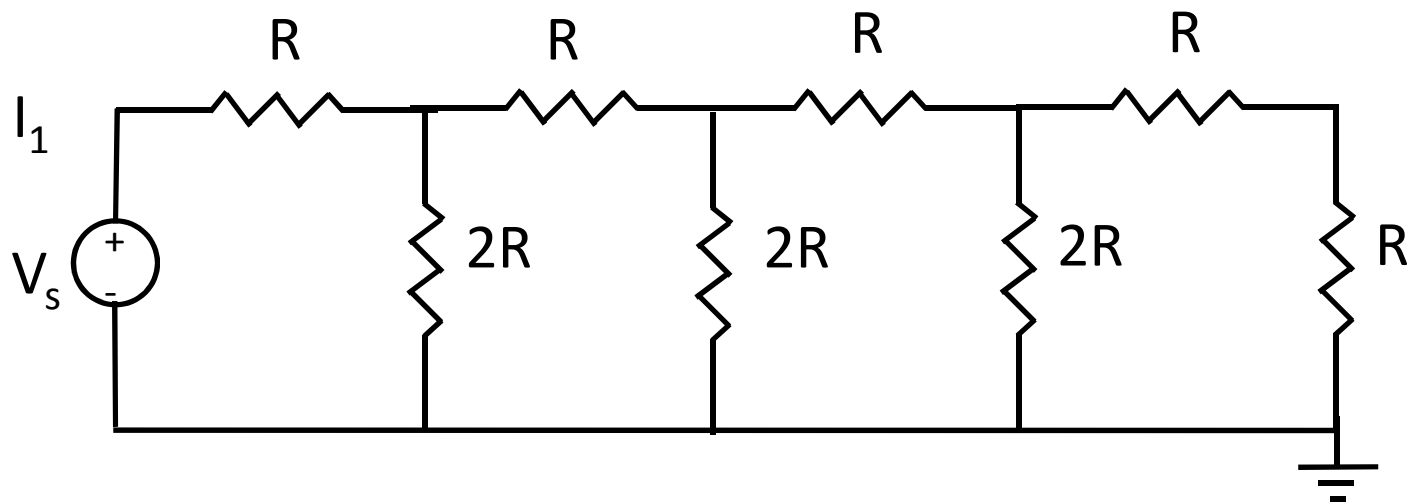Example: Ladder Networks

- Current and voltage everywhere for this 4-loop network? What about N loops?




Example Solution

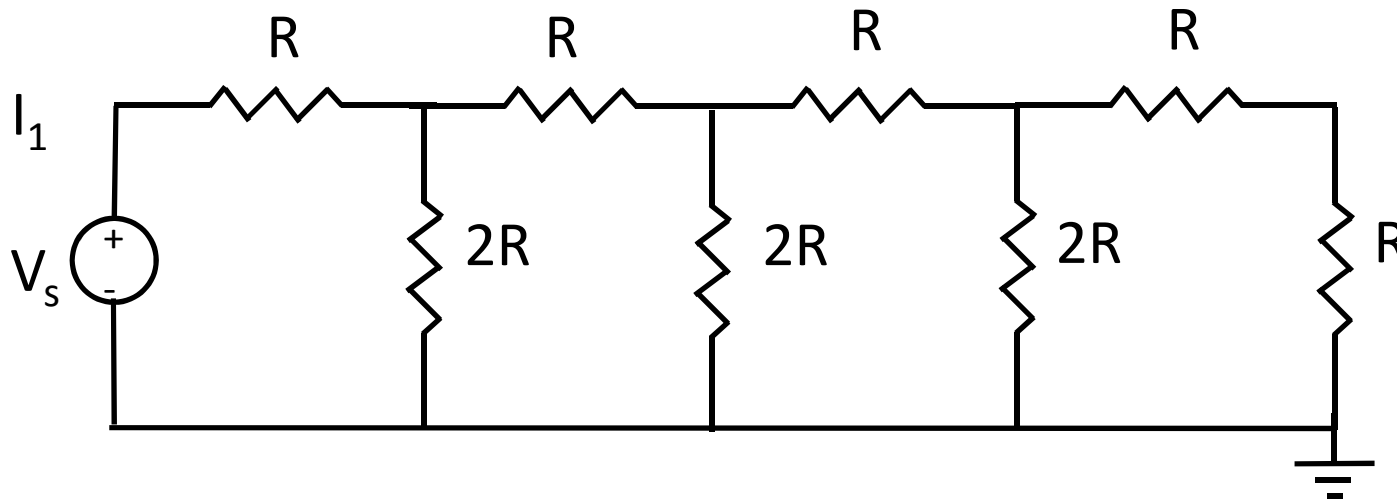


- Assume 1V across resistor at end
- 2V across first loop
- 4V across second loop
- 16 V across fourth loop
- 2^N V with N loops
- Actual voltages: $V_s * 2^{M-N}$

Source Transformations

Combining voltage sources:

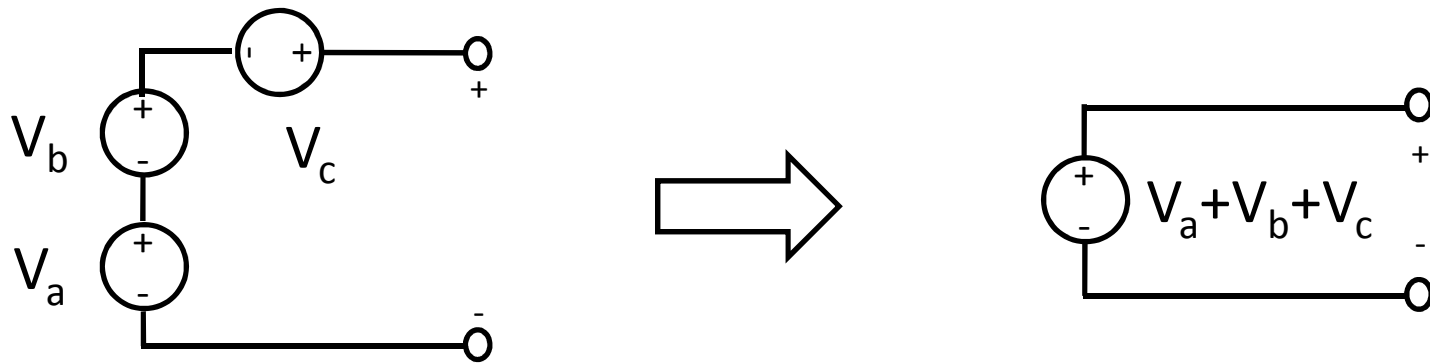


Combining current sources:

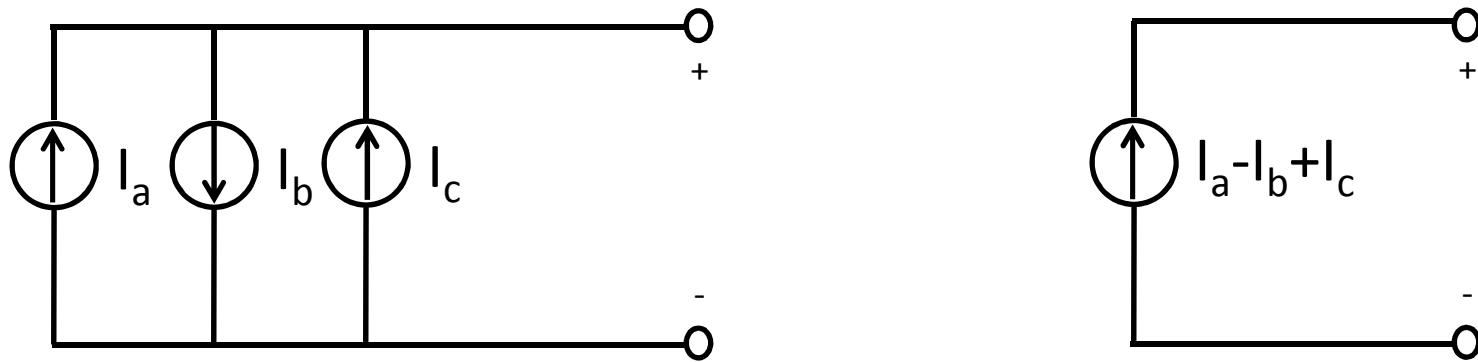

Source Transformation Theorem

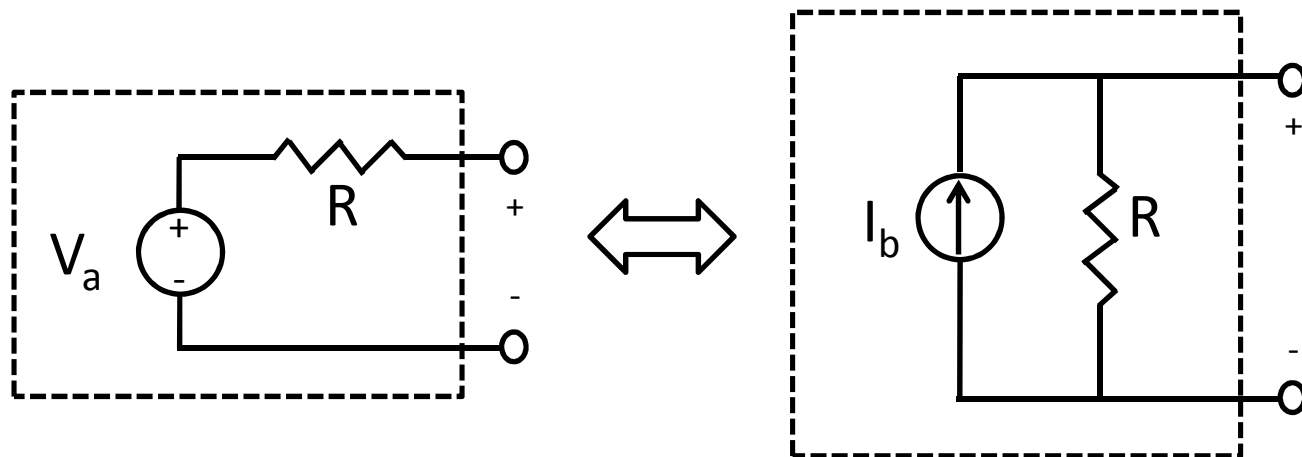- These 2-terminal networks are equivalent:
 - Voltage source V_a in series with resistor R
 - Current source $I_b = V_a/R$ in parallel with resistor R



$$V = V_a + IR$$


$$\text{If } V_a = RI_b, V = R(I_b + I)$$

$$I = V/R - I_b$$


$$V = R(I_b + I)$$

Example 1

- What current flows through the central $3\ \Omega$ resistor?

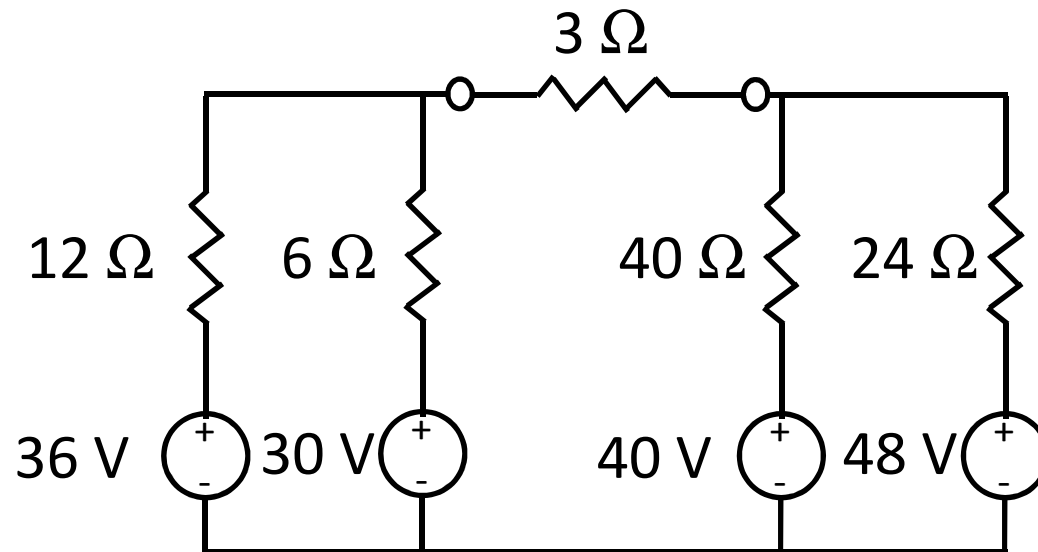


Example 1: Solution

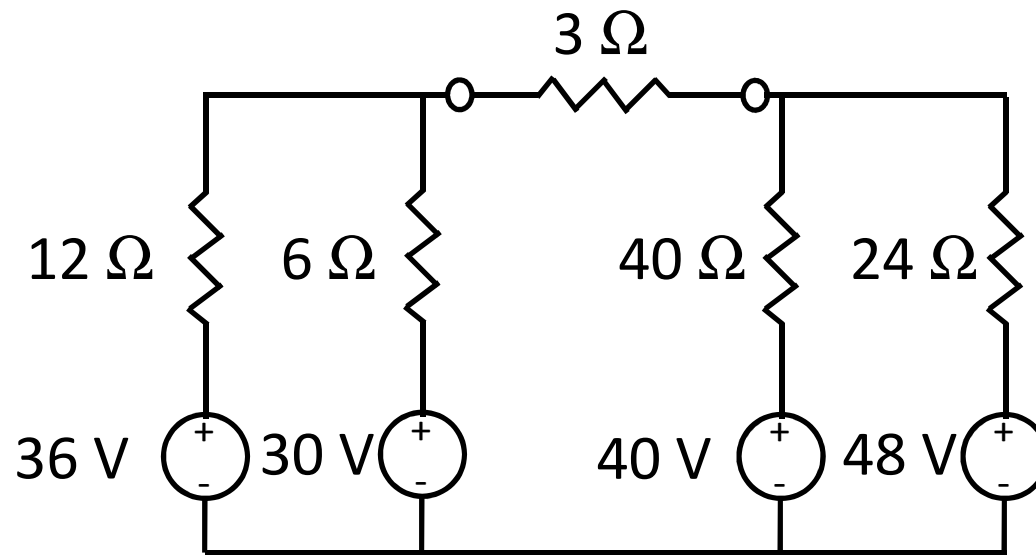

- Rewrite each of the resistor/voltage source pairs as parallel resistor/current source pairs with currents of $36/12=3\text{A}$; $30/6=5\text{A}$; $40/40=1\text{A}$; $48/24=2\text{A}$

Example 1: Solution

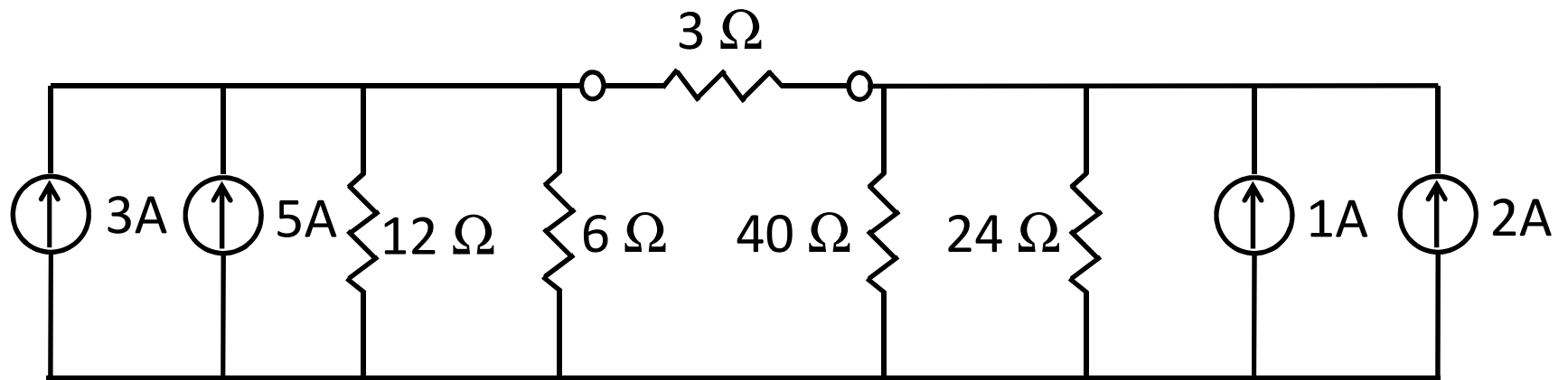


Combine parallel current sources and resistors.

$$I_L = 3 + 5 = 8\text{ A}; I_R = 1 + 2 = 3\text{ A}$$

$$R_L = (1/6 + 1/12)^{-1} = 4\ \Omega; R_R = (1/24 + 1/40)^{-1} = 15\ \Omega$$


Example 1: Solution

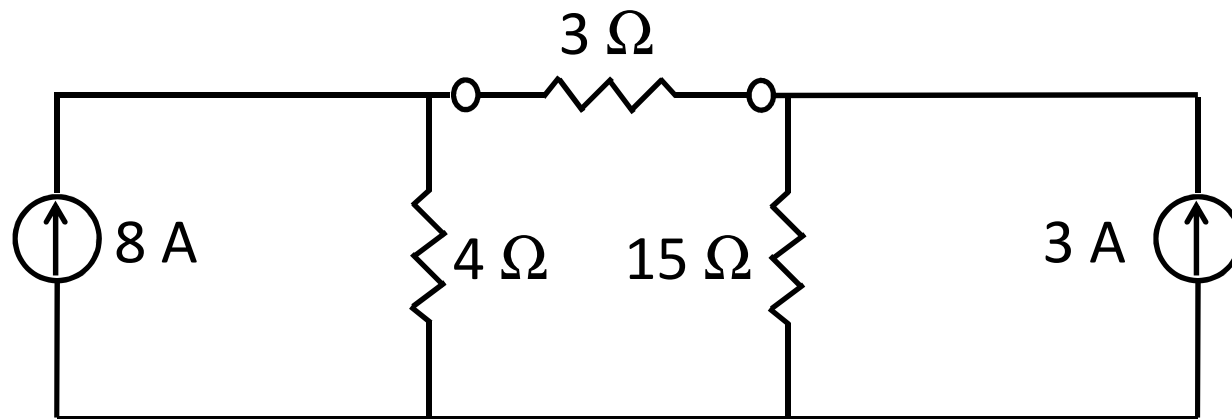

Transform back into V-R pairs:

$$V_L = 32 \text{ V}; V_R = 45 \text{ V}$$

Example 1: Solution

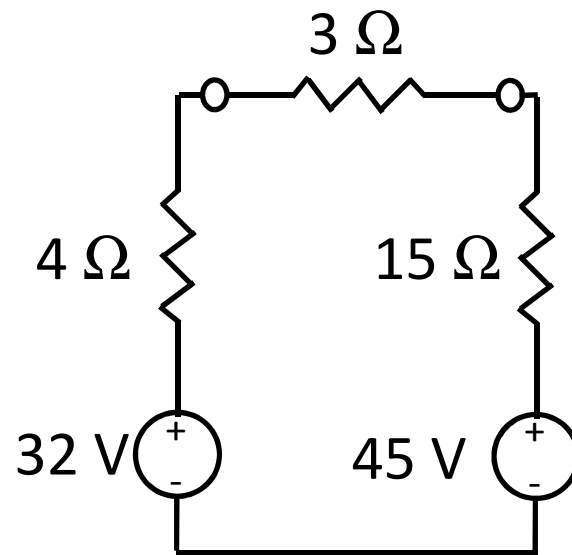




Combine in series:

$$V=13 \text{ V}; R=22 \text{ } \Omega$$

$$I=V/R=0.59 \text{ A}$$

Equivalent Networks

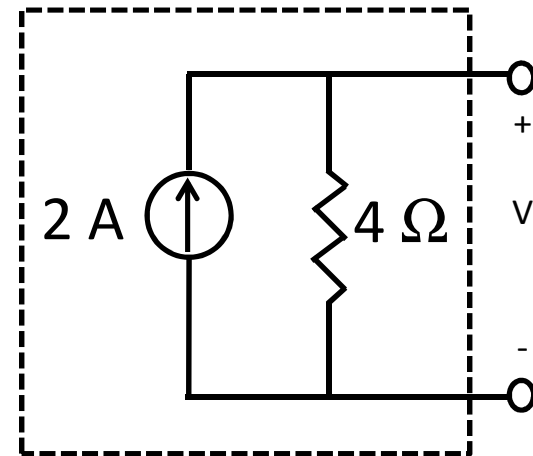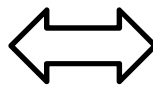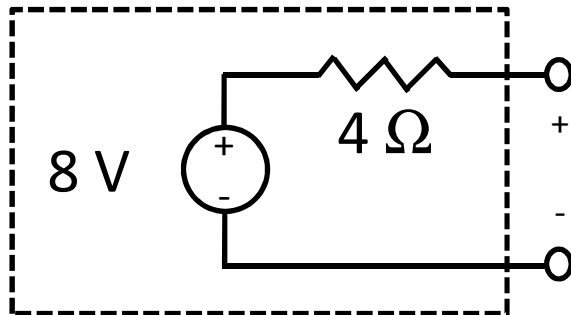
- Equivalent networks: distinct 2-terminal circuits which exhibit the same current-voltage relationship
- Examples:




$$V = 8 + 4I$$

$$I = V/4 - 2$$

Equivalent Network Examples

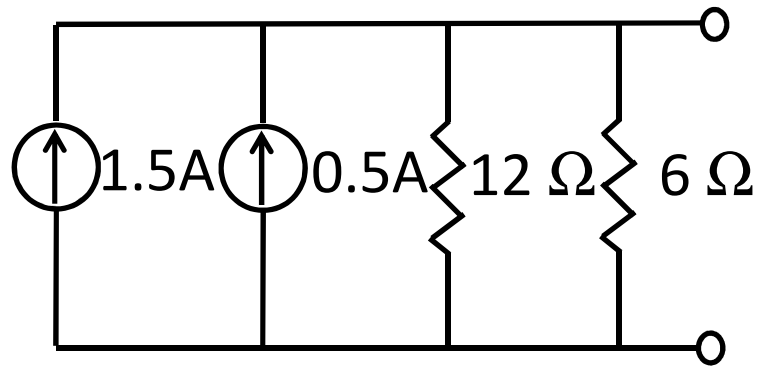


$$I = V/4 - 2$$

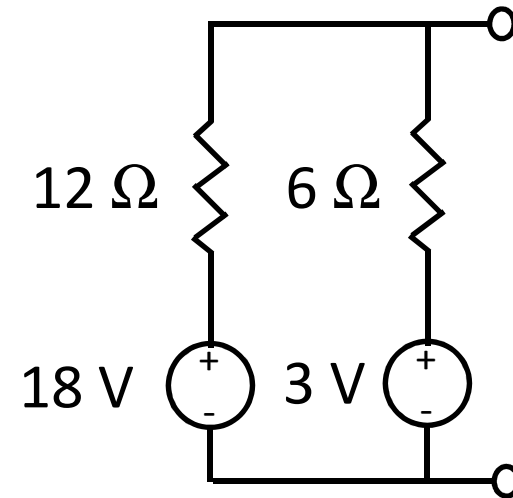


$$V = 8 + 4I$$

Car Battery Problem

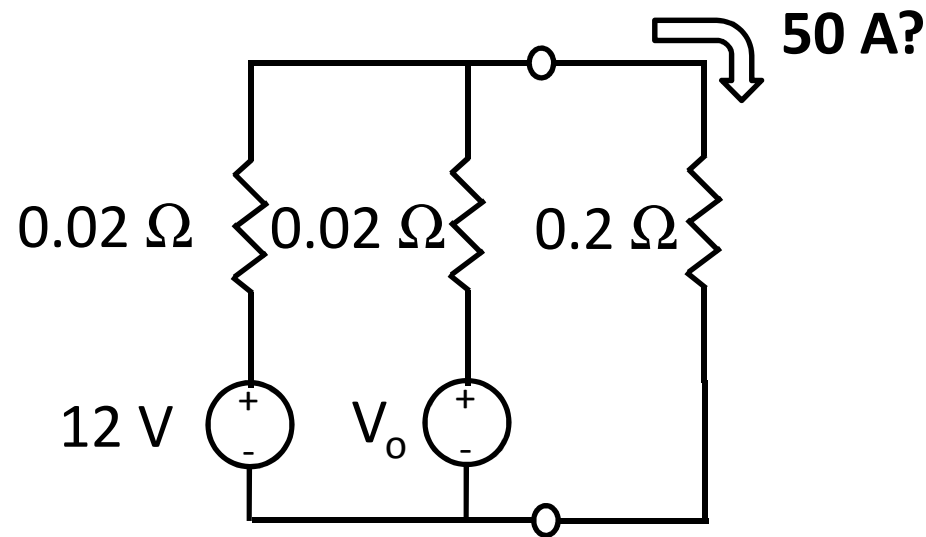- What is the minimum value of V_o required to achieve a 50 A starter voltage?



Car Battery Solution

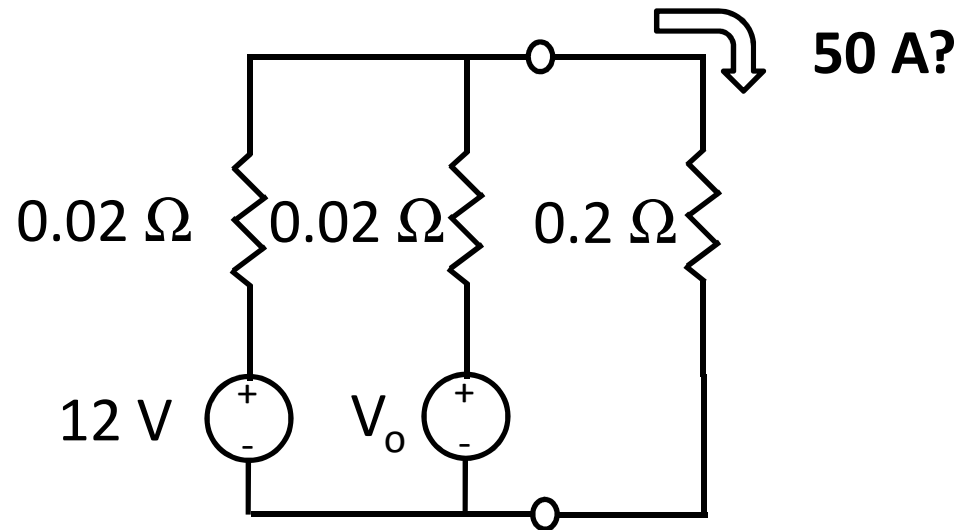


- Source transformation yields
 $I = (12 + V_o) / 0.02$; $R_{eq} = 0.01 \Omega$
 $V = 6 + 0.5V_o$
 $I = 50 = (6 + 0.5V_o) / 0.21 \rightarrow V_o = 9 \text{ V}$

Last Lecture on Exam #1

Monday begins Exam #2 material


Thévenin's Theorem

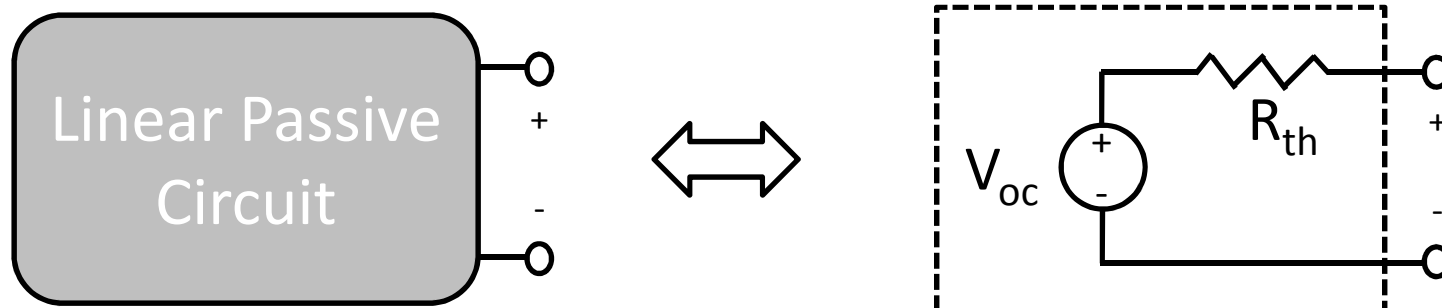- An arbitrary 2-terminal network of independent sources and resistors can be represented by its Thévenin equivalent circuit



Norton's Theorem

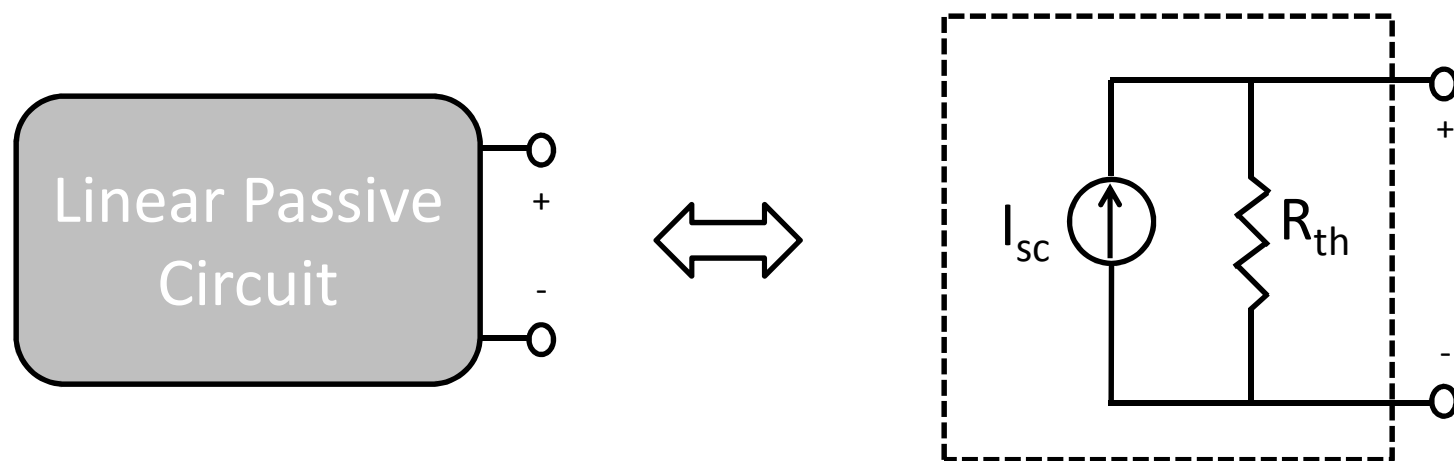- An arbitrary 2-terminal network of independent sources and resistors can be represented by its Norton equivalent circuit



Thevenin and Norton Circuits

- A bare voltage source doesn't have a Norton equivalent
- A bare current source doesn't have a Thévenin equivalent
- When both exist, $V_{oc} = R_{th} I_{sc}$
- Can also deduce Thévenin resistance from:

$$R_{th} = \frac{V_{oc}(t)}{I_{sc}(t)}$$

Homework

- HW #10 due today by 4:30 pm in EE 325B (if no one's there, leave it in an envelope on the door)
- HW #11 due Monday: DeCarlo & Lin, Chapter 5:
 - Problem 40
 - Problem 42
 - Problem 45