

ECE 201, Section 3

Lecture 12

Prof. Peter Bermel
September 17, 2012

Exam #1: Thursday, Sep. 20

6:30-7:30 pm

- Most of you will be in WTHR 200, unless told otherwise
- Review session tonight at 8 pm (MATH 175) – will go over posted Review Exam #1
- Posted answers to 3 sample exams on Blackboard to help you study
- I'll have office hours 12:30-1:30 pm MWF in EE 331A and by appointment

Exam #1 Key Concepts

- Basic concepts: current, voltage, charge, Ohm's law, KCL, KVL, current & voltage division
- Combining resistors in series and parallel
- Resistor networks: node, supernode, loop analysis
- Source transformation

Basic Concepts

- Current I represents the flow of charge:

$$I = \frac{dq}{dt}$$

- Voltage V creates potential energy U for charges:

$$U = qV$$

- Power dissipated (passive sign convention):

$$P = IV$$

- Ohm's Law for resistors:

$$V = IR$$

Basic Concepts: Kirchhoff's Laws

Kirchoff's Current Law (KCL)

- Sum of all currents entering a node or Gaussian surface is zero at all times:

$$\sum_{k=1}^N I_k(t) = 0, \text{ for all } t$$

Kirchoff's Voltage Law (KVL)

- Voltage drop between any two nodes is direction-dependent and path-independent (i.e., $V_{AB} = V_A - V_B$)
- Sum of voltage drops over any closed loop is zero

Voltage and Current Division in Resistors; Resistor Networks

- Series resistors:

$$R_{eq} = \sum R_l$$

$$V_k = VR_k/R_{eq}; \text{ currents equal}$$

- Parallel resistors

$$G_{eq} = \sum G_l$$

$$I_k = IR_{eq}/R_k; \text{ voltages equal}$$

- Series-parallel circuits
 - Analyzed iteratively

Resistor Network Analysis Approaches

- **Nodal analysis**
- Modified nodal analysis
- Nodal analysis with floating voltage sources
- **Loop analysis**
- All approaches should generally yield the same physical results
- Best choice generally involves least number of unknowns, and will depend on details of problem

Formula Sheet for Exam 1

$$I = dQ/dt$$

In series:

In parallel:

$$V = IR \text{ or } I = GV$$

$$R_{eq} = \sum_k R_k$$

$$G_{eq} = \sum_k G_k$$

$$R = 1/G$$

$$V_k = VR_k/R_{eq}$$


$$I_k = V/R_k = IR_{eq}/R_k$$

$$P = IV$$

Test-Taking Strategies

- Preparing for the exam:
 - Review relevant notes (especially these)
 - Practice exams (time at least one)
 - Previous exams from this semester
- Read each question carefully and figure out exactly what to calculate; no 'trick' questions
- Time management:
 - No more than 4 minutes per question until all done
 - Guess among plausible options, if needed
 - Take 30 sec break if feeling stressed

Thevenin and Norton Circuits

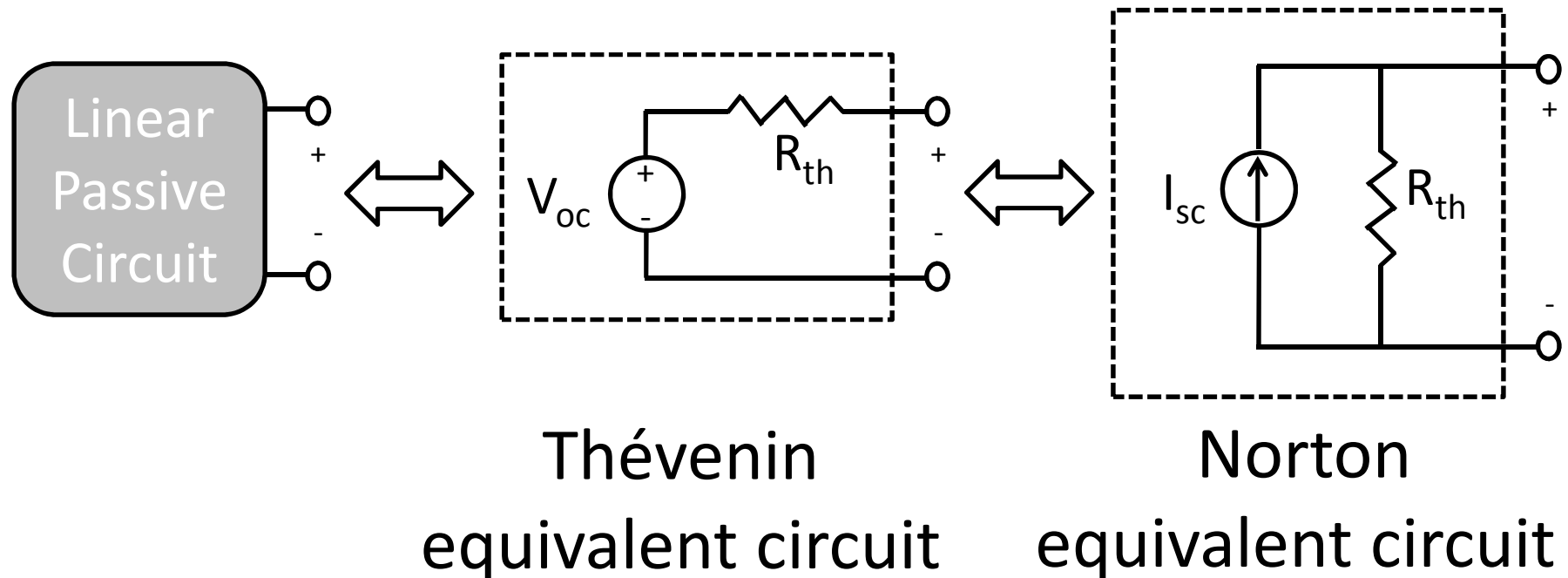


Equivalent circuits related by:

$$V_{oc} = I_{sc} R_{th}$$

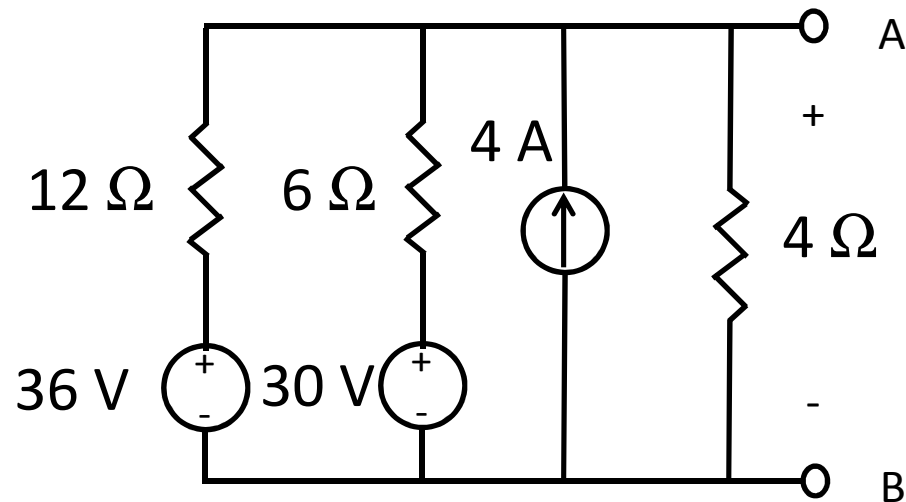
Example 1

- For this network:
 - What is the Thévenin equivalent circuit?
 - What is the Norton equivalent circuit?




Solution

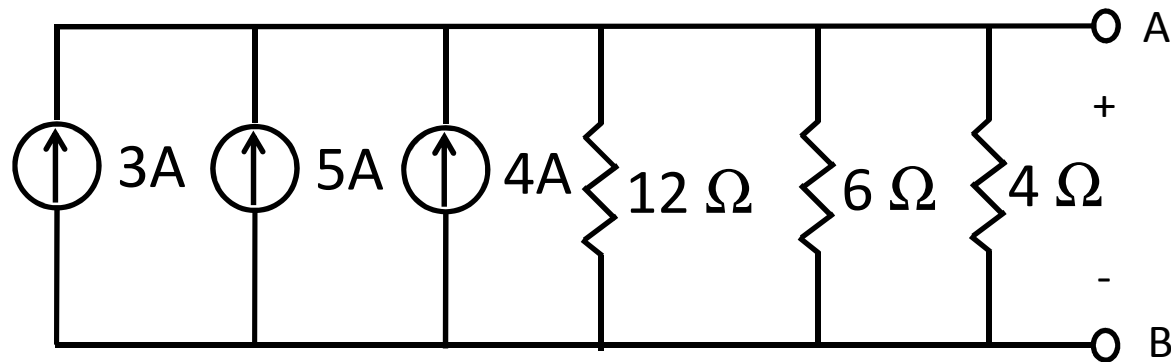- Use source transformation theorem to write this equivalent circuit:




Solution

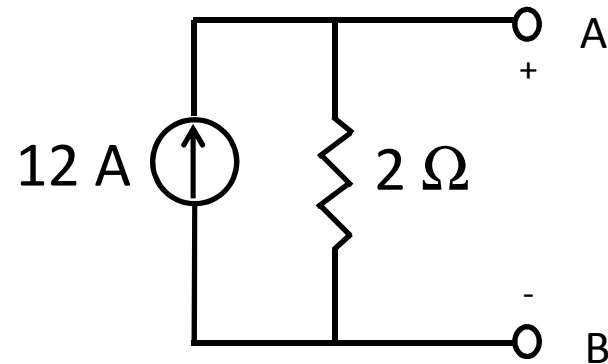- Combine resistors and current sources in parallel to obtain Norton equivalent:




- Transform into Thévenin equivalent:

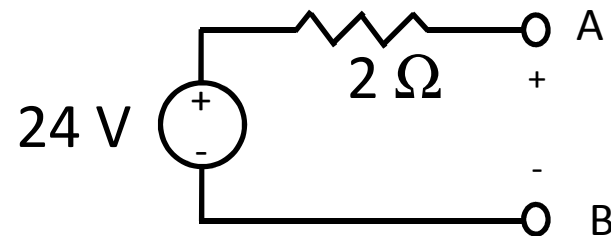

Alternate Solution

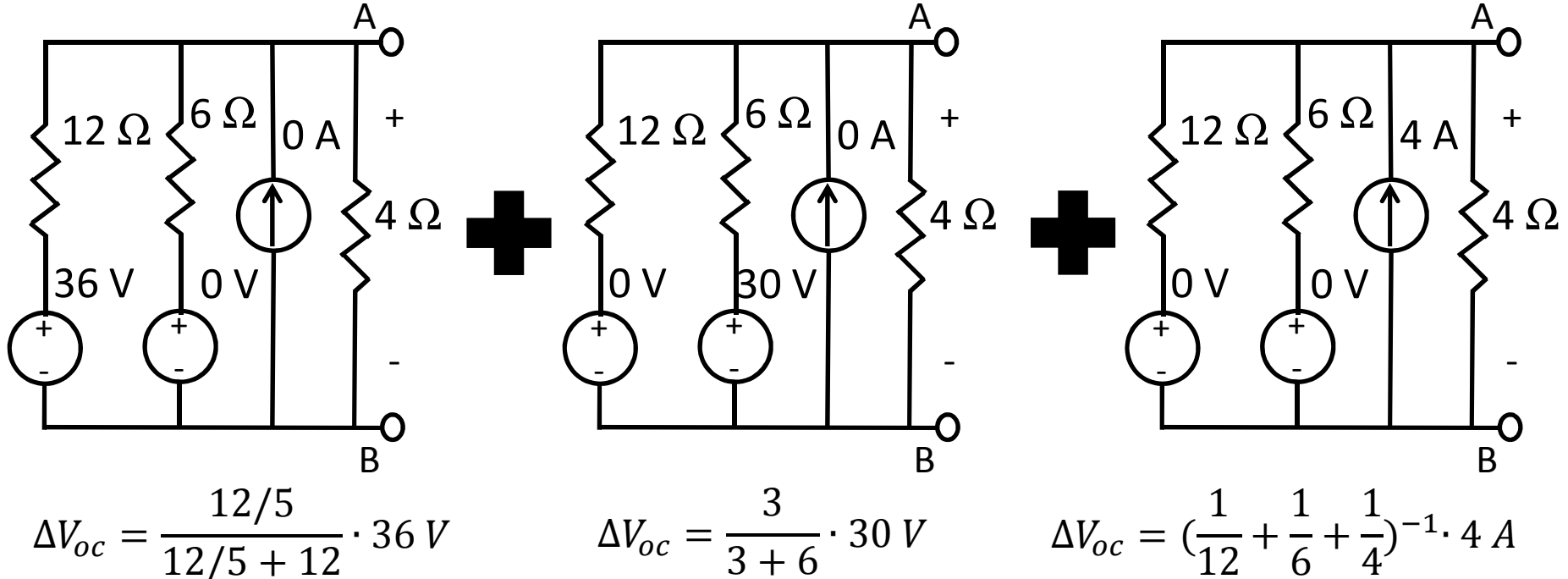
- Use superposition to obtain:
 - Open circuit voltage from individual contributions



$V_{oc} = 6 + 10 + 8 \text{ V} = 24 \text{ V}$ yields Thévenin equivalent voltage

Alternate Solution


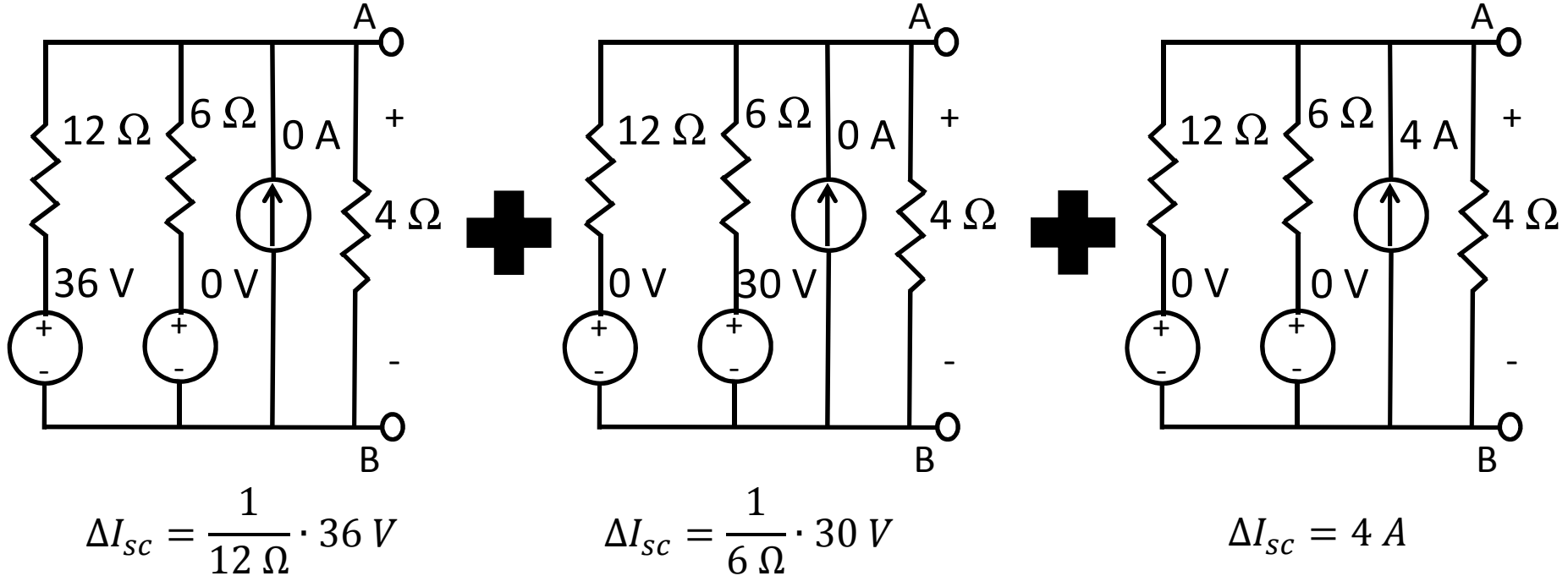
- Use superposition to obtain:
 - Short circuit current from individual contributions



$I_{sc} = 3 + 5 + 4 A = 12 A$ yields Norton equivalent current

Alternate Solution

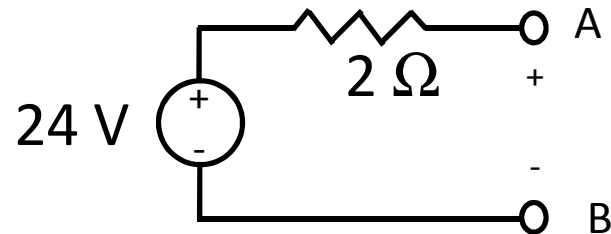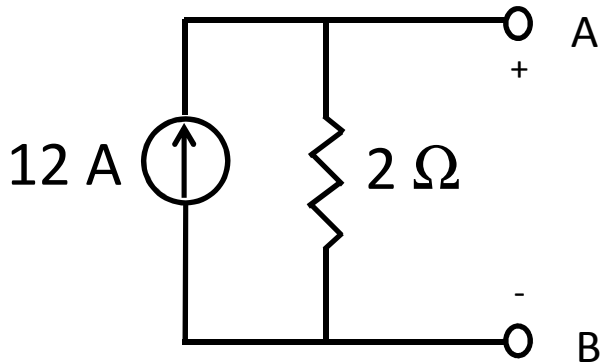- Take quotient of Thévenin voltage and Norton current yields $R_{th}=2\ \Omega$ and the following equivalent circuits:




Equivalencies for Complex Circuits


- Thevenin theorem \rightarrow general 2-terminal linear network obeying $V_{AB} = \rho I_A + v$ must have $R_{th} = \rho, V_{oc} = v$
- Norton theorem \rightarrow general 2-terminal linear network following $I_A = \gamma V_{AB} - \sigma$ must have $G_{th} = \gamma, I_{sc} = \sigma$

Example 2

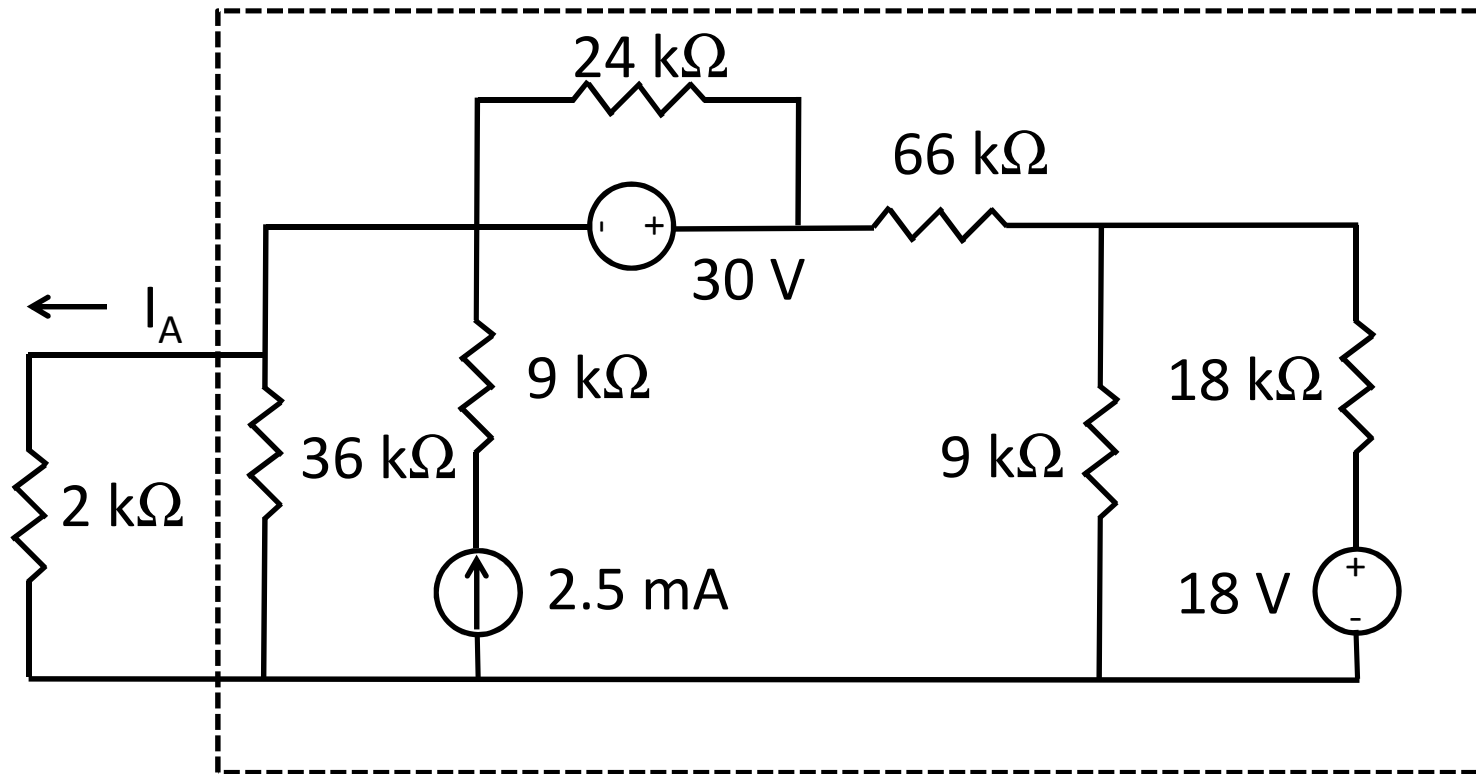- (a) Find the Thévenin equivalent of the circuit below
- (b) Find the output current and power at the load




Solution

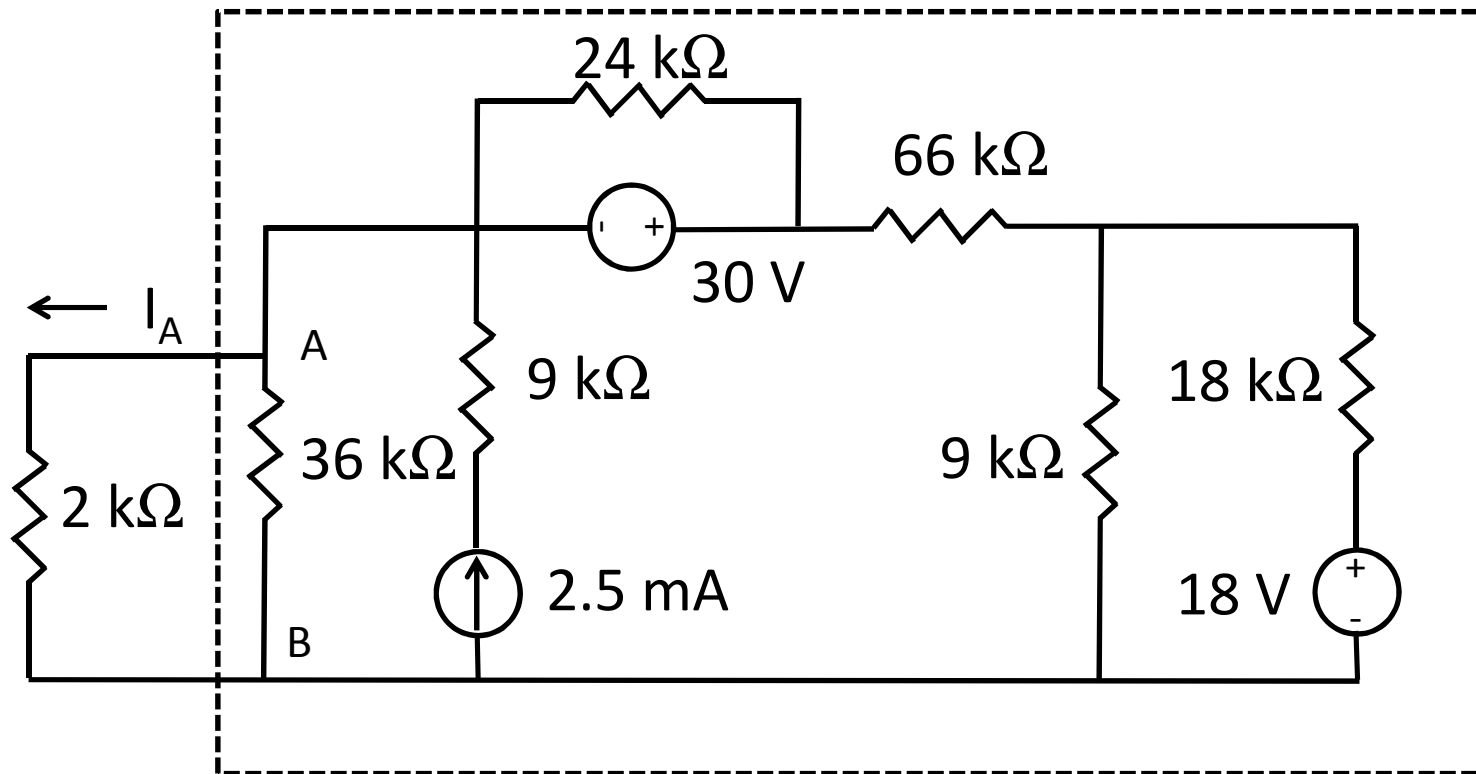

$$R_R = \left(\frac{1}{9} + \frac{1}{18} \right)^{-1} = 6 \text{ k}\Omega; I = 1 \text{ mA}; V = 6 \text{ V}$$


Solution

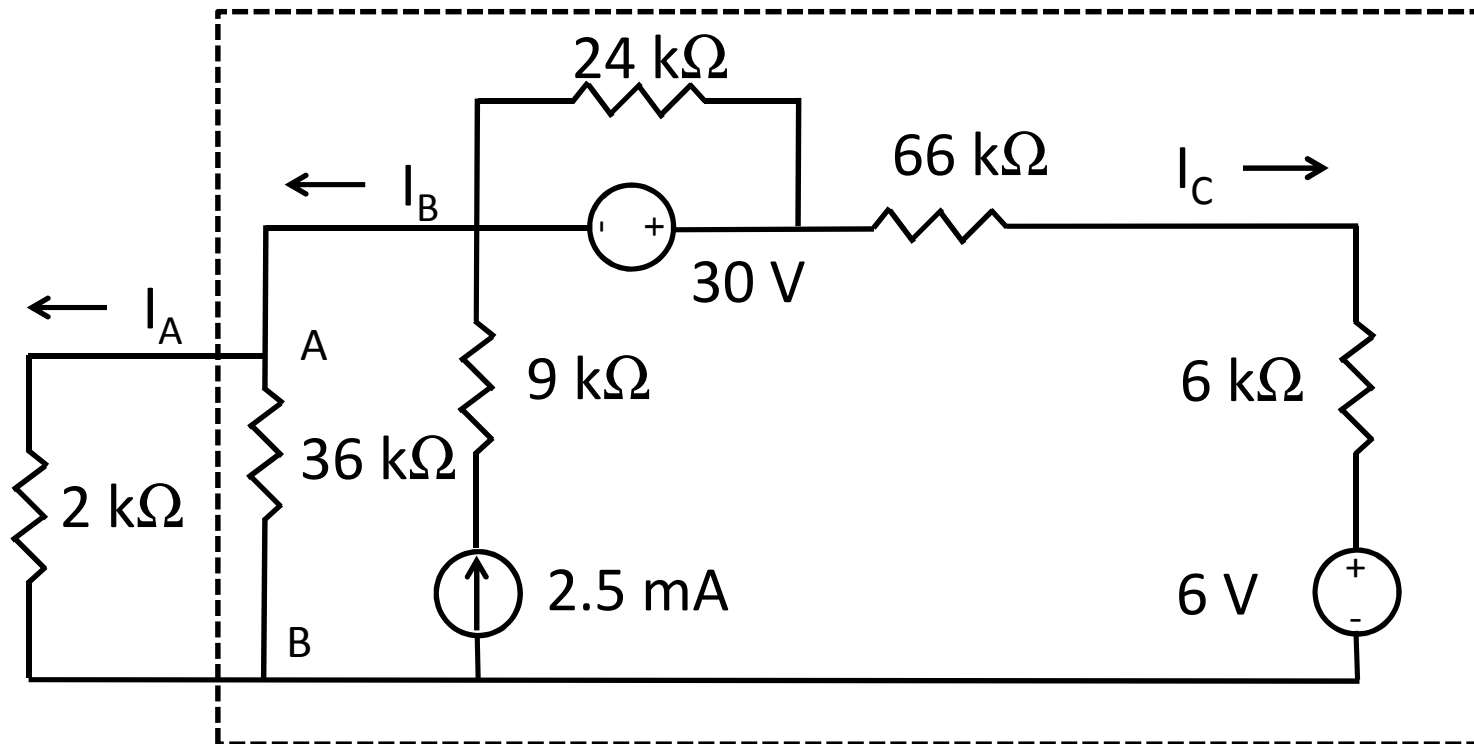

$$R_{th} = \left(\frac{1}{72} + \frac{1}{36} \right)^{-1} = 24 \text{ k}\Omega$$

$$I_B + I_C = 2.5 \text{ mA}; \quad 36I_B = V'; \quad (66 + 6)I_C = 30 - 6 + V'$$

Solution

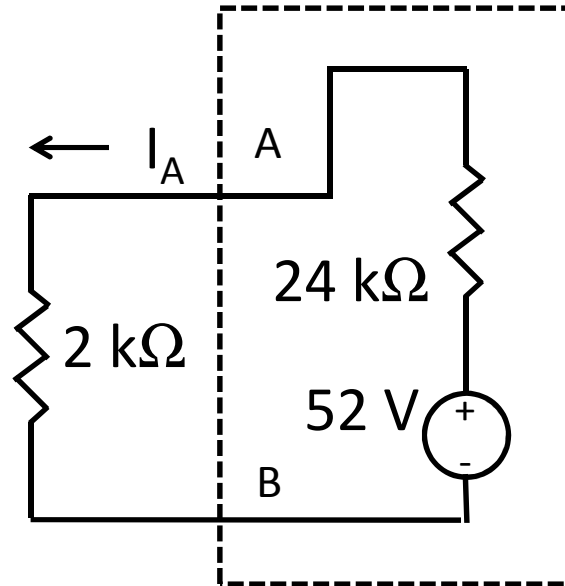

$$R_{th} = \left(\frac{1}{72} + \frac{1}{36} \right)^{-1} = 24 \text{ k}\Omega$$

$$I_B = 13/9 \text{ mA}; V_{oc} = 52 \text{ V}; I_A = 2 \text{ mA}; P_A = 8 \text{ mW}$$

Homework

- HW #11 due today by 4:30 pm in EE 325B
- HW #12 due Fri.: DeCarlo & Lin, Chapter 6:
 - Problem 3
 - Problem 6
 - Problem 8(a),(b)