

ECE 201, Section 3

Lecture 14

Prof. Peter Bermel
September 21, 2012

Exam #1: Thursday, Sep. 20

- Posted a copy of the exam on Blackboard
- Will post scores and return copies of your scantron responses ASAP

Inductors




$$V = L \, dI/dt$$


- Inductors resist changes in the flow of current
- Physically derived from:
 - Ampere's law: a flowing current creates a constant magnetic field
 - Faraday's law: a changing magnetic field induces an emf
- Mathematically, $V = L \, dI/dt$

Example 1

- With a wall AC voltage source of $V(t) = 160 \sin(120\pi t)$, turned on at $t=0$, with an inductor $L=40$ H, what is the current as a function of time for this circuit?

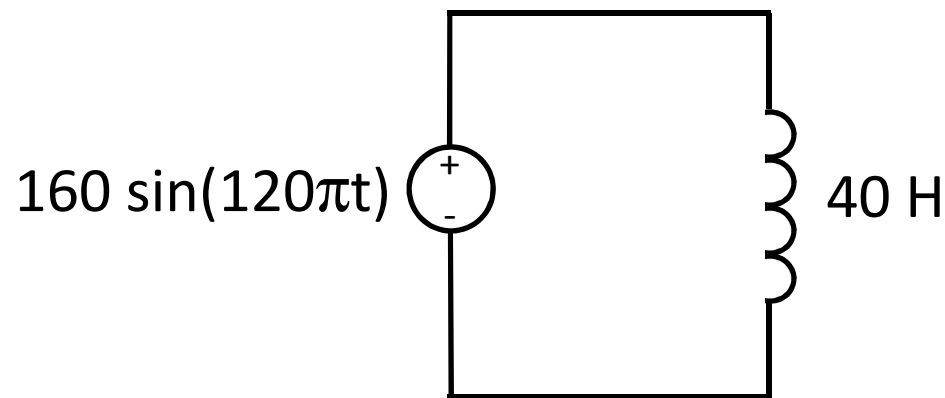

Example 1: Solution

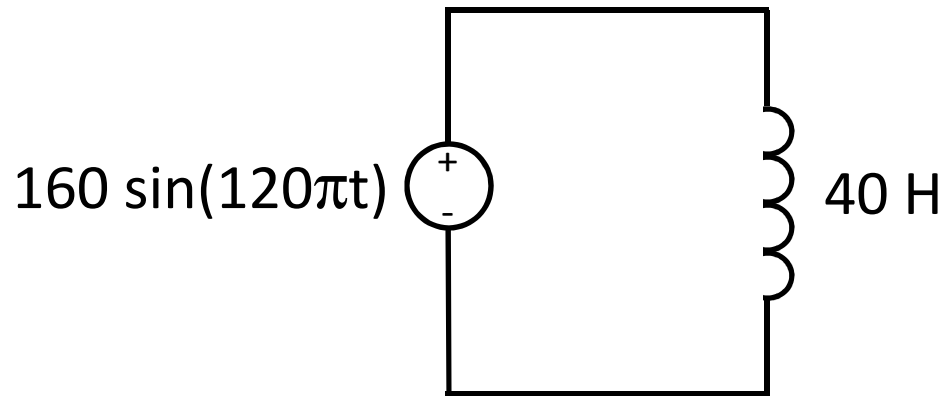

With the inductor:

$$0 = 160 \sin(120\pi t) - 40 \frac{dI}{dt}$$

$$I(t) = \int_0^t 4 \sin(120\pi t) dt$$

$$I(t) = \frac{1}{30\pi} [1 - \cos(120\pi t)]$$

Calculating Inductance

- General formula for inductance:


$$L = \frac{\mu}{4\pi} \oint_C \oint_{C'} \frac{ds \cdot ds'}{|s - s'|}$$

- For solenoid:

$$L = \mu N^2 A / l$$

where:

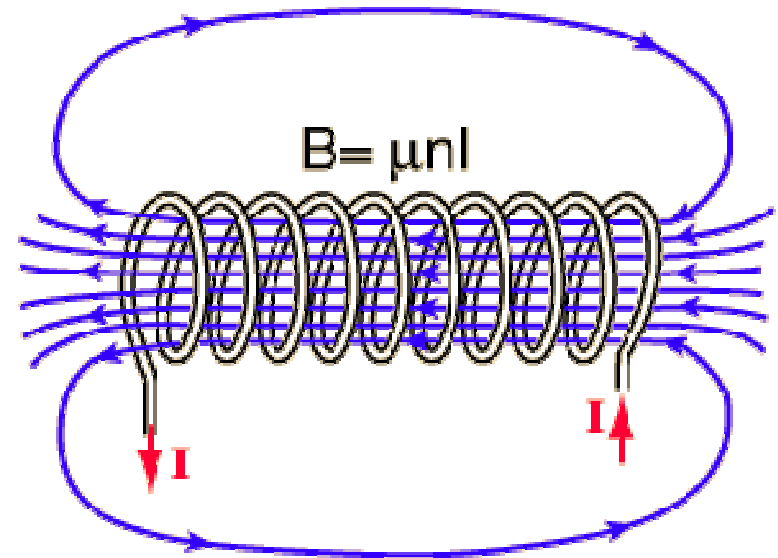- μ =magnetic constant (usu. $\mu_0=4\pi \times 10^{-7}$ H/m)
- N =number of loops
- A =cross-sectional area of solenoid
- l =length of solenoid



Deriving Inductance

- Faraday's law states:

$$\mathcal{E} = N \frac{d\Phi}{dt} \equiv L \frac{dI}{dt}$$

From the definitions for L , Φ , and A :

$$L = \frac{N\Phi}{I} = \frac{N}{I} \int da \cdot B = \frac{N}{I} \oint_C ds \cdot A$$

From Ampère's law:

$$L = \frac{N}{I} \oint_C ds \cdot \oint_{C'} \frac{\mu I ds'}{4\pi |s - s'|}$$

Combining Inductors

- Define $L = \mu n N A$
- In series:

$$L_{eq} = \mu n (N_1 + N_2) A$$
$$L_{eq} = L_1 + L_2$$

Alternative proof:

$$L_1 \frac{dI_1}{dt} + L_2 \frac{dI_2}{dt} = L_{eq} \frac{dI}{dt}$$

By KCL, $I_1 = I_2 = I$, and $dI_1/dt = dI_2/dt = dI/dt$, so:

$$L_{eq} = L_1 + L_2$$

Combining Inductors

- In parallel:

$$L_1 \frac{dI_1}{dt} = L_2 \frac{dI_2}{dt} = L_{eq} \frac{dI}{dt}$$

Conservation of current ($I_1 + I_2 = I$) implies:

$$L_1 \left(\frac{dI}{dt} - \frac{dI_2}{dt} \right) = L_{eq} \frac{dI}{dt}$$

$$L_1 \left(\frac{dI}{dt} - \frac{L_{eq}}{L_2} \frac{dI}{dt} \right) = L_{eq} \frac{dI}{dt}$$

Combining Inductors

- Assuming dI/dt is non-zero:

$$L_1 \left(1 - \frac{L_{eq}}{L_2} \right) = L_{eq}$$

$$L_1 = \left(1 + \frac{L_1}{L_2} \right) L_{eq}$$

$$L_{eq} = \frac{L_1}{1 + L_1/L_2}$$

$$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$$

Combining Inductors

- We can use induction to prove the following:
- Combining inductors in series:


$$L_{eq} = \sum_{k=1}^N L_k$$

- Combining inductors in parallel:


$$\frac{1}{L_{eq}} = \sum_{k=1}^N \frac{1}{L_k}$$

Example 2

- What is the equivalent inductance, current division, and power dissipated between the 2 branches of this circuit?

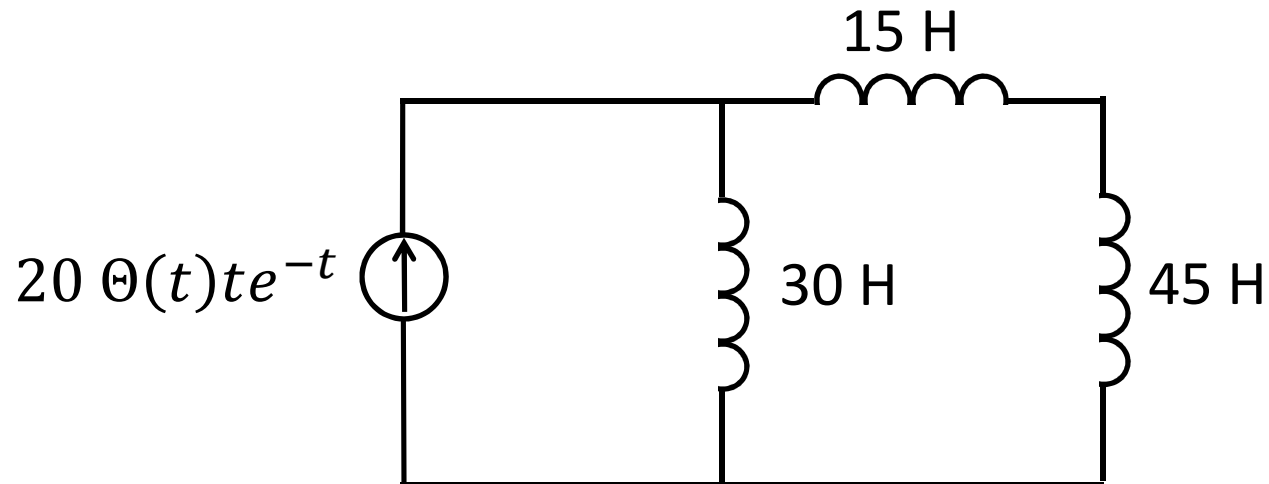

Example 2: Solution

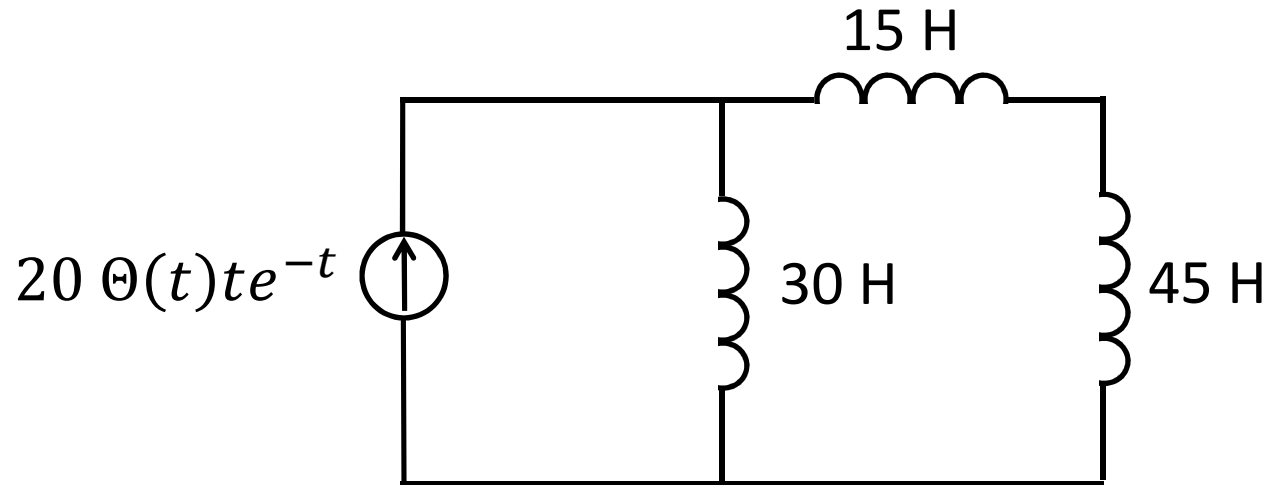


$$L_{eq} = \left(\frac{1}{30} + \frac{1}{15+45} \right)^{-1} = 20 \text{ H}$$

$$30 \, dI_1/dt = 20 \, dI/dt$$

$$I_1 = (2/3)I; \quad I_2 = (1/3)I$$

Example 2: Solution

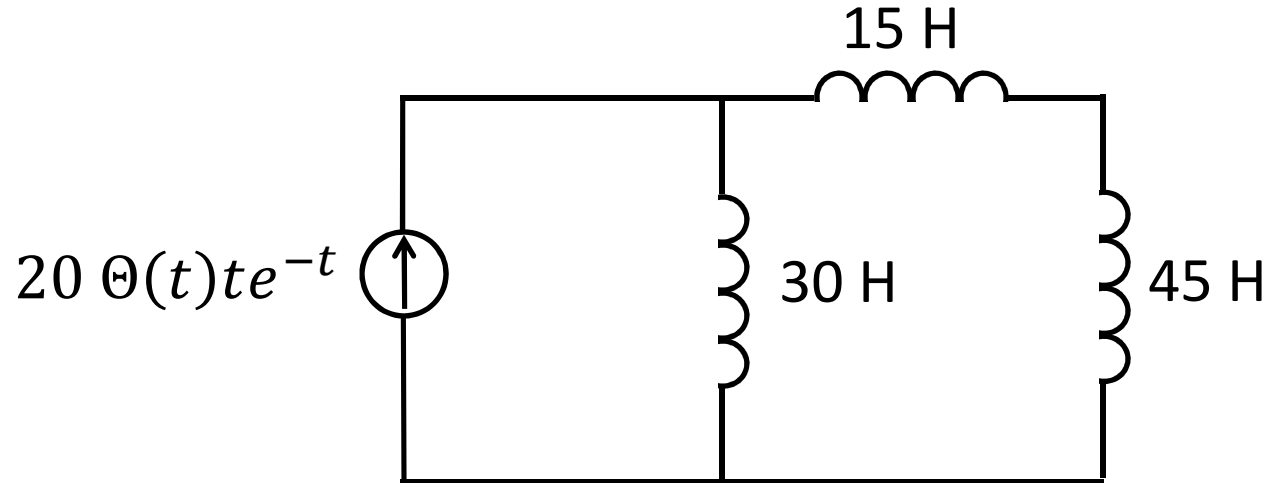

$$\frac{dI}{dt} = 20[\delta(t)te^{-t} + \Theta(t)e^{-t}(1 - t)] \text{ A/s}$$

$$P = I_1 \cdot 30 \, dI_1/dt + I_2 \cdot 60 \, dI_2/dt$$

$$P = 20I \cdot dI/dt$$

$$P = 400 \Theta(t)e^{-2t} t(1 - t)$$

Power in Inductors

- Since the instantaneous power in an inductor:

$$P = IV = IL \frac{dI}{dt}$$

- The energy stored between t_o and t_1 is:

$$U = \int_{t_o}^{t_1} LI \frac{dI}{dt} dt = \int_{I_o}^{I_1} LI dI = \frac{1}{2} L [I_1^2 - I_o^2]$$

- For ac wave with period $T=1/f$:

$$U = 0, \text{ if } t_1 = t_o + mT, \text{ for integer } m$$

Homework

- HW #12 due today by 4:30 pm in EE 326B
- HW #13 due Mon.: DeCarlo & Lin, Chapter 6:
 - Problem 14
 - Problem 16
 - Problem 21
 - Problem 24