
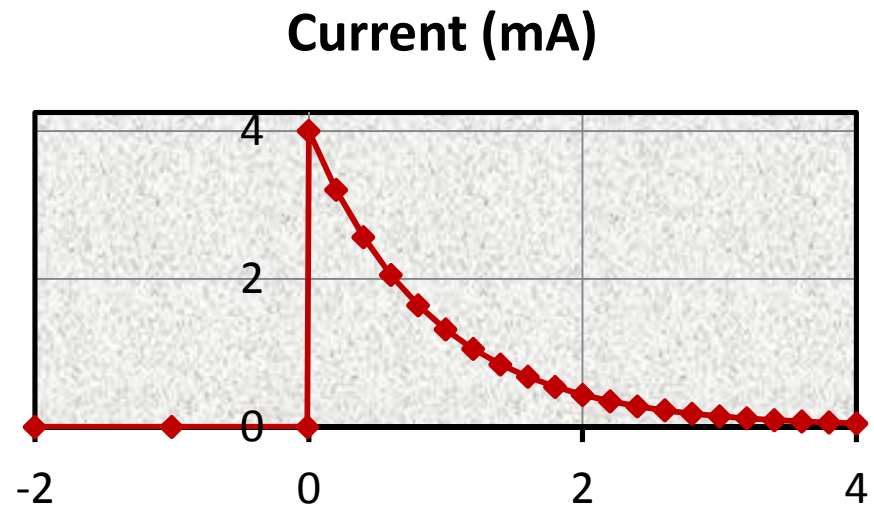


ECE 201, Section 3

Lecture 17

Prof. Peter Bermel
September 28, 2012


Recap: RC Circuits

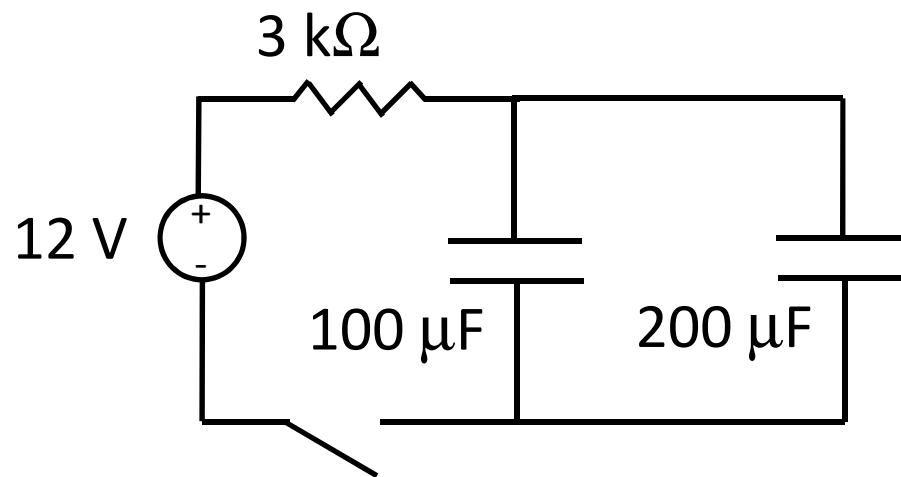

$$Q = Q_f [1 - e^{-t/\tau}]$$


$$I = I_o e^{-t/\tau} \quad (t > 0)$$
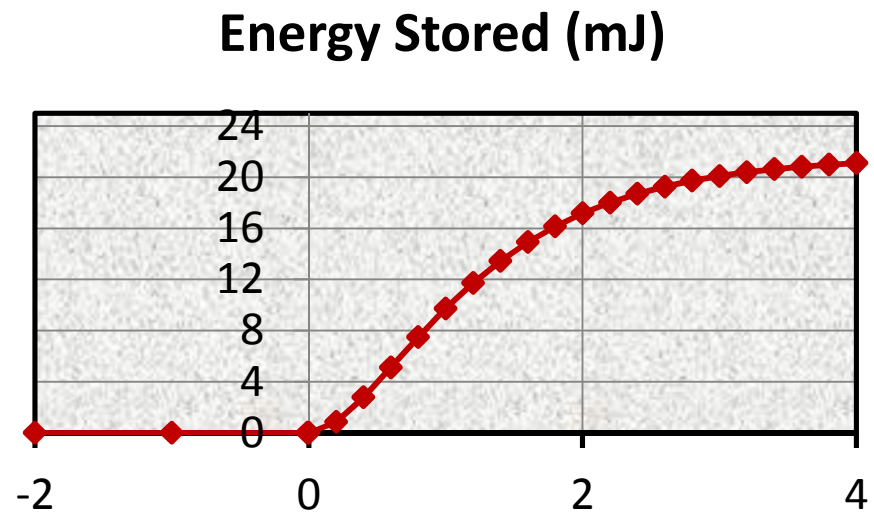
$$U = \frac{1}{2C} [Q_f (1 - e^{-t/\tau})]^2$$



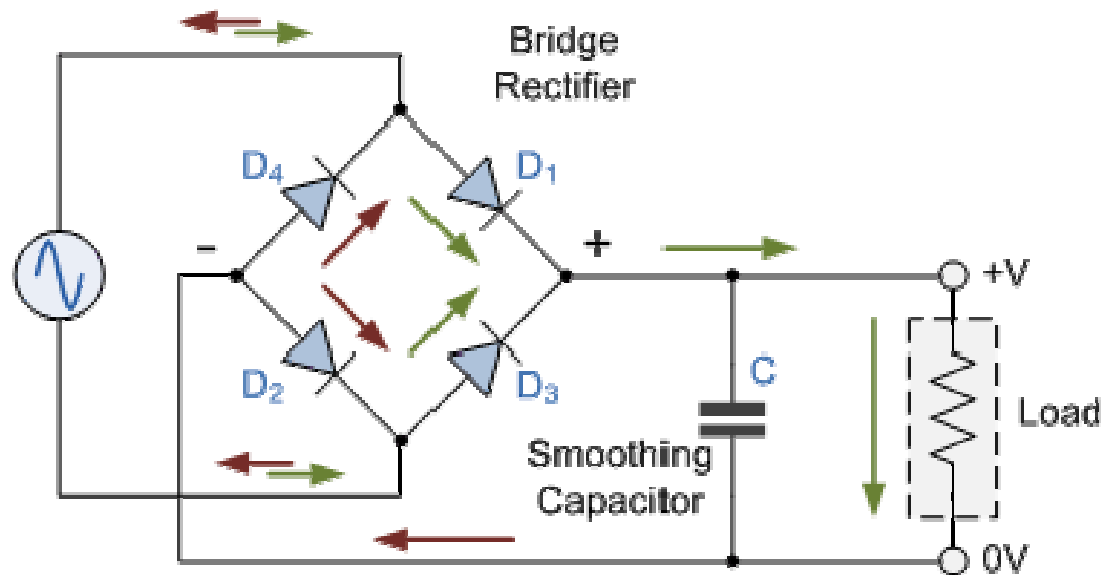Example

- How does this circuit modify a standard AC input voltage? What is its likely purpose?




Solution

- Diodes are a “one-way street” for electrons
- Ideal Diode:

$$I_{out}(t) = \begin{cases} I_{in}(t), & I_{in} > 0 \\ 0, & \text{otherwise} \end{cases}$$




- Realistic (Shockley) Diode:

$$I_{out}(t) = I_s(e^{qV/nkT} - 1)$$

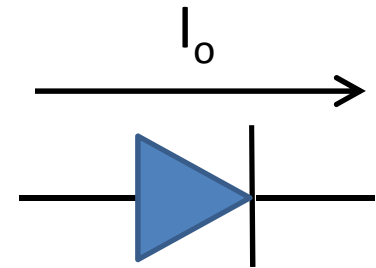

Solution

- Analyzing the diode bridge:

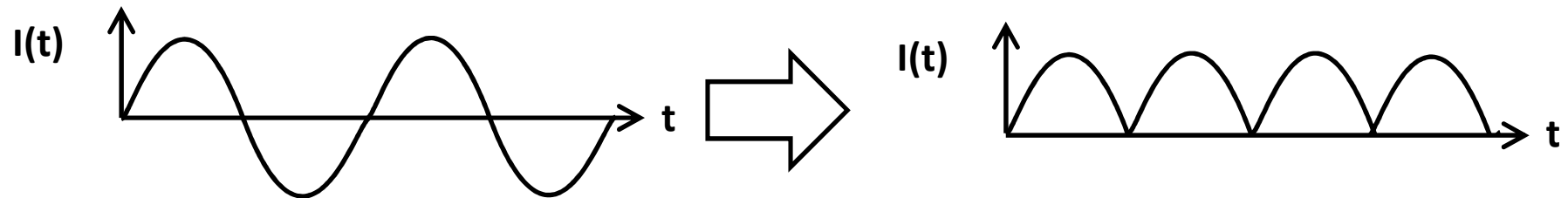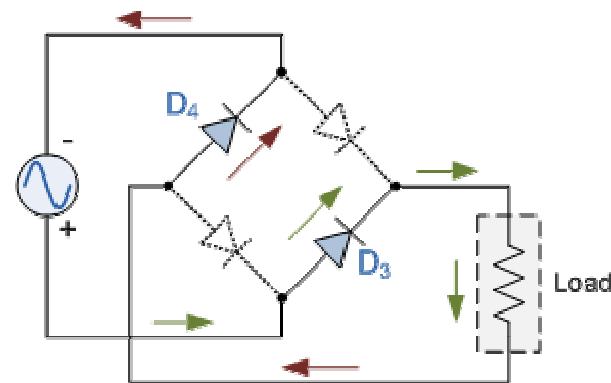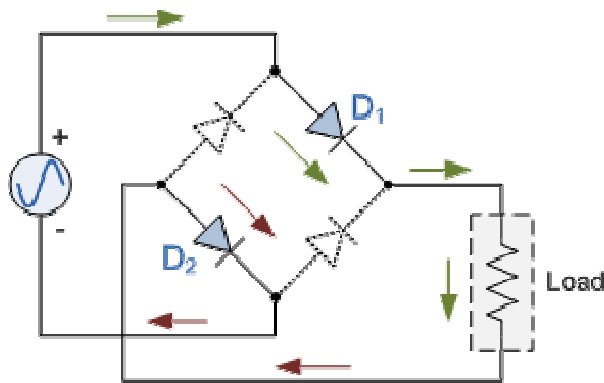


Solution

- Combining the diode bridge output with the capacitor yields:

$$Q = CV(t) = \int_0^t dt' (|I| - I_L)$$

$$V_{rip} \approx I/fC$$

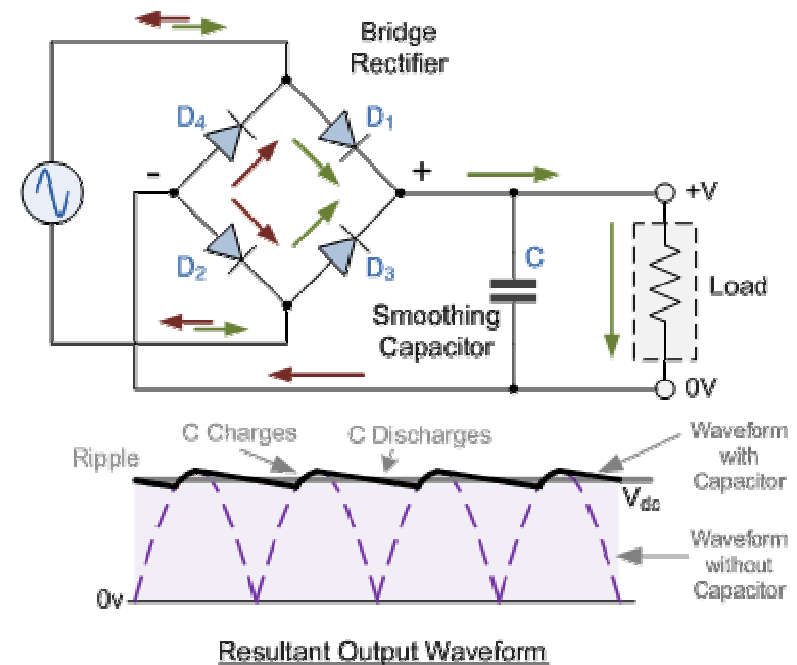- For AC wall plug
 - $R_L = 1 \text{ k}\Omega$, $I = 160 \text{ mA}$, $V_r = 1 \text{ V}$
 - $C > \frac{I}{f(1 \text{ V})} = 2.7 \text{ mF}$



Solving Differential Equations

- Using KVL, RL circuits obey:

$$V = IR + L \frac{dI}{dt}$$

- RC circuits can be written as:

$$V = \frac{1}{C} Q + R \frac{dQ}{dt}$$

- General form decomposes into homogeneous and inhomogeneous equations:

$$0 = Y_h + \tau \frac{dY_h}{dt}$$
$$f = Y_i + \tau \frac{dY_i}{dt}$$

Solving Differential Equations

- Can solve each part separately
 - Homogeneous part:

$$Y_h = -\tau \frac{dY_h}{dt}$$
$$\frac{dY_h}{Y_h} = -\frac{dt}{\tau}$$

- Inhomogeneous part:

$$f = Y_i + \tau \frac{dY_i}{dt}$$
$$Y_i = f, \quad f \text{ constant}$$

Solving Differential Equations

- Use separation of variables and the following rules:

$$\int_{t_o}^{t_1} t^n dt = \frac{t_1^{n+1} - t_o^{n+1}}{n+1}$$

$$\int_{u_o}^{u_1} \frac{du}{u} = \ln u_1 - \ln u_o$$

$$\ln a - \ln b = \ln \frac{a}{b}$$

$$a \ln b = \ln b^a$$

$$e^{a \ln b} = b^a$$

Solving Differential Equations

- We can integrate our homogeneous ODE:

$$\frac{dY_h}{Y_h} = -\frac{dt}{\tau}$$

- To obtain:

$$\int_{Y_i}^{Y_f} \frac{dY_h}{Y_h} = - \int_{t_i}^{t_f} \frac{dt}{\tau}$$

$$\ln \frac{Y_f}{Y_i} = - \left(\frac{t_f - t_i}{\tau} \right)$$

$$Y_f = Y_i e^{-(t_f - t_i)/\tau}$$

Solving Differential Equations

- Overall solution is given by:

$$Y = Y_h + Y_i$$


- For RC or RL circuits, we obtain:

$$Y = Y_i e^{-(t-t_i)/\tau} + f, \quad f \text{ constant}$$


- Where the time constant τ is given by:
 - RL circuits: $\tau=L/R$
 - RC circuits: $\tau=RC$

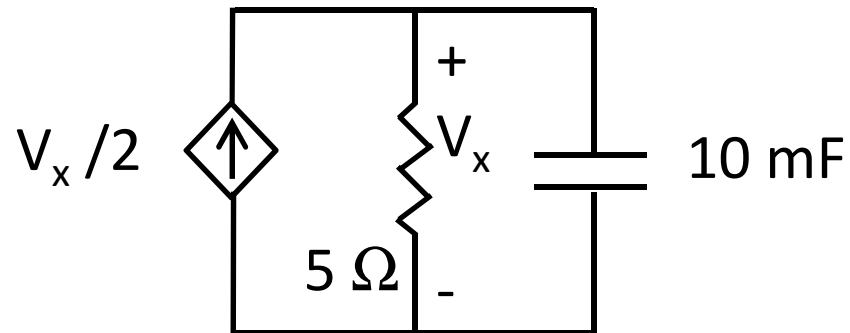Example 1

- What is the voltage response of this circuit as a function of time if $V(0)=1$ mV?



Solution

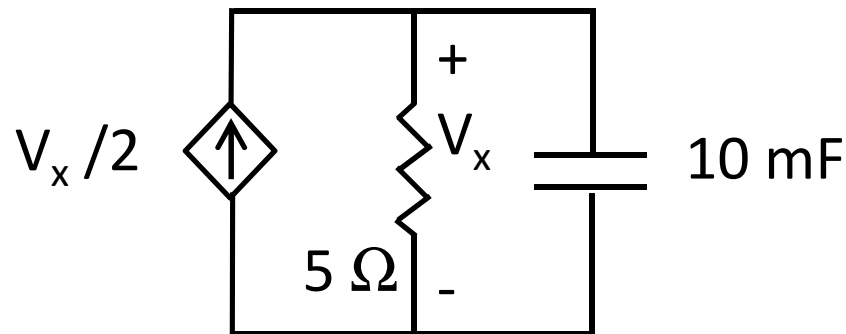


- Calculate Thévenin equivalent for left-hand side:
 - No independent sources, so $V_{oc}=0$
 - Thévenin resistance obtained from KCL:

$$I_A + V_{ab}/2 = V_{ab}/5$$

$$I_A = -3V_{ab}/10$$

$$R_{th} = -10/3$$

Solution

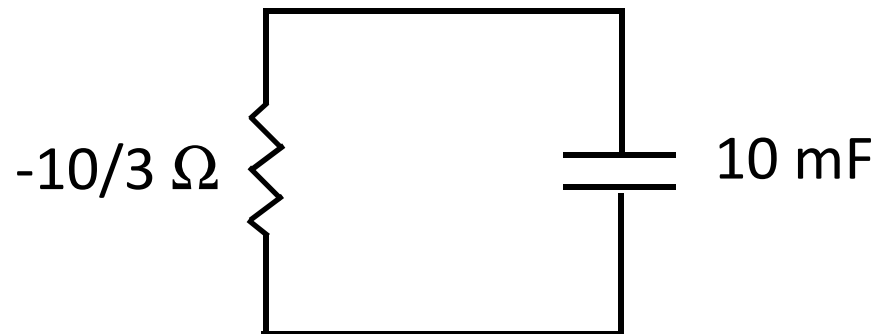

- Applying homogeneous solution from before:

$$Q = Q_o e^{-t/\tau}$$

Since $\tau = RC = -(1/30) \text{ s}$, $V_o = 1 \text{ mV}$, $Q_o = 10 \mu\text{C}$:


$$Q = (10 \mu\text{C}) e^{30t}$$

Charge exceeds that of known universe in:


$$t = \frac{1}{30} \ln \left(\frac{10^{80} \cdot 10^{-19}}{10^{-5}} \right) = 5.06 \text{ s!}$$

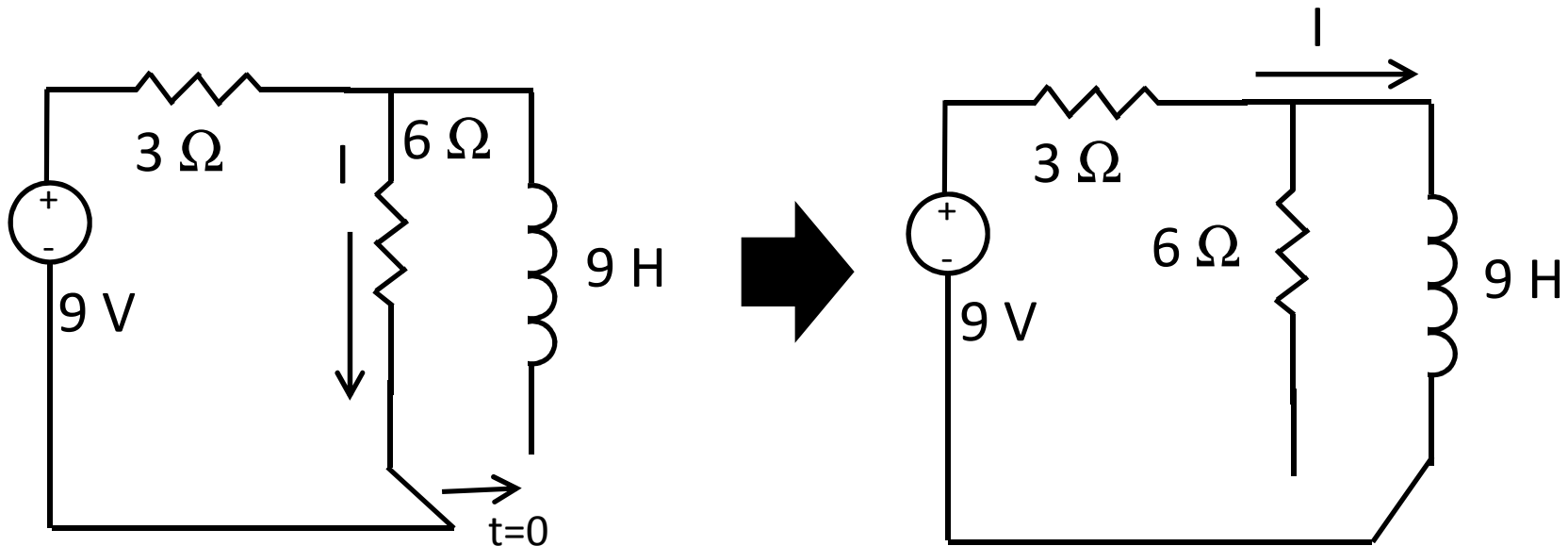Example 2

What is the current flow in this circuit before and after the switch is flipped at time $t=0$?



Solution

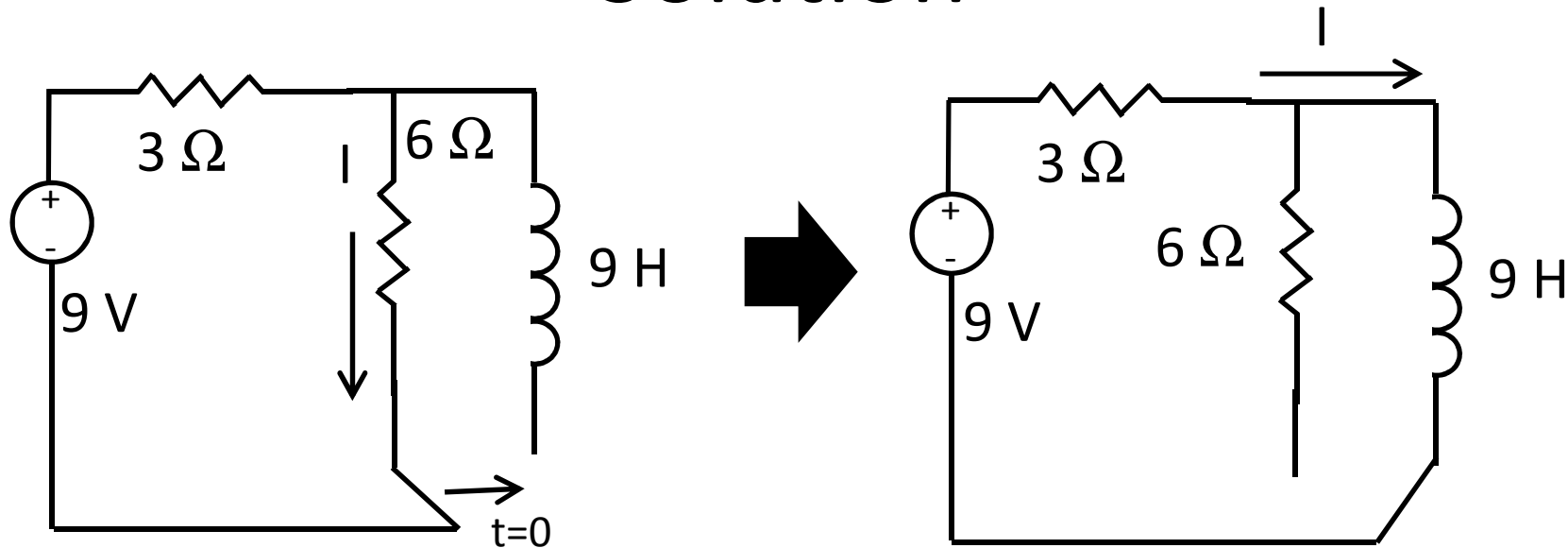


For $t < 0$: $I = (9 \text{ V}) / (9 \text{ } \Omega) = 1 \text{ A}$

For $t > 0$: KVL yields $9 = (3 \text{ } \Omega)I + (9 \text{ H}) \, dI/dt$

Since $L/R=3$, assume solution takes the form:

$$I = 3 - Be^{-t/3}$$

Solution

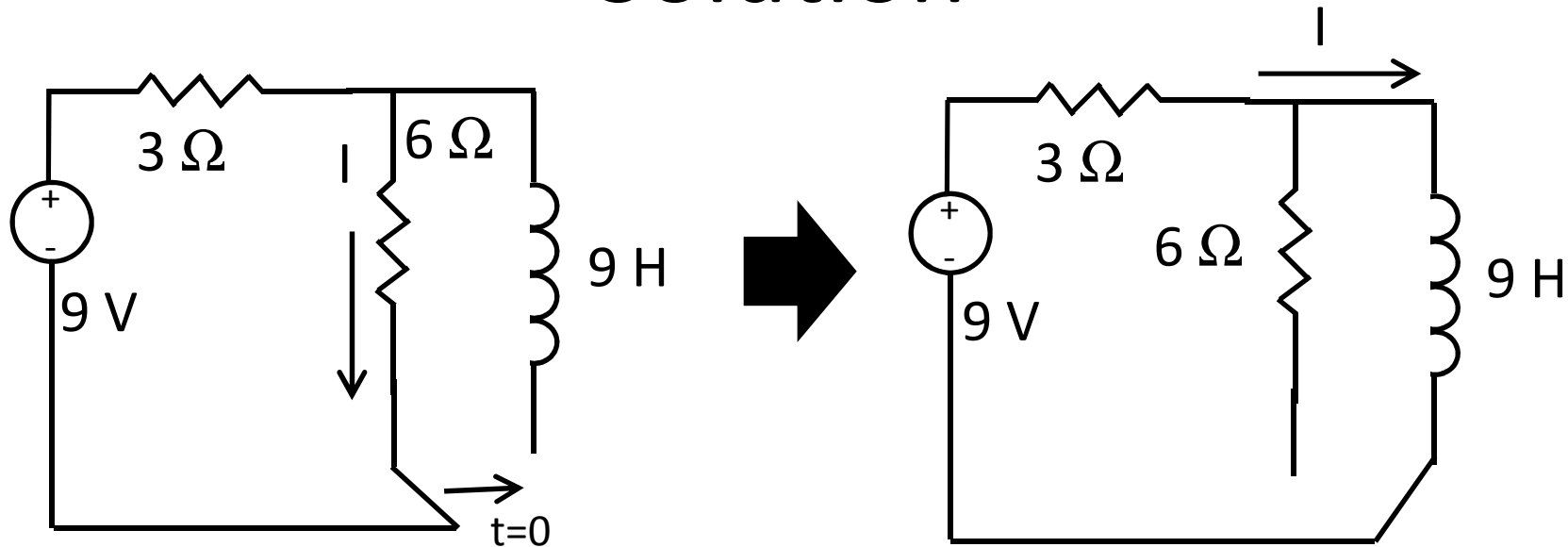

For $t > 0$: $9 = 3 \left[3 - B e^{-\frac{t}{3}} \right] + 9 \frac{B}{3} e^{-\frac{t}{3}}$

B is set by continuity condition for current:

$$I(0) = 0 = 3 - B e^{-t/3}$$

Thus, $B=3$, and $I(t) = 3 \left[1 - e^{-t/3} \right]$, $t > 0$

Homework

- HW #15 due today by 4:30 pm in EE 326B
- HW #16 due Mon.: DeCarlo & Lin, Chapter 7:
 - Problem 11
 - Problem 17 [Corrections: In (a), omit “Is the output ... C_1 ? Why?” In (c), replace “[0, t]” with “[0, 10 ms]”.]