

ECE 201, Section 3

Lecture 18

Prof. Peter Bermel

October 1, 2012

Ordinary Differential Equation Recap

- RL circuits obey:

$$V = IR + L \frac{dI}{dt}$$

- RC circuits can be written as:

$$V = \frac{1}{C} Q + R \frac{dQ}{dt}$$

- Overall solution is given by:

$$Y = Y_h + Y_i$$

- For RC and RL circuits, we obtain:

$$Y = Y_{\infty} + (Y_o - Y_{\infty})e^{-(t-t_o)/\tau}$$


- Where the time constant τ is given by:
 - RL circuits: $\tau=L/R$
 - RC circuits: $\tau=RC$

Solving ODEs


- In presence of stepped voltages, apply conservation laws
- Use values at end of previous interval as initial conditions for next interval
- Best illustrated through examples

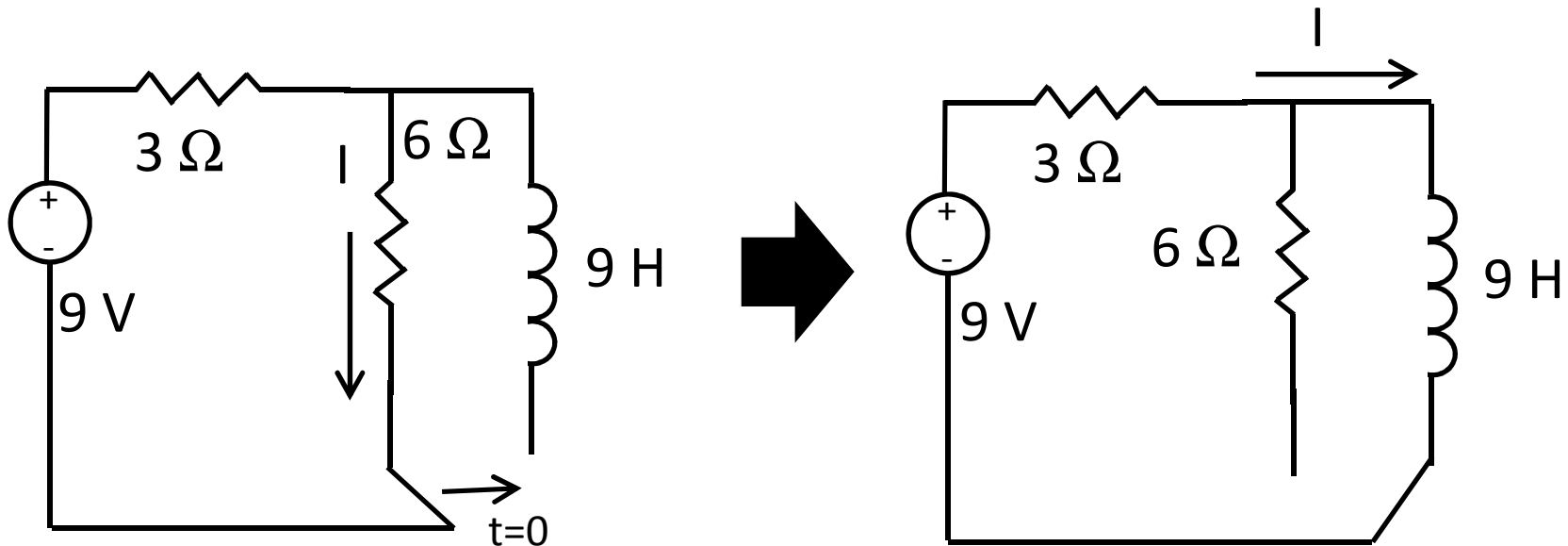Example

What is the current flow in this circuit before and after the switch is flipped at time $t=0$?



Solution

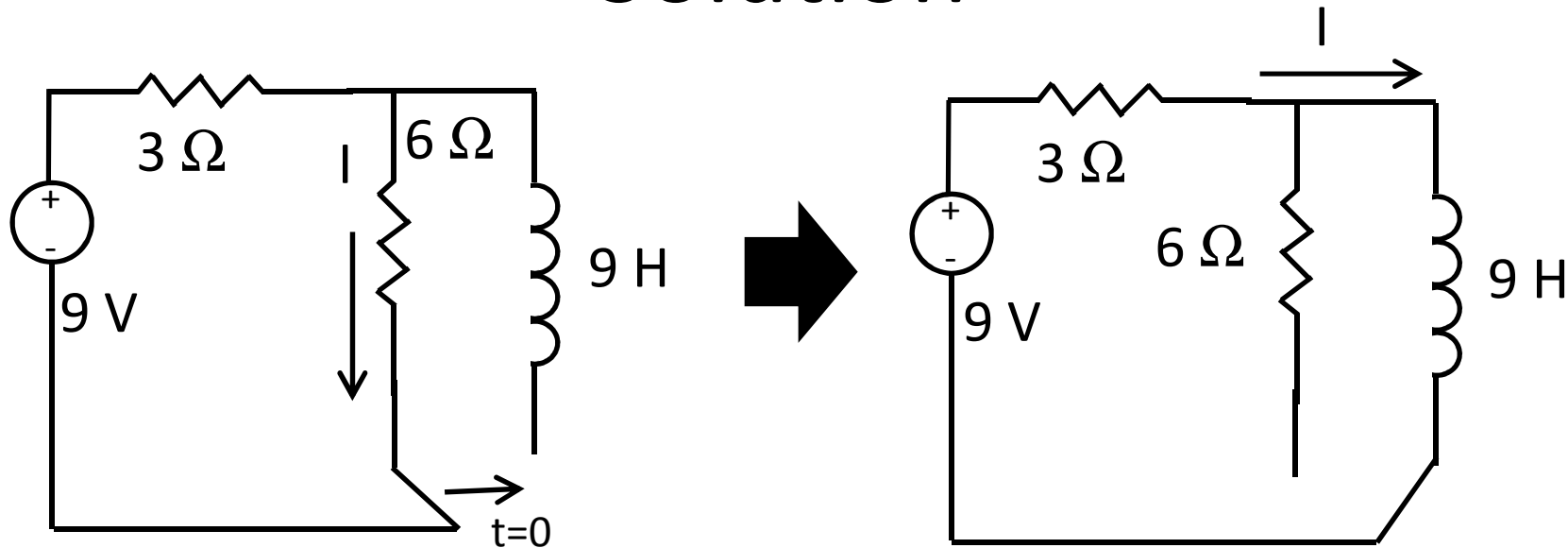


For $t < 0$: $I = (9\text{ V}) / (9\ \Omega) = 1\text{ A}$

For $t > 0$: KVL yields $9 = (3\ \Omega)I + (9\text{ H})\, dI/dt$

Since $L/R=3$, assume solution takes the form:

$$I = 3 - Be^{-t/3}$$

Solution

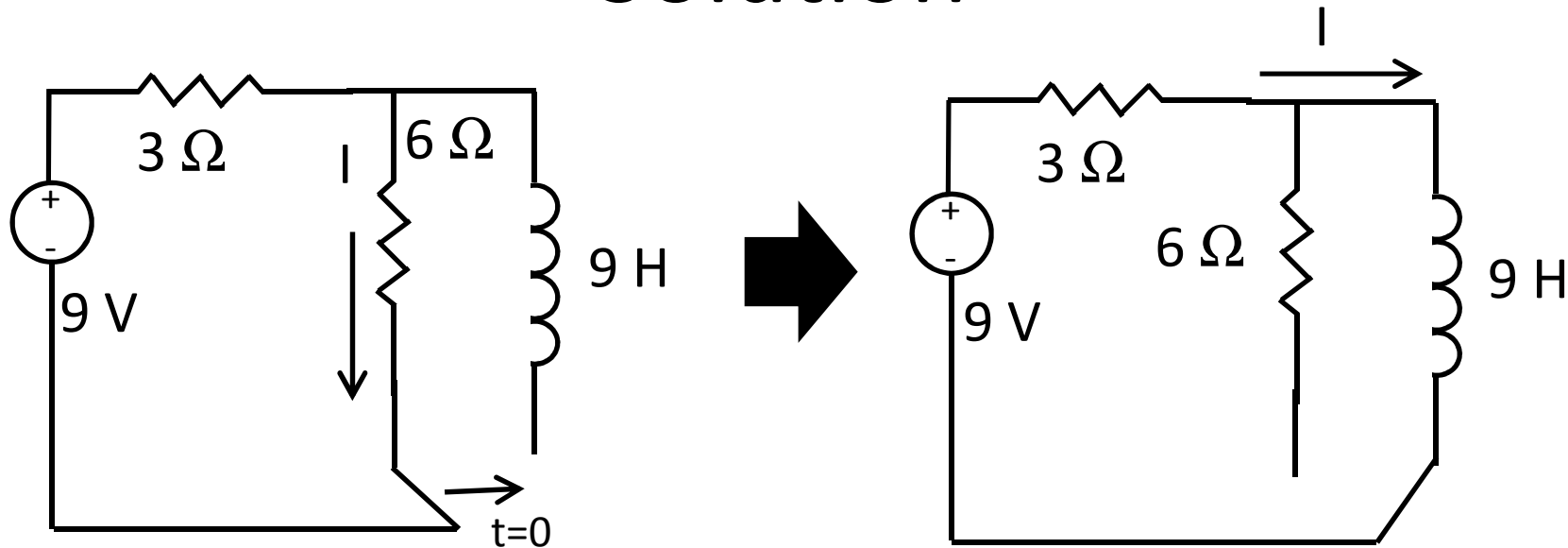

For $t > 0$: $9 = 3\left[3 - Be^{-\frac{t}{3}}\right] + 9\frac{B}{3}e^{-\frac{t}{3}}$


B is set by continuity condition for current:

$$I(0) = 0 = 3 - Be^{-t/3}$$

Thus, $B=3$, and $I(t) = 3\left[1 - e^{-t/3}\right]$, $t > 0$

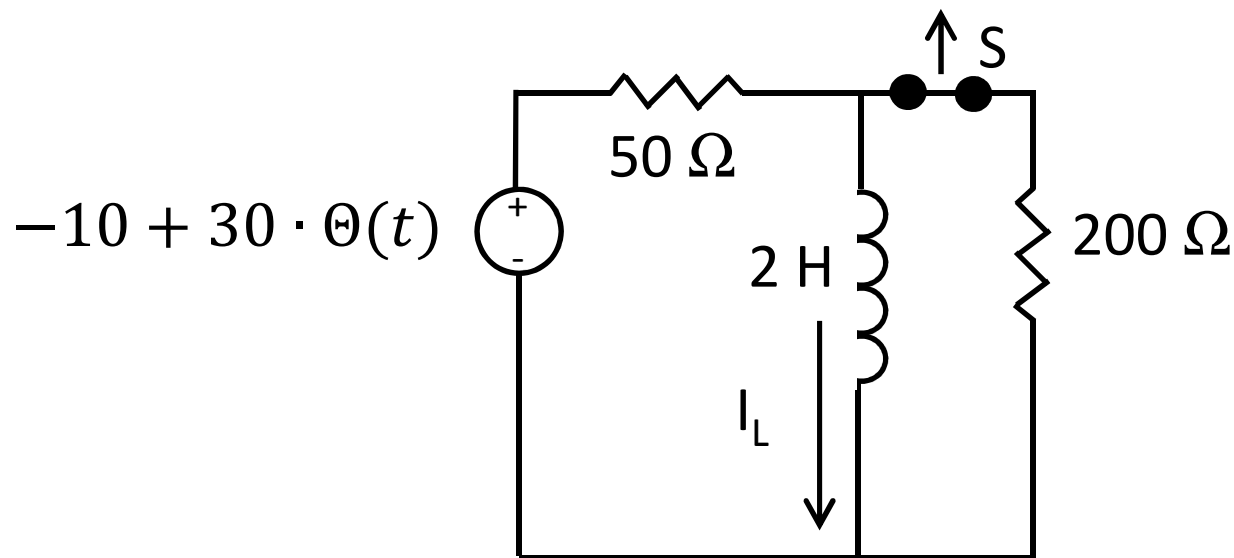
Example

- What current flows through the inductor for $t > 0$? How does that change if the switch S opens after 50 ms?



Solution

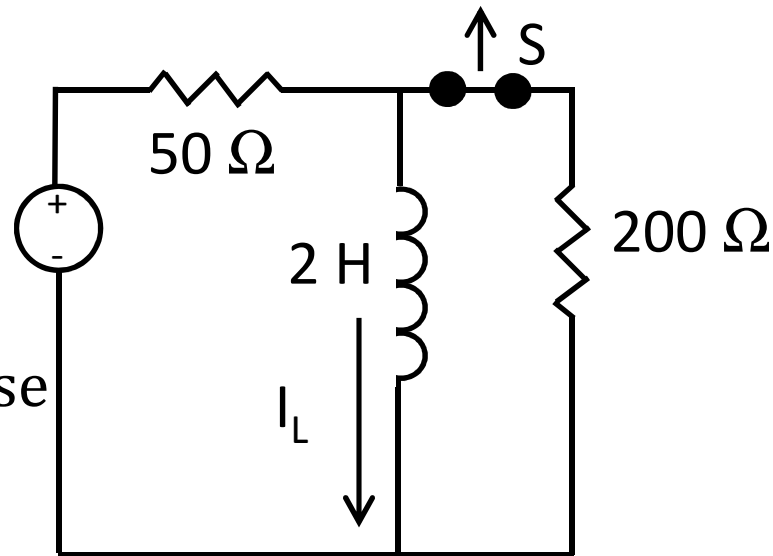
$$\Theta(t) = \begin{cases} -10 + 30 \cdot \Theta(t) & t < 0 \\ 0, & t < 0 \\ 1, & \text{otherwise} \end{cases}$$



- Steady state response for $t < 0$: $I = -10/50 = -0.2$ A
- After $t=0$: $R_{th} = 40$ Ω; $\tau = L/R_{th} = 2/40 = 0.05$ s;
 $I_{\infty} = 20/50 = 0.4$ A

$$I_L = 0.4 + (-0.2 - 0.4)e^{-20t}$$

Solution

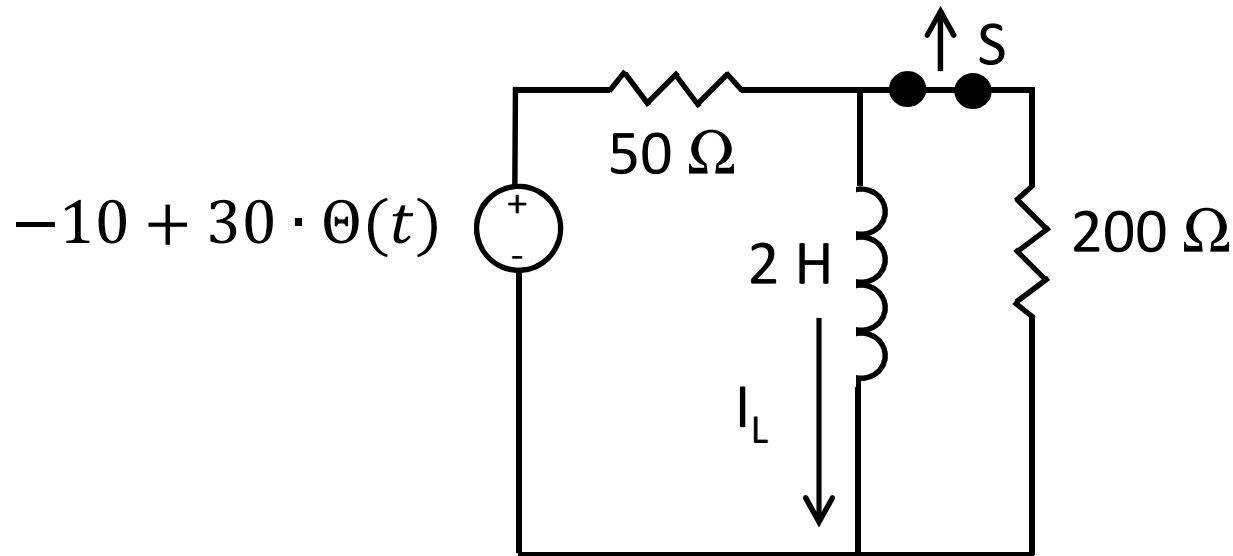


- If switch activates after 50 ms:


$$I_L = \begin{cases} 0.4 - 0.6e^{-20t}, & 0 \leq t < 0.05 \\ 0.4 - 0.222e^{-25t}, & 0.05 \leq t \end{cases}$$

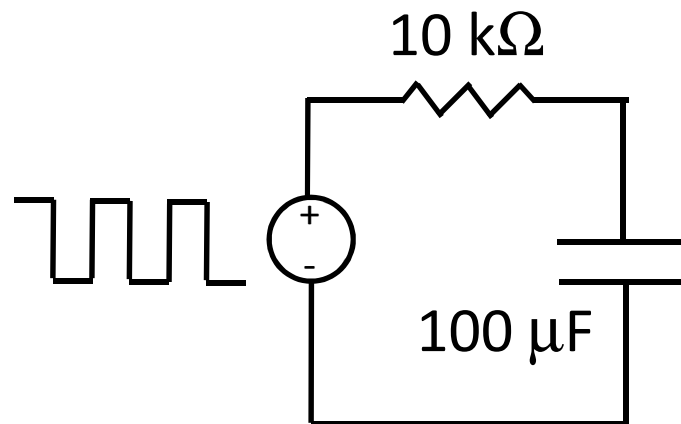Example

- What is the voltage as a function of time in this RC circuit with an AC square wave source at 1 Hz, and voltage varying from 0 to 1 V?




Solution

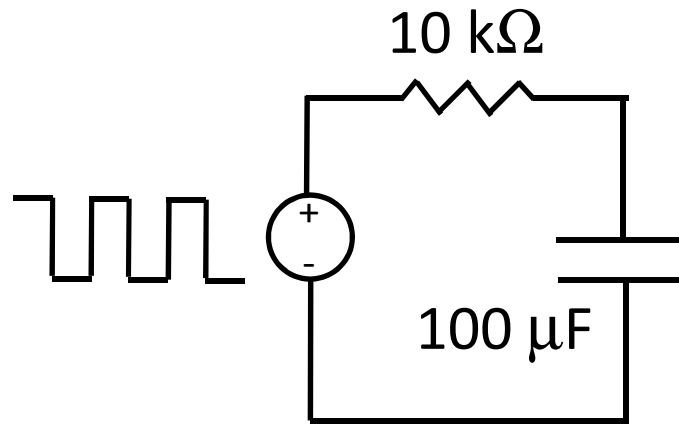

- In the presence of a periodic waveform, we must also have a periodic solution $V_c(t + mT) = V_c(t)$, for all integer m . The latter function is:

$$V_c(t) = \begin{cases} 1 + (v_o - 1)e^{-t}, & 0 \leq t < 0.5 \\ v_{1/2}e^{-(t-1/2)}, & 0.5 \leq t < 1 \end{cases}$$

Solution

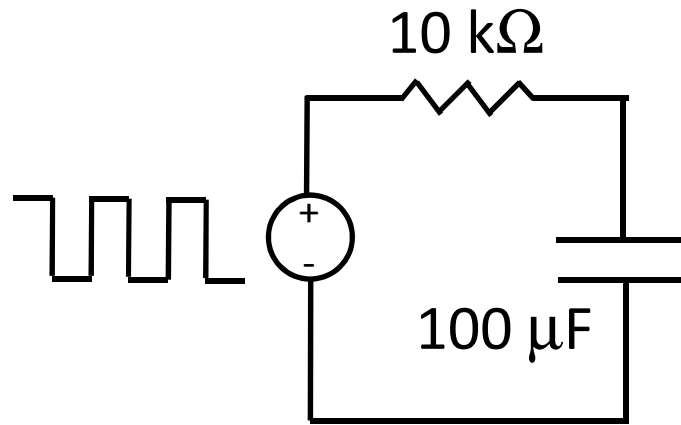

- Our continuity conditions yield:


$$v_{1/2} = 1 + (v_o - 1)e^{-1/2}$$

$$v_o = v_{1/2} e^{-1/2}$$

- Combining terms:

$$v_o e^{1/2} = 1 + (v_o - 1)e^{-1/2}$$

Solution

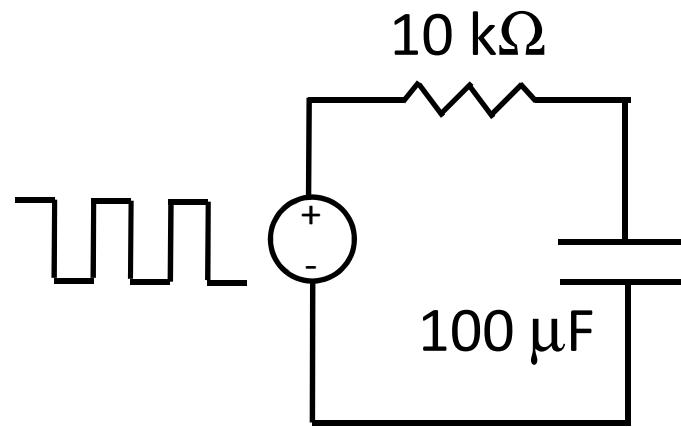

- Rearranging:

$$v_o(e^{1/2} - e^{-1/2}) = 1 - e^{-1/2}$$


- Numerically evaluating:

$$v_o = 0.377$$

$$v_{1/2} = 0.622$$

Solution

Voltage (V)

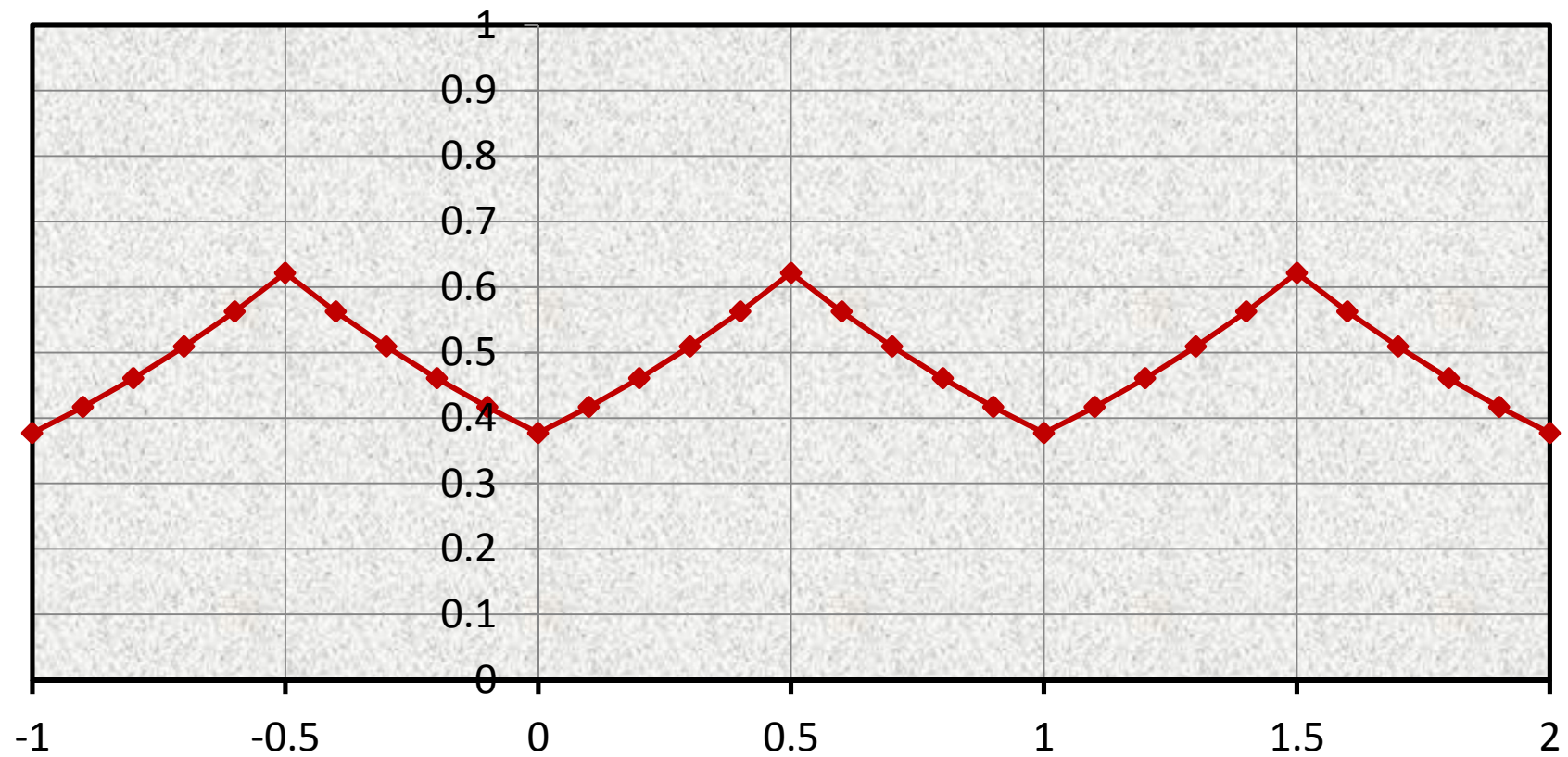


Linearity


- Much like with networks of resistors and sources, networks with capacitors and resistors obey these principles:
 - Linearity
 - Superposition
 - Proportionality
- Initial conditions can be viewed as another superimposed source that shuts off at the beginning

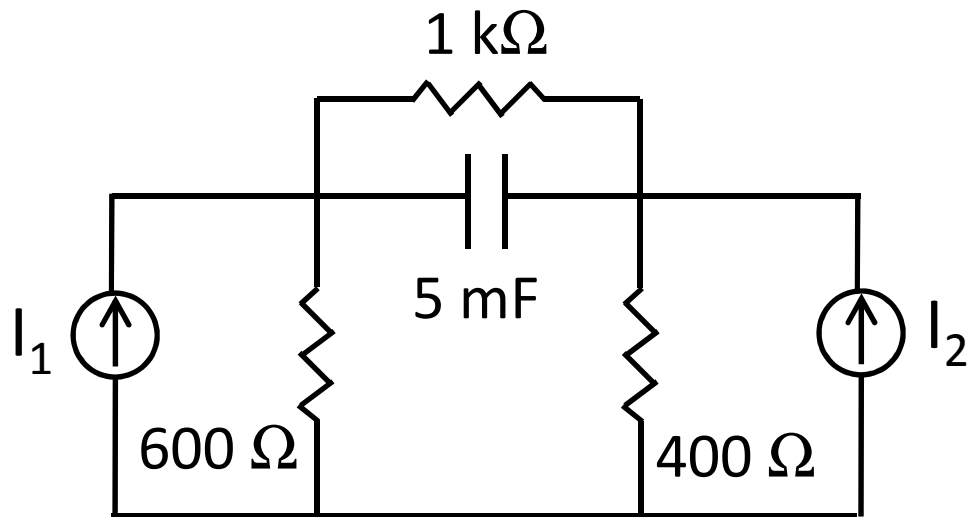Example

- Using superposition, calculate V_C for zero input ($V_o=25$ V), I_1 only (50 mA), I_2 only (25 mA), all combined, and when the sources are cut in half.




Solution

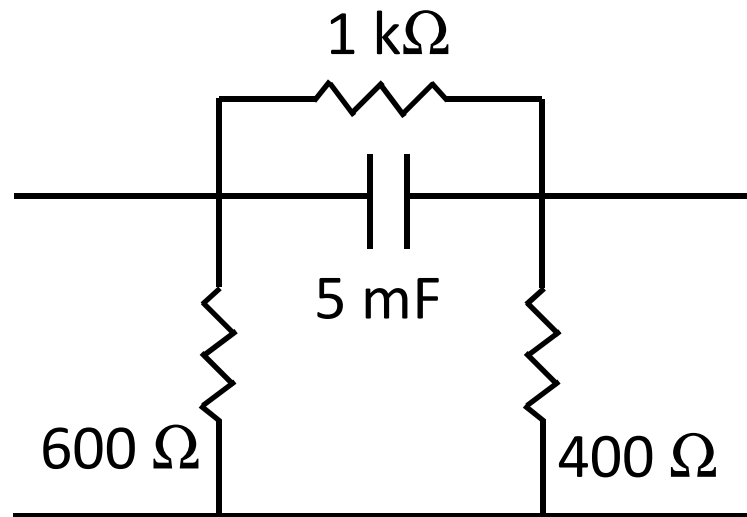

- V_C for zero input: capacitor sees two resistors of $1\text{ k}\Omega$; $R_{th} = 500\text{ }\Omega$:

$$V_C = 25 e^{-0.4t}$$


Solution

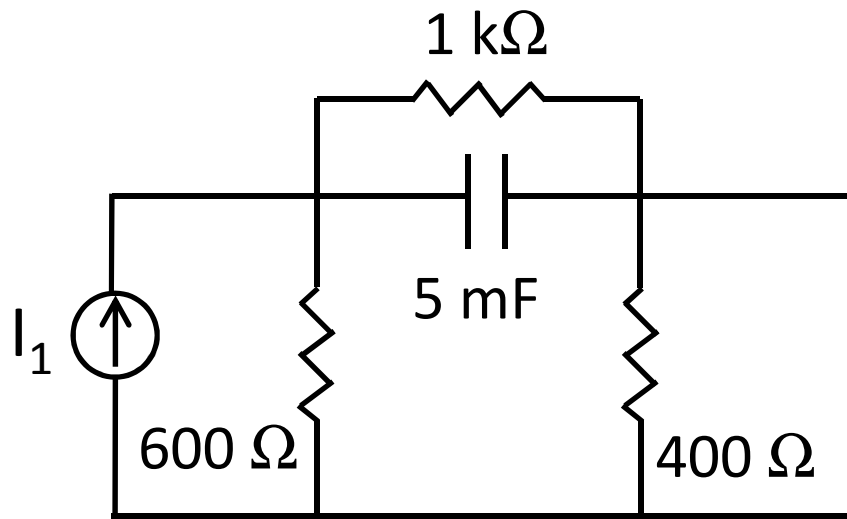

V_C from I_1 only: source transformation yields $V_{oc}=30\ \text{V}$;
combine series resistors; transform for $I_{sc}=30\ \text{mA}$;
 $R_{th}=500\ \Omega$; transform again for $V_{oc}=15\ \text{V}$. With
 $\tau=(5\ \text{mF})(500\ \Omega)=2.5\ \text{s}$, we obtain:

$$V = 15(1 - e^{-0.4t})$$


Solution

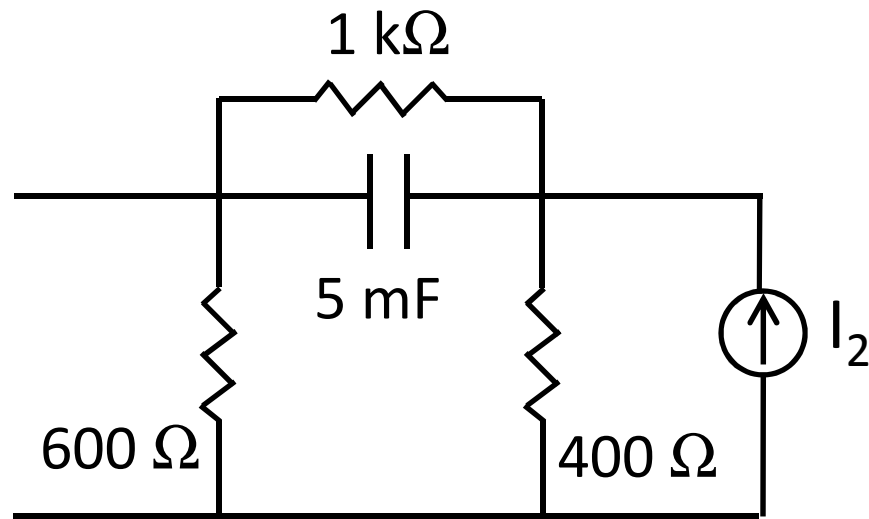

V_C from I_2 only: source transformation yields $V_{oc} = -10\ \text{V}$; combine series resistors; transform for $I_{sc} = -10\ \text{mA}$; $R_{th} = 500\ \Omega$; transform again for $V_{oc} = -5\ \text{V}$. With $\tau = (5\ \text{mF})(500\ \Omega) = 2.5\ \text{s}$, we obtain:

$$V = -5(1 - e^{-0.4t})$$

Solution

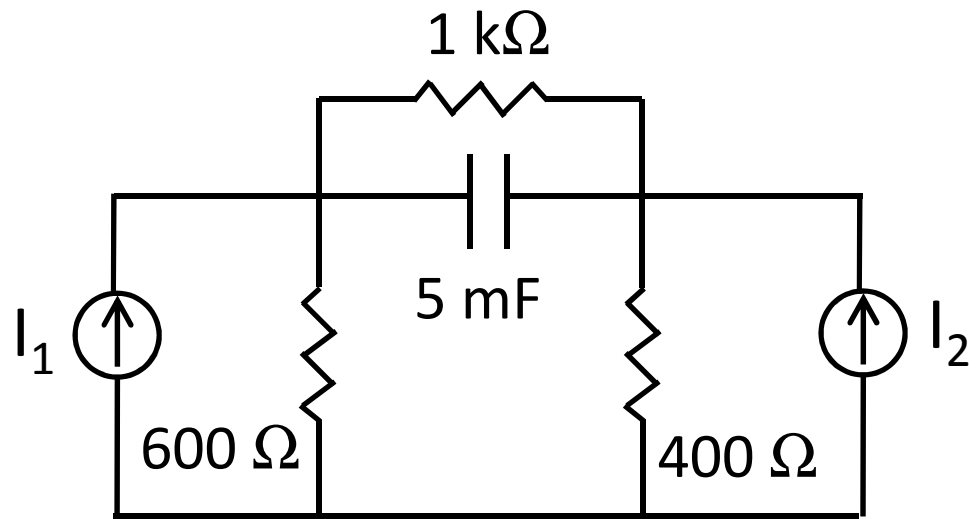

Putting everything together, we obtain:

$$V = 10 + 15e^{-0.4t}$$

If the input sources are both cut in half, we get:

$$V = 5 + 20e^{-0.4t}$$

Homework

- HW #16 due today by 4:30 pm in EE 326B
- HW #17 due Wed.: DeCarlo & Lin, Chapter 7:
 - Problem 35
 - Problem 37
 - Problem 43
 - Problem 45
- HW #18 due Fri.: DeCarlo & Lin, Chapter 8:
 - Problem 1
 - Problem 5
 - Problem 6