

ECE 201, Section 3

Lecture 19

Prof. Peter Bermel

October 5, 2012

Solving Ordinary Differential Equations


- For RC and RL circuits, we obtain:

$$X = X_{\infty} + (X_o - X_{\infty})e^{-(t-t_o)/\tau}$$


- Solution steps:
 - Choose X
 - RC circuits: $X=Q$ or $X=V$
 - LR circuits: $X=I$
 - Find X_o (simplifying diagram)
 - Find X_{∞} (simplifying diagram)
 - Find R_{th} (for inductor/capacitor)
 - Find time constant τ :
 - RL circuits: $\tau = L/R_{th}$
 - RC circuits: $\tau = R_{th}C$
 - If circuit changes at t_1 , use $X(t_1)$ from prior solution for initial values

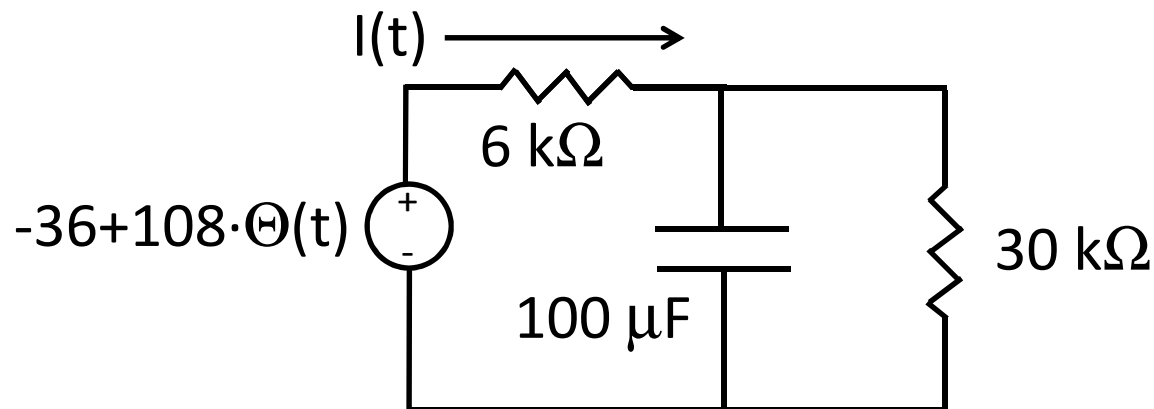Example 1

- For this RC circuit, find the current flow $I(t)$ at all times, including the discontinuity at $t=0$.




Solution

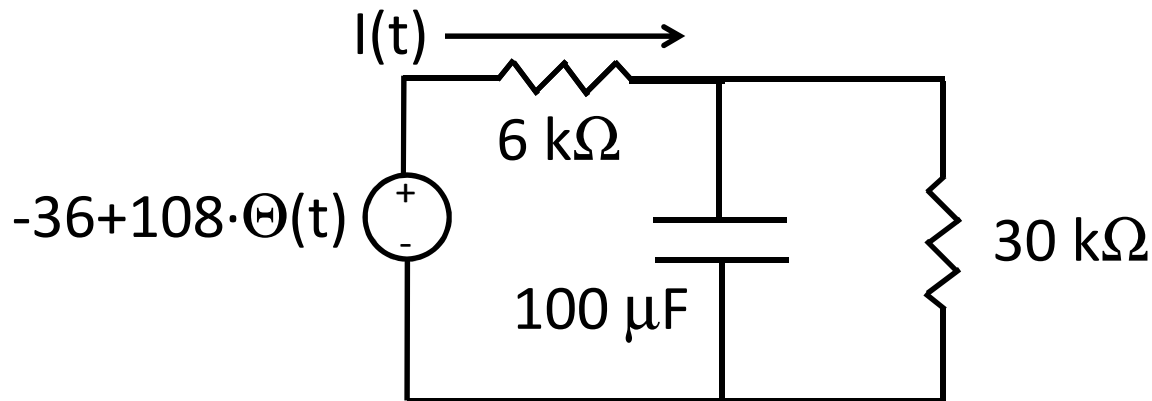

- For $t < 0$: no capacitor current,
 $I = (-36 \text{ V}) / (30 + 6 \text{ k}\Omega) = -1 \text{ mA}$
 $V_C = (30/36) * (-36 \text{ V}) = -30 \text{ V}$
- At $t = 0^+$, V_C is continuous, so $I = (72 + 30) / 6 = 17 \text{ mA}$
- As $t \rightarrow \infty$, $I = 2 \text{ mA}$
- Time constant $\tau = R_{th} C = (5 \text{ k}\Omega) * (100 \mu\text{F}) = 0.5 \text{ s}$

Solution

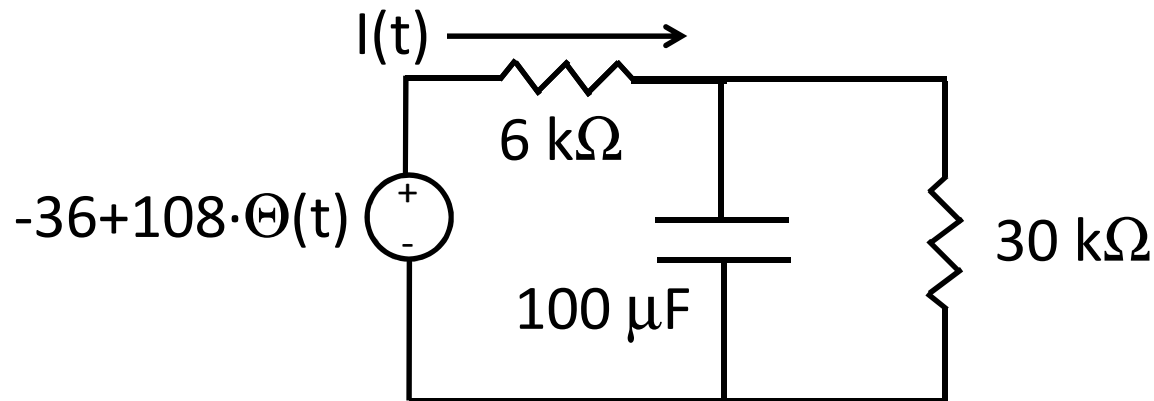


- Matching our solution with the boundary conditions yields:

$$I = \begin{cases} -1 \text{ mA}, & t < 0 \\ 2 + 15e^{-2t}, & t > 0 \end{cases}$$

Solution

Current (mA)

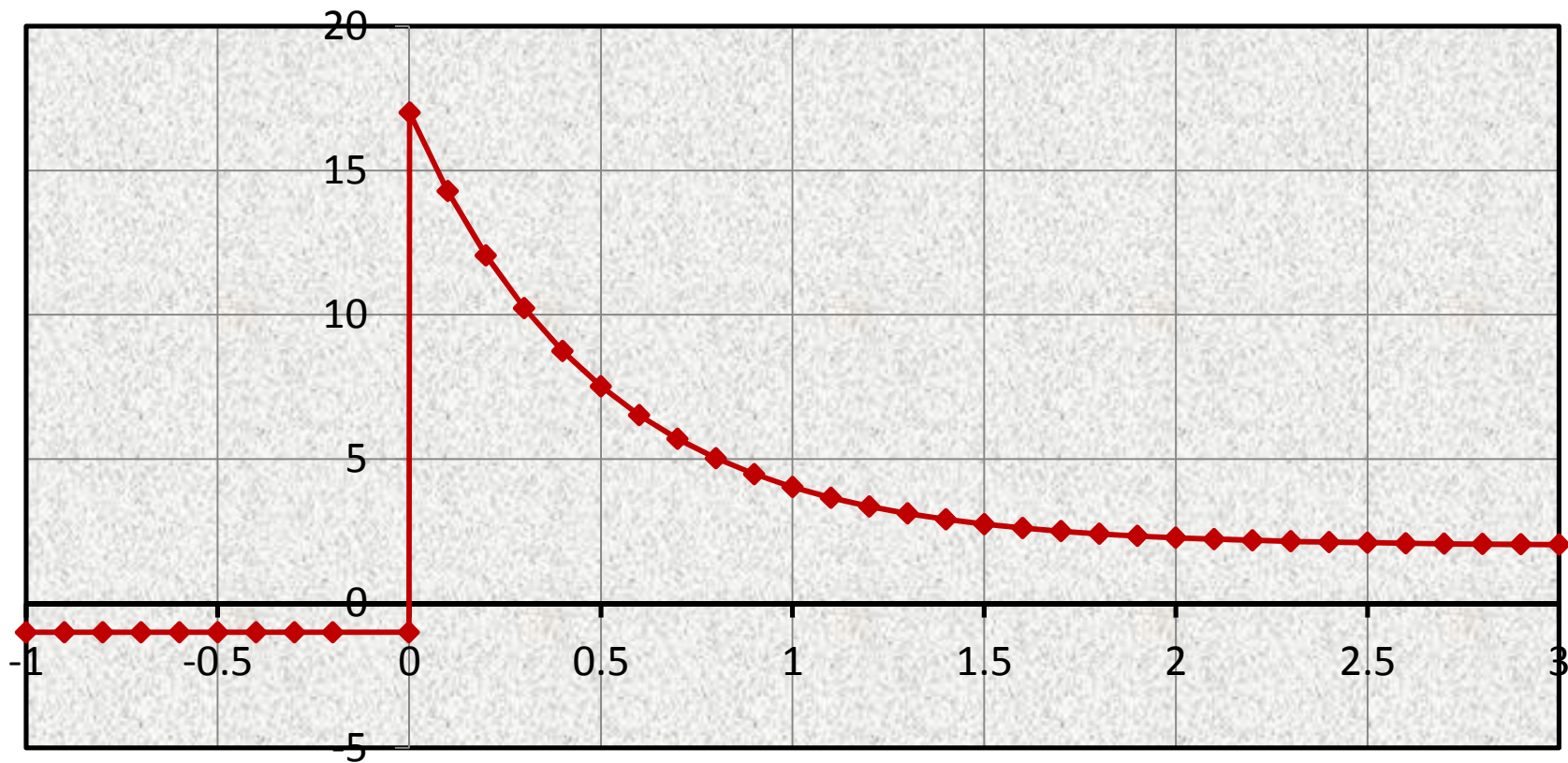


Linearity


- Much like with networks of resistors and sources, networks with capacitors and resistors obey these principles:
 - Linearity
 - Superposition
 - Proportionality
- Initial conditions can be viewed as another superimposed source that shuts off at the beginning

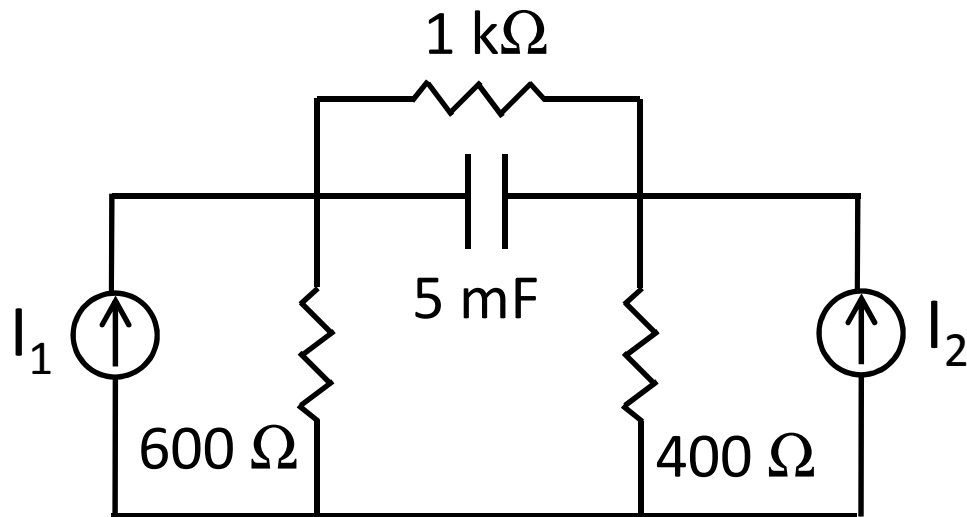Example 2

- Using superposition, calculate V_C for zero input ($V_o=25$ V), I_1 only (50 mA), I_2 only (25 mA), all combined, and when the sources are cut in half.




Solution

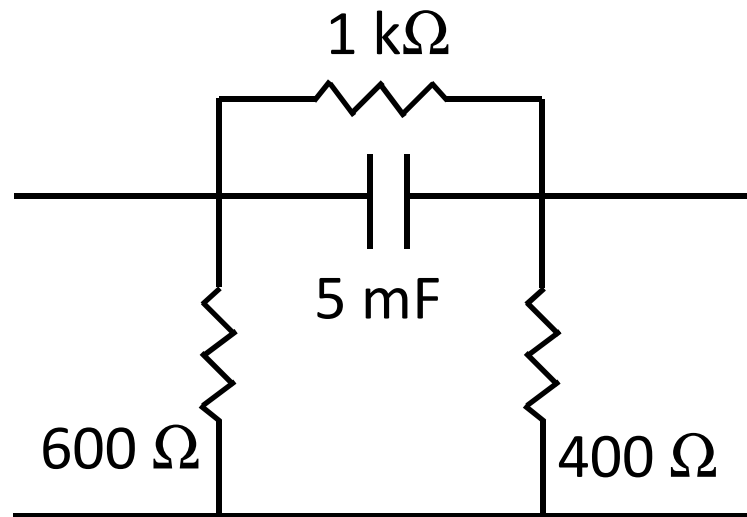

- V_C for zero input: capacitor sees two resistors of $1 \text{ k}\Omega$; $R_{th} = 500 \text{ }\Omega$:

$$V_C = 25 e^{-0.4t}$$


Solution

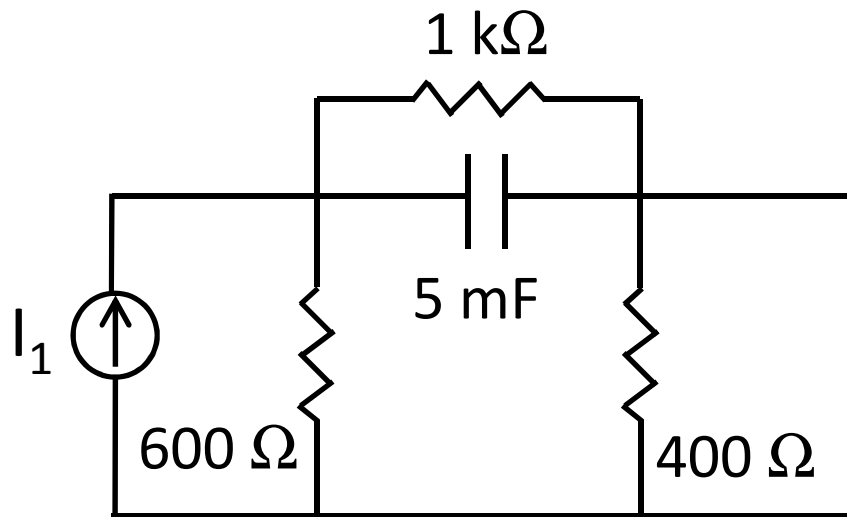

V_C from I_1 only: source transformation yields $V_{oc}=30\ \text{V}$;
combine series resistors; transform for $I_{sc}=30\ \text{mA}$;
 $R_{th}=500\ \Omega$; transform again for $V_{oc}=15\ \text{V}$. With
 $\tau=(5\ \text{mF})(500\ \Omega)=2.5\ \text{s}$, we obtain:

$$V = 15(1 - e^{-0.4t})$$


Solution

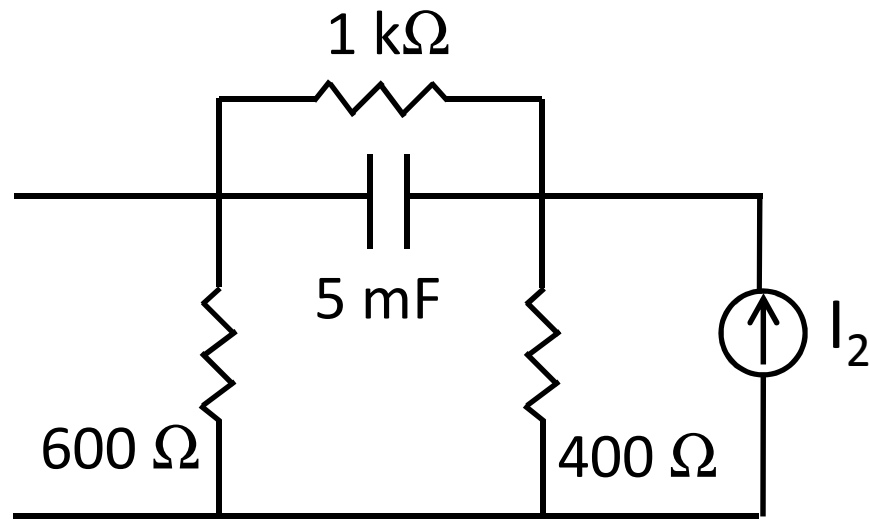

V_C from I_2 only: source transformation yields $V_{oc} = -10\ \text{V}$; combine series resistors; transform for $I_{sc} = -10\ \text{mA}$; $R_{th} = 500\ \Omega$; transform again for $V_{oc} = -5\ \text{V}$. With $\tau = (5\ \text{mF})(500\ \Omega) = 2.5\ \text{s}$, we obtain:

$$V = -5(1 - e^{-0.4t})$$

Solution

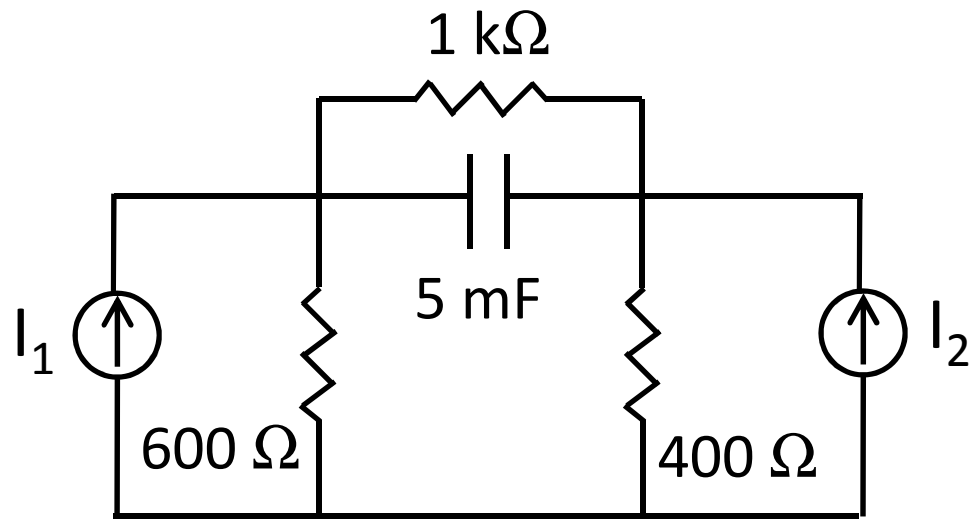

Putting everything together, we obtain:


$$V = 10 + 15e^{-0.4t}$$

If the input sources are both cut in half, we get:


$$V = 5 + 20e^{-0.4t}$$

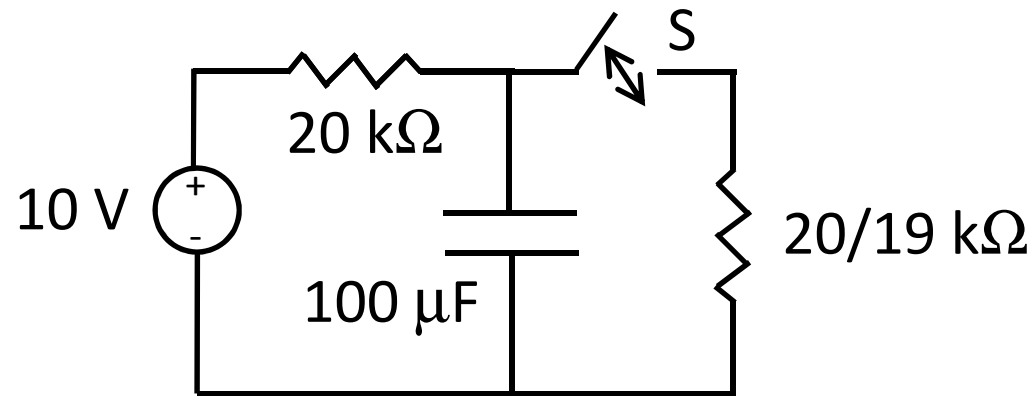Example 3

- What waveform is produced by this circuit with a mechanical switch S that flips on for 1 s, then off for 1 s, and so on?




Solution

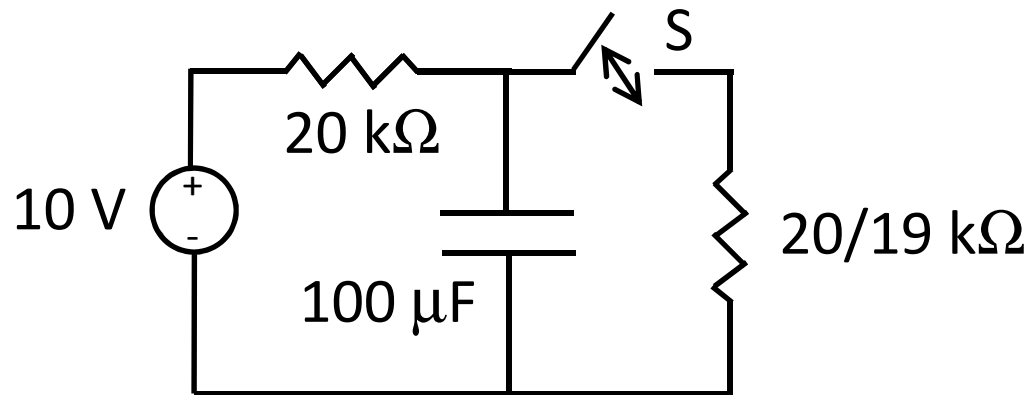

- Consider 2 cases separately:
 - Switch open: $RC = (20 \text{ k}\Omega)(100 \text{ }\mu\text{F}) = 2 \text{ s}$, $V_{\infty} = 10 \text{ V}$
 - Switch closed: $RC = (1 \text{ k}\Omega)(100 \text{ }\mu\text{F}) = 0.1 \text{ s}$, $V_{\infty} = 0.5 \text{ V}$
- After closing switch, will quickly reach final value

Solution

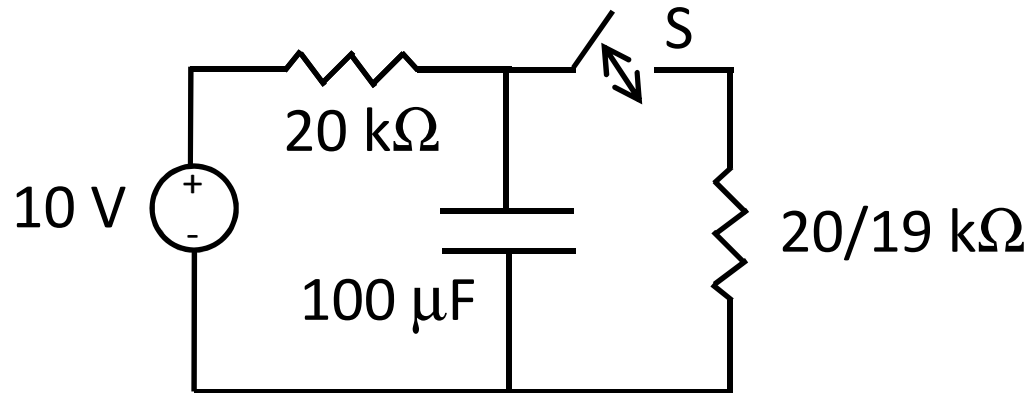


- Thus, to an excellent approximation:

$$V_C(t) = \begin{cases} 10 - 9.5e^{-t/2}, & 0 \leq t < 1 \\ 0.5 + 3.74e^{-10(t-1)}, & 1 \leq t < 2 \end{cases}$$

Solution

Voltage (V)

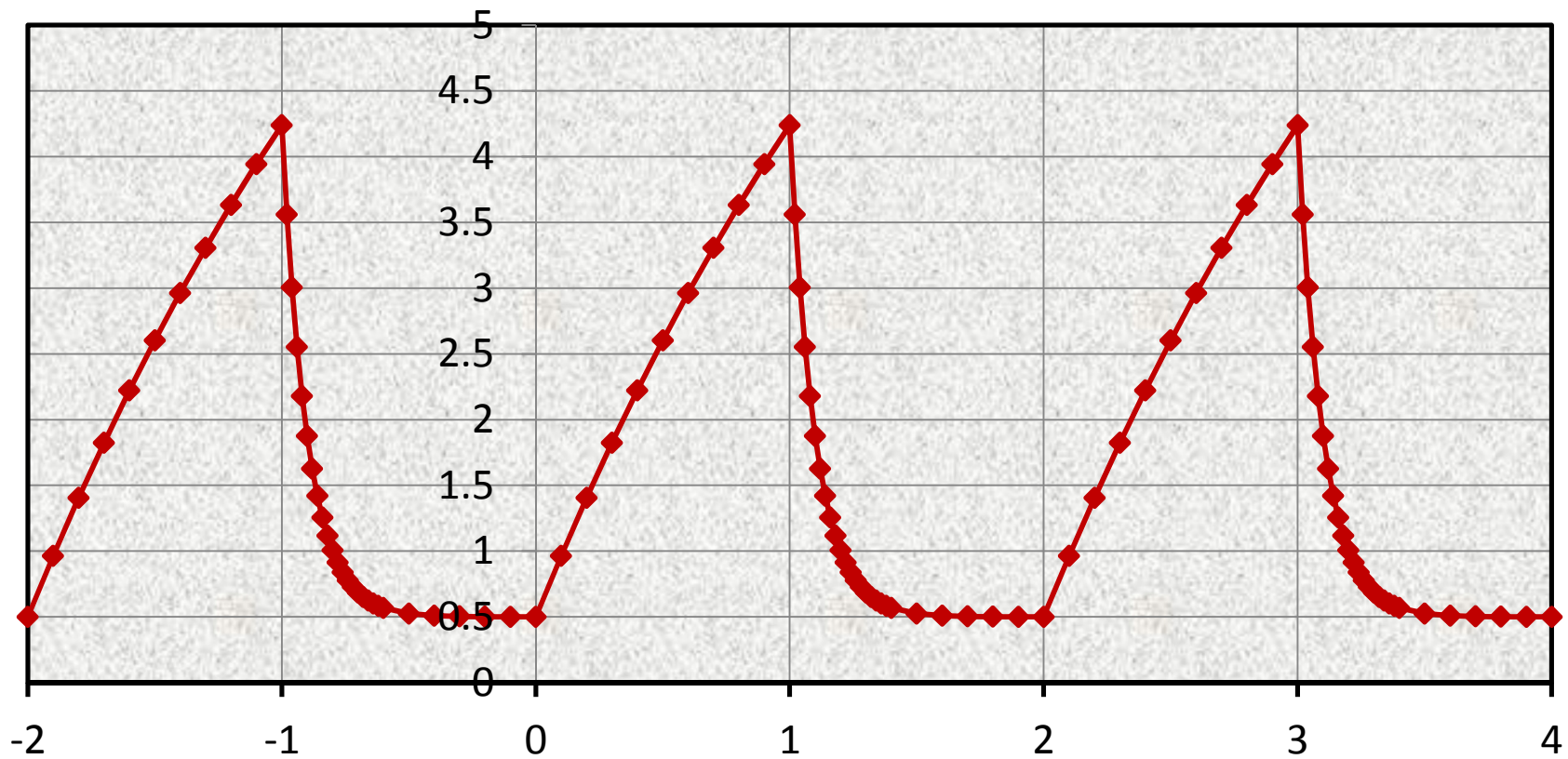

Homework

- HW #18 due today by 4:30 pm in EE 326B
- HW #19 due Wed.: DeCarlo & Lin, Chapter 8:
 - Problem 18(a),(b)
 - Problem 21(a),(b)
 - Problem 22