

ECE 201, Section 3

Lecture 2

Prof. Peter Bermel

August 22, 2012

Homework Announcements

- Due at 4:30 pm on the listed date at EE 325B (Wanda Dallinger's office)
- Please write "ECE201-3" and your name at the top legibly when you submit the homework


Office Hours in EE 026

Time	Monday	Tuesday	Wednesday	Thursday	Friday	
8:30 - 9:00						
9:00 - 9:30						
9:30 - 10:00						
10:00 - 10:30						
10:30 - 11:00						
11:00 - 11:30						
11:30 - 12:00						
12:00 - 12:30						
12:30 - 1:00						
1:00 - 1:30						
1:30 - 2:00						
2:00 - 2:30						
2:30 - 3:00						
3:00 - 3:30						
3:30 - 4:00						
4:00 - 4:30						
4:30 - 5:00						
						Total
Andrew	3.5	4.5	3.5	1.5		13
Bharath		1.5	3.5	2	4	13
John	3	3	3	4		13
Tanmay	3.5	1	3.5	2	3	13
Amir					3	3
Alejandro	5.5		2.5	3	2.5	13.5


Voltage

- Defined as a difference in electric potential
- Given in units of volts, or joules per coulomb
- Energy $E = qV$
- Voltage drop V_{AB} between two points is:
 - Path-independent ($V_{AB} = V_A - V_B$)
 - Unique
 - Directionally dependent (e.g., $V_{AB} = -V_{BA}$,
 $V_A - V_B = -(V_B - V_A)$)

Example 1

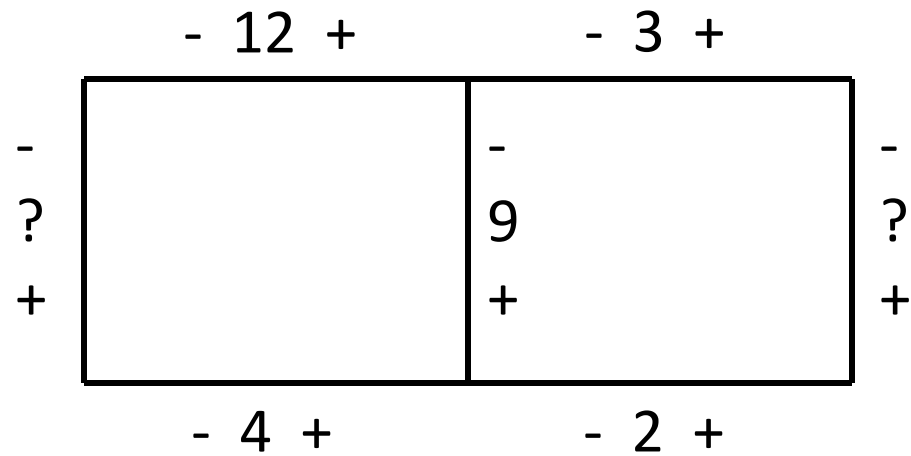

Example 1: Solution

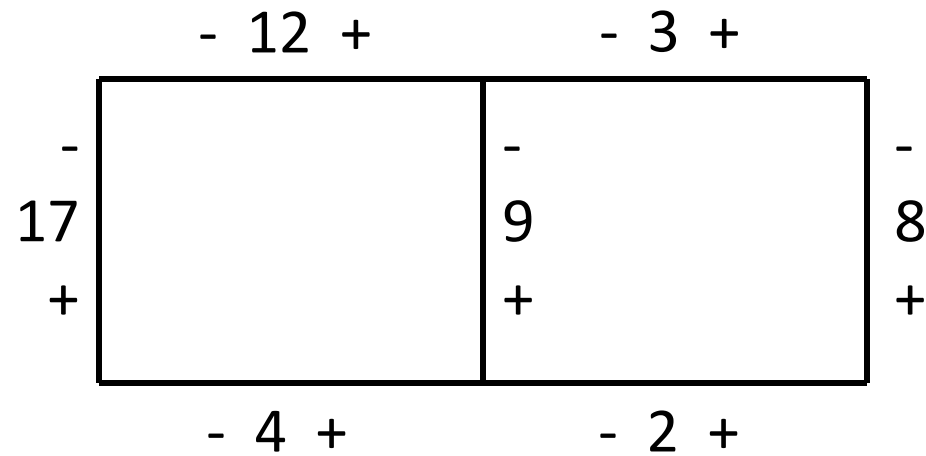

Circuit Elements

- Two terminal devices:


- Batteries – $V(t)$



- Resistors – $V=IR$



- Capacitors – $V=Q/C$

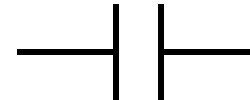

- Inductors – $V=L \, di/dt$



- Three terminal device: op-amp

- Four terminal device: transformer


Power in Circuits

$$P(t) = I(t)V(t)$$

$$U = \int I(t)V(t) dt$$


$\sum_{i=1}^N P_i(t) = 0$, for a closed circuit of N elements,
at all times

Passive Sign Convention

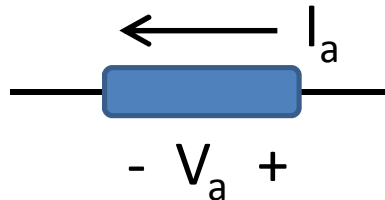

- Defined as when current flows from positive to negative voltage
- Allows one to read $P=IV$ (with correct sign)
- Positive values associated with resistors
- Negative values associated with voltage sources
- Active sign convention is the opposite

Example 2

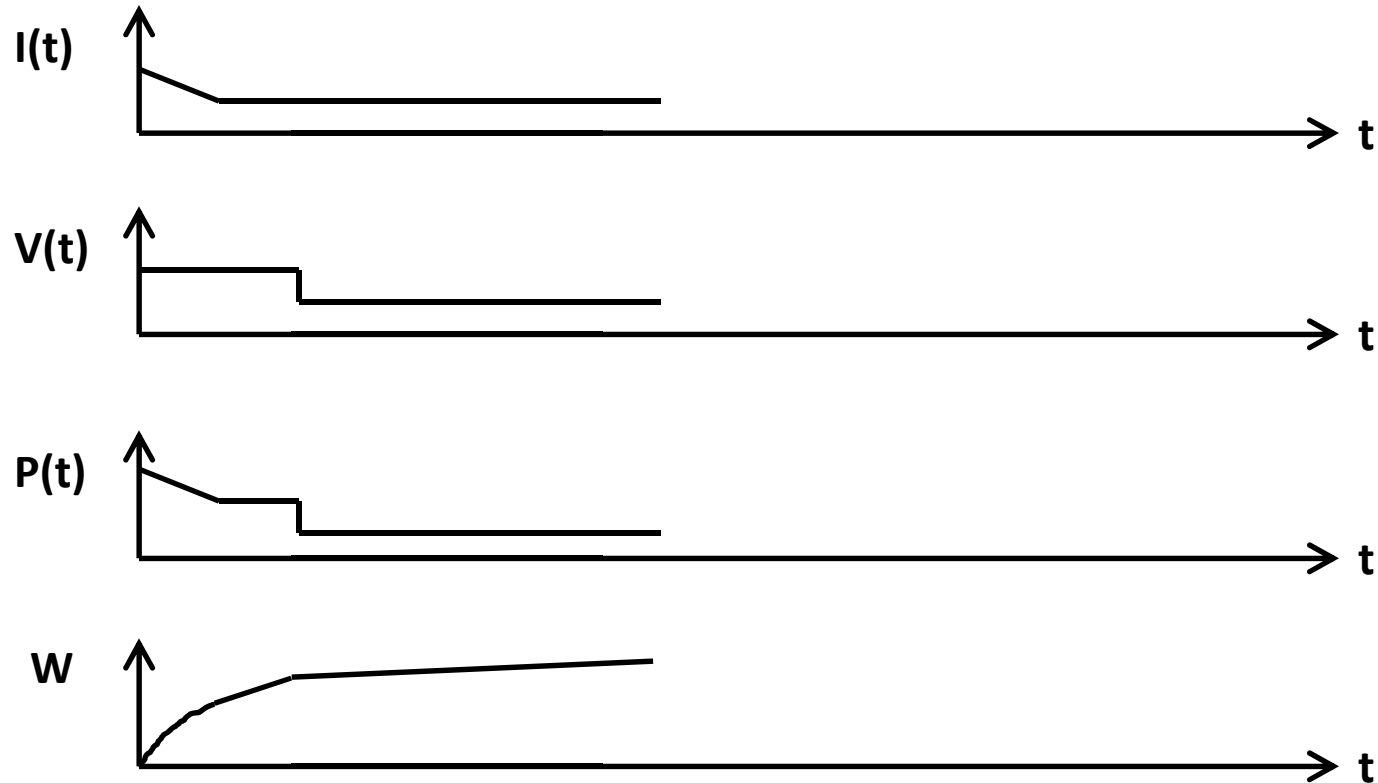

Ideal Sources

- An abstraction of real devices, insensitive to operating environment
- Ideal voltage source
 - Fixed voltage $V(t)$
 - Example: battery
- Ideal current source
 - Fixed current $I(t)$
 - Example: lightning

Controlled Ideal Sources

- Can use current or voltage to control output current or voltage

		Control type	
		Voltage	Current
Output type	Voltage	VCVS ($V=\mu v_x$)	CCVS ($V=IR$)
	Current	VCCS ($I=gV$)	CCCS ($I=\beta I_x$)

Key Definitions

- **Short Circuit** – connection with zero resistance
- **Open Circuit**– connection with infinite resistance
- **Power**– rate at which work is performed

Homework #2 for Friday

- DeCarlo & Lin, 3rd Edition, Chapter 1
 - Problem 10
 - Problem 12 [Note 'F' above I_D should be 'D']
 - Problem 17
- All homework posted on Blackboard