

ECE 201, Section 3

Lecture 21

Prof. Peter Bermel

October 12, 2012

Exam #2: Monday, October 15

- Runs from 6:30-7:30 pm in EE 129, unless specifically told otherwise
- Will cover Lectures 12-21:
 - Source transformation
 - Thévenin and Norton equivalent circuits
 - Maximum power transfer
 - Inductors, parallel & series; LR circuits
 - Capacitors, parallel & series; RC circuits
 - Linear response; waveform generation
 - Undriven LC and RLC resonators


Exam #2: Monday, October 15

- Posted 4 sample exams on Blackboard – also includes equation “sheet” at bottom
- The one marked “Exam 2 – Review Session” from ‘98 will be reviewed tonight starting at 6:30 pm, here in EE 170


General Solutions: RC & RL Circuits

$$X = X_{\infty} + (X_o - X_{\infty})e^{-(t-t_o)/\tau}$$

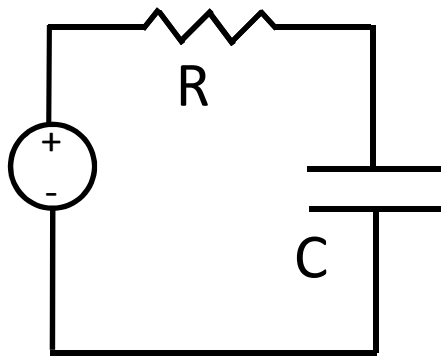- Solution steps:
 - Choose X : RC circuits: $X=Q$ or $X=V$; LR circuits: $X=I$
 - Find X_o (simplifying diagram)
 - Find X_{∞} (simplifying diagram)
 - Find R_{th} (for inductor/capacitor)
 - Find τ : RC circuits: $\tau = R_{th}C$; LR circuits: $\tau = L/R_{th}$
 - If circuit changes at t_1 , use $X(t_1)$ from prior solution for initial values



RC Circuit

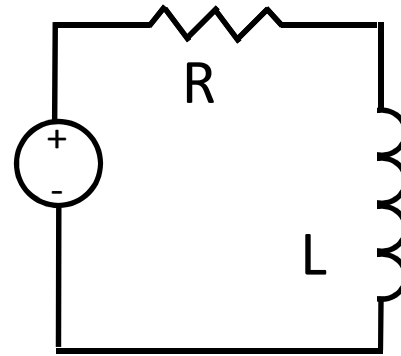

RL Circuit

General Solutions: LC Circuits

- For an undamped, free (undriven) LC circuit:


$$Q(t) = A \cos \omega t + B \sin \omega t$$

- $Q(t)$ is capacitor charge at time t
- A and B determined by initial conditions
- ω is the resonant frequency; $\omega = 1/\sqrt{LC}$

- Alternatively, can write:

$$Q(t) = A' \cos(\omega t + \phi)$$

- ϕ is the phase angle

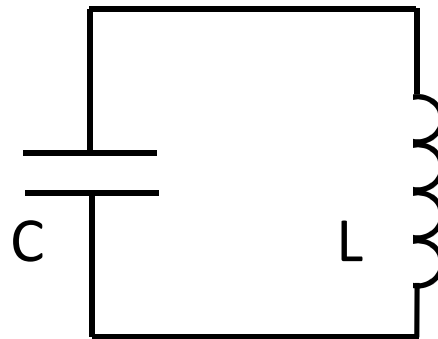

LC Circuit

Complex Exponentials

- Some key equations:

$$e^{i\omega t} = \cos \omega t + i \sin \omega t$$

$$e^{(i\omega - \Gamma)t} = e^{-\Gamma t} (\cos \omega t + i \sin \omega t)$$

$$\cos \omega t = \frac{e^{i\omega t} + e^{-i\omega t}}{2}$$

$$\sin \omega t = \frac{e^{i\omega t} - e^{-i\omega t}}{2i}$$

Trigonometric Identities

Can use Euler's equation to write:

$$\begin{aligned}e^{i(\alpha+\beta)} &= e^{i\alpha} e^{i\beta} \\&= (\cos \alpha + i \sin \alpha)(\cos \beta + i \sin \beta) \\&= \cos \alpha \cos \beta - \sin \alpha \sin \beta \\&\quad + i(\sin \alpha \cos \beta + \cos \alpha \sin \beta)\end{aligned}$$

Which yields:

$$\begin{aligned}\cos(\alpha + \beta) &= \cos \alpha \cos \beta - \sin \alpha \sin \beta \\ \sin(\alpha + \beta) &= \sin \alpha \cos \beta + \cos \alpha \sin \beta\end{aligned}$$


General Solutions: LC Circuits

- Can rewrite our previous solution:

$$\begin{aligned} Q(t) &= A \cos \omega t + B \sin \omega t = A \left(\frac{e^{i\omega t} + e^{-i\omega t}}{2} \right) + B \left(\frac{e^{i\omega t} - e^{-i\omega t}}{2i} \right) \\ &= \left(\frac{A}{2} + \frac{B}{2i} \right) e^{i\omega t} + \left(\frac{A}{2} - \frac{B}{2i} \right) e^{-i\omega t} \end{aligned}$$


- We can define new coefficients in front to obtain:
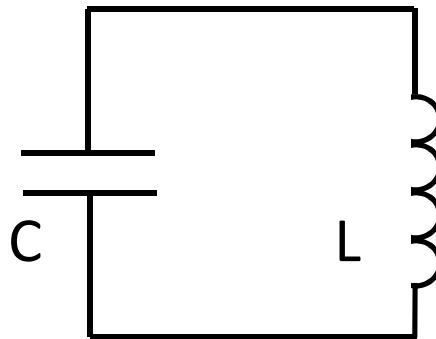
$$Q(t) = A_+ e^{i\omega t} + A_- e^{-i\omega t}$$



LC Circuit

RLC Circuits

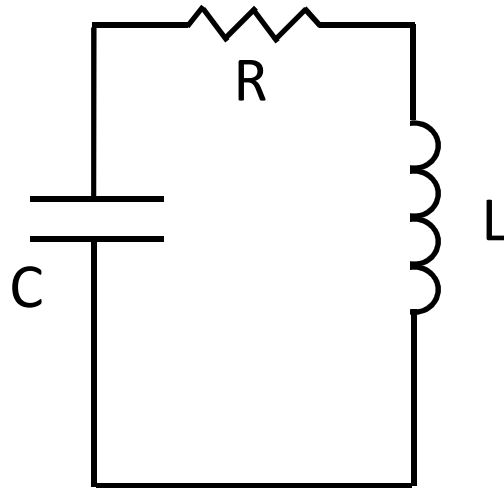


- Using KVL yields:

$$\frac{d^2 Q}{dt^2} + \frac{R}{L} \frac{dQ}{dt} + \frac{1}{LC} Q = 0$$

- Solutions should oscillate and decay:

$$Q(t) = \sum_k A_k e^{s_k t}$$

RLC Circuits

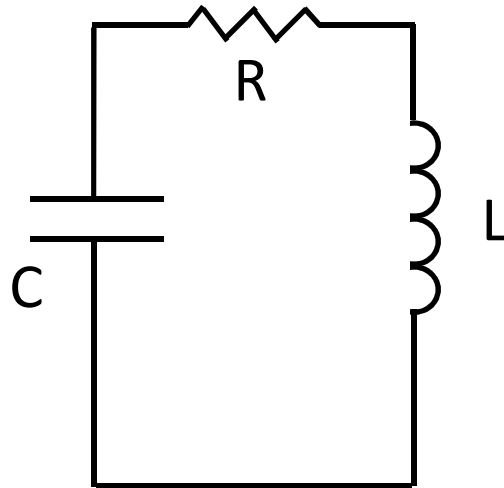


- *Characteristic equation* becomes:

$$s_k^2 + \frac{R}{L}s_k + \frac{1}{LC} = 0$$

- Using the quadratic equation:

$$s_k = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

RLC Circuits

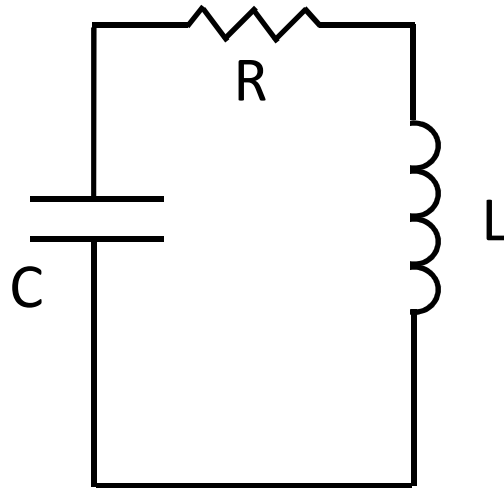

- General solution:

$$Q(t) = Ae^{s_+t} + Be^{s_-t}$$


- If $V(0)=V_o$, $I(0)=0$, then:

$$Q(0) = CV_o = A + B$$

$$I(0) = 0 = As_+ + Bs_-$$

$$0 = As_+ + (CV_o - A)s_-$$

RLC Circuits

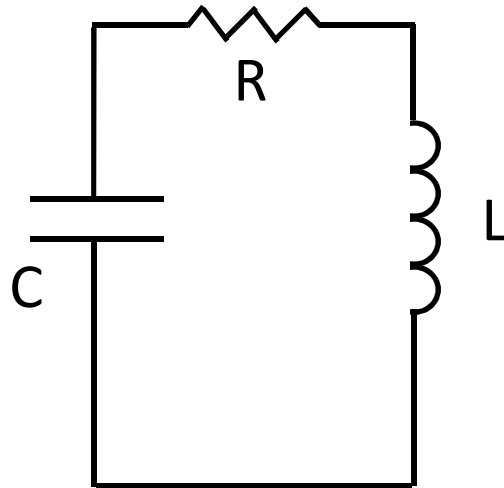

- Particular solution:

$$A = CV_o s_- / (s_- - s_+)$$

$$B = -CV_o s_+ / (s_- - s_+)$$

$$Q(t) = CV_o \left(\frac{s_- e^{s_+ t} - s_+ e^{s_- t}}{s_- - s_+} \right)$$


General Solutions: RLC Circuits

- General solution:

$$Q(t) = A_+ e^{s_+ t} + A_- e^{s_- t}$$
$$s_{\pm} = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

- If $V(0)=V_o$, $I(0)=0$, then:
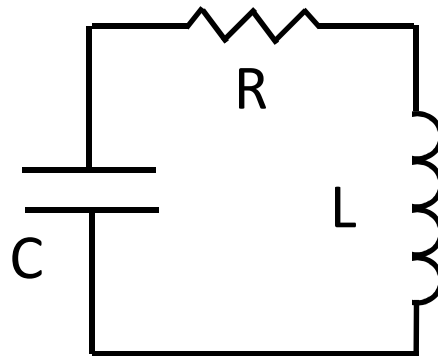
$$Q(t) = CV_o \left(\frac{s_- e^{s_+ t} - s_+ e^{s_- t}}{s_- - s_+} \right)$$



RLC Circuit


Special Cases: RLC Circuits

- When $R=0$:

$$s_{\pm} = -\frac{0}{2L} \pm \sqrt{\left(\frac{0}{2L}\right)^2 - \frac{1}{LC}} = \pm \sqrt{-\frac{1}{LC}} = \frac{\pm i}{\sqrt{LC}} \\ = \pm i\omega$$

- Solution becomes:
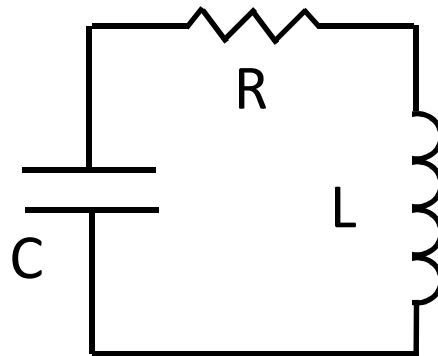
$$Q(t) = A_+ e^{i\omega t} + A_- e^{-i\omega t}$$



RLC Circuit

Special Cases: RLC Circuits

- To capture other regimes, define damping $\Gamma = R/2L$, and write solutions:

$$s_{\pm} = -\Gamma \pm \sqrt{\Gamma^2 - \omega_o^2}$$

Regime	Value Range	Root type	Behavior
Undamped	$\Gamma = 0$	Pure imaginary	Oscillates forever
Underdamped	$0 < \Gamma < \omega_o$	Complex	Oscillate & decay
Critically damped	$\Gamma = \omega_o$	Pure real	Decay
Overdamped	$\Gamma > \omega_o$	Pure real	Decay

Special Cases: RLC Circuits

- In general, one can define a *quality factor*:

$$Q = \frac{\omega_o}{2\Gamma}$$

Measures the lifetime of an excitation

- Here, $\Gamma = R/2L$, and $\omega_o = 1/\sqrt{LC}$, so

$$Q = \frac{1/\sqrt{LC}}{2 \cdot (R/2L)} = \frac{1}{R} \sqrt{\frac{L}{C}}$$


As $R \rightarrow 0$, $Q \rightarrow \infty$, and vice versa

Mathematica Demonstration


[Click to begin](#)

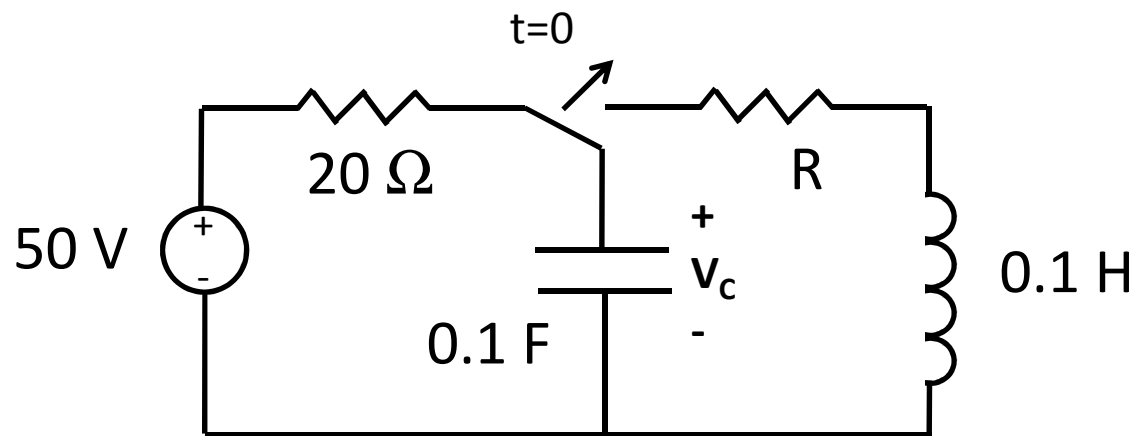Example 1

- Consider a circuit which charges a capacitor for $t < 0$ then switches to an RLC circuit at $t = 0$. What is $V_C(t)$ for $R = 0$, and 180 ?



Solution

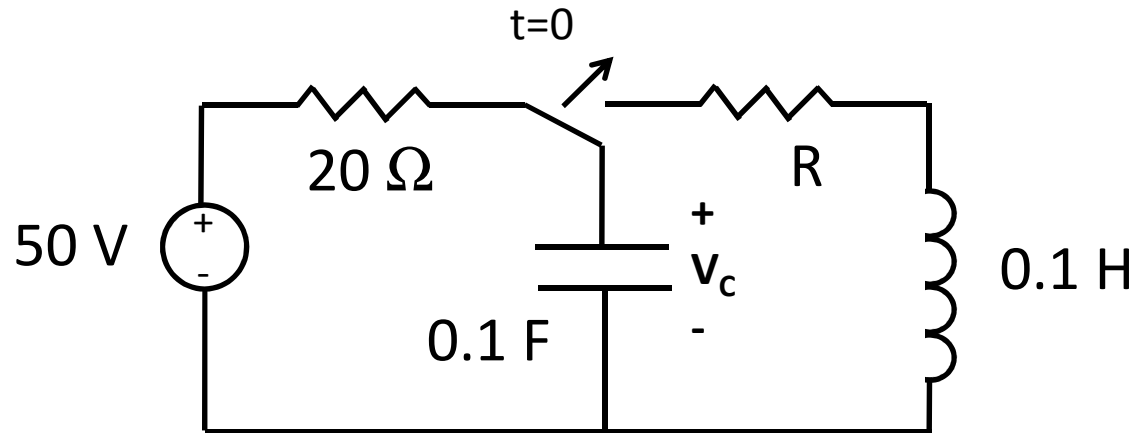


- For $t < 0$: $V_c = 50 \text{ V}$
- For $t > 0$: $I(0) = 0$, and:

$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.1 \cdot 0.1}} = 10 \text{ rad/s}$$

$$\Gamma = \frac{R}{2L} = \frac{R}{2 \cdot (0.1 \text{ H})} = 5R$$

$$Q = \frac{\omega}{2\Gamma} = \frac{10}{2 \cdot (5R)} = \frac{1}{R}$$

Solution

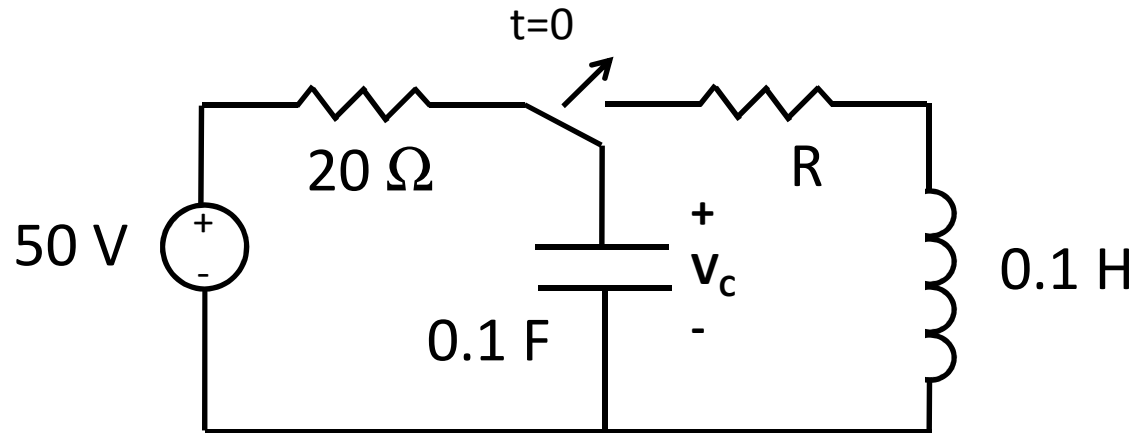

- From before:

$$V_C(t) = Q(t)/C = A_+ e^{s_+ t} + A_- e^{s_- t}$$

$$V_C(t) = e^{-\Gamma t} \left(A_+ e^{i\sqrt{\omega^2 - \Gamma^2} t} + A_- e^{-i\sqrt{\omega^2 - \Gamma^2} t} \right)$$


$$V_C(t) = e^{-\Gamma t} (A_+ e^{i\omega' t} + A_- e^{-i\omega' t})$$

Matching boundary conditions:

$$A_+ + A_- = V_o$$

$$(-\Gamma + i\omega')A_+ + (-\Gamma - i\omega')A_- = 0$$


Solution

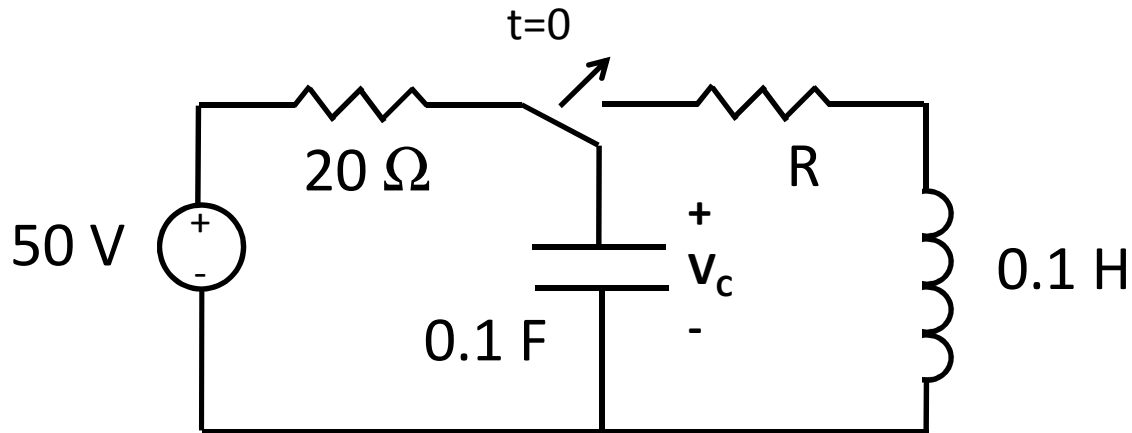

- Substituting:

$$\begin{aligned}
 A_+ + A_- &= V_o \\
 (-\Gamma + i\omega')A_+ + (-\Gamma - i\omega')(V_o - A_+) &= 0 \\
 2i\omega'A_+ &= (\Gamma + i\omega')V_o \\
 A_+ &= \frac{V_o}{2} \left(1 - i \frac{\Gamma}{\omega'} \right) \\
 (-\Gamma + i\omega')(V_o - A_-) + (-\Gamma - i\omega')A_- &= 0 \\
 -2i\omega'A_- &= (\Gamma - i\omega')V_o \\
 A_- &= \frac{V_o}{2} \left(1 + i \frac{\Gamma}{\omega'} \right)
 \end{aligned}$$

Solution

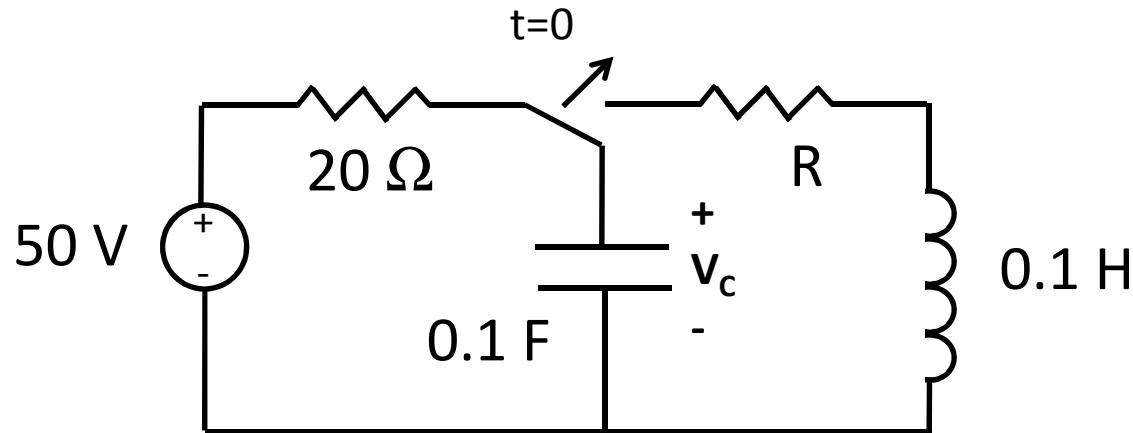

- From before:

$$V_C(t) = \frac{V_o e^{-\Gamma t}}{2} \left[\left(1 - i \frac{\Gamma}{\omega'} \right) e^{i\omega' t} + \left(1 + i \frac{\Gamma}{\omega'} \right) e^{-i\omega' t} \right]$$

$$V_C(t) = V_o e^{-\Gamma t} \left[\cos \omega' t + \left(\frac{\Gamma}{\omega'} \right) \sin \omega' t \right]$$

Homework

- HW #19 solution posted
- HW #20 due today by 4:30 pm in EE 326B
- HW #21 due Wed.: DeCarlo & Lin, Chapter 8:
 - Problem 30
 - Problem 34