

ECE 201, Section 3

Lecture 22

Prof. Peter Bermel

October 17, 2012


Series RLC Circuits

General solution to RLC circuits:

$$X(t) = A_+ e^{s_+ t} + A_- e^{s_- t}$$

$$s_{\pm} = -\Gamma \pm \sqrt{\Gamma^2 - \omega_o^2}$$
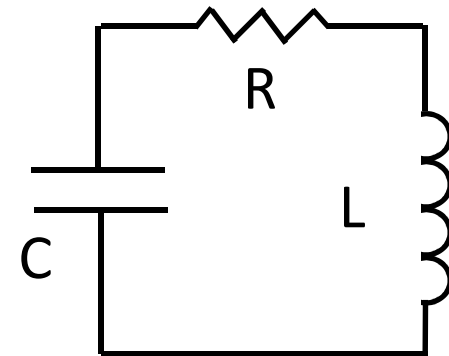
$$\Gamma = R/2L; \omega_o = 1/\sqrt{LC}$$




RLC Circuit

Regime	Value Range	Root type	Behavior
Undamped	$\Gamma = 0$	Pure imaginary	Oscillates forever
Underdamped	$0 < \Gamma < \omega_o$	Complex	Oscillate & decay
Critically damped	$\Gamma = \omega_o$	Pure real	Decay
Overdamped	$\Gamma > \omega_o$	Pure real	Decay

Problem 2

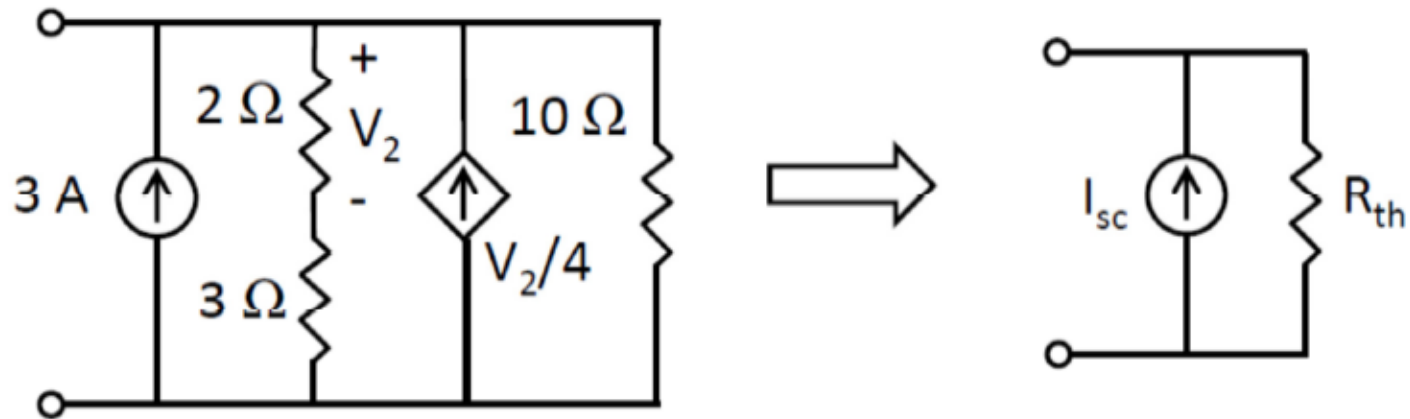2. Given the circuit below on the left, find the Norton equivalent current source and resistance values (as shown on the right):



Answers:

- (1) $I_{sc}=0\text{ A}$; $R_{th}=10/3\ \Omega$
- (2) $I_{sc}=3\text{ A}$; $R_{th}=5\ \Omega$
- (3) $I_{sc}=7/2\text{ A}$; $R_{th}=5\ \Omega$
- (4) $I_{sc}=9/2\text{ A}$; $R_{th}=10/3\ \Omega$
- (5) $I_{sc}=9/2\text{ A}$; $R_{th}=10\ \Omega$
- (6) $I_{sc}=6\text{ A}$; $R_{th}=10/3\ \Omega$
- (7) $I_{sc}=6\text{ A}$; $R_{th}=10\ \Omega$
- (8) None of the above

Problem 3

3. If the following relationship between input current and output voltage is observed for a linear circuit, what are its Norton equivalent current source and resistance values?


I_A	V_{AB}
2	36
5	48
12	76

Answers:

- (1) $I_{sc}=0$ A; $R_{th}=18\ \Omega$
- (2) $I_{sc}=2$ A; $R_{th}=9\ \Omega$
- (3) $I_{sc}=5$ A; $R_{th}=4.8\ \Omega$
- (4) $I_{sc}=7$ A; $R_{th}=4\ \Omega$
- (5) $I_{sc}=12$ A; $R_{th}=3\ \Omega$
- (6) $I_{sc}=14$ A; $R_{th}=3\ \Omega$
- (7) $I_{sc}=19$ A; $R_{th}=2\ \Omega$
- (8) None of the above

Problem 6

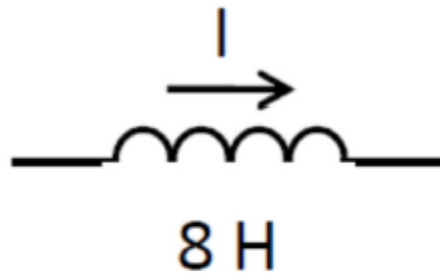6. If $I = 2^{-t}$ A (i.e., $I = 1$ A at $t = 0$ s, and $I = 0.25$ A at $t = 2$ s), then how much stored energy (in J) is lost from the inductor between $t = 0$ and $t = 1$ s?




Answers:

- (1) 1
- (2) 2
- (3) 3
- (4) 4
- (5) 5
- (6) 6
- (7) 7
- (8) None of the above

Problem 9

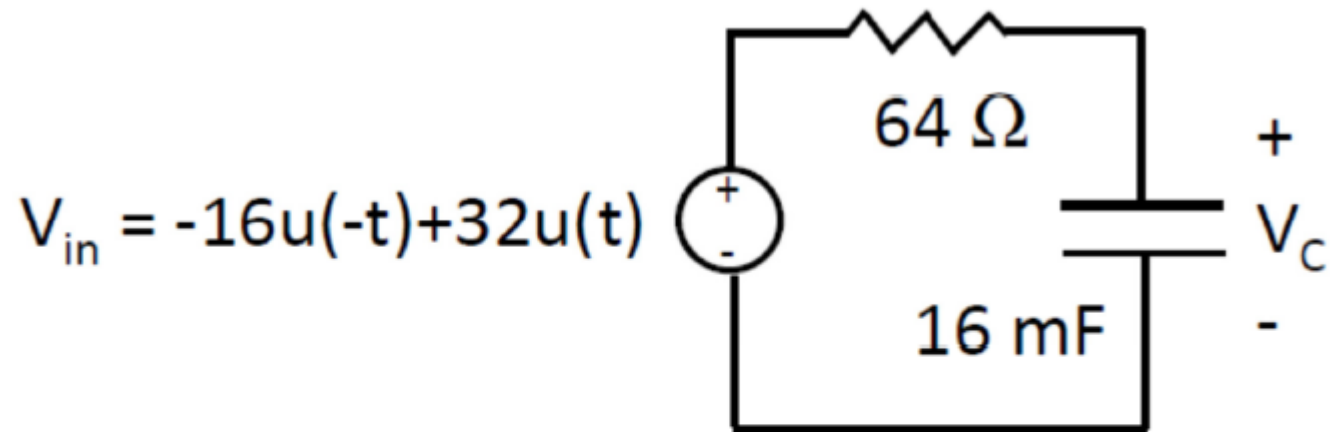9. Find the voltage $V_C(t)$ (in V), for $t > 0$. Note: $u(t) = 1$ if $t > 0$, and 0 otherwise.




Answers:

- (1) $-16e^{-t/1.024}$
- (2) $16(1 - e^{-t/1.024})$
- (3) $32(1 - e^{-t/1.024})$
- (4) $32 - 48e^{-t/1.024}$
- (5) $32 - 48e^{-t/2.048}$
- (6) $32 - 64e^{t/1.024}$
- (7) $64(1 - e^{-t/2.048})$
- (8) None of the above

Problem 12

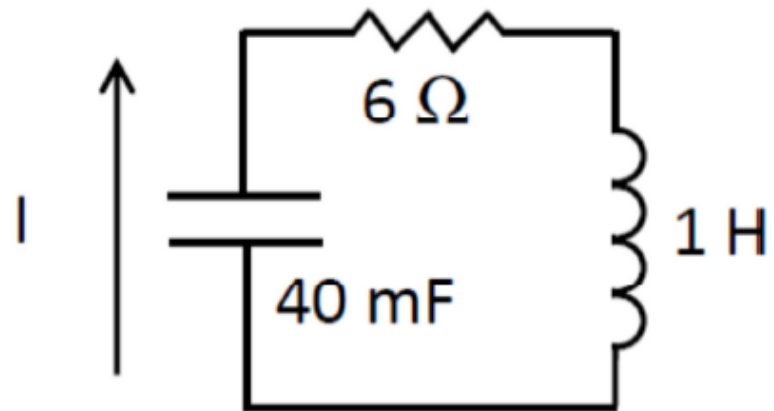12. Find the frequency (in Hz) at which this undriven RLC circuit will oscillate:




Answers:

- (1) 1
- (2) 2
- (3) 3
- (4) 4
- (5) 5
- (6) 6
- (7) 7
- (8) None of the above


Problem 13

13. Find the voltage across the capacitor V_c (in V) as a function of time after the switch moves from left to right at $t=0$:

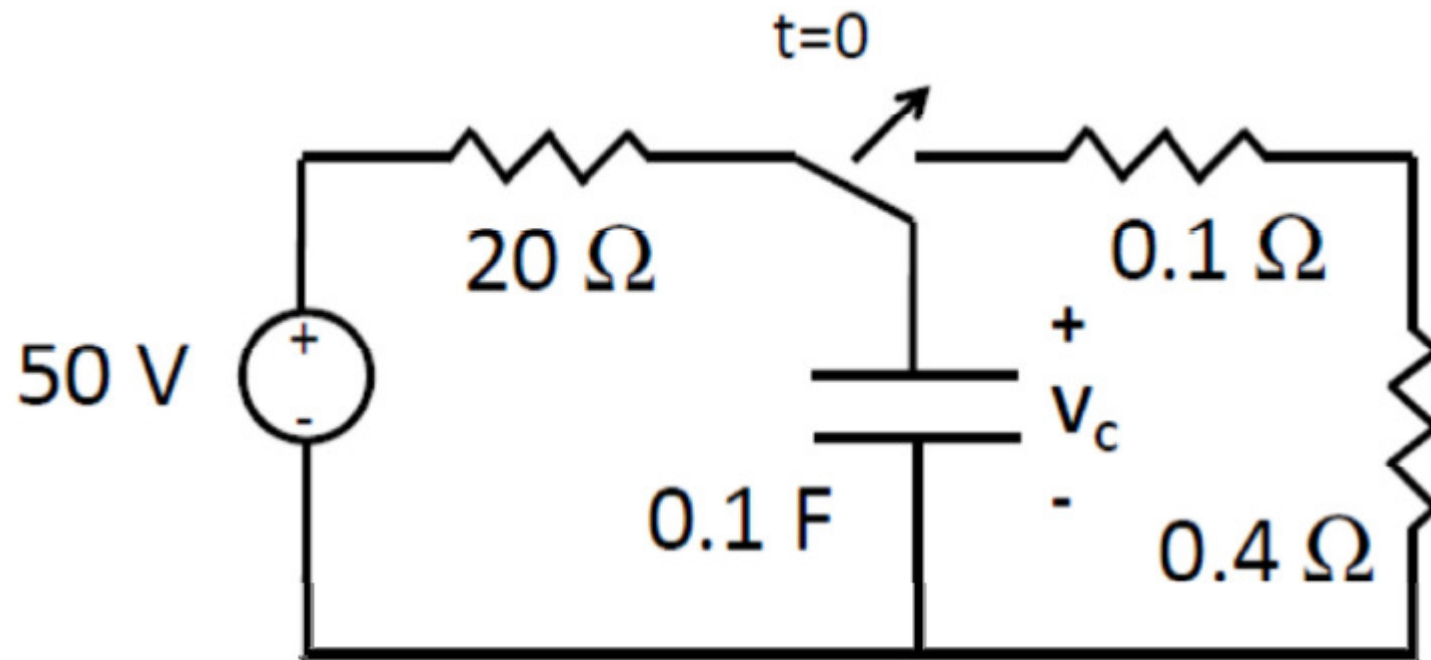


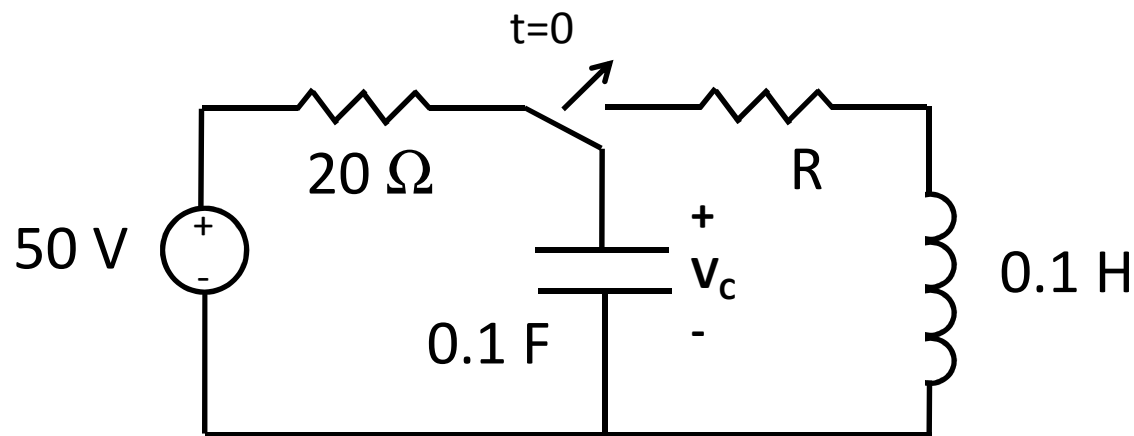Example 1

- Consider a circuit which charges a capacitor for $t < 0$ then switches to an RLC circuit at $t = 0$. What is $V_C(t)$ for $R = 0$, and 180 ?



Solution

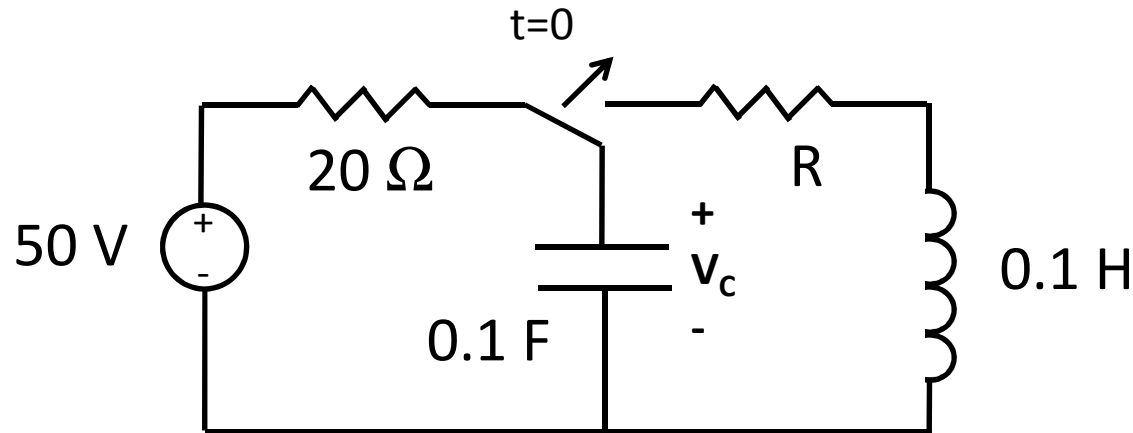


- For $t < 0$: $V_c = 50 \text{ V}$
- For $t > 0$: $I(0) = 0$, and:

$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.1 \cdot 0.1}} = 10 \text{ rad/s}$$

$$\Gamma = \frac{R}{2L} = \frac{R}{2 \cdot (0.1 \text{ H})} = 5R$$

$$Q = \frac{\omega}{2\Gamma} = \frac{10}{2 \cdot (5R)} = \frac{1}{R}$$

Solution

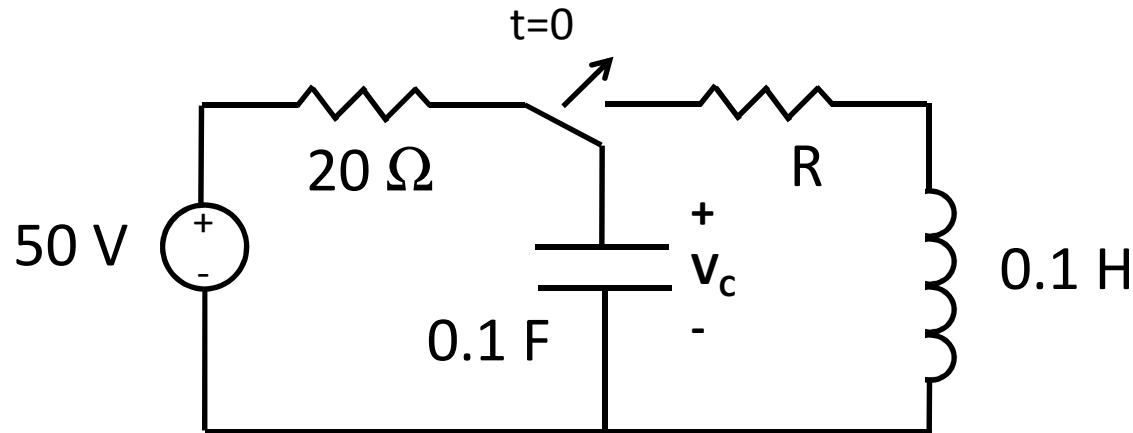

- From before:

$$V_C(t) = Q(t)/C = A_+ e^{s_+ t} + A_- e^{s_- t}$$

$$V_C(t) = e^{-\Gamma t} \left(A_+ e^{i\sqrt{\omega^2 - \Gamma^2} t} + A_- e^{-i\sqrt{\omega^2 - \Gamma^2} t} \right)$$


$$V_C(t) = e^{-\Gamma t} (A_+ e^{i\omega' t} + A_- e^{-i\omega' t})$$

Matching boundary conditions:

$$A_+ + A_- = V_0$$

$$(-\Gamma + i\omega')A_+ + (-\Gamma - i\omega')A_- = 0$$


Solution

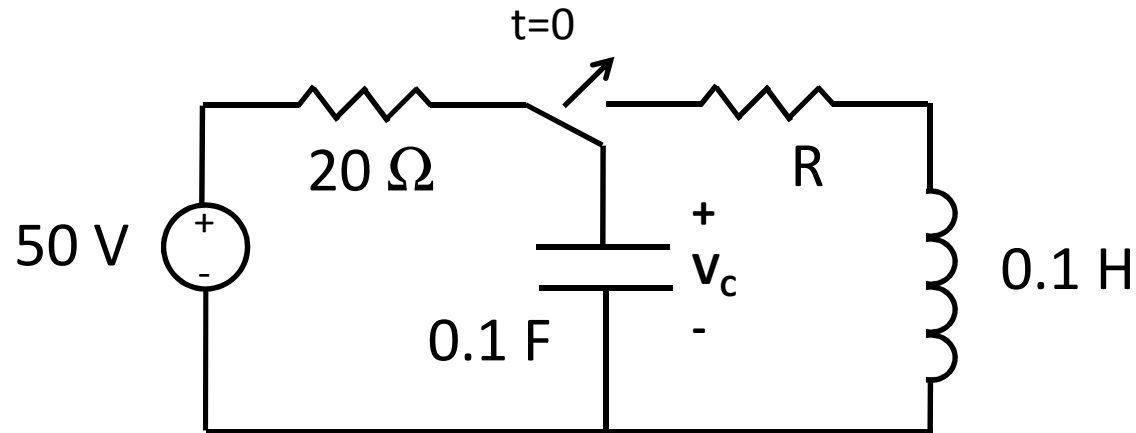

- Substituting:

$$\begin{aligned}
 A_+ + A_- &= V_o \\
 (-\Gamma + i\omega')A_+ + (-\Gamma - i\omega')(V_o - A_+) &= 0 \\
 2i\omega'A_+ &= (\Gamma + i\omega')V_o \\
 A_+ &= \frac{V_o}{2} \left(1 - i \frac{\Gamma}{\omega'} \right) \\
 (-\Gamma + i\omega')(V_o - A_-) + (-\Gamma - i\omega')A_- &= 0 \\
 -2i\omega'A_- &= (\Gamma - i\omega')V_o \\
 A_- &= \frac{V_o}{2} \left(1 + i \frac{\Gamma}{\omega'} \right)
 \end{aligned}$$

Solution

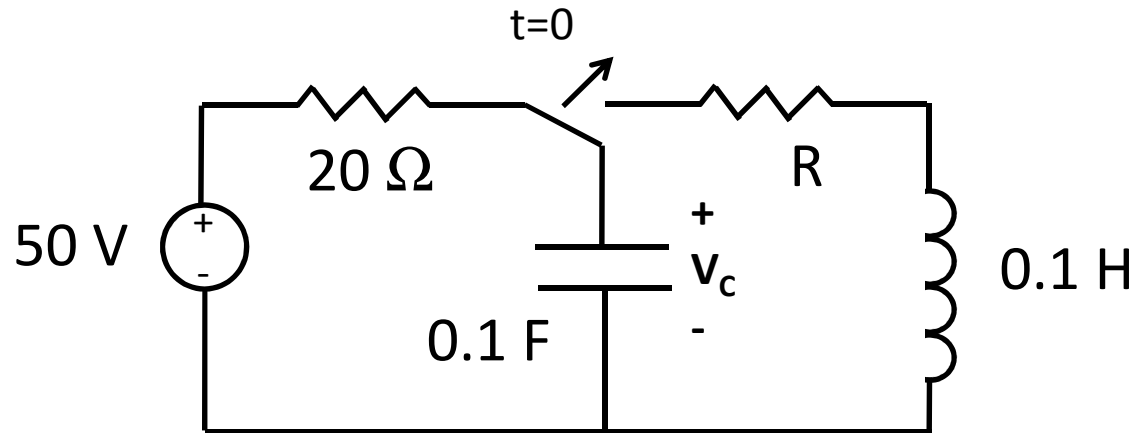


- From before:

$$V_C(t) = \frac{V_o e^{-\Gamma t}}{2} \left[\left(1 - i \frac{\Gamma}{\omega'} \right) e^{i\omega' t} + \left(1 + i \frac{\Gamma}{\omega'} \right) e^{-i\omega' t} \right]$$


$$V_C(t) = V_o e^{-\Gamma t} \left[\cos \omega' t + \left(\frac{\Gamma}{\omega'} \right) \sin \omega' t \right]$$

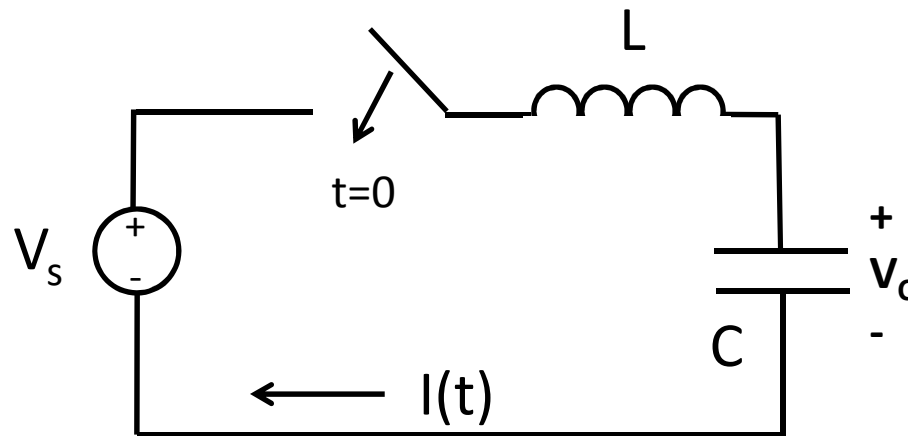Example

- Consider an LC circuit connected to a voltage source at $t=0$. How will the current and voltage vary with time?



Solution

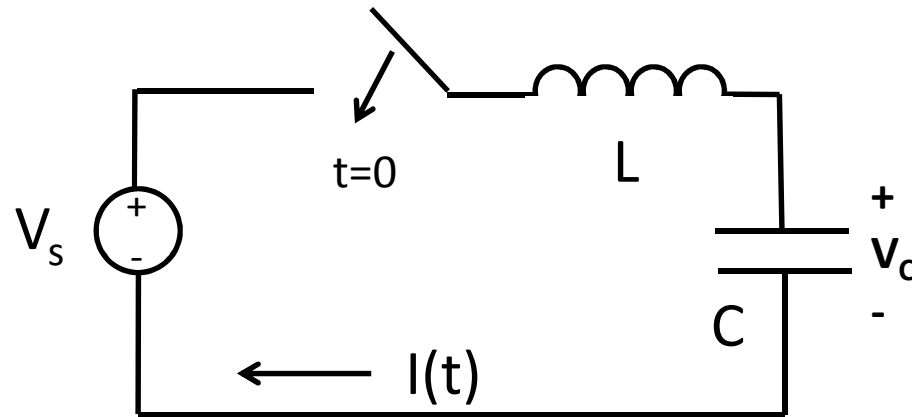

- Employing our solution:


$$I(t) = A_+ e^{s_+ t} + A_- e^{s_- t}$$

$$s_{\pm} = -\Gamma \pm \sqrt{\Gamma^2 - \omega_o^2}$$

$$\Gamma = \frac{R}{2L} = 0; \omega_o = 1/\sqrt{LC}$$

$$s_{\pm} = \pm i\omega_o$$


Solution

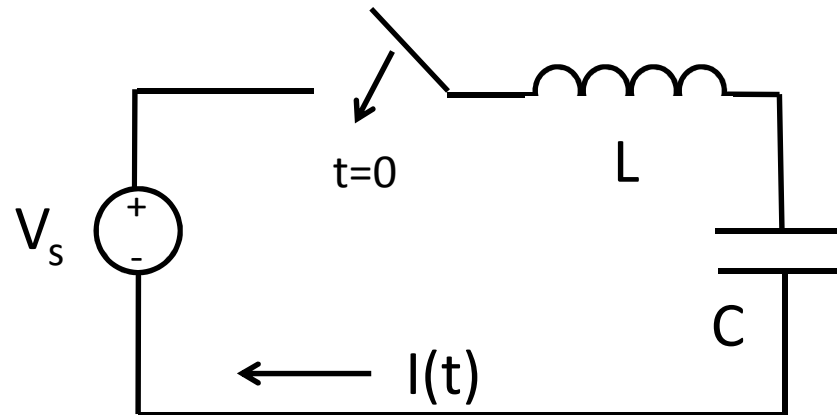

- Employing our solution:

$$\begin{aligned} I(t) &= A_+ e^{i\omega_o t} + A_- e^{-i\omega_o t} \\ \frac{dI}{dt} &= i\omega_o (A_+ e^{i\omega_o t} - A_- e^{-i\omega_o t}) \\ I(0) &= A_+ + A_- = 0 \\ V_s &= L \frac{dI}{dt} (t=0) = Li\omega_o (A_+ - A_-) \\ V_s &= 2iL\omega_o A_+ = -2iL\omega_o A_- \\ I(t) &= \frac{V_s (e^{i\omega_o t} - e^{-i\omega_o t})}{2iL\omega_o} = \frac{V_s}{L\omega_o} \sin(\omega_o t) \end{aligned}$$

Solution

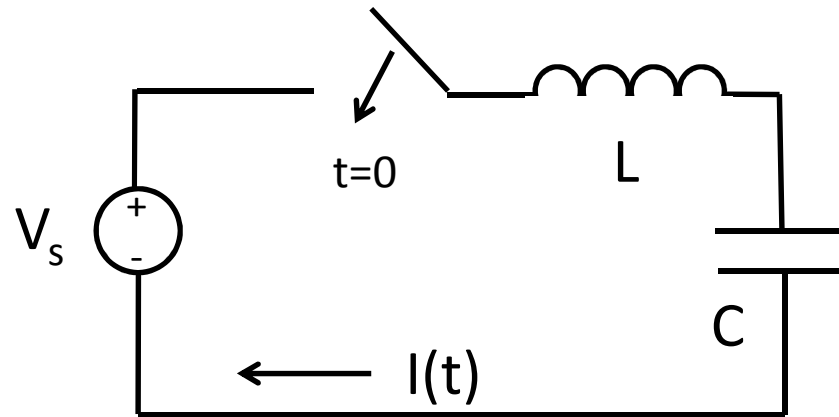

- Given that:

$$I(t) = \frac{V_s}{L\omega_o} \sin(\omega_o t)$$

We can integrate to obtain:


$$V_C(t) = \frac{1}{C} \int_0^t dt' \frac{V_s}{L\omega_o} \sin(\omega_o t') = V_s \int_0^t \omega_o dt' \sin(\omega_o t')$$

$$V_C(t) = -V_s \cos(\omega_o t') \Big|_0^t$$


$$V_C(t) = V_s [1 - \cos(\omega_o t)]$$

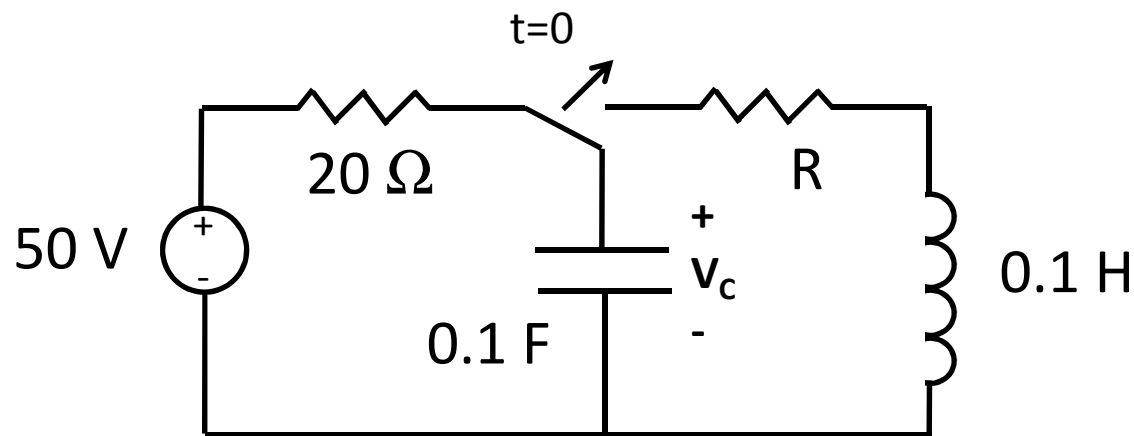Example

- Consider a circuit which charges a capacitor for $t < 0$ then switches to an RLC circuit at $t = 0$. What is $V_C(t)$ for $R = 0$, and 180 ?



Solution

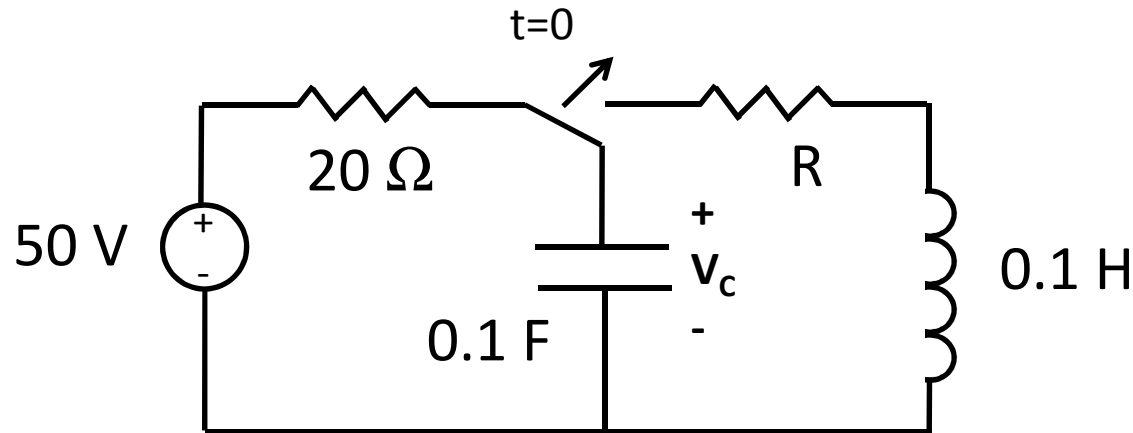


- For $t < 0$: $V_c = 50 \text{ V}$
- For $t > 0$: $I(0) = 0$, and:

$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.1 \cdot 0.1}} = 10 \text{ rad/s}$$

$$\Gamma = \frac{R}{2L} = \frac{R}{2 \cdot (0.1 \text{ H})} = 5R$$

$$Q = \frac{\omega}{2\Gamma} = \frac{10}{2 \cdot (5R)} = \frac{1}{R}$$

Solution

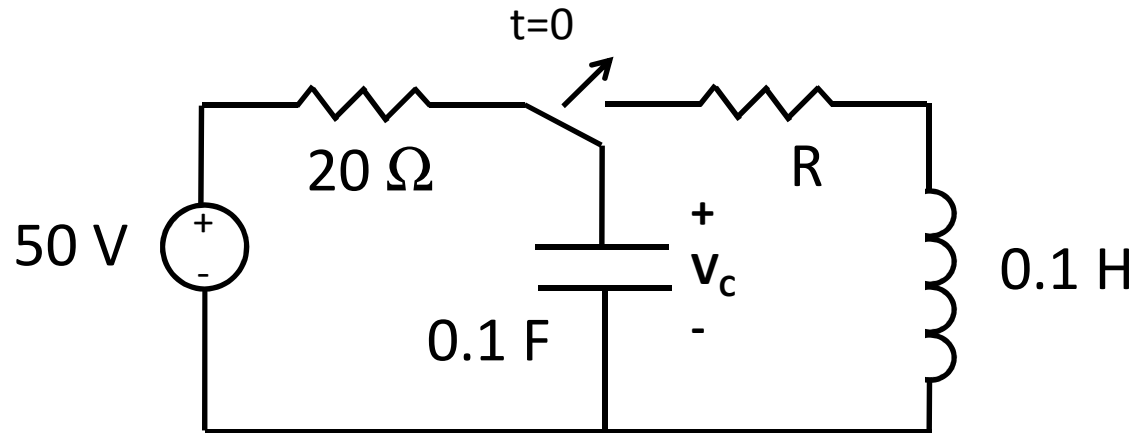

- From before:

$$V_C(t) = Q(t)/C = A_+ e^{s_+ t} + A_- e^{s_- t}$$

$$V_C(t) = e^{-\Gamma t} \left(A_+ e^{i\sqrt{\omega^2 - \Gamma^2} t} + A_- e^{-i\sqrt{\omega^2 - \Gamma^2} t} \right)$$


$$V_C(t) = e^{-\Gamma t} (A_+ e^{i\omega' t} + A_- e^{-i\omega' t}), \text{ where } \omega' = \sqrt{\omega^2 - \Gamma^2}$$

Matching boundary conditions:

$$A_+ + A_- = V_o$$

$$(-\Gamma + i\omega')A_+ + (-\Gamma - i\omega')A_- = 0$$


Solution

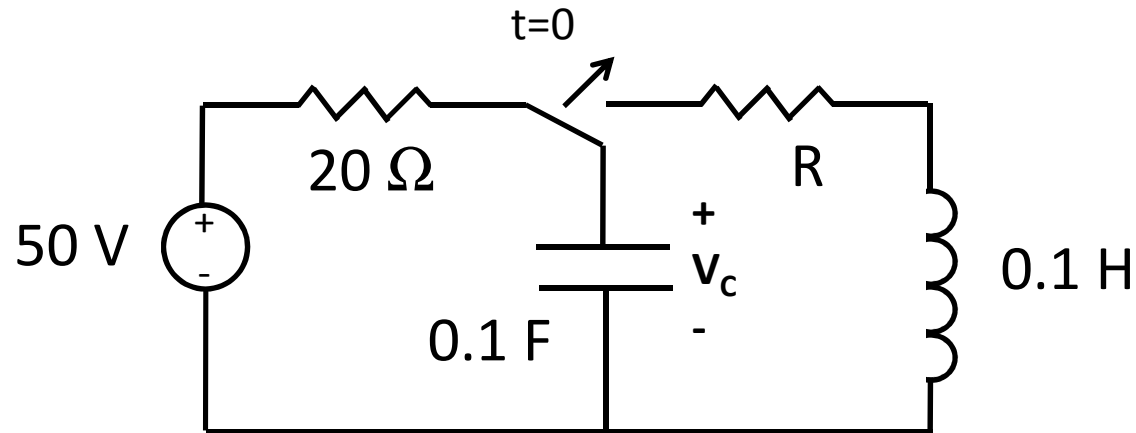

- Substituting:

$$\begin{aligned}
 A_+ + A_- &= V_o \\
 (-\Gamma + i\omega')A_+ + (-\Gamma - i\omega')(V_o - A_+) &= 0 \\
 2i\omega'A_+ &= (\Gamma + i\omega')V_o \\
 A_+ &= \frac{V_o}{2} \left(1 - i \frac{\Gamma}{\omega'} \right) \\
 (-\Gamma + i\omega')(V_o - A_-) + (-\Gamma - i\omega')A_- &= 0 \\
 -2i\omega'A_- &= (\Gamma - i\omega')V_o \\
 A_- &= \frac{V_o}{2} \left(1 + i \frac{\Gamma}{\omega'} \right)
 \end{aligned}$$

Solution

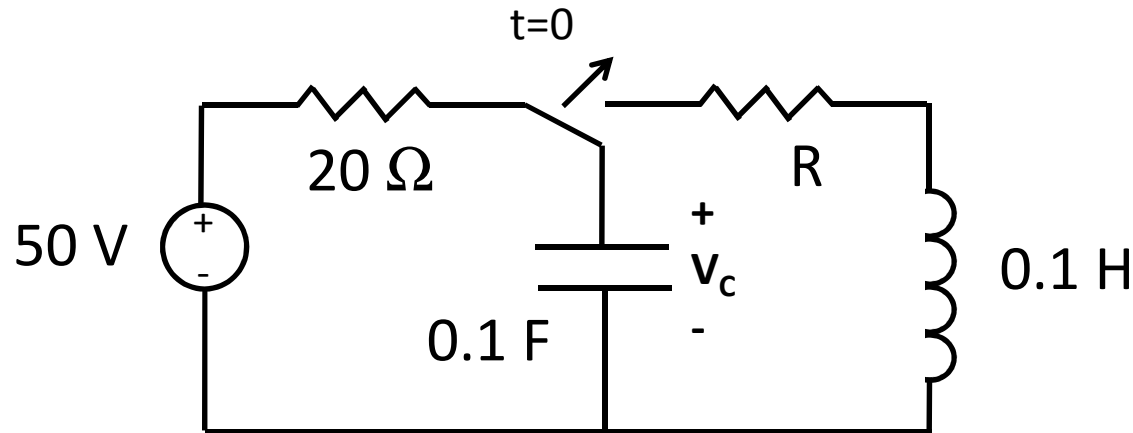

- From before:

$$V_C(t) = \frac{V_o e^{-\Gamma t}}{2} \left[\left(1 - i \frac{\Gamma}{\omega'} \right) e^{i\omega' t} + \left(1 + i \frac{\Gamma}{\omega'} \right) e^{-i\omega' t} \right]$$

$$V_C(t) = V_o e^{-\Gamma t} \left[\cos \omega' t + \left(\frac{\Gamma}{\omega'} \right) \sin \omega' t \right]$$


Underdamped for $R < 2$

Critically damped when $R = 2$


Overdamped when $R > 2$

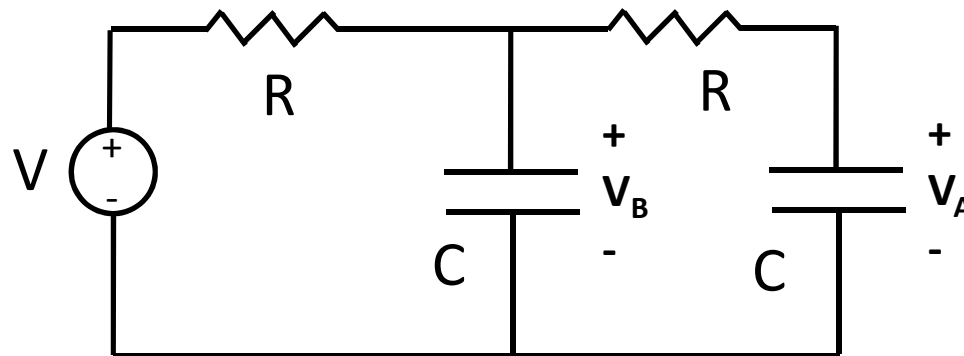Example

- What is the equation of motion for the voltage $v_A(t)$ of the right capacitor? What other system does this resemble, and where might you use this design?




Solution

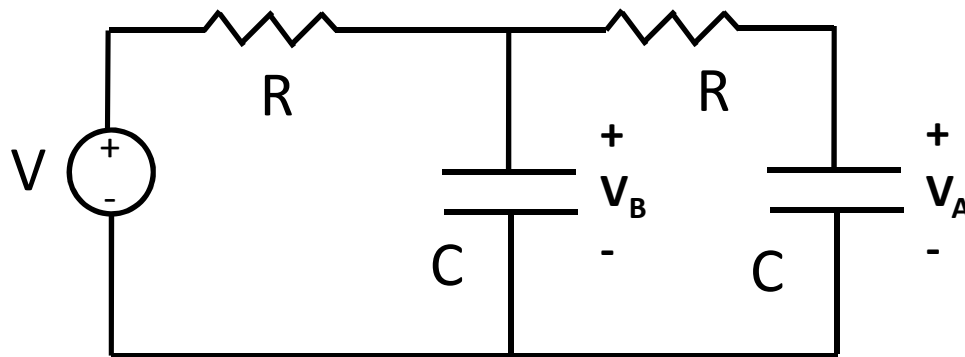

- Taking the derivative of $Q=CV$ and $V=IR$:

$$\frac{V_B - V_A}{R} = C \frac{dV_A}{dt}$$
$$\frac{V - V_B}{R} + \frac{V_A - V_B}{R} = C \frac{dV_B}{dt}$$

Solution

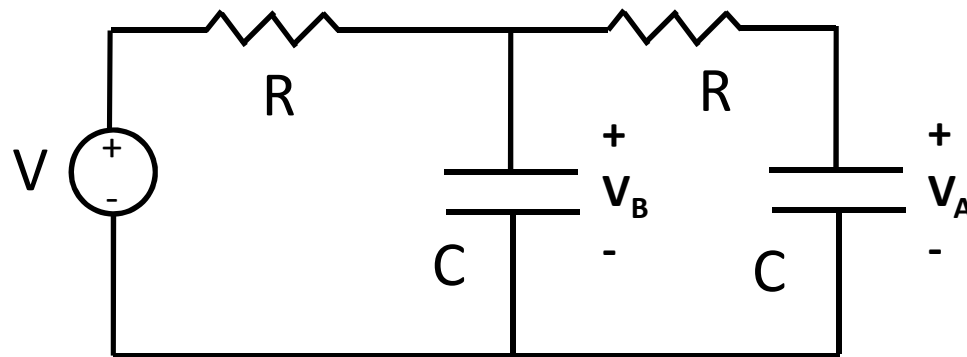


$$V_B - V_A = \tau \frac{dV_A}{dt}$$

$$V + V_A - 2V_B = \tau \frac{dV_B}{dt}$$

Substituting, $V + V_A - 2 \left(V_A + \tau \frac{dV_A}{dt} \right) = \tau \frac{dV_B}{dt}$

Time derivative yields, $\frac{dV_B}{dt} - \frac{dV_A}{dt} = \tau \frac{d^2 V_A}{dt^2}$

Solution

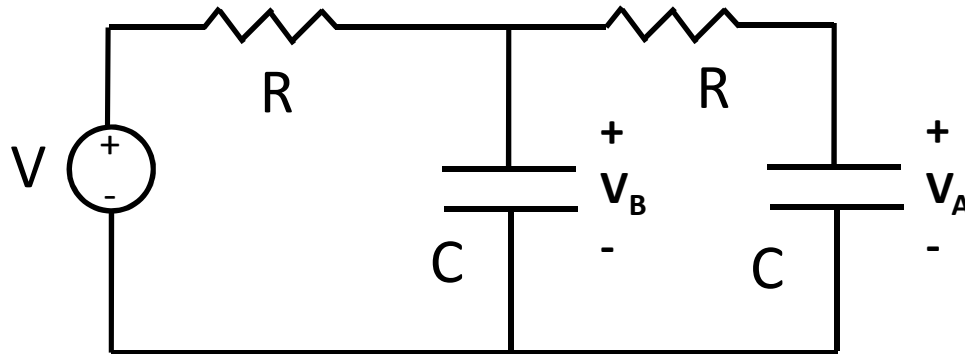


$$V + V_A - 2V_A - 2\tau \frac{dV_A}{dt} = \tau \left(\tau \frac{d^2 V_A}{dt^2} + \frac{dV_A}{dt} \right)$$

$$V - V_A - 3\tau \frac{dV_A}{dt} = \tau^2 \frac{d^2 V_A}{dt^2}$$

$$\tau^2 \frac{d^2 V_A}{dt^2} + 3\tau \frac{dV_A}{dt} + V_A = V$$

Two first order ODEs became one second order ODE:
 “Conservation of misery”

Solution

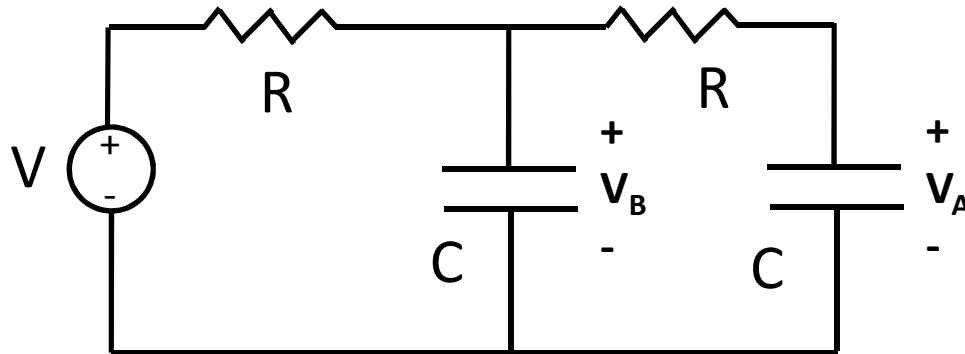


$$\tau^2 \frac{d^2 V_A}{dt^2} + 3\tau \frac{dV_A}{dt} + V_A = V$$

$$\text{Cf. } \frac{d^2 Q}{dt^2} + \frac{R}{L} \frac{dQ}{dt} + \frac{1}{LC} Q = 0$$

$$\frac{d^2 V_A}{dt^2} + \frac{3}{\tau} \frac{dV_A}{dt} + \frac{1}{\tau^2} V_A = \frac{V}{\tau^2}$$

$$\text{Thus, } \Gamma = \frac{R}{2L} = \frac{3}{2\tau} \text{ and } \omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\tau}$$

Solution

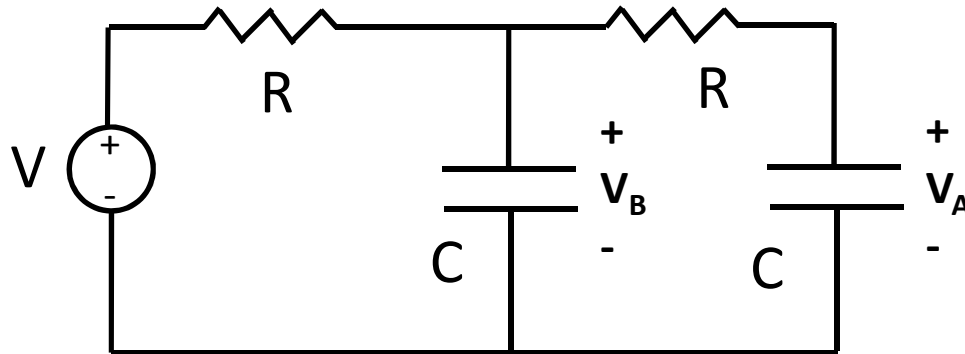


Since $\Gamma = \frac{3}{2\tau}$ and $\omega_o = \frac{1}{\tau}$, $\Gamma > \omega_o$

$$s_{\pm} = -\Gamma \pm \sqrt{\Gamma^2 - \omega_o^2}$$

$$= -\frac{3}{2\tau} \pm \sqrt{\left(\frac{3}{2\tau}\right)^2 - \left(\frac{1}{\tau}\right)^2} = -\frac{3}{2\tau} \pm \frac{\sqrt{5}}{2\tau}$$

Overdamped circuit

Solution

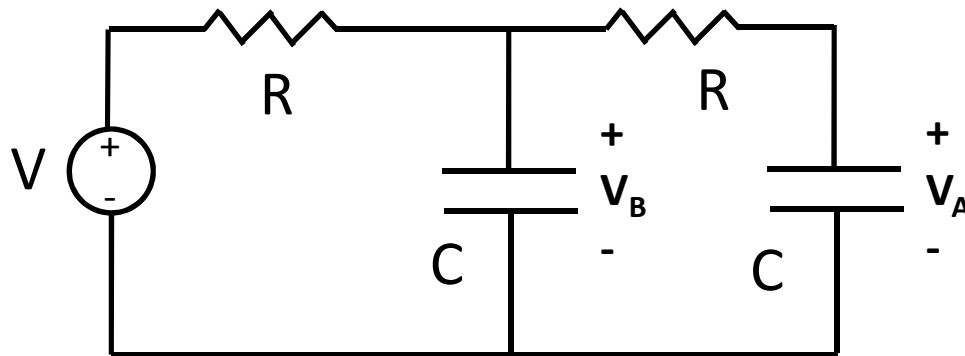

- This circuit offers an alternative oscillator
- Application: timing on a microchip!
- Hard to fit inductors on microchips, but relatively easy to put resistors and capacitors on
- Real clock signals generated in a conceptually related fashion, but more sophisticated

Homework

- HW #21 due today by 4:30 pm in EE 326B
- HW #22 due Fri.: DeCarlo & Lin, Chapter 9:
 - Problem 8
 - For the circuit in the previous problem, find the instantaneous power absorbed by each of the elements. What is the sum of these powers?