

# ECE 201, Section 3

## Lecture 23

Prof. Peter Bermel


October 19, 2012

# Driven Series RLC Circuits

From KVL:

$$\frac{d^2 Q}{dt^2} + \frac{R}{L} \frac{dQ}{dt} + \frac{1}{LC} Q = \frac{V_s}{L}$$
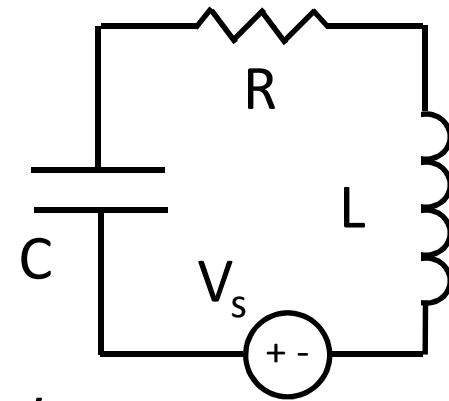
$$\frac{d^2 V_C}{dt^2} + 2\Gamma \frac{dV_C}{dt} + \omega_o^2 V_C = \omega_o^2 V_s$$



$$\Gamma = R/2L; \omega_o = 1/\sqrt{LC}; \omega' = \sqrt{\omega_o^2 - \Gamma^2} = -i\Gamma'$$


Regime	Range	Solution	Behavior
Under-damped	$\Gamma < \omega_o$	$V_C(t) = e^{-\Gamma t} \cos(\omega' t + \phi) + V_s$	Oscillate & decay
Critically damped	$\Gamma = \omega_o$	$V_C(t) = e^{-\Gamma t} (A_1 + A_2 t) + V_s$	Decay
Over-damped	$\Gamma > \omega_o$	$V_C(t) = e^{-\Gamma t} (A_+ e^{\Gamma' t} + A_- e^{-\Gamma' t}) + V_s$	Decay

# Driven Parallel RLC Circuits

From KCL:

$$\frac{d^2 I_L}{dt^2} + \frac{1}{RC} \frac{dI_L}{dt} + \frac{1}{LC} I_L = \frac{I_s}{LC}$$
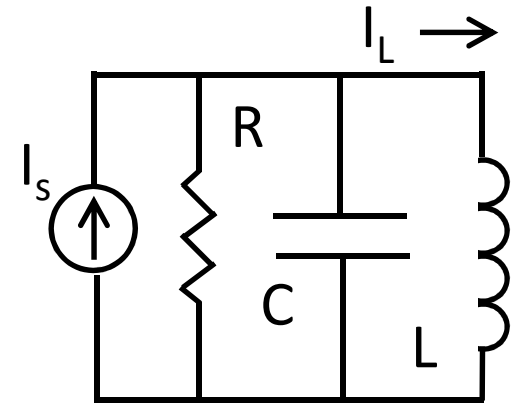
$$\frac{d^2 I_L}{dt^2} + 2\Gamma \frac{dI_L}{dt} + \omega_o^2 I_L = \omega_o^2 I_s$$




$$\Gamma = 1/(2RC); \omega_o = 1/\sqrt{LC}; \omega' = \sqrt{\omega_o^2 - \Gamma^2} = -i\Gamma'$$


Regime	Range	Solution	Behavior
Under-damped	$\Gamma < \omega_o$	$I_L(t) = e^{-\Gamma t} \cos(\omega' t + \phi) + I_s$	Oscillate & decay
Critically damped	$\Gamma = \omega_o$	$I_L(t) = e^{-\Gamma t} (A_1 + A_2 t) + I_s$	Decay
Over-damped	$\Gamma > \omega_o$	$I_L(t) = e^{-\Gamma t} (A_+ e^{\Gamma' t} + A_- e^{-\Gamma' t}) + I_s$	Decay
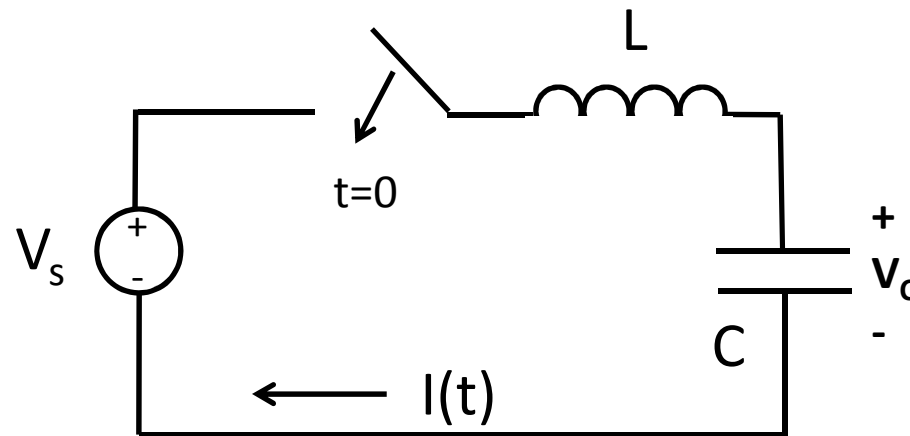
# Example

- Consider an LC circuit connected to a voltage source at  $t=0$ . How will the current and voltage vary with time?



# Solution

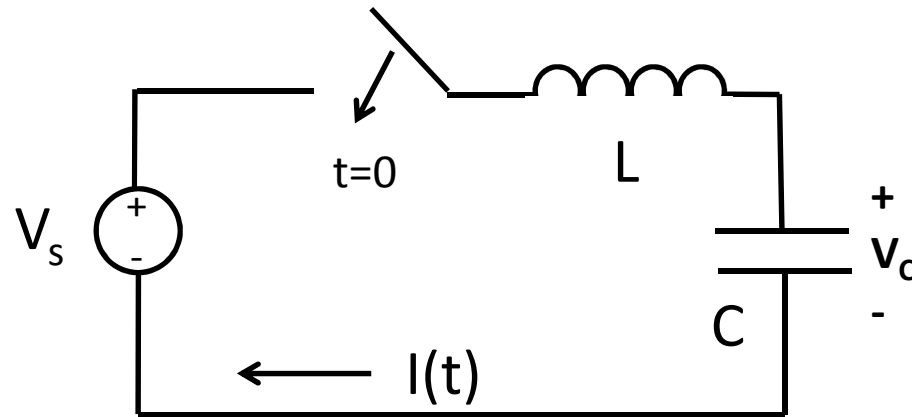

- Employing our solution:


$$I(t) = A_+ e^{s_+ t} + A_- e^{s_- t}$$

$$s_{\pm} = -\Gamma \pm \sqrt{\Gamma^2 - \omega_o^2}$$

$$\Gamma = \frac{R}{2L} = 0; \omega_o = 1/\sqrt{LC}$$

$$s_{\pm} = \pm i\omega_o$$


# Solution

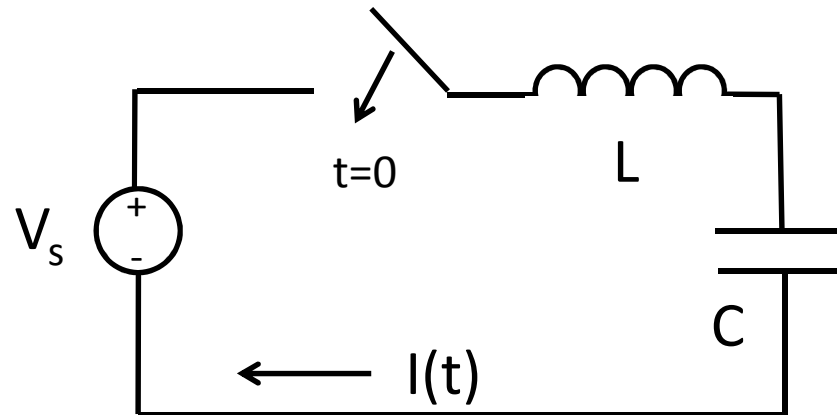

- Employing our solution:

$$\begin{aligned}
 I(t) &= A_+ e^{i\omega_o t} + A_- e^{-i\omega_o t} \\
 \frac{dI}{dt} &= i\omega_o (A_+ e^{i\omega_o t} - A_- e^{-i\omega_o t}) \\
 I(0) &= A_+ + A_- = 0 \\
 V_s &= L \frac{dI}{dt} (t=0) = Li\omega_o (A_+ - A_-) \\
 V_s &= 2iL\omega_o A_+ = -2iL\omega_o A_- \\
 I(t) &= \frac{V_s (e^{i\omega_o t} - e^{-i\omega_o t})}{2iL\omega_o} = \frac{V_s}{L\omega_o} \sin(\omega_o t)
 \end{aligned}$$

# Solution

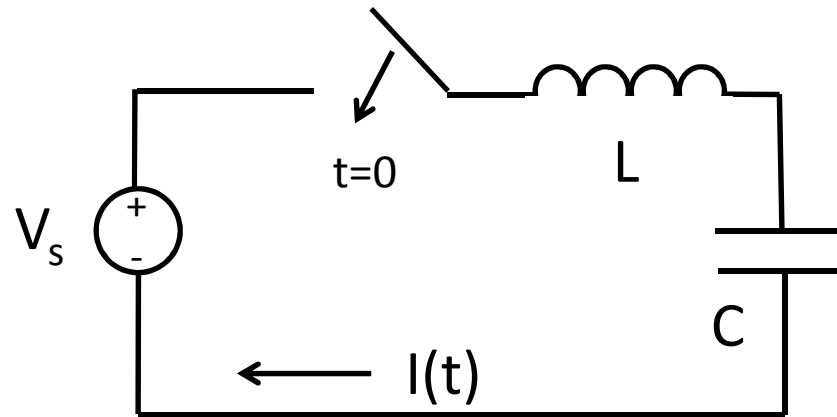

- Given that:

$$I(t) = \frac{V_s}{L\omega_o} \sin(\omega_o t)$$

We can integrate to obtain:


$$V_C(t) = \frac{1}{C} \int_0^t dt' \frac{V_s}{L\omega_o} \sin(\omega_o t') = V_s \int_0^t \omega_o dt' \sin(\omega_o t')$$

$$V_C(t) = -V_s \cos(\omega_o t') \Big|_0^t$$

$$V_C(t) = V_s [1 - \cos(\omega_o t)]$$

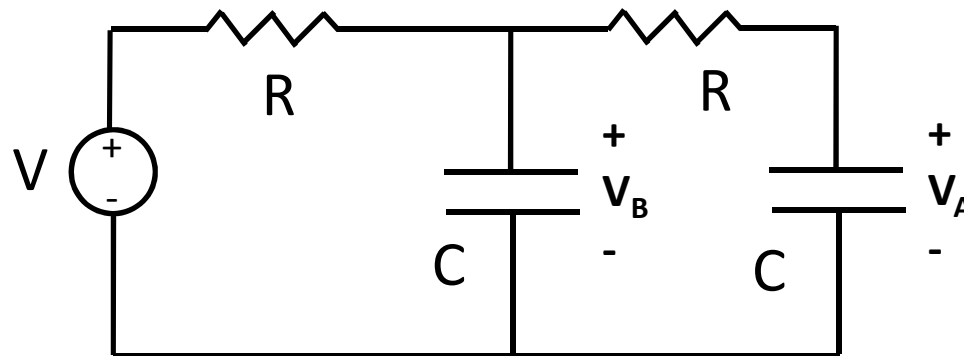
# Example

- What is the equation of motion for the voltage  $v_A(t)$  of the right capacitor? What other system does this resemble, and where might you use this design?






# Solution

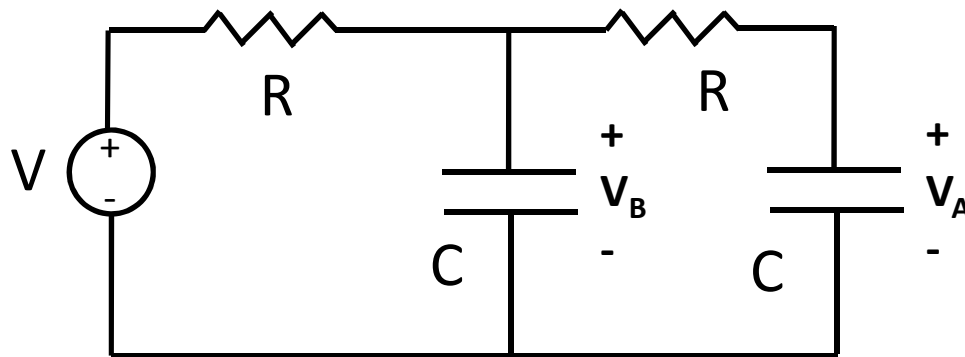

- Taking the derivative of  $Q=CV$  and  $V=IR$ :

$$\frac{V_B - V_A}{R} = C \frac{dV_A}{dt}$$
$$\frac{V - V_B}{R} + \frac{V_A - V_B}{R} = C \frac{dV_B}{dt}$$

# Solution

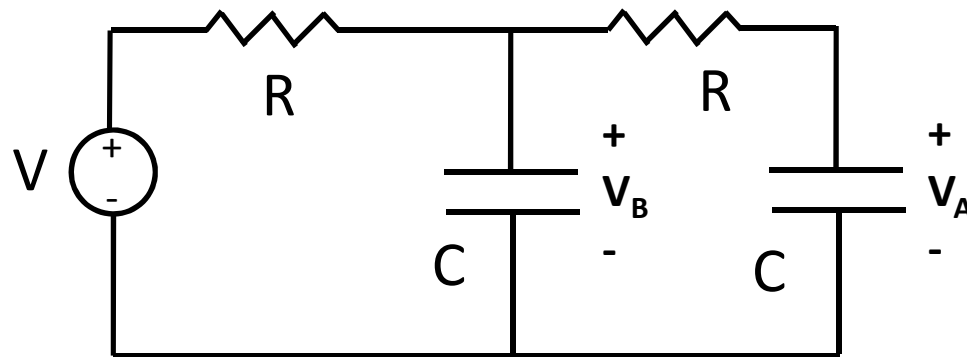


$$V_B - V_A = \tau \frac{dV_A}{dt}$$

$$V + V_A - 2V_B = \tau \frac{dV_B}{dt}$$

Substituting,  $V + V_A - 2 \left( V_A + \tau \frac{dV_A}{dt} \right) = \tau \frac{dV_B}{dt}$

Time derivative yields,  $\frac{dV_B}{dt} - \frac{dV_A}{dt} = \tau \frac{d^2 V_A}{dt^2}$

# Solution

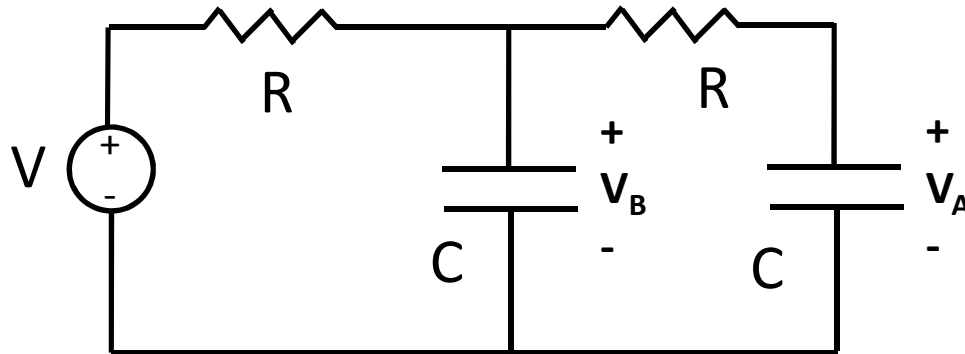


$$V + V_A - 2V_A - 2\tau \frac{dV_A}{dt} = \tau \left( \tau \frac{d^2 V_A}{dt^2} + \frac{dV_A}{dt} \right)$$

$$V - V_A - 3\tau \frac{dV_A}{dt} = \tau^2 \frac{d^2 V_A}{dt^2}$$

$$\tau^2 \frac{d^2 V_A}{dt^2} + 3\tau \frac{dV_A}{dt} + V_A = V$$

Two first order ODEs became one second order ODE:  
 “Conservation of misery”

# Solution

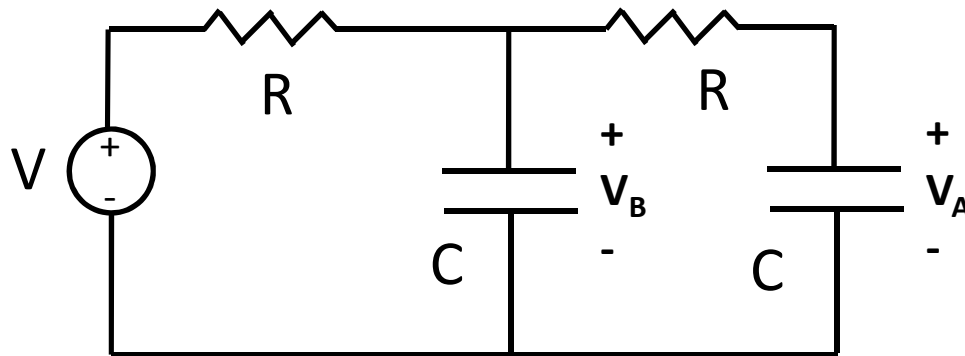


$$\tau^2 \frac{d^2 V_A}{dt^2} + 3\tau \frac{dV_A}{dt} + V_A = V$$

$$\text{Cf. } \frac{d^2 Q}{dt^2} + \frac{R}{L} \frac{dQ}{dt} + \frac{1}{LC} Q = 0$$

$$\frac{d^2 V_A}{dt^2} + \frac{3}{\tau} \frac{dV_A}{dt} + \frac{1}{\tau^2} V_A = \frac{V}{\tau^2}$$

$$\text{Thus, } \Gamma = \frac{R}{2L} = \frac{3}{2\tau} \text{ and } \omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\tau}$$

# Solution

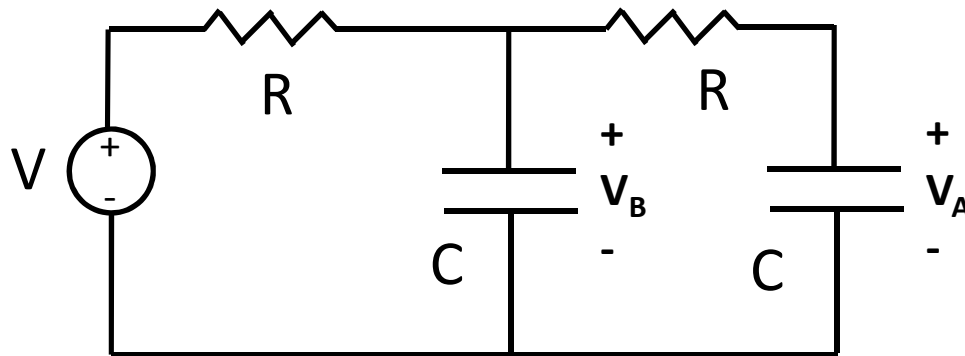


Since  $\Gamma = \frac{3}{2\tau}$  and  $\omega_o = \frac{1}{\tau}$ ,  $\Gamma > \omega_o$

$$s_{\pm} = -\Gamma \pm \sqrt{\Gamma^2 - \omega_o^2}$$

$$= -\frac{3}{2\tau} \pm \sqrt{\left(\frac{3}{2\tau}\right)^2 - \left(\frac{1}{\tau}\right)^2} = -\frac{3}{2\tau} \pm \frac{\sqrt{5}}{2\tau}$$

Overdamped circuit


# Solution

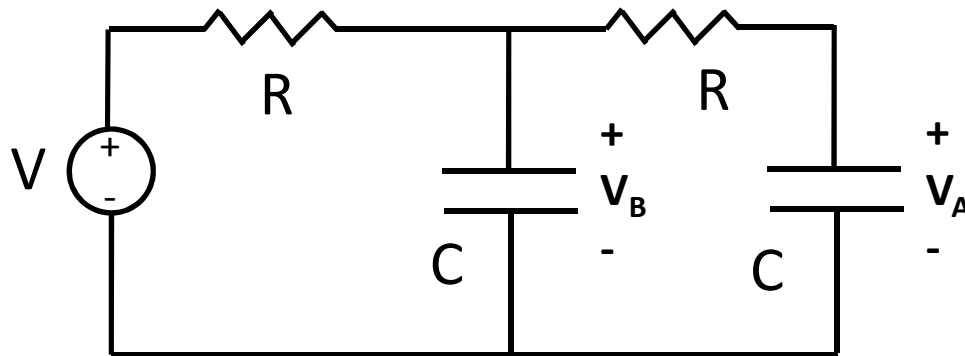


- This circuit offers an alternative oscillator
- Application: timing on a microchip!
- Hard to fit inductors on microchips, but relatively easy to put resistors and capacitors on
- Real clock signals generated in a conceptually related fashion, but more sophisticated
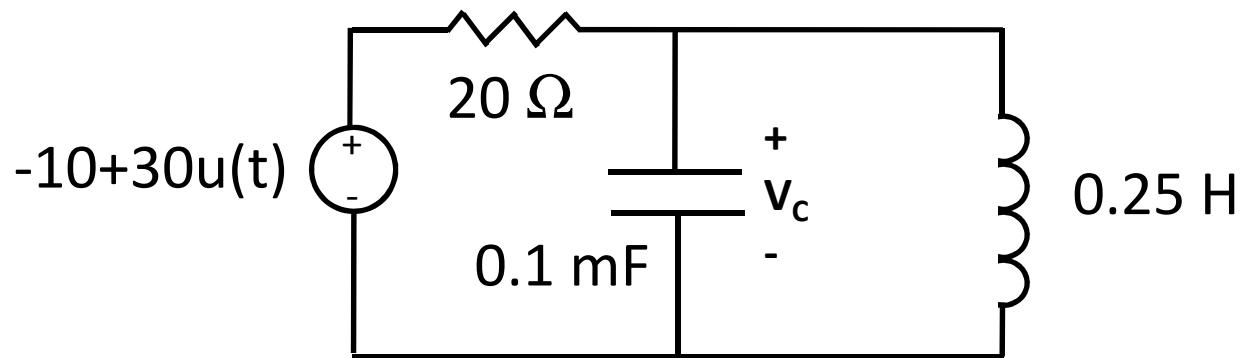
# Example

- Consider a circuit in which input voltage switches from -10 V to +20 V at  $t=0$  (i.e.,  $V = -10 + 30u(t)$ ). What is  $V_c(t)$  at all times?



# Solution

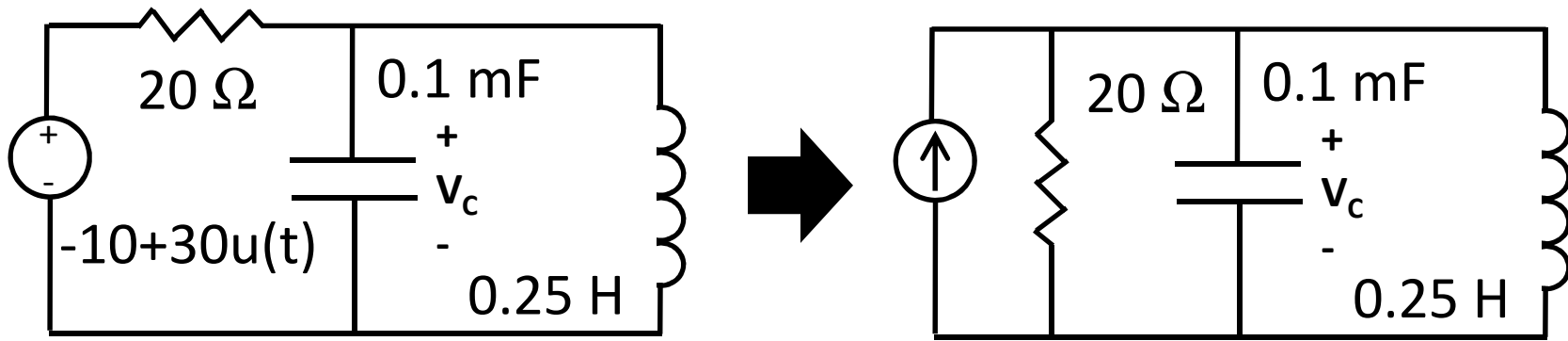


- Use source transformation to recover original parallel RLC circuit problem:

$$I_s = \frac{[-10 + 30u(t)]}{20} = -\frac{1}{2} + \frac{3}{2}u(t)$$



# Solution

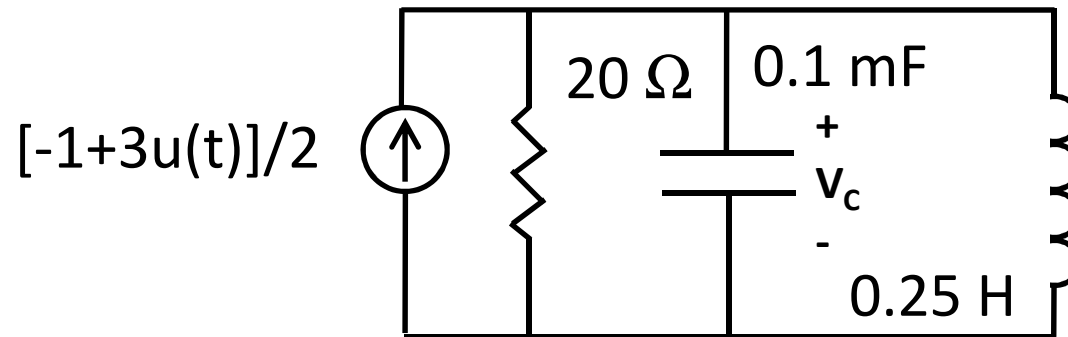


- From earlier definitions:

$$\Gamma = \frac{1}{2RC} = \frac{1}{2 \cdot 20 \cdot 10^{-4}} = 250$$

$$\omega_o = \frac{1}{\sqrt{0.25 \cdot 10^{-4}}} = 200$$

- Circuit is overdamped

# Solution

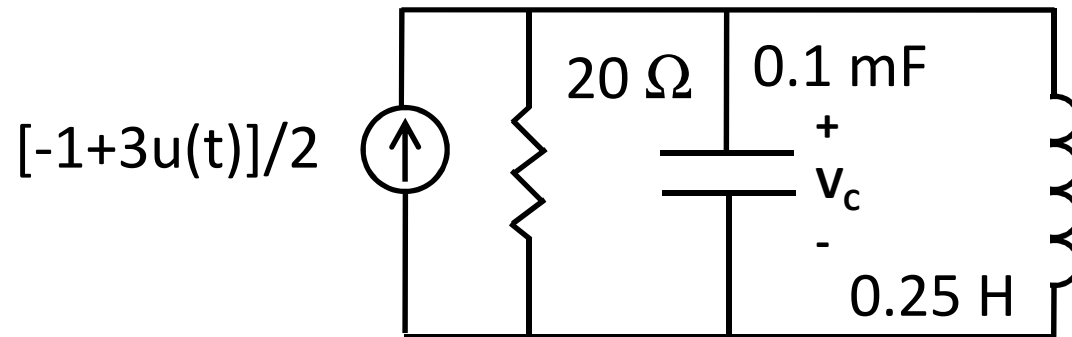


- For  $t < 0$ , inductor looks like short and  $V_c(t < 0) = 0$
- For  $t > 0$ , non-zero voltage temporarily possible; start by solving for  $I_L$  in overdamped regime:

$$I_L(t) = e^{-\Gamma t} (A_+ e^{\Gamma' t} + A_- e^{-\Gamma' t}) + I_s$$

Here,  $\Gamma = 250$ , and

$$\Gamma' = \sqrt{\Gamma^2 - \omega_0^2} = \sqrt{250^2 - 200^2} = 150$$

# Solution

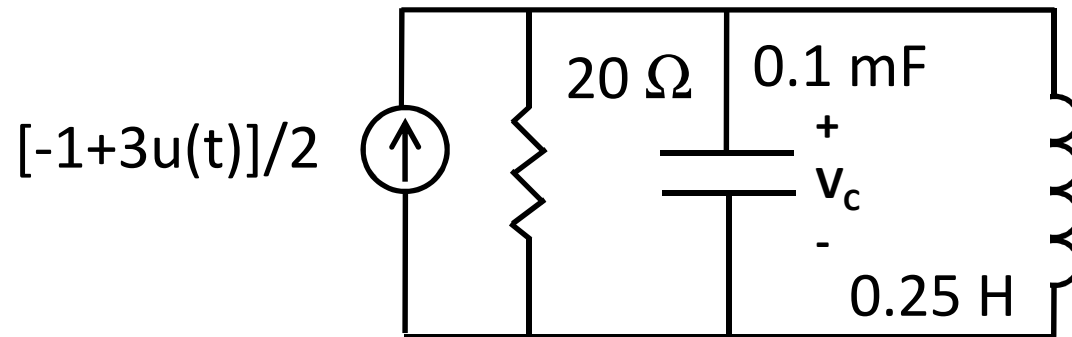

- Given that:

$$I_L(t \geq 0) = e^{-250t}(A_+e^{150t} + A_-e^{-150t}) + 1$$

$$= A_+e^{-100t} + A_-e^{-400t} + 1$$


- Since  $I_L(0) = -1/2$ , and  $V_C(0) = 0$ :

$$-\frac{1}{2} = A_+ + A_- + 1 \rightarrow A_+ = -\frac{3}{2} - A_-$$

$$0.25(-100A_+ - 400A_-) = 0 \rightarrow A_+ = -4A_-$$

- Thus,  $A_- = 1/2$ , and  $A_+ = -2$

# Solution

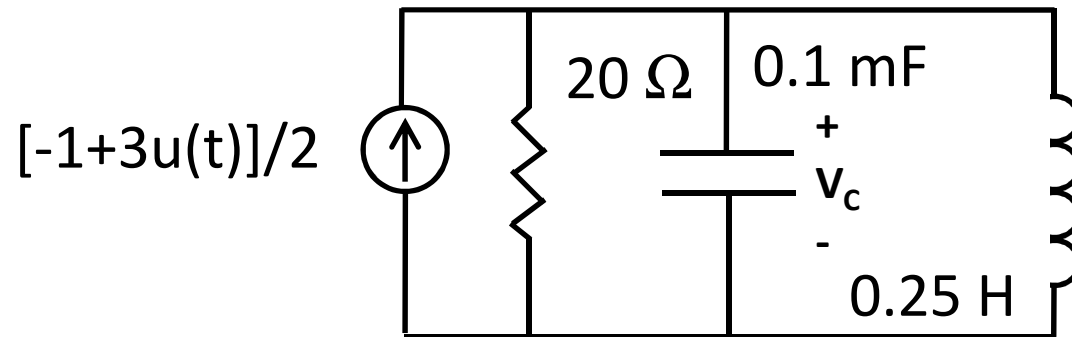


$$I_L(t \geq 0) = -2e^{-100t} + \frac{1}{2}e^{-400t} + 1$$

- Since circuit elements are in parallel:

$$\begin{aligned} V_C(t \geq 0) &= L \frac{dI_L}{dt} \\ &= 0.25 \left( -2(-100)e^{-100t} + \frac{1}{2}(-400)e^{-400t} \right) \\ &= 50(e^{-100t} - e^{-400t}) \end{aligned}$$

# Solution

Voltage ( $V_c$ )

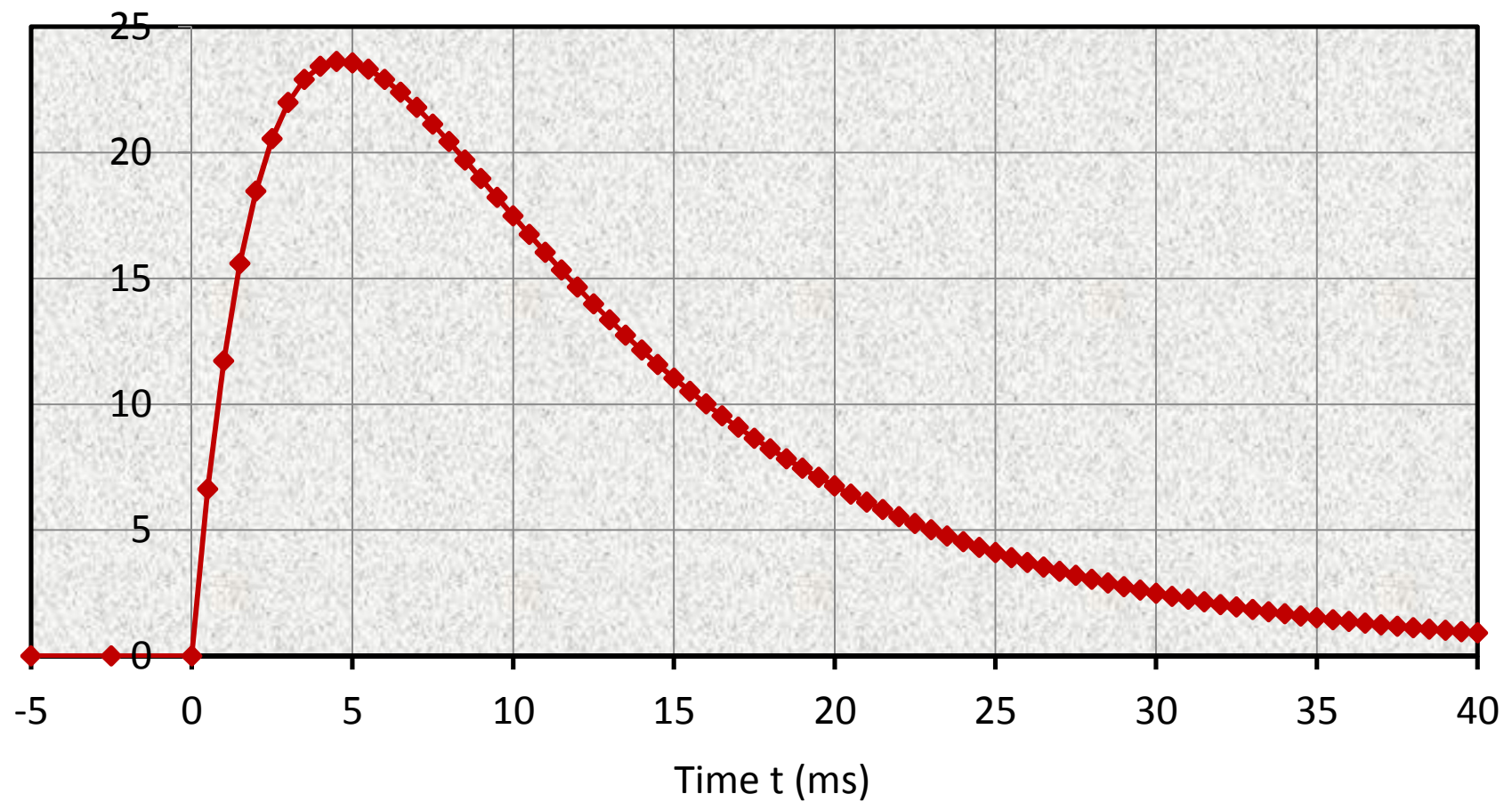

# Homework

- HW #22 due today by 4:30 pm in EE 326B
- HW #23 due Mon.: DeCarlo & Lin, Chapter 9:
  - Problem 11(a) [Correction: the second  $i_L(0^-)$  should be  $i_L(0^+)$ ]
  - Problem 18
  - Problem 27