

ECE 201, Section 3

Lecture 24

Prof. Peter Bermel


October 22, 2012

Driven Parallel RLC Circuits

From KCL:

$$\frac{d^2 I_L}{dt^2} + \frac{1}{RC} \frac{dI_L}{dt} + \frac{1}{LC} I_L = \frac{I_s}{LC}$$
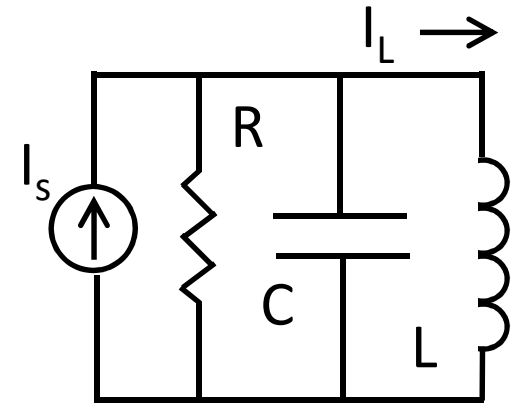
$$\frac{d^2 I_L}{dt^2} + 2\Gamma \frac{dI_L}{dt} + \omega_o^2 I_L = \omega_o^2 I_s$$




$$\Gamma = 1/(2RC); \omega_o = 1/\sqrt{LC}; \omega' = \sqrt{\omega_o^2 - \Gamma^2} = -i\Gamma'$$


Regime	Range	Solution	Behavior
Under-damped	$\Gamma < \omega_o$	$I_L(t) = I_o e^{-\Gamma t} \cos(\omega' t + \phi) + I_s$	Oscillate & decay
Critically damped	$\Gamma = \omega_o$	$I_L(t) = e^{-\Gamma t} (A_1 + A_2 t) + I_s$	Decay
Over-damped	$\Gamma > \omega_o$	$I_L(t) = e^{-\Gamma t} (A_+ e^{\Gamma' t} + A_- e^{-\Gamma' t}) + I_s$	Decay

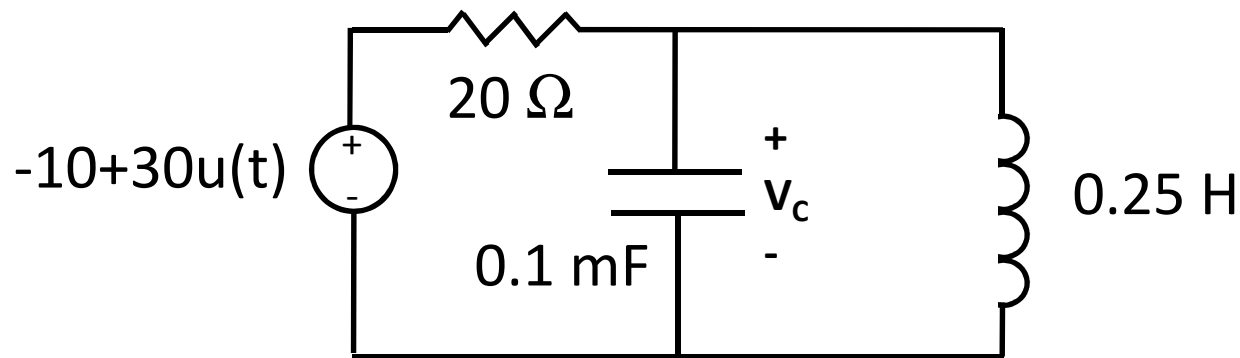Example (continued from last time)

- Consider a circuit in which input voltage switches from -10 V to +20 V at $t=0$ (i.e., $V = -10 + 30u(t)$). What is $V_C(t)$ at all times?



Solution

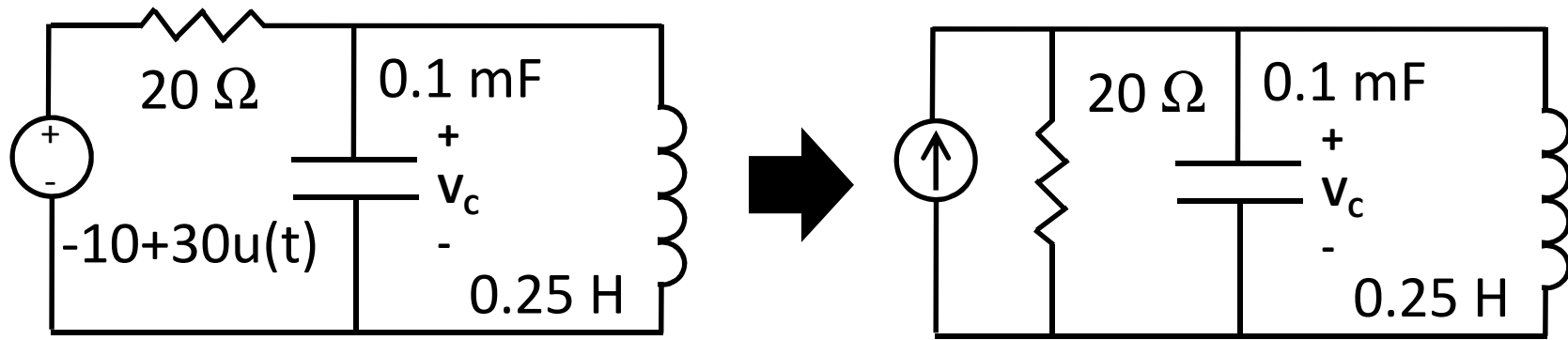


- Recall:

$$I_s = -\frac{1}{2} + \frac{3}{2}u(t)$$

$$\Gamma = \frac{1}{2RC} = \frac{1}{2 \cdot 20 \cdot 10^{-4}} = 250$$

$$\omega_o = \frac{1}{\sqrt{0.25 \cdot 10^{-4}}} = 200$$

Solution

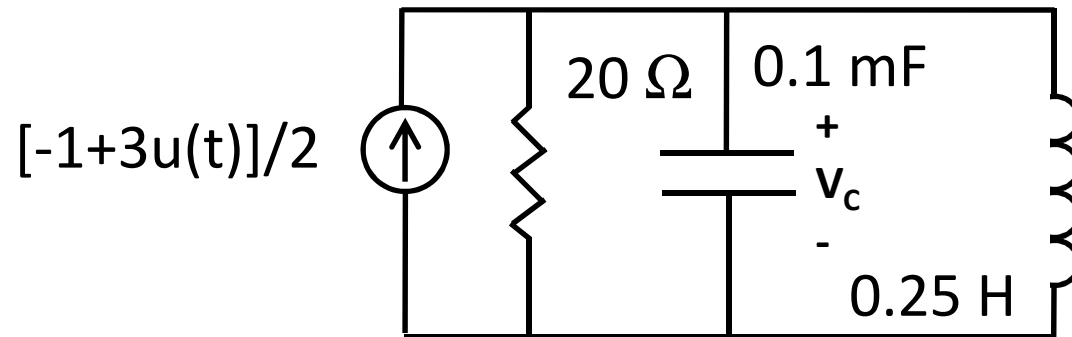


- For $t < 0$, inductor looks like short and $V_c(t < 0) = 0$
- For $t > 0$, non-zero voltage temporarily possible; start by solving for I_L in overdamped regime:

$$I_L(t) = e^{-\Gamma t} (A_+ e^{\Gamma' t} + A_- e^{-\Gamma' t}) + I_s$$

Here, $\Gamma = 250$, and

$$\Gamma' = \sqrt{\Gamma^2 - \omega_0^2} = \sqrt{250^2 - 200^2} = 150$$

Solution

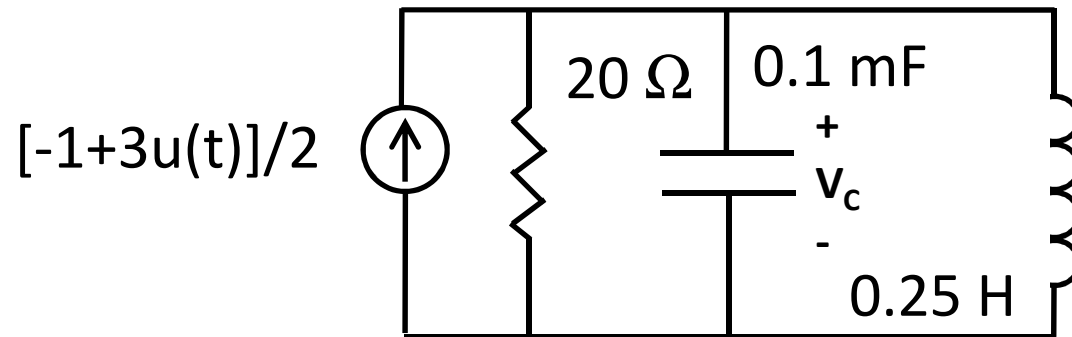

- Given that:

$$I_L(t \geq 0) = e^{-250t}(A_+e^{150t} + A_-e^{-150t}) + 1$$

$$= A_+e^{-100t} + A_-e^{-400t} + 1$$


- Since $I_L(0) = -1/2$, and $V_C(0) = 0$:

$$-\frac{1}{2} = A_+ + A_- + 1 \rightarrow A_+ = -\frac{3}{2} - A_-$$

$$0.25(-100A_+ - 400A_-) = 0 \rightarrow A_+ = -4A_-$$

- Thus, $A_- = 1/2$, and $A_+ = -2$

Solution

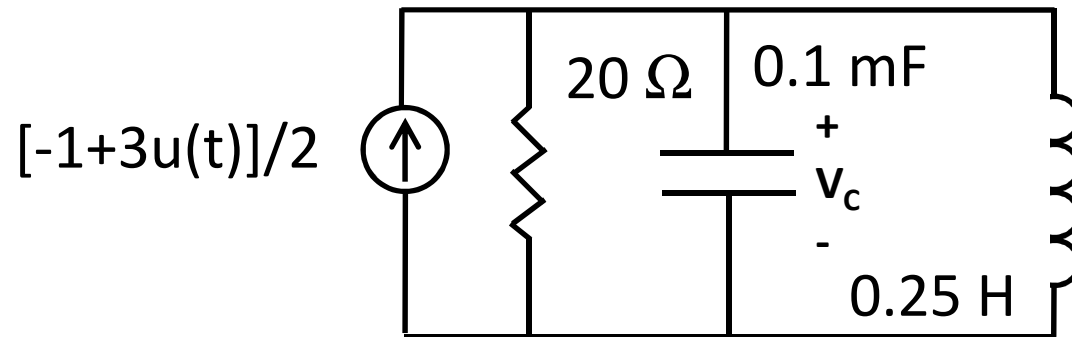


$$I_L(t \geq 0) = -2e^{-100t} + \frac{1}{2}e^{-400t} + 1$$

- Since circuit elements are in parallel:

$$\begin{aligned} V_C(t \geq 0) &= L \frac{dI_L}{dt} \\ &= 0.25 \left(-2(-100)e^{-100t} + \frac{1}{2}(-400)e^{-400t} \right) \\ &= 50(e^{-100t} - e^{-400t}) \end{aligned}$$



Solution

Voltage (V_c)

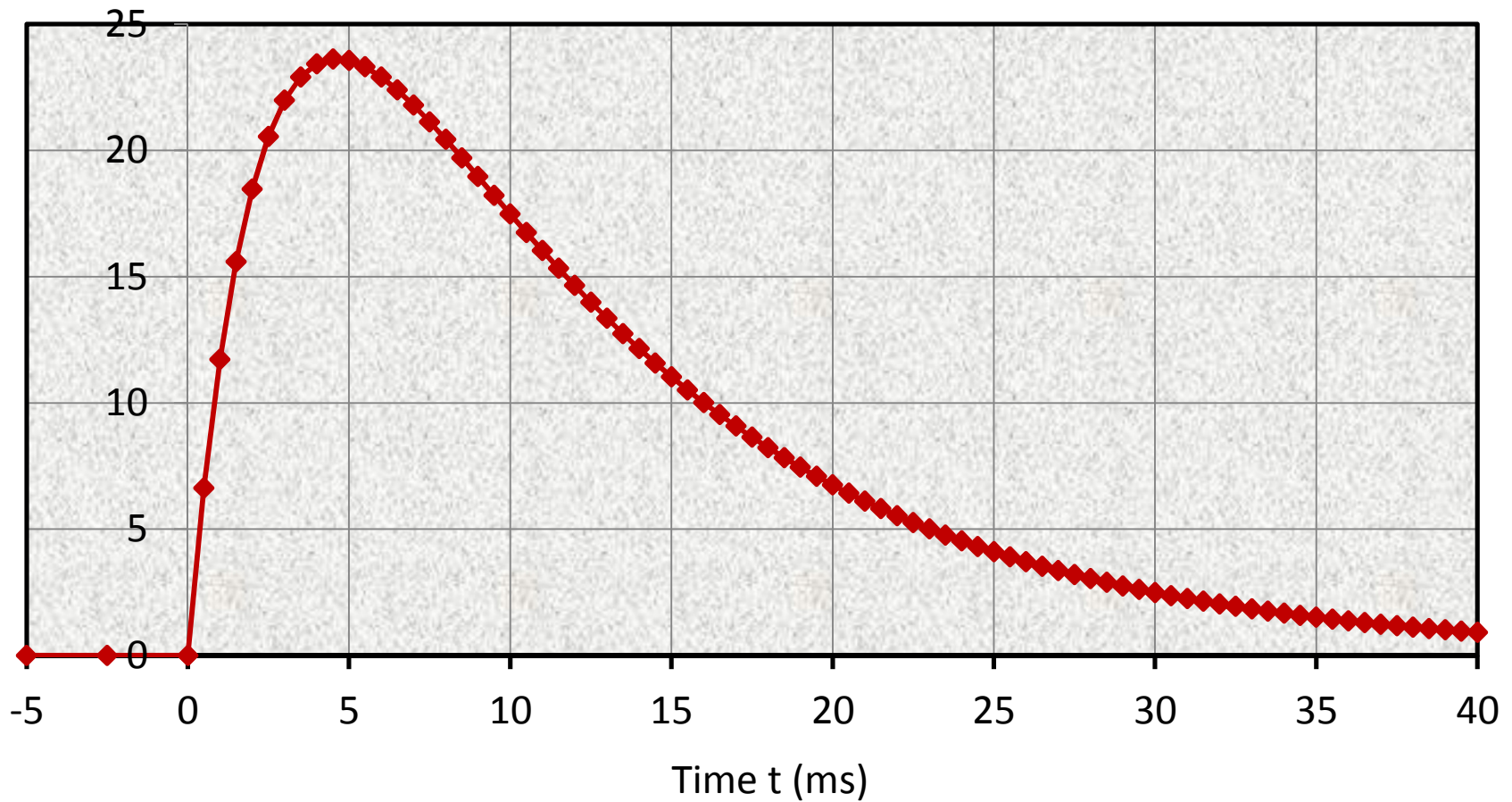

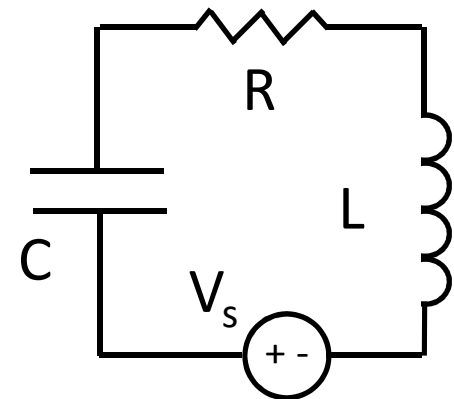
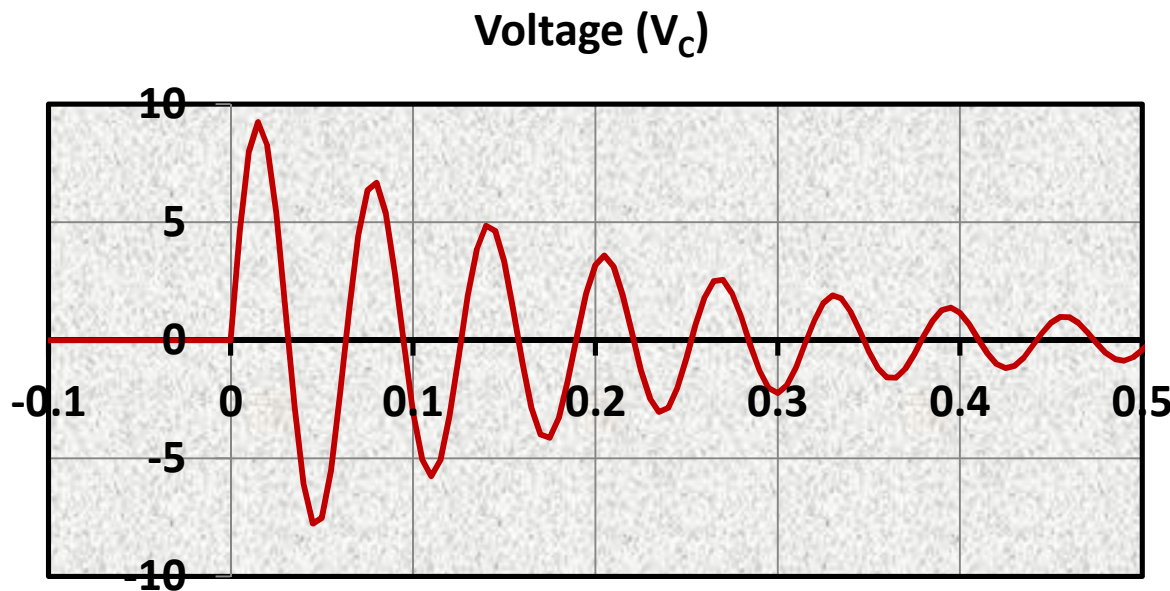
Example 2

- Given the RLC voltage data below, a $1\ \Omega$ resistor, and an input of 10 V turned on at $t=0$, what are the approximate values of L and C ?



Solution

Voltage (V_C)

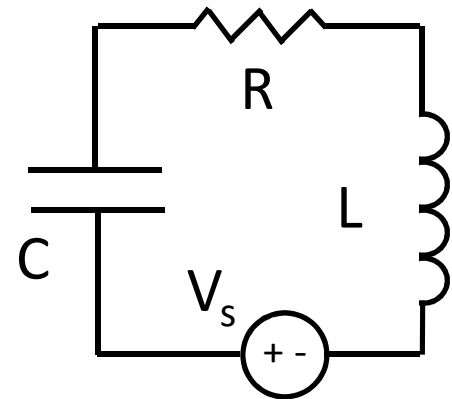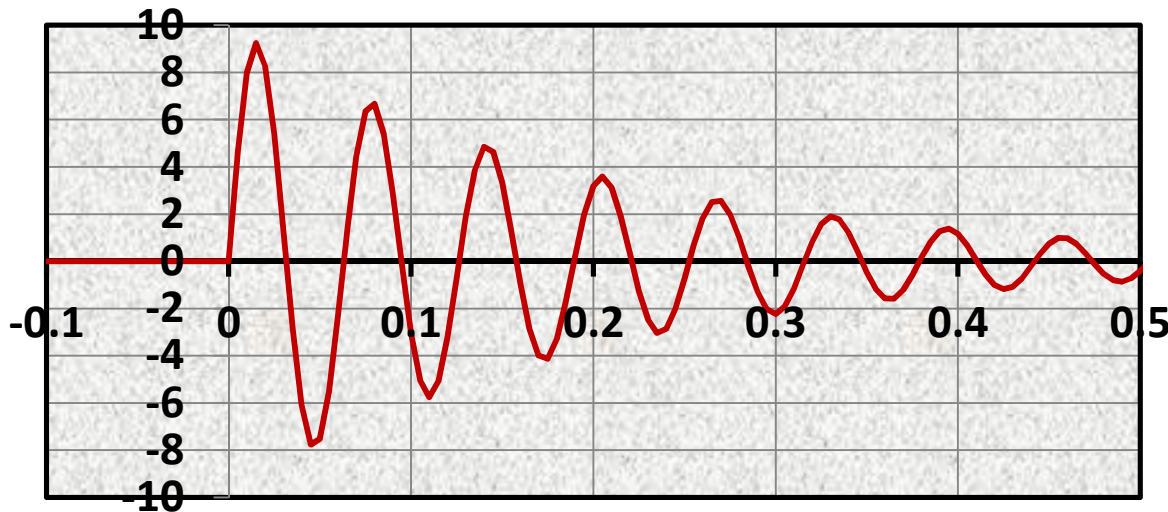



- Recall that underdamped RLC circuits obey:

$$V_C(t) = e^{-\Gamma t} \cos(\omega' t + \phi) + V_s$$

From inspection, completes 8 periods in about 0.5 seconds, implying $\omega' = 2\pi/(0.5/8) = 32\pi \approx 100$

Solution



Voltage (V_C)

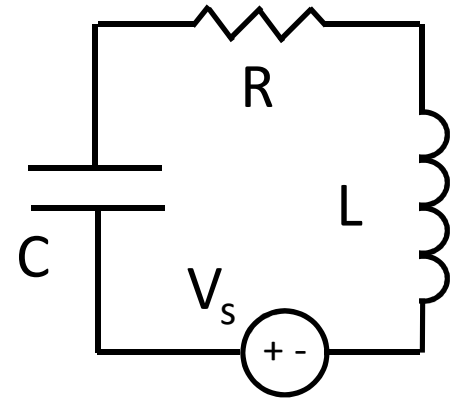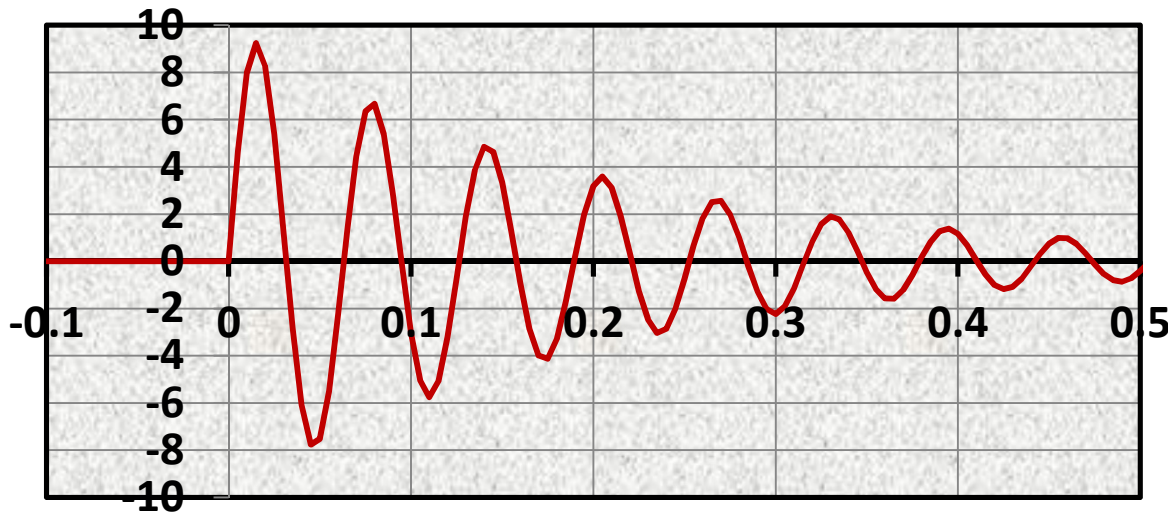

- Also decays by a factor of 10 in about 0.5 seconds. Since $\Gamma t = \ln[V_C(0)/V_C(t)] = \ln 10 \approx 2.3 = \Gamma(0.5)$, we estimate $\Gamma = 4.6$.
- Given that $R=1\ \Omega$, and $\Gamma = R/2L$, we obtain
$$L = \frac{R}{2\Gamma} \approx \frac{1}{2 \cdot 4.6} \approx 0.109$$

Solution

Voltage (V_C)

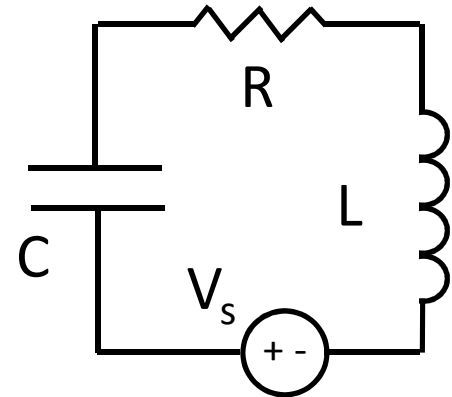
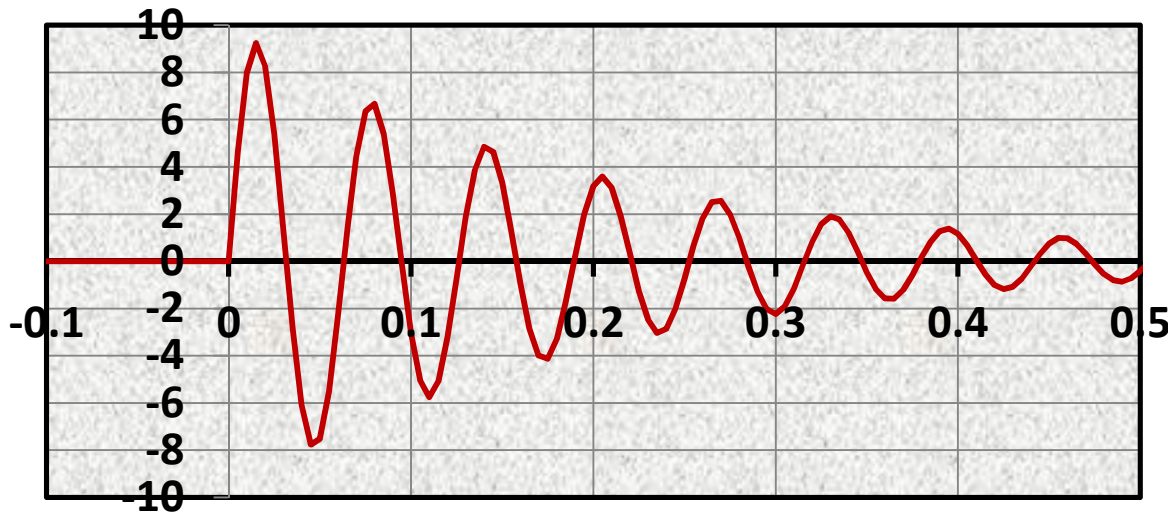


- Combining our previous results of $L \approx 0.109$ and $\omega' \approx 100$, and noting $Q \gg 1$, we can estimate $\omega' \approx \omega_o$. Since $\omega_o = \frac{1}{\sqrt{LC}}$,

$$C = 1/(L\omega_o^2) \approx 1/(0.109 \cdot 100^2) \approx 0.92 \text{ mF}$$

Solution


Voltage (V_C)

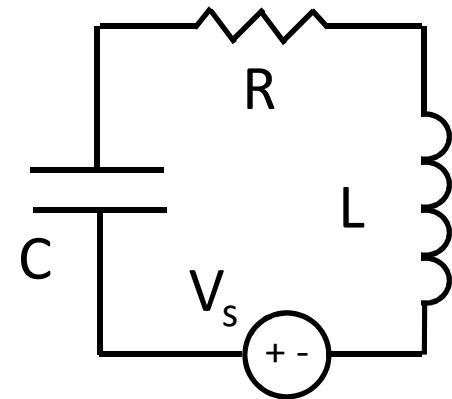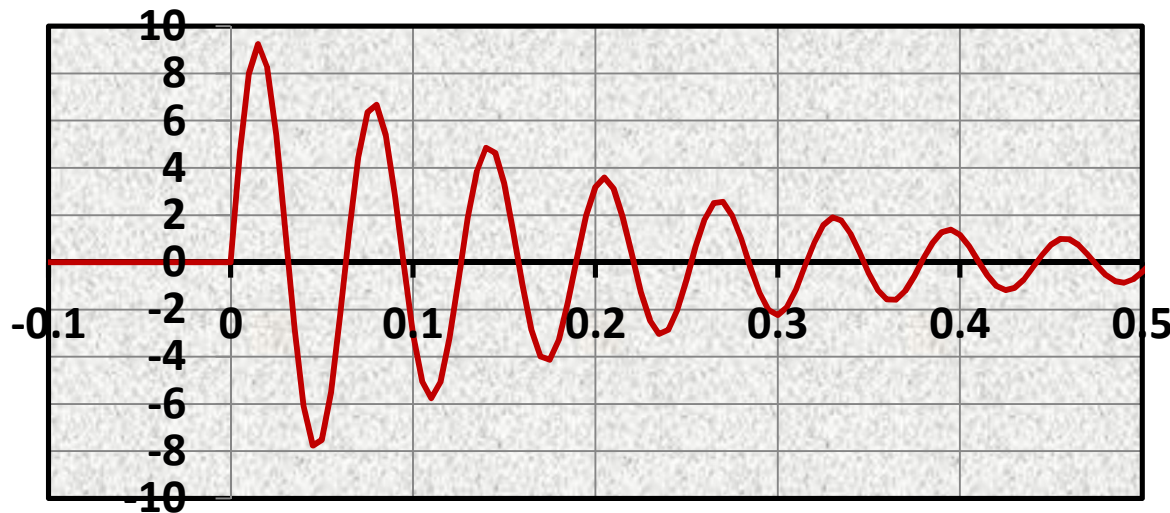


Quantity	Actual Value	Estimated value	Error
Inductance	0.1 H	0.109 H	9%
Capacitance	1 mF	0.92 mF	8%

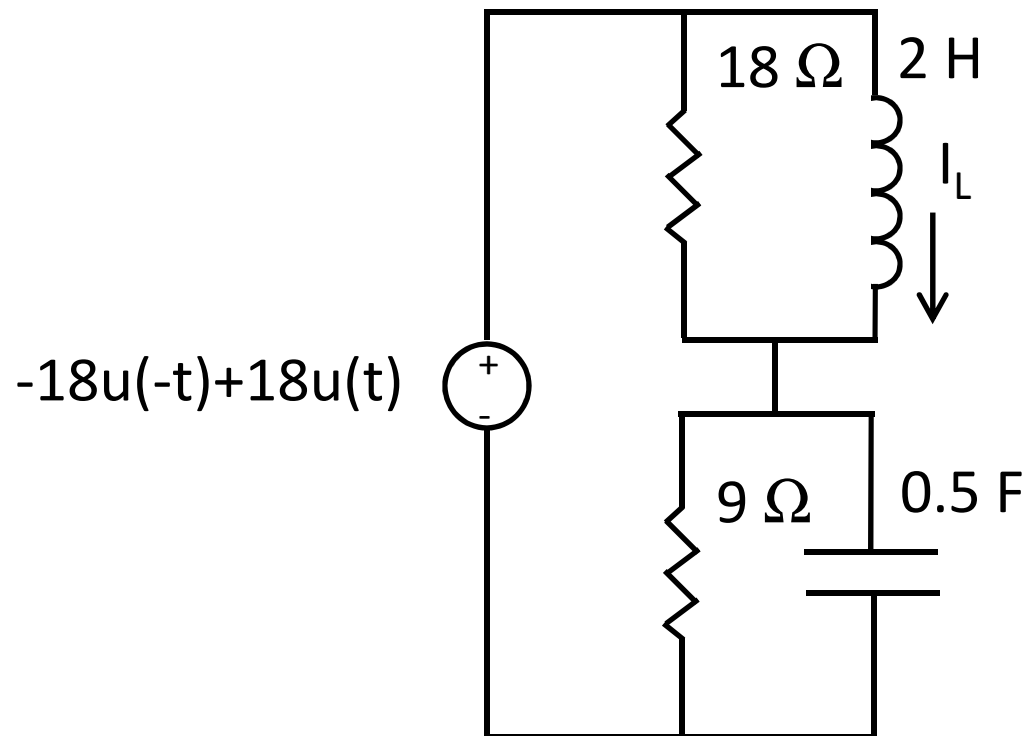Example 3

- For this circuit, with an independent source stepped up at $t=0$, what is $I_L(t)$ at all times?




Solution

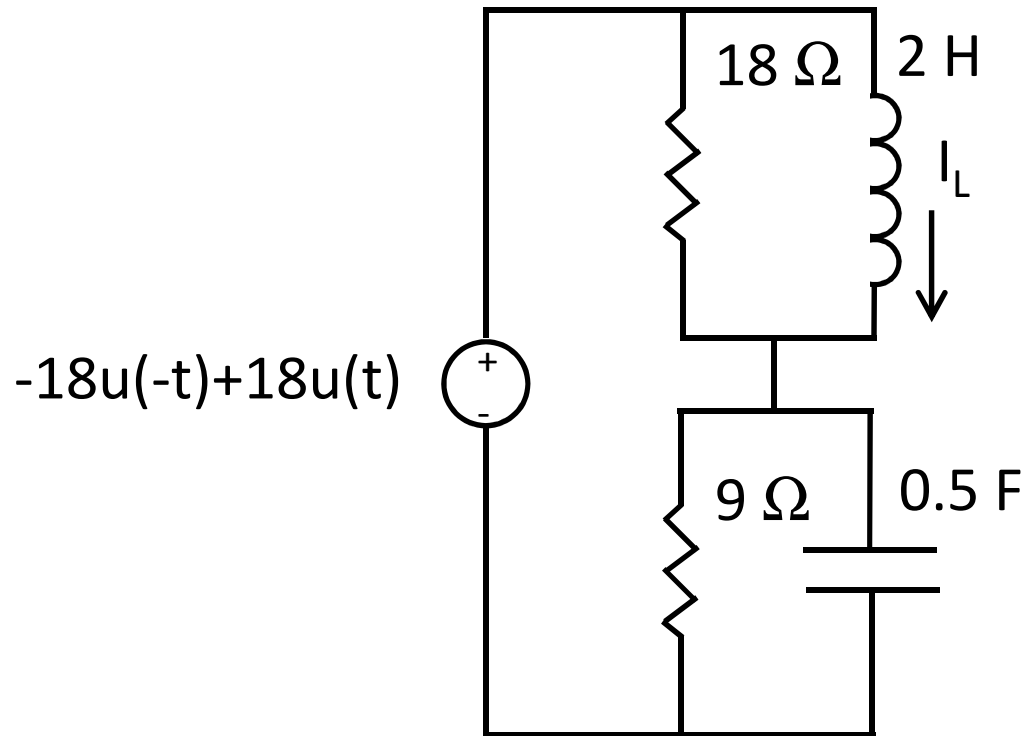


- For $t < 0$, steady state means inductor acts as wire, $V_C(t < 0) = -24\text{ V}$; $I_L(t < 0) = -18/9 = -2\text{ A}$
- At $t = 0$, inductor acts as current source; capacitor as voltage source

Solution

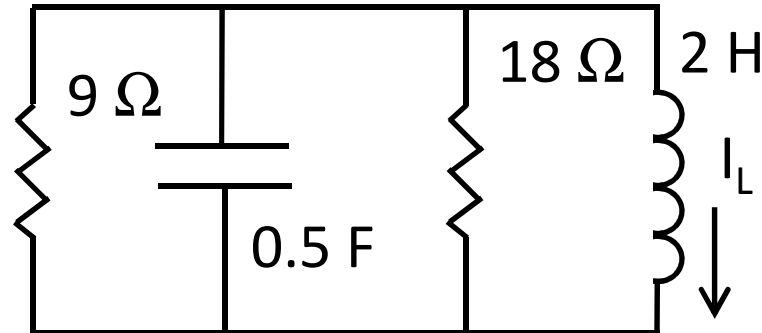


- Ignoring voltage source, circuit reduces to parallel RLC circuit, so that $\Gamma = \frac{1}{2RC} = \frac{1}{2 \cdot 6\Omega \cdot 0.5 F} = 1/6$;
 $\omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{2 H \cdot 0.5 F}} = 1 \text{ rad/s}$;
 $\omega' = \sqrt{\omega_o^2 - \Gamma^2} = \sqrt{1 - (1/6)^2} = \sqrt{35}/6 \text{ rad/s}$

Solution

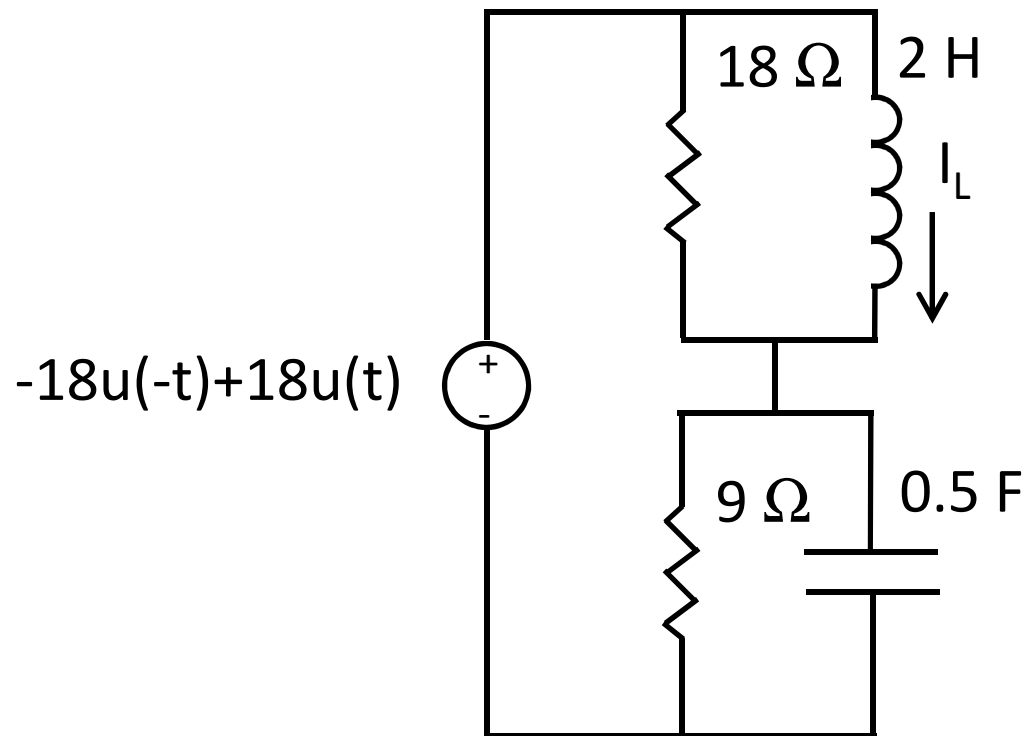

- We know $I_L(t) = I_o e^{-\Gamma t} \cos(\omega' t + \phi) + I_s$
- $I_L(0) = -2\text{ A}$; $L \frac{dI_L}{dt} = [18 - (-18)]\text{ V}$; $I_s = 2\text{ A}$

Solution

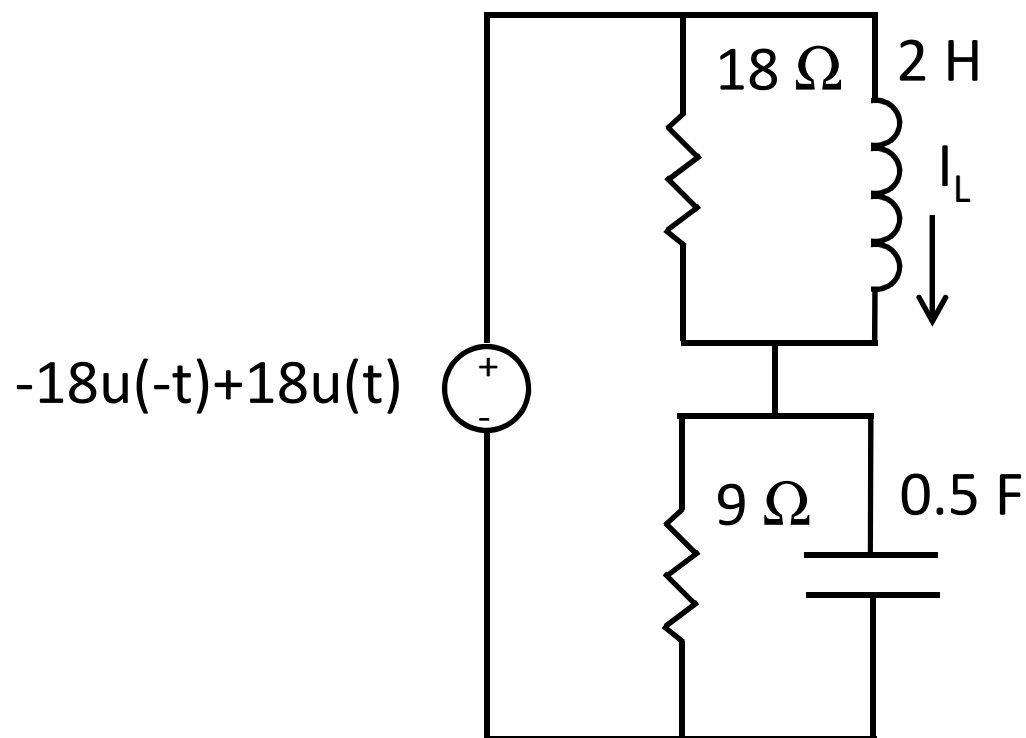


- From our initial conditions:

$$I_L(0) = -2 = 2 + I_o e^{-t/6} \cos\left(\frac{\sqrt{35}}{6}t + \phi\right)$$

$$\frac{dI_L}{dt}(0) = 18 = I_o e^{-t/6} \left[-\frac{1}{6} \cos\left(\frac{\sqrt{35}}{6}t + \phi\right) - \frac{\sqrt{35}}{6} \sin\left(\frac{\sqrt{35}}{6}t + \phi\right) \right]$$

Solution

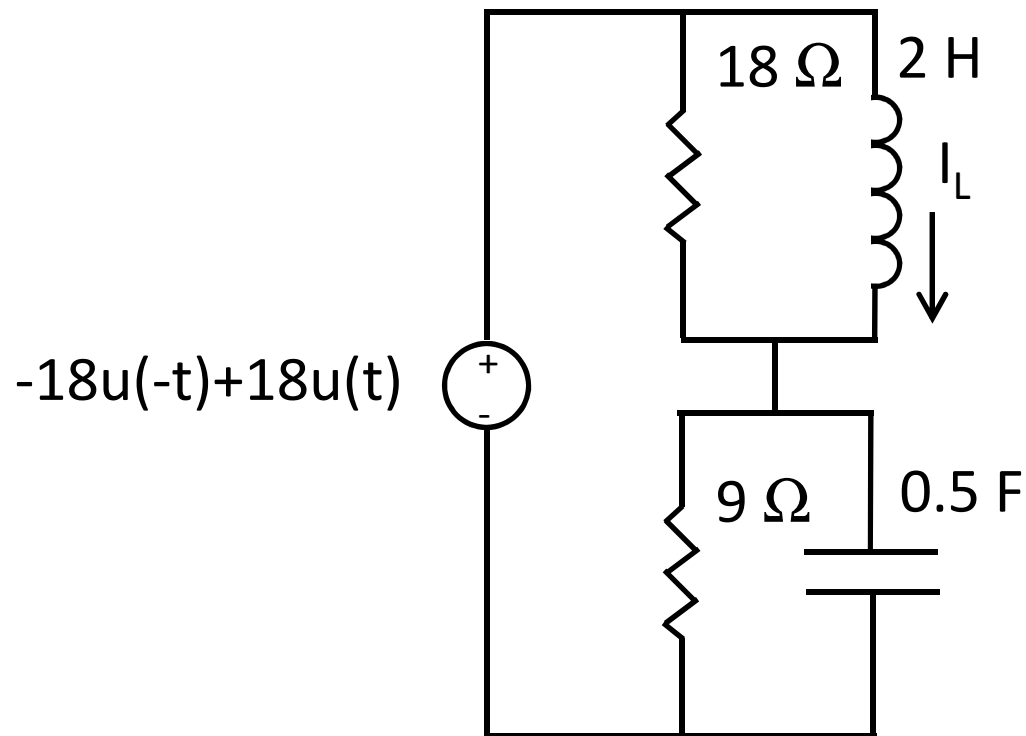

- Set $t=0$ explicitly, and define $C = \cos(\phi)$:

$$-4 = I_o C$$

$$(-6) \cdot 18 = I_o \left[C - \sqrt{35(1 - C^2)} \right]$$

Solution

- Substituting yields:

$$-108 = \left(-\frac{4}{C}\right) \left[C - \sqrt{35(1 - C^2)}\right]$$


$$-104 = 4 \sqrt{35 \left(\frac{1}{C^2} - 1\right)}$$

$$26^2 = \frac{35}{C^2} - 35$$

$$C^2 = \frac{35}{676+35} = 0.049; C = 0.222; \phi = 77.2^\circ$$

$$I_o = -\frac{4}{C} = -18.02$$

Solution

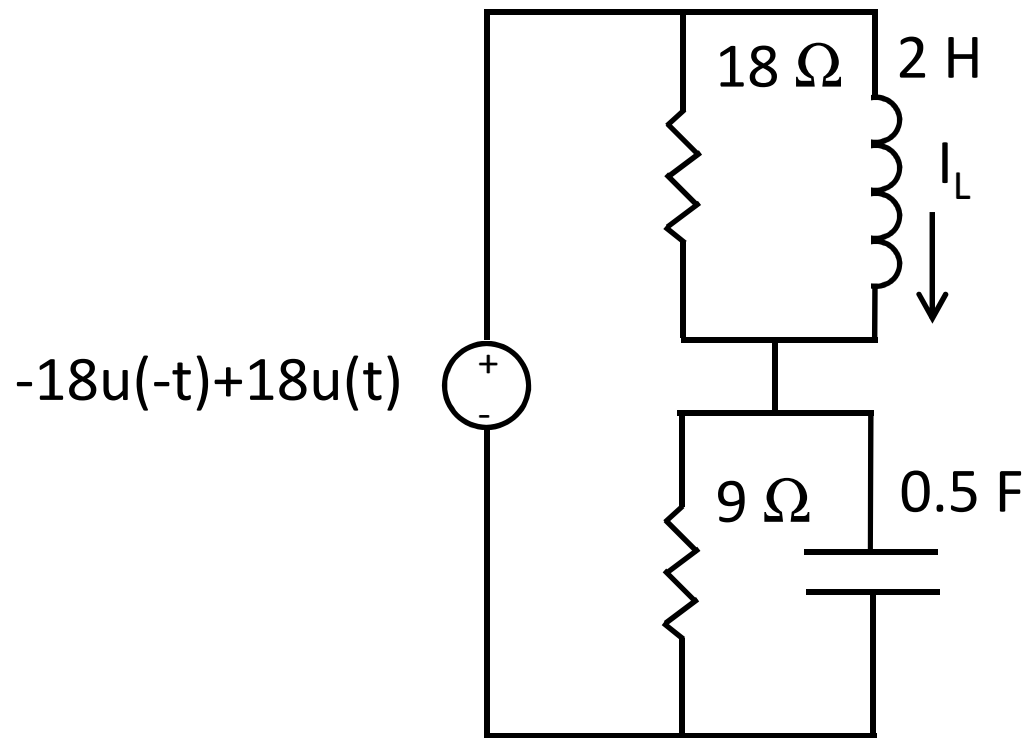


- Substituting, we obtain:

$$I_L(t) = 2 - 18.02e^{-t/6} \cos\left(\frac{\sqrt{35}}{6}t + 77.2^\circ\right)$$

Solution

Current (I_L)

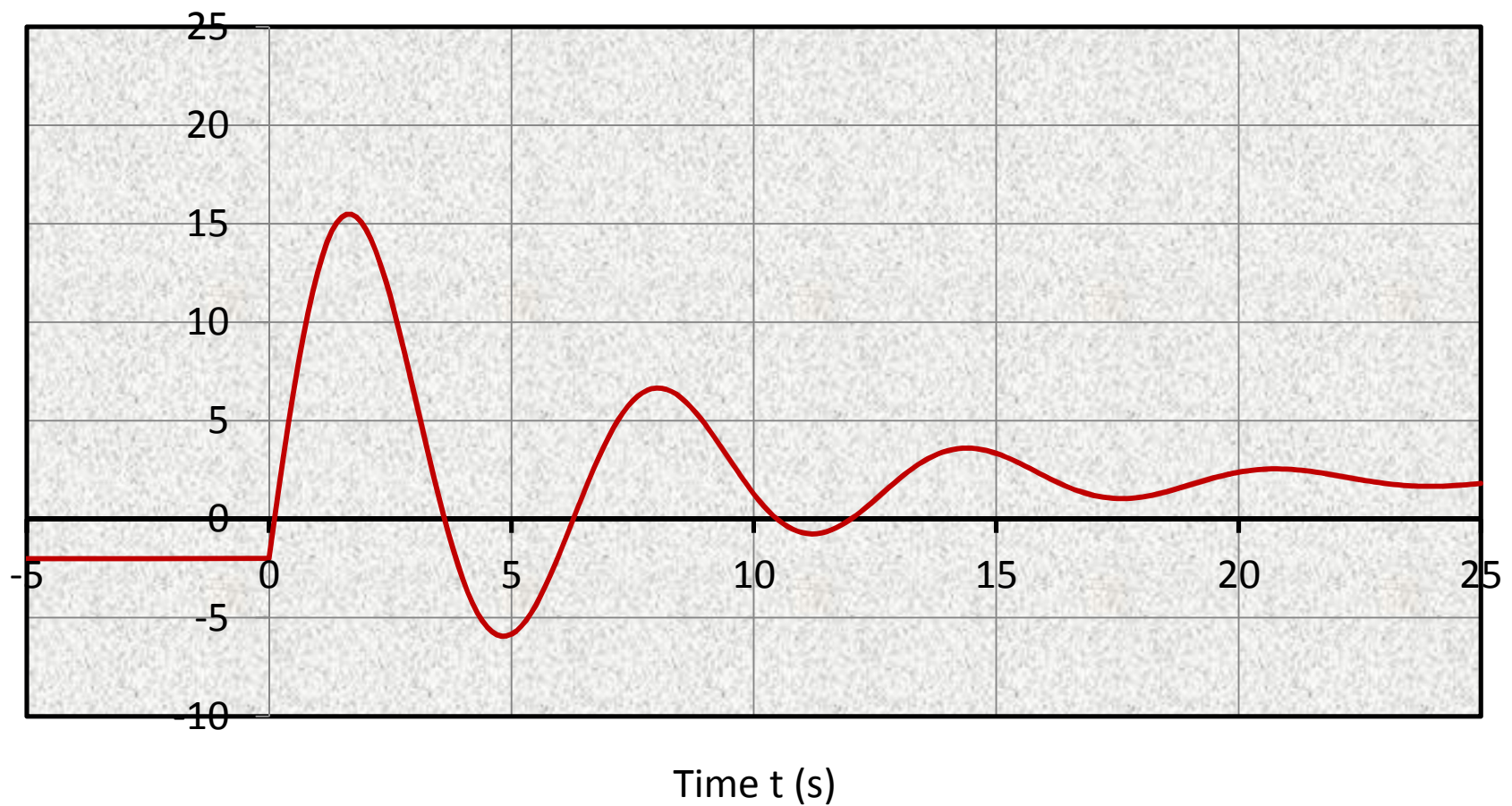

Homework

- HW #23 due today by 4:30 pm in EE 326B
- HW #24 due Wed.: DeCarlo & Lin, Chapter 9:
 - Problem 24
 - Problem 29