


ECE 201, Section 3

Lecture 26



Prof. Peter Bermel

October 26, 2012

3 Views of Op-Amps

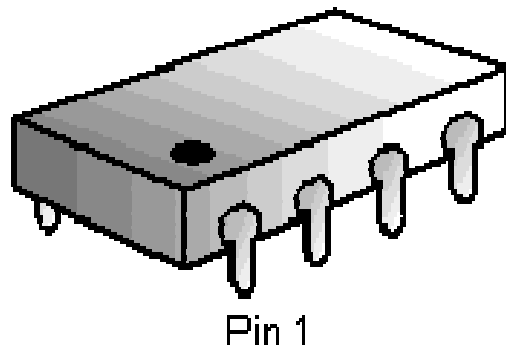

741 Op amp

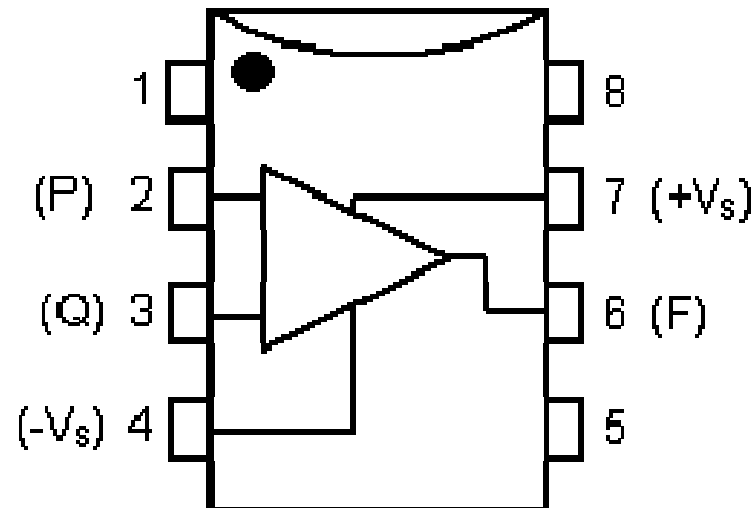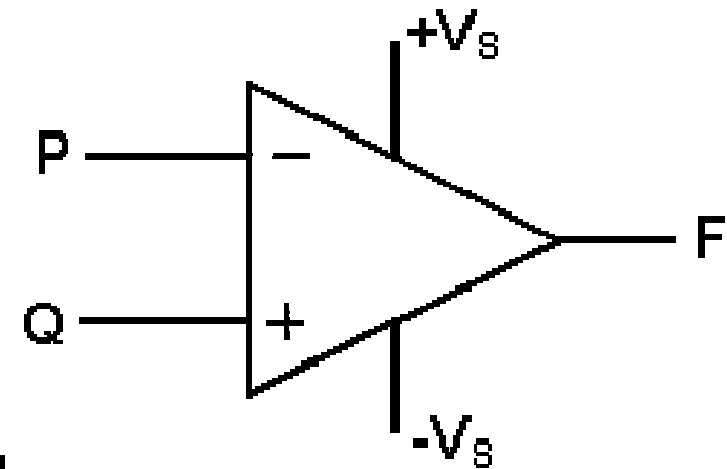

Op-Amp Applications

- Differential and summing amplifiers
- Filters
- Rectifiers
- Differentiators + Integrators
- Audio, video, and charge amplifiers
- Gyration
- Ordinary, relaxation, and Wien bridge oscillators
- Comparators
- Waveform generators
- Active filters
- Capacitance multipliers
- Zero-level detectors
- Logarithmic and exponential outputs
- Negative impedance converter

Op-Amp Application Examples


Mechanical motor controller

LED audio detector


Cell phone detector

Ideal Op-Amps

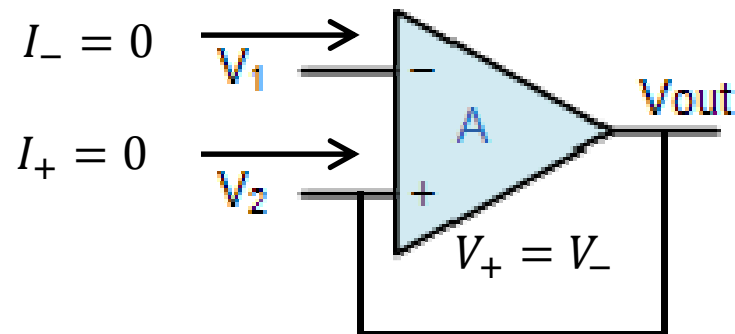- Golden rules:
 - Both input currents are zero
 - For closed loops: both input voltages are equal




Saturable Op-Amps

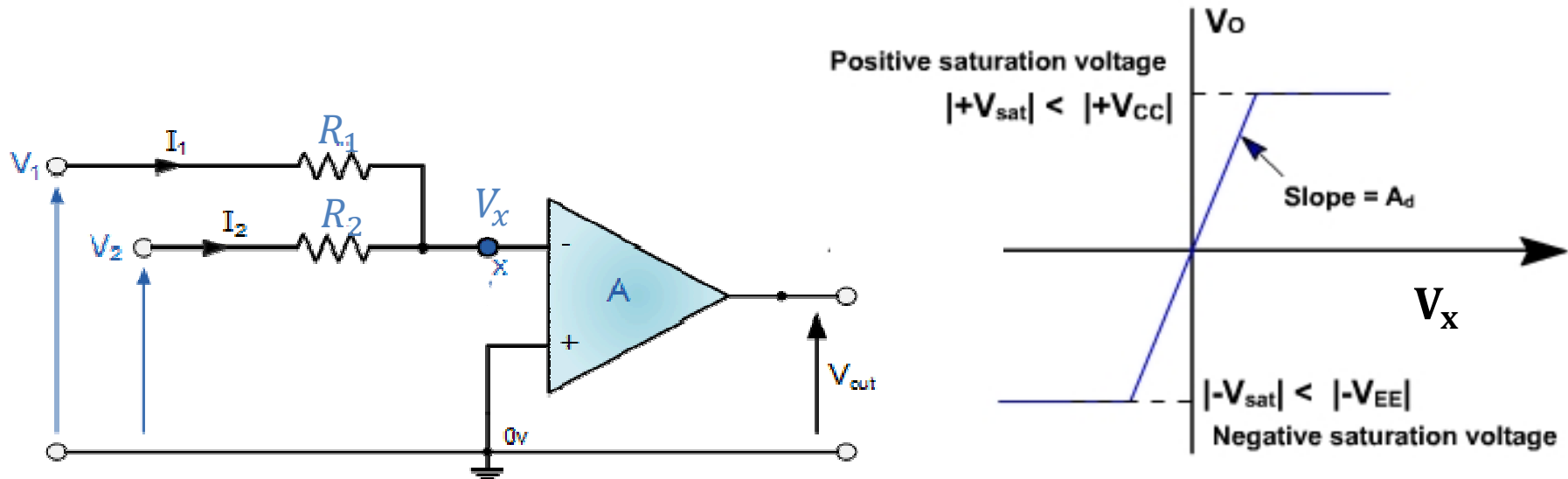


- Given that $V_x = \frac{R_2 V_1 + R_1 V_2}{R_1 + R_2}$, 3 solution regimes

Region Name	Input Values	Output Values
Positive saturation	$AV_x > V_{sat}$	V_{sat}
Active	$-V_{sat} < AV_x < V_{sat}$	AV_x
Negative saturation	$AV_x < -V_{sat}$	$-V_{sat}$


Op-Amps with Feedback

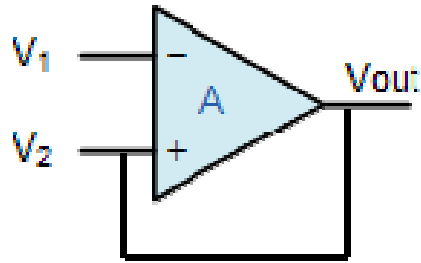

Voltage follower: $A = 1$

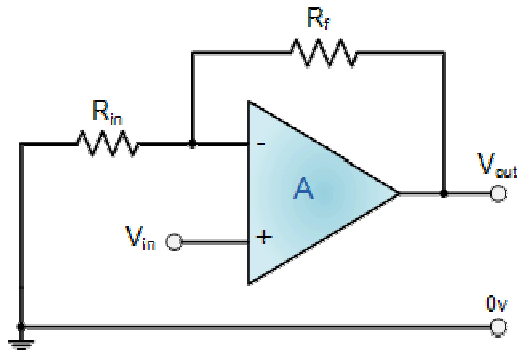

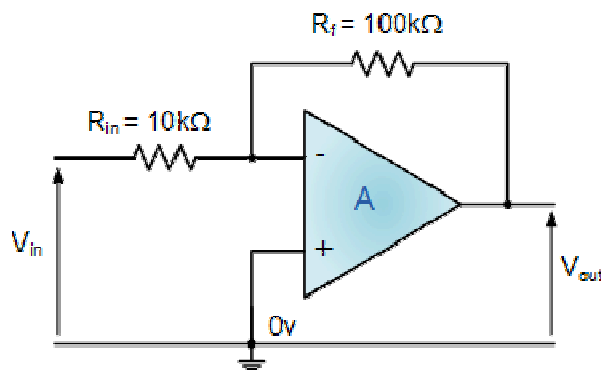
Non-inverting amp: $A = 1 + \frac{R_f}{R_i}$




Inverting amp: $A = -\frac{R_f}{R_i}$

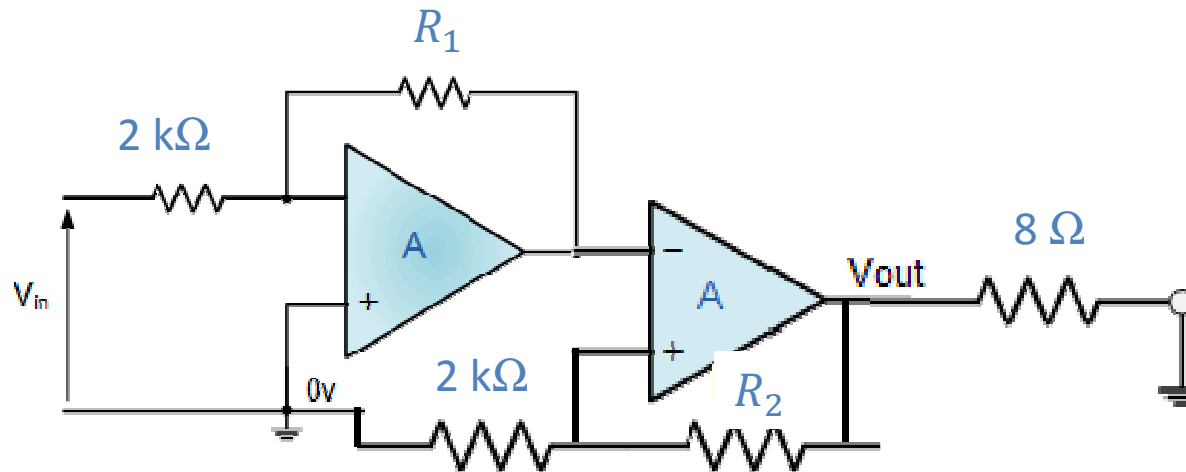Example

- If $R_1=R_2$, what value is necessary to amplify the input amplitude by 20x? How can you achieve the same with $R_1=5\text{ k}\Omega$, or $R_2=18\text{ k}\Omega$?




Solution

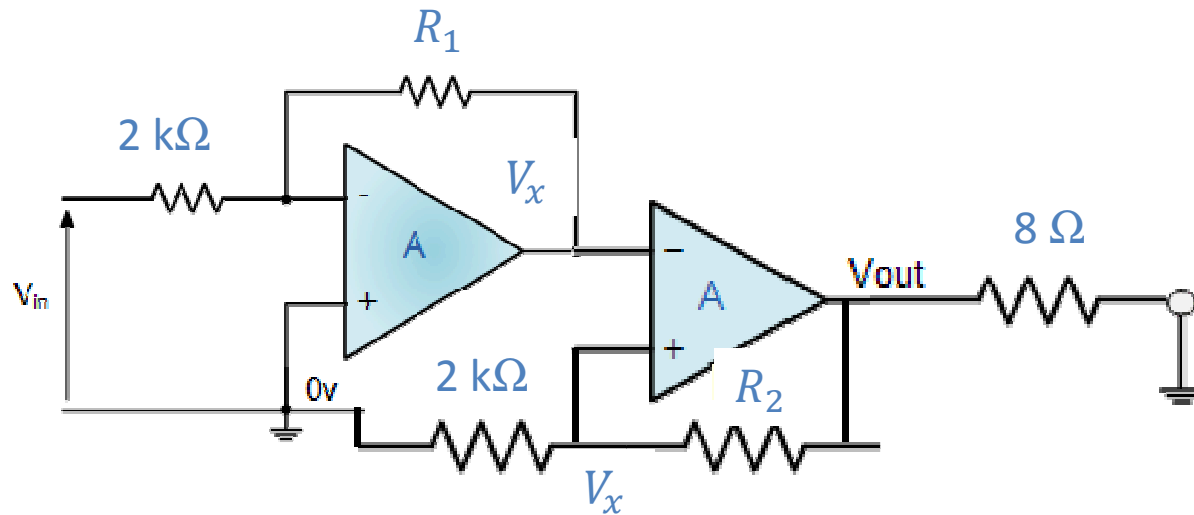

- Applying both golden rules, we know: $V_x = -\frac{R_1}{2\text{ k}\Omega} V_{in}$
- Thus, current on bottom $I = V_x / 2\text{ k}\Omega$
- So: $V_{out} = V_x + IR_2 = (1 + R_2 / 2\text{ k}\Omega) V_x$
- Thus, $V_{out} = (1 + R_2 / 2\text{ k}\Omega) (-R_1 V_{in} / 2\text{ k}\Omega)$

Solution

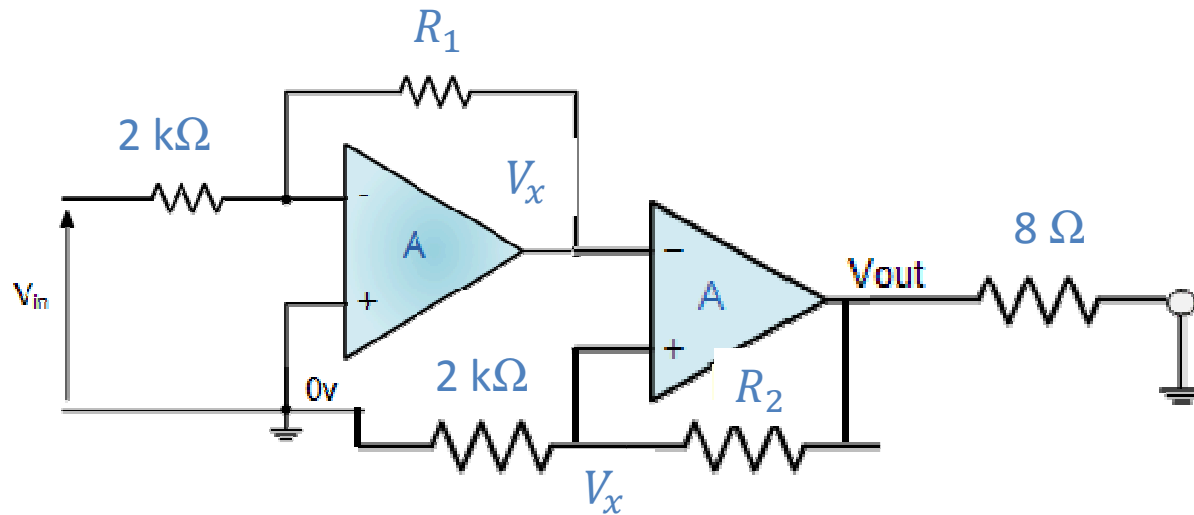


- Thus, $A = V_{\text{out}} / V_{\text{in}} = (1 + R_2/2k\Omega)(-R_1/2k\Omega)$
- If $R_1 = R_2$ and $A = -20 = \left(1 + \frac{R_1}{2}\right)\left(-\frac{R_1}{2}\right)$

$$5 \cdot (-4) = \left(1 + \frac{R_1}{2}\right)\left(-\frac{R_1}{2}\right)$$

$$5 = 1 + \frac{R_1}{2}$$

$$R_1 = 8 \text{ k}\Omega$$

Solution

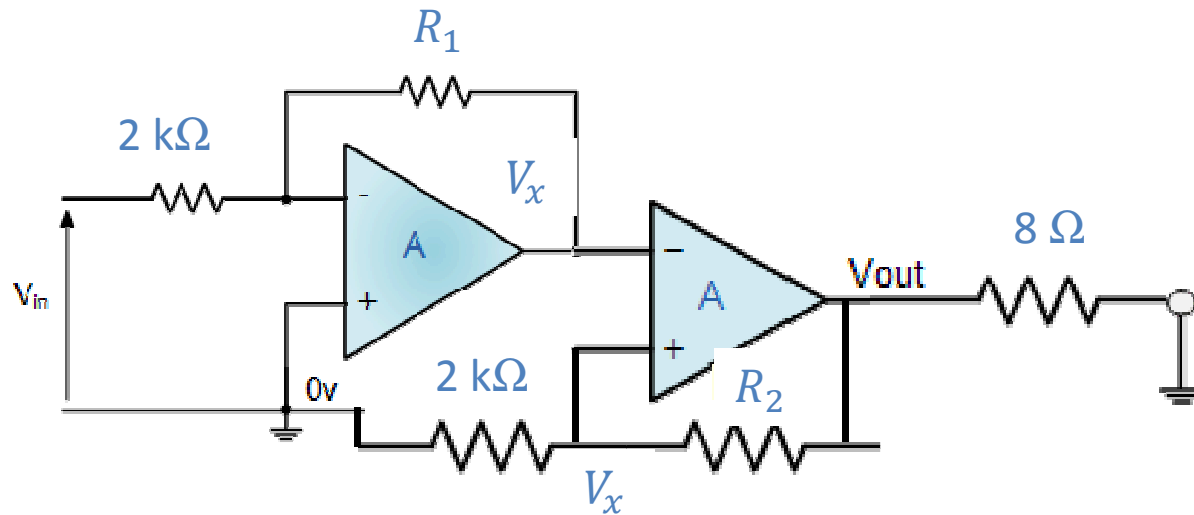


- Thus, $A = V_{out} / V_{in} = (1 + R_2/2k\Omega)(-R_1/2k\Omega)$
- If $R_1 = 5 \text{ k}\Omega$ and $A = -20 = \left(1 + \frac{R_2}{2}\right) \left(-\frac{5}{2}\right)$

$$\left(-\frac{2}{5}\right) \cdot (-20) = \left(1 + \frac{R_2}{2}\right)$$

$$8 = 1 + \frac{R_2}{2}$$

$$R_2 = 14 \text{ k}\Omega$$

Solution

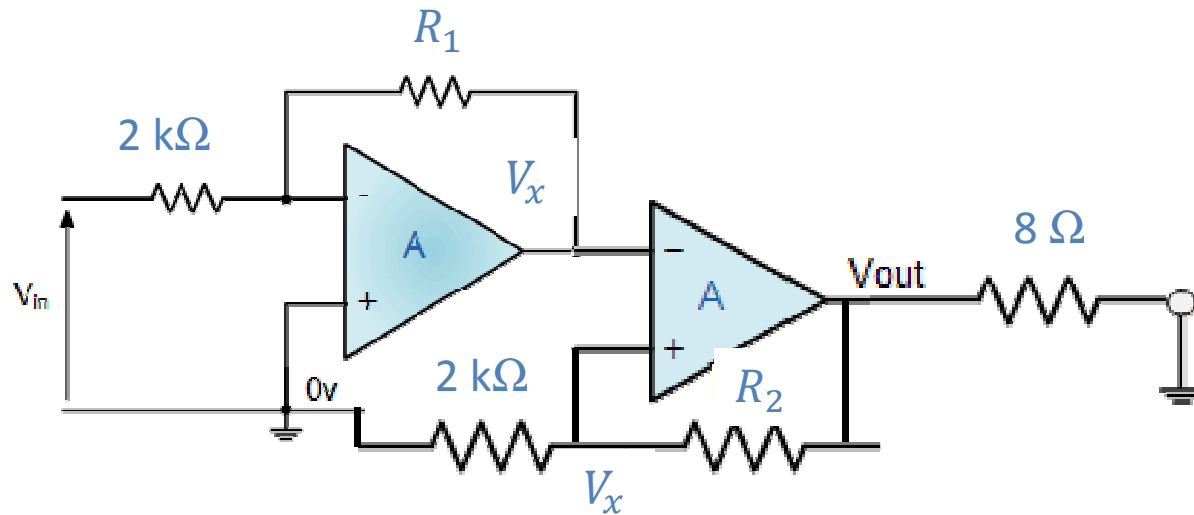


- Thus, $A = V_{\text{out}} / V_{\text{in}} = (1 + R_2/2k\Omega)(-R_1/2k\Omega)$
- If $R_2 = 18 k\Omega$ and $A = -20 = \left(1 + \frac{18}{2}\right) \left(-\frac{R_1}{2}\right)$

$$\frac{1}{10} \cdot (-20) = -\frac{R_1}{2}$$

$$R_1 = 4 k\Omega$$

Solution

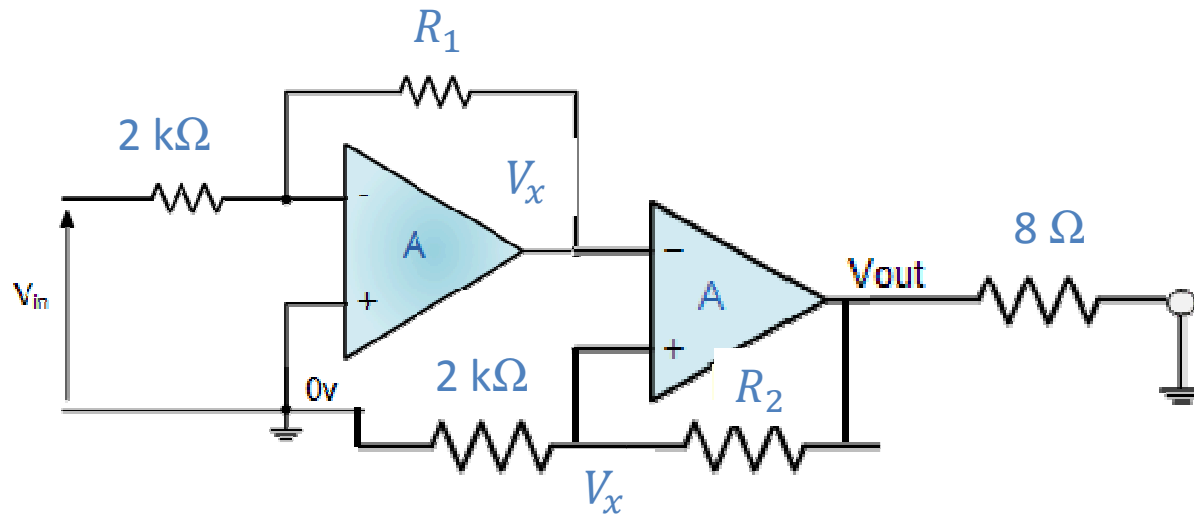


- If $V_{in} = 2\text{ V}$ and $A = -20$, how much power is dissipated in the load on the right?


$$P = V^2/R = (-20 \cdot 2)^2/8 = 200\text{ W}$$

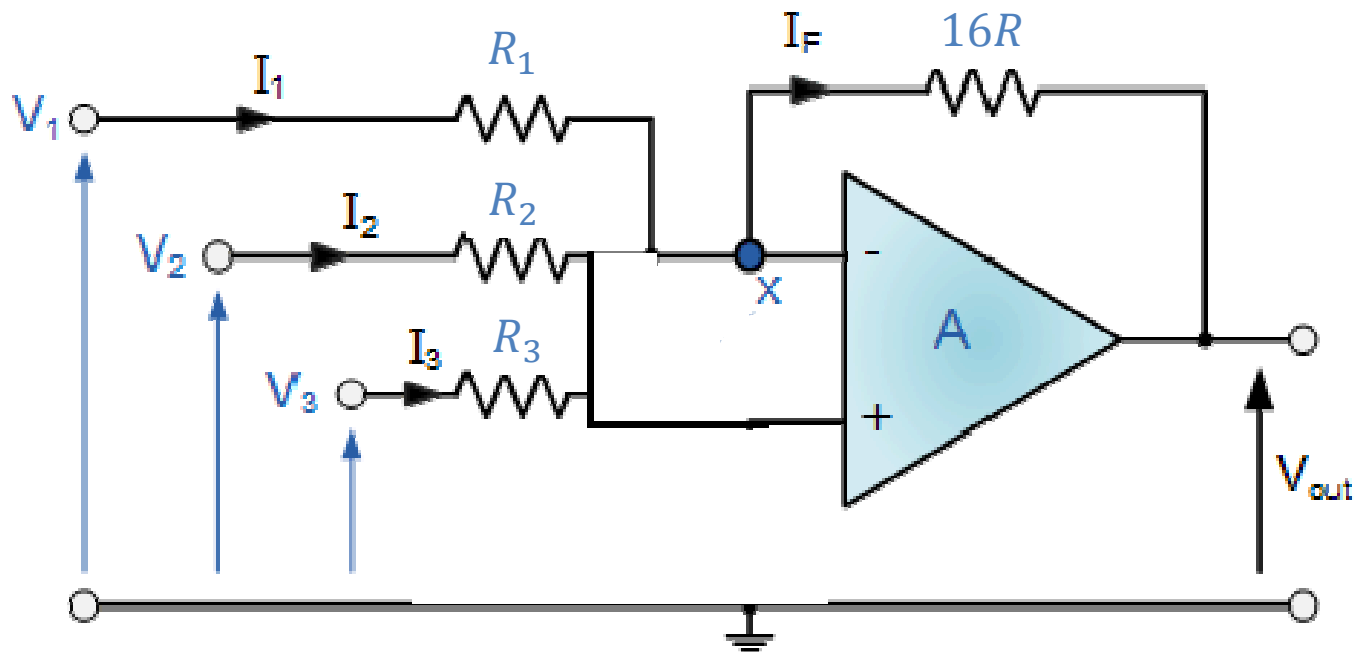Example #2

- What is the total output voltage for this circuit in general? What if $R_2 = R_3$, $V_1 = 0$, $V_2 - V_3 = 4\text{ V}$, and $R_1 = 8R$?




Solution

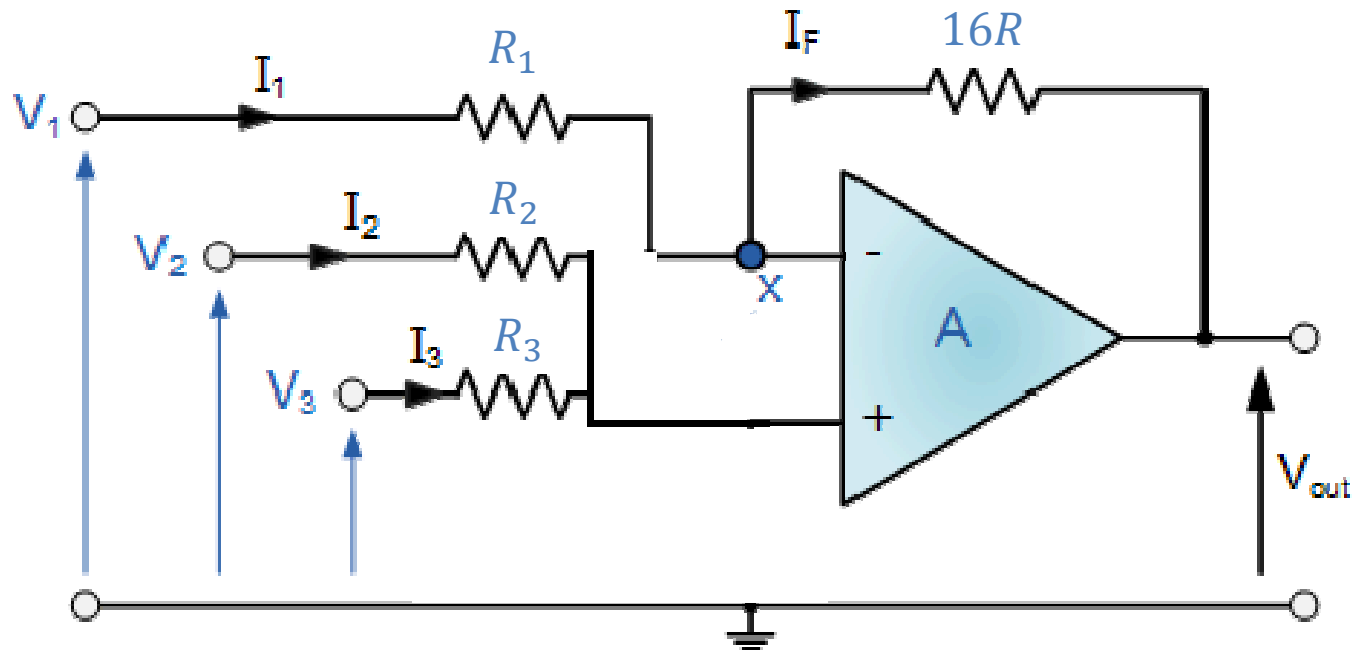

- By golden rule #1, $V_x = V_1 - I_1 R_1 = V_2 - I_2 R_2$
- By golden rule #2, $I_2 = -I_3$, and $I_1 = I_F$
- By Ohm's law, $V_x - V_{out} = I_1 \cdot 16R$

Solution

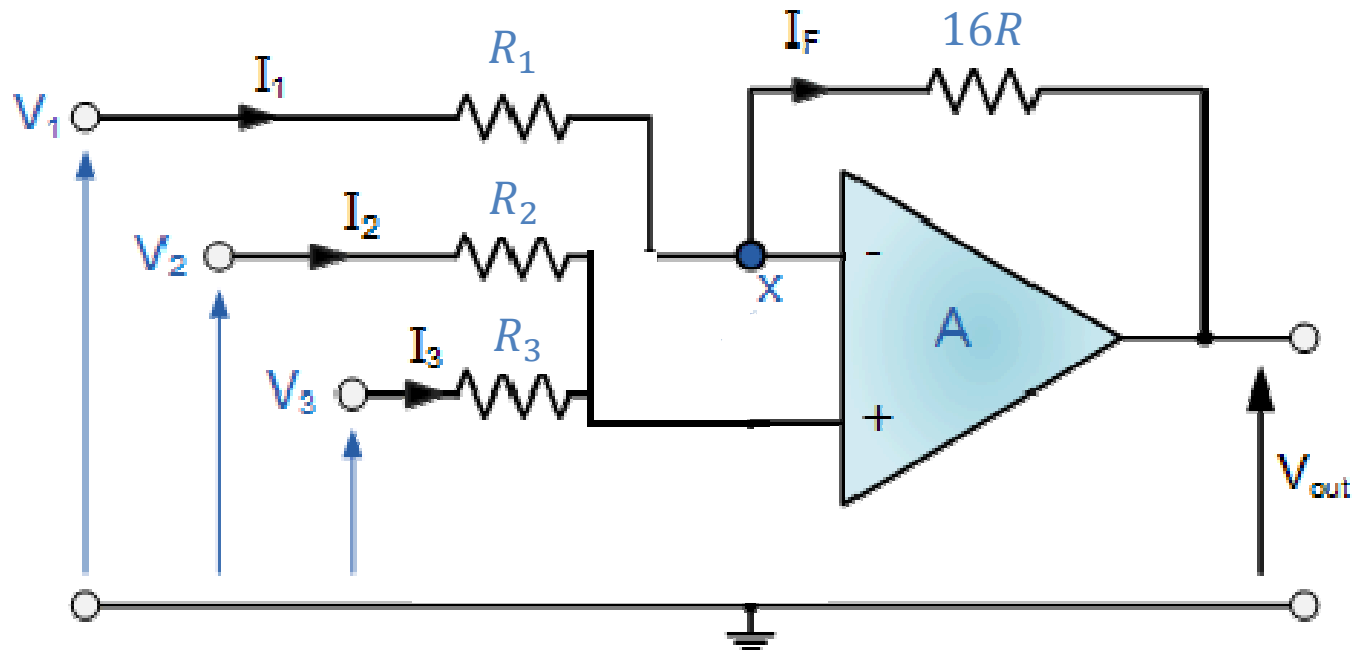


- Since $V_{out} = V_x - I_1 \cdot 16R$ and $V_1 - V_x = I_1 R_1$, we can write:

$$V_{out} = V_x - (16R/R_1)(V_1 - V_x)$$

- Need an expression for V_x !

Solution

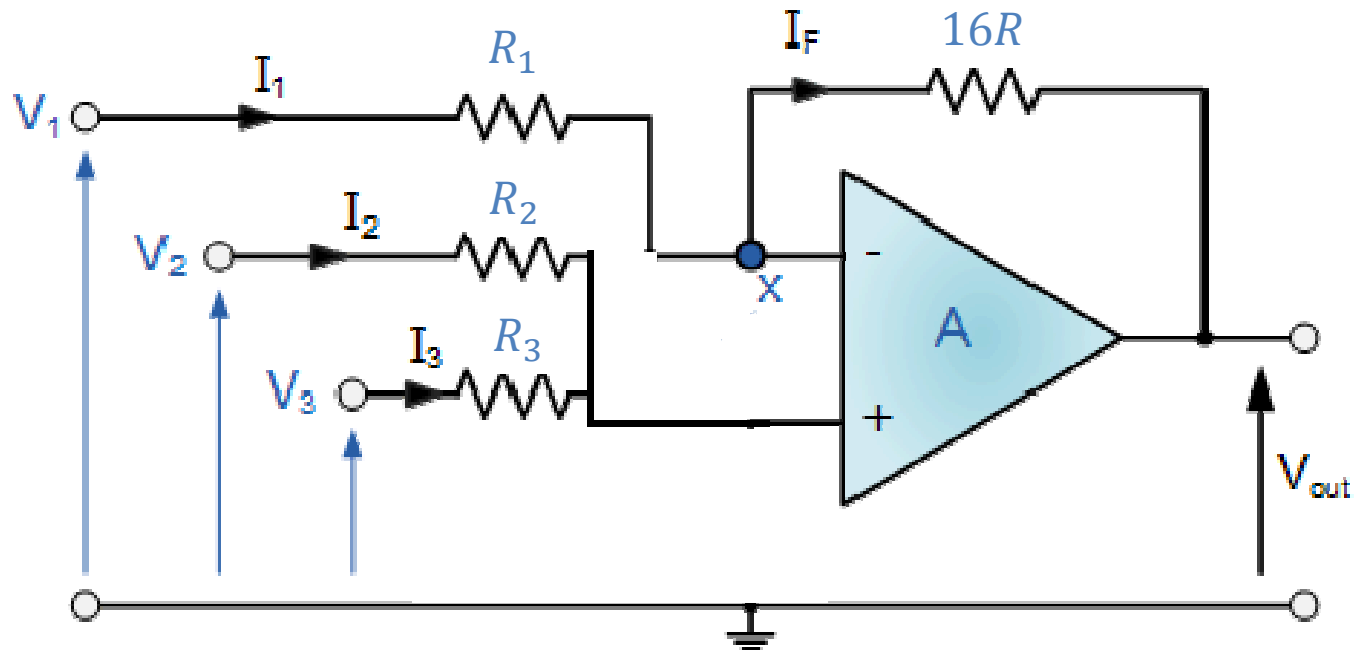

- We now obtain:

$$V_{out} = (1 + 16R/R_1)(V_2 - V_3)R_3/(R_2 + R_3) - (16R/R_1)V_1$$
- If $R_2 = R_3$, $V_1 = 0$, $V_2 - V_3 = 4 \text{ V}$, and $R_1 = 8R$:

$$V_{out} = (1 + 16R/8R) \cdot 4R_2/(R_2 + R_2) - (16R/8R) \cdot 0$$

$$V_{out} = (1 + 2) \cdot 4/2 = 6 \text{ V}$$

Homework

- HW #25 due today by 4:30 pm in EE 325B
- HW #26 due Mon.: DeCarlo & Lin, Chapter 4:
 - Problem 6
 - Problem 7