


# ECE 201, Section 3

## Lecture 27

Prof. Peter Bermel


October 29, 2012

# Op-Amp Review

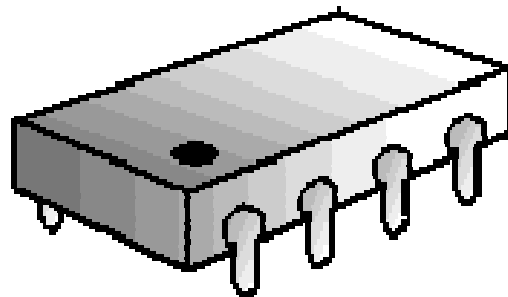


741 Op amp


Pin 1

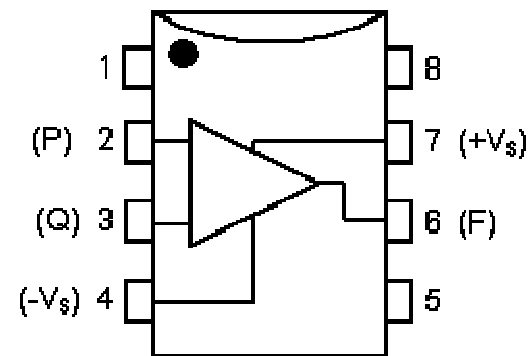

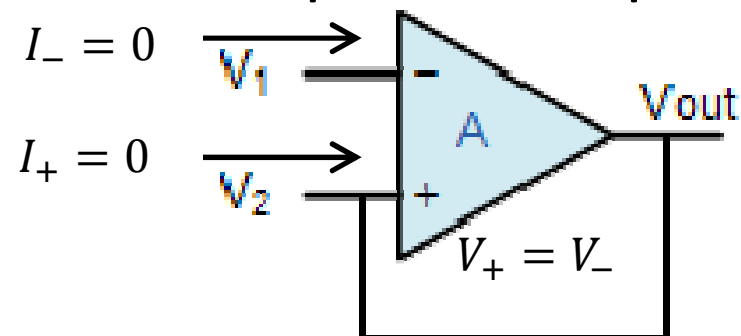
- Golden rules:
  - Both input currents are zero
  - For closed loops: both input voltages are equal




# Op-Amps with Feedback

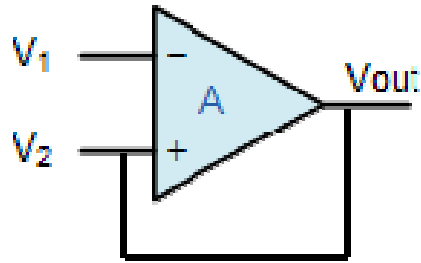

Voltage follower:  $A = 1$

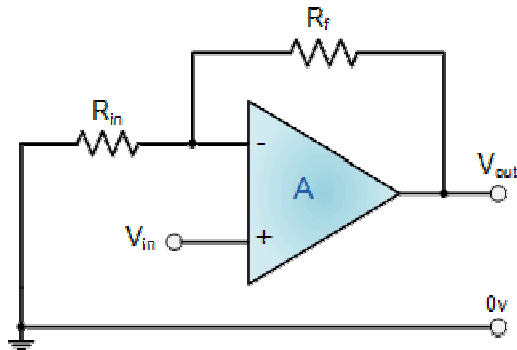

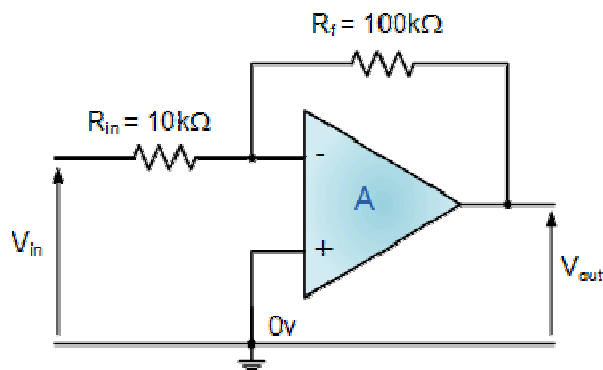Non-inverting amp:  $A = 1 + \frac{R_f}{R_i}$




Inverting amp:  $A = -\frac{R_f}{R_i}$

# General Procedure to Solve Op-Amp Problems with Feedback


- Find  $V_+$  or  $V_-$  with golden rule,  $I_+ = I_- = 0$  (usually easiest for input unconnected to output)
- Find other voltage with golden rule:  $V_+ = V_-$
- Apply KCL to input terminal connected to output to find residual current and output voltage
- If necessary, apply KCL at output node
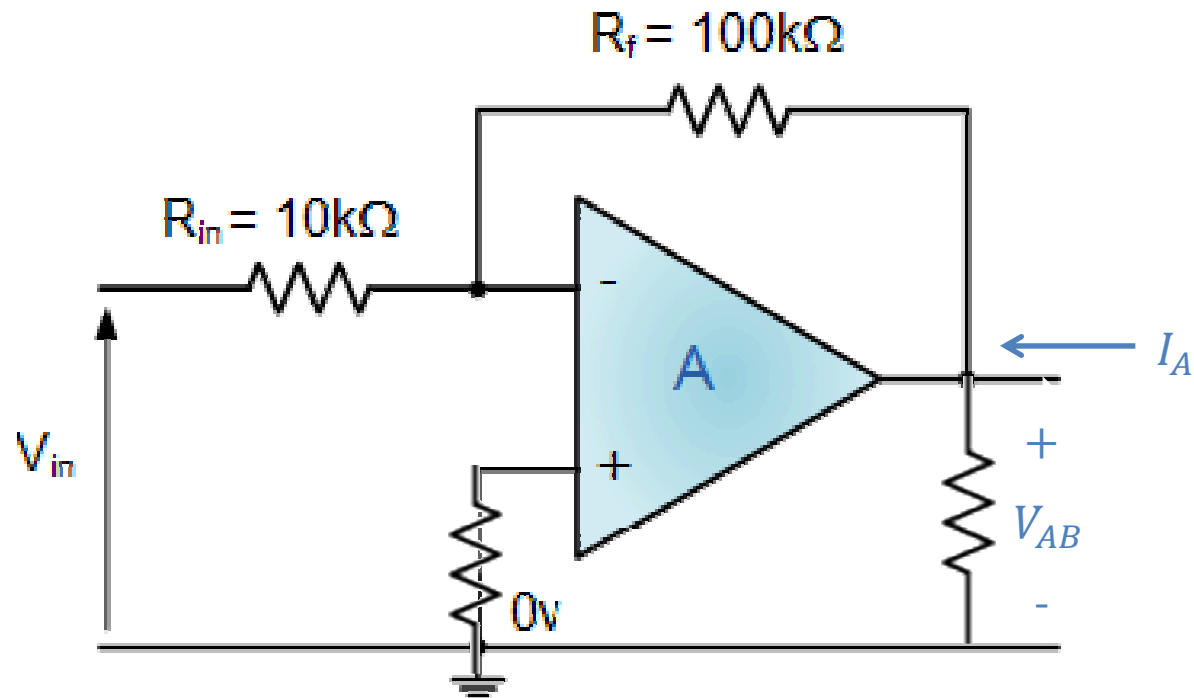
# Example

- What is the Thevenin equivalent of this inverted amplifier op-amp circuit?




# Solution

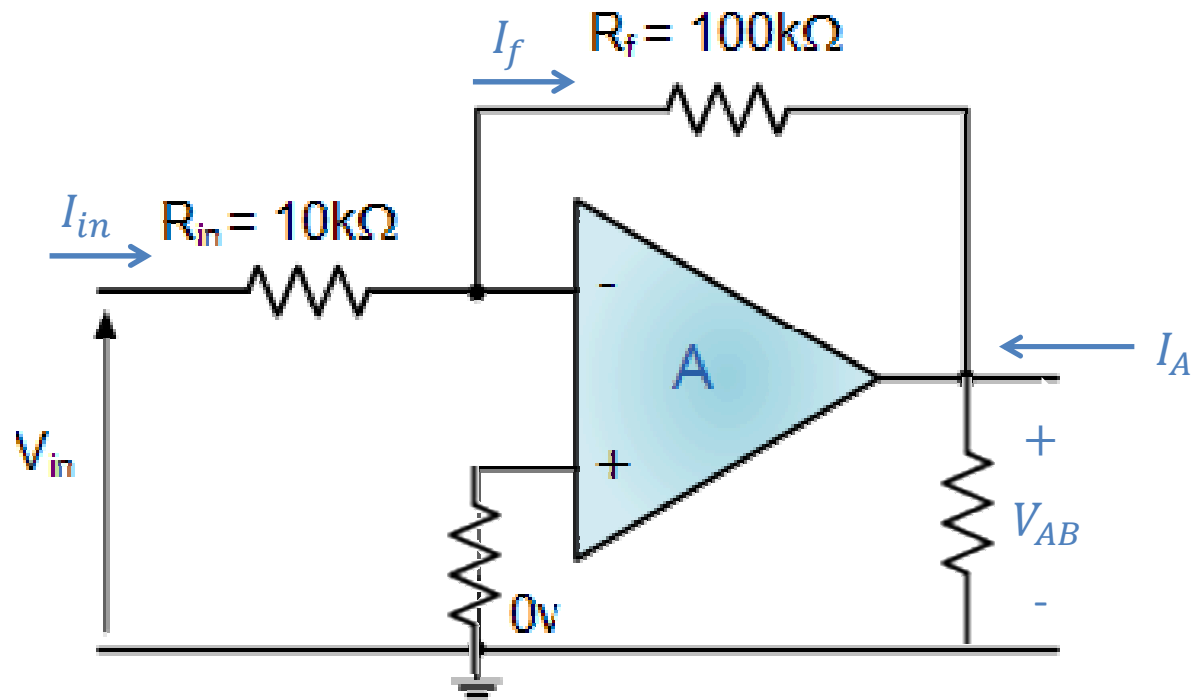


- Since  $I_+ = 0 \text{ A}$ ,  $V_+ = 0 \text{ V}$ , and thus,  $V_- = 0$
- By Ohm's law,  $I_{in} = \frac{V_{in}-0}{R_{in}}$ , and  $V_{AB} = -I_f R_f$
- By KCL,  $I_{in} = I_f$ , so  $V_{AB} = -\frac{R_f}{R_{in}} V_{in}$ ; independent of  $I_A$ , so  $R_{th} = 0 \Omega$ !
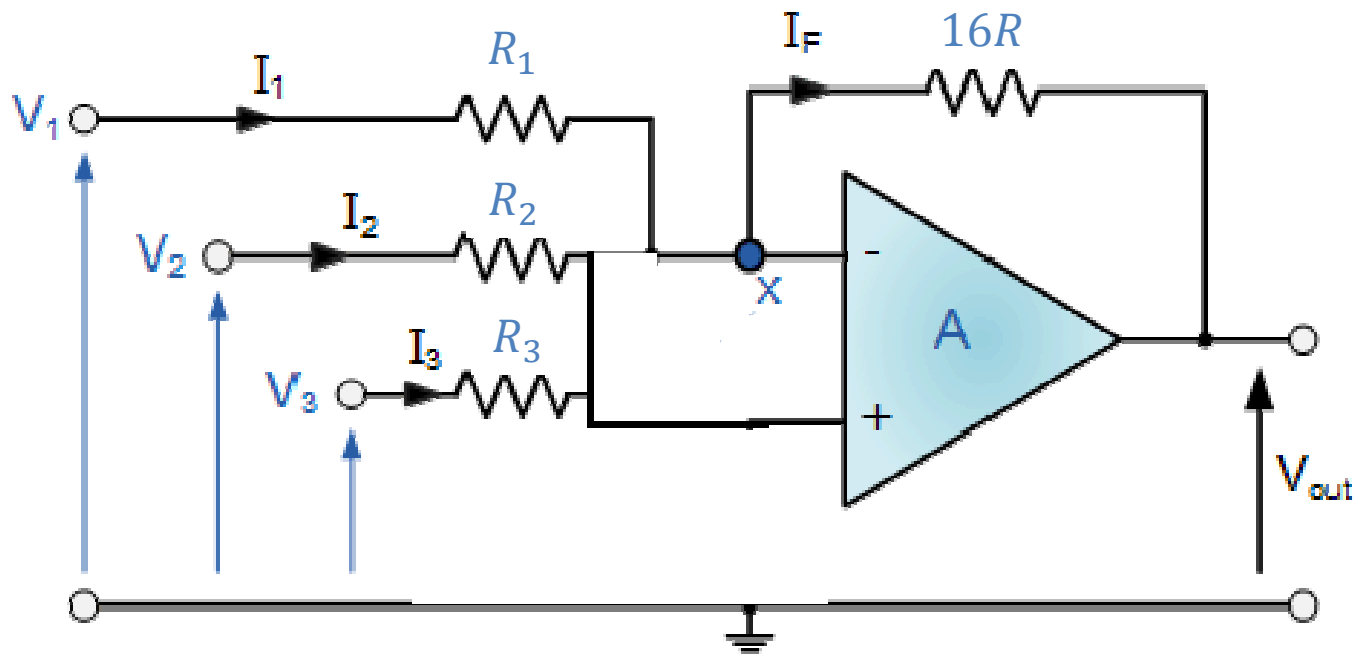
# Example

- What is the total output voltage for this circuit in general? What if  $R_2 = R_3$ ,  $V_1 = 0$ ,  $V_2 - V_3 = 4\text{ V}$ , and  $R_1 = 8R$ ?




# Solution

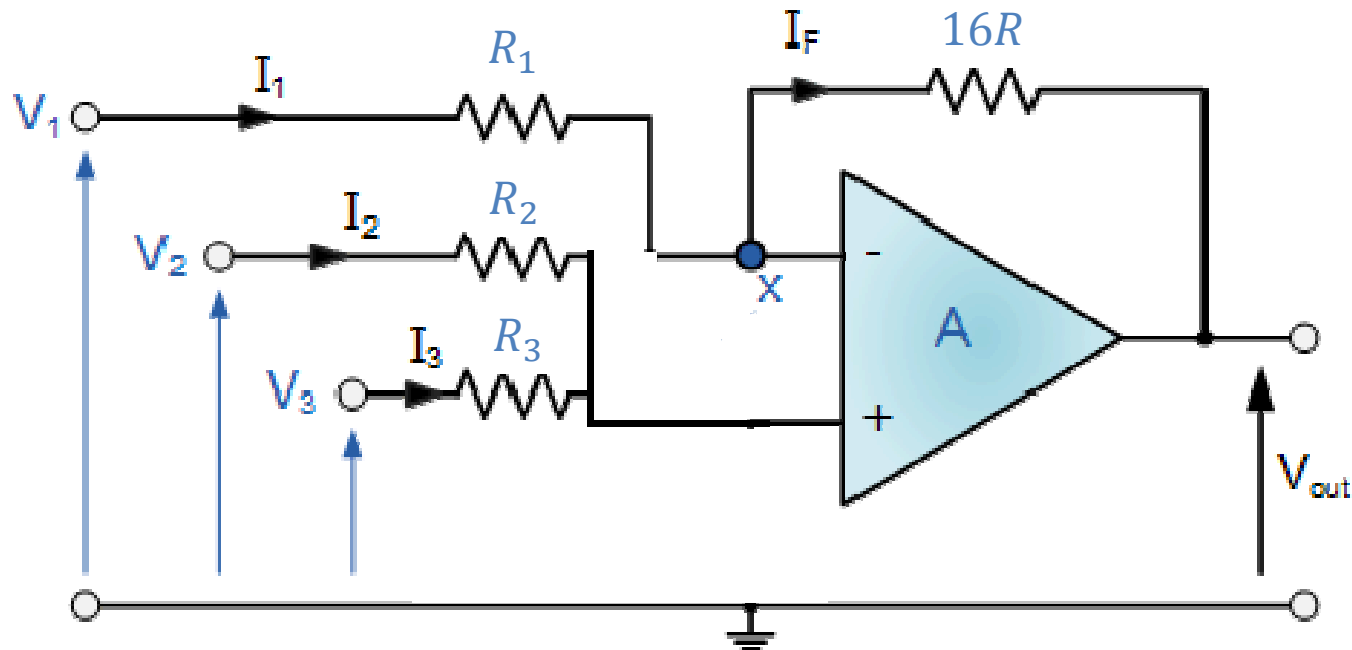

- By golden rule #1,  $V_x = V_1 - I_1 R_1 = V_2 - I_2 R_2$
- By golden rule #2,  $I_2 = -I_3$ , and  $I_1 = I_F$
- By Ohm's law,  $V_x - V_{out} = I_1 \cdot 16R$

# Solution

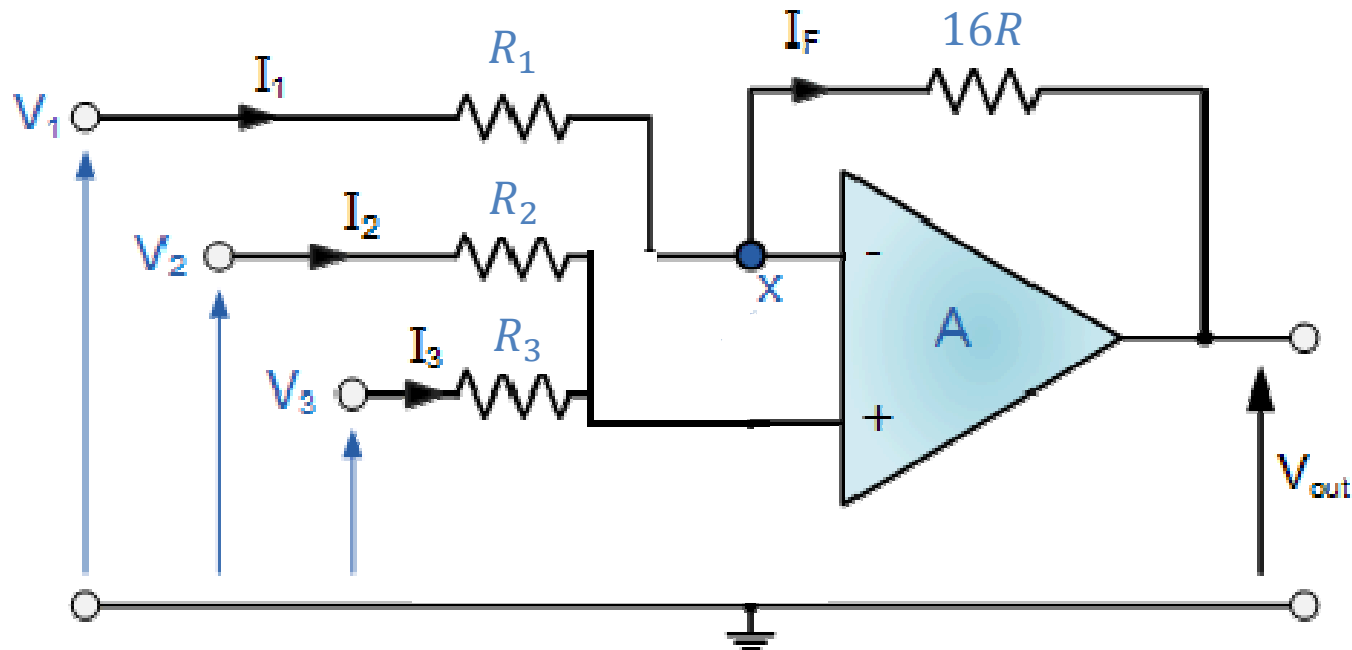


- Since  $V_{out} = V_x - I_1 \cdot 16R$  and  $V_1 - V_x = I_1 R_1$ , we can write:

$$V_{out} = V_x - (16R/R_1)(V_1 - V_x)$$

- Need an expression for  $V_x$ !

# Solution

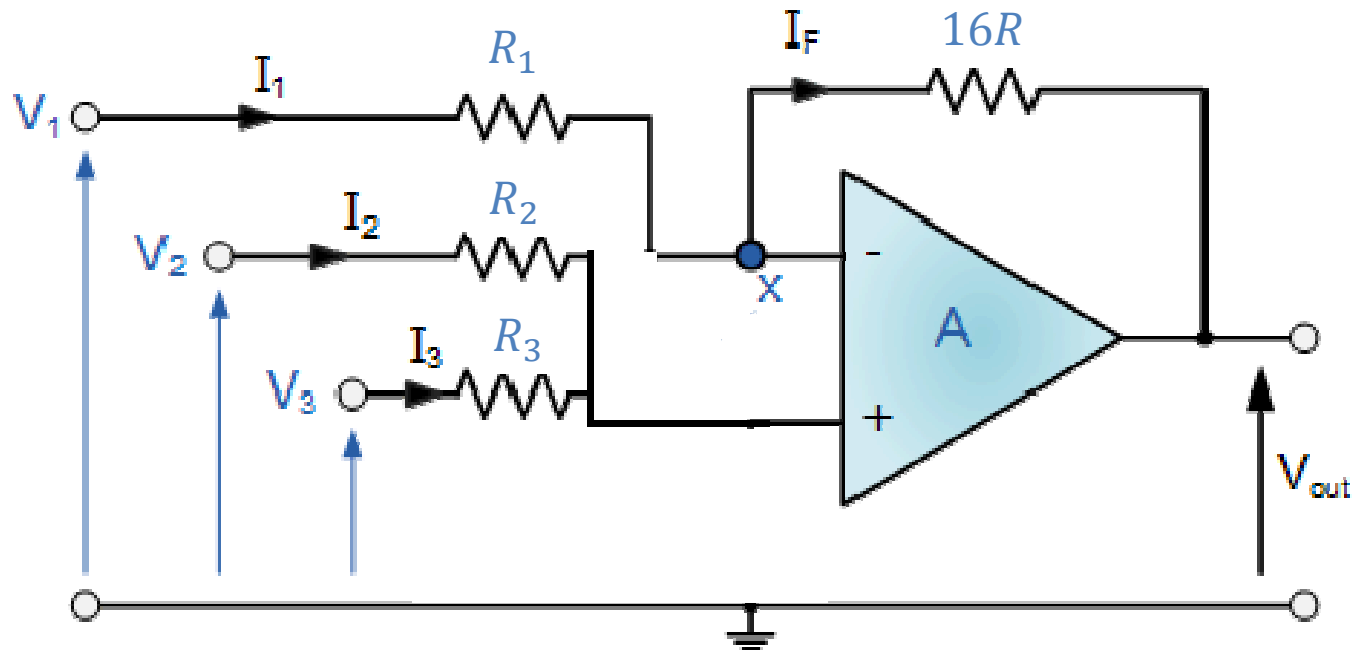

- We now obtain:  


$$V_{out} = (1 + 16R/R_1)(V_2 - V_3)R_3/(R_2 + R_3) - (16R/R_1)V_1$$
- If  $R_2 = R_3$ ,  $V_1 = 0$ ,  $V_2 - V_3 = 4 \text{ V}$ , and  $R_1 = 8R$ :  

$$V_{out} = (1 + 16R/8R) \cdot 4R_2/(R_2 + R_2) - (16R/8R) \cdot 0$$


$$V_{out} = (1 + 2) \cdot 4/2 = 6 \text{ V}$$
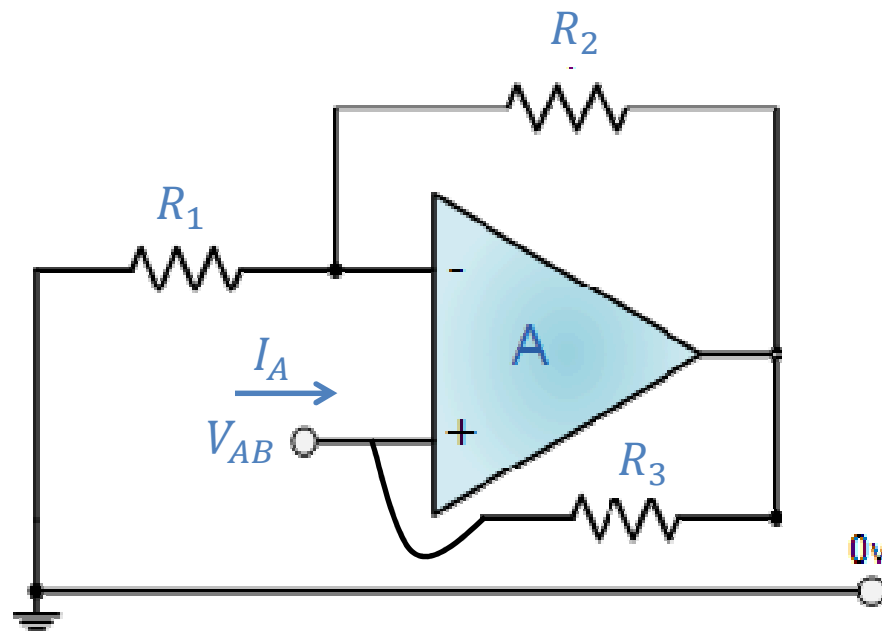
# Example

- What is the Thevenin equivalent circuit for this setup? What unusual behavior distinguishes it from a non-inverting amplifier?




# Solution

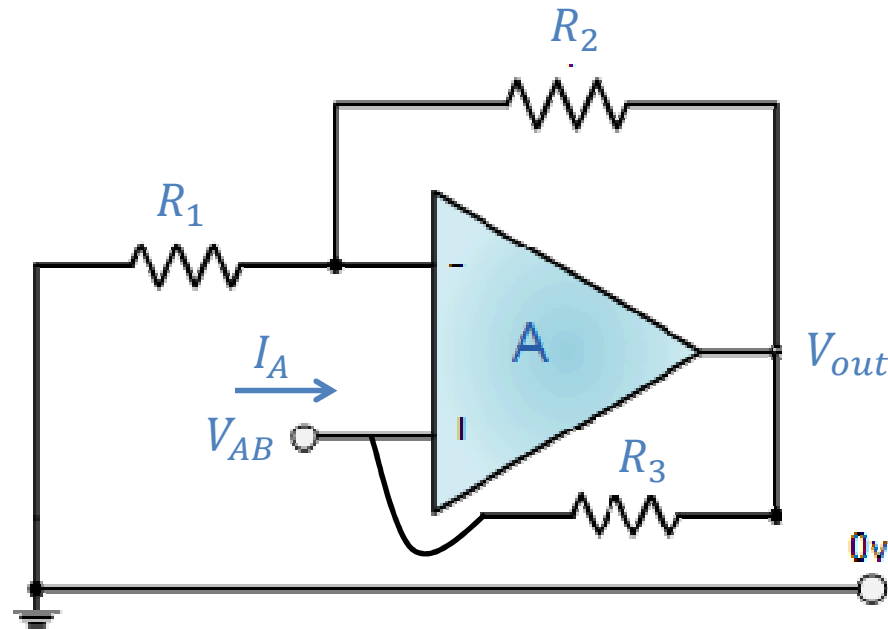

- Let's find  $V_{out}$  through 2 KVL paths:
  - Lower branch:  $V_{out} = V_{AB} - I_A R_3$
  - Upper branch:  $I_1 = V_{AB}/R_1$ ;  $V_{out} = V_{AB} + I_1 R_2$

# Solution

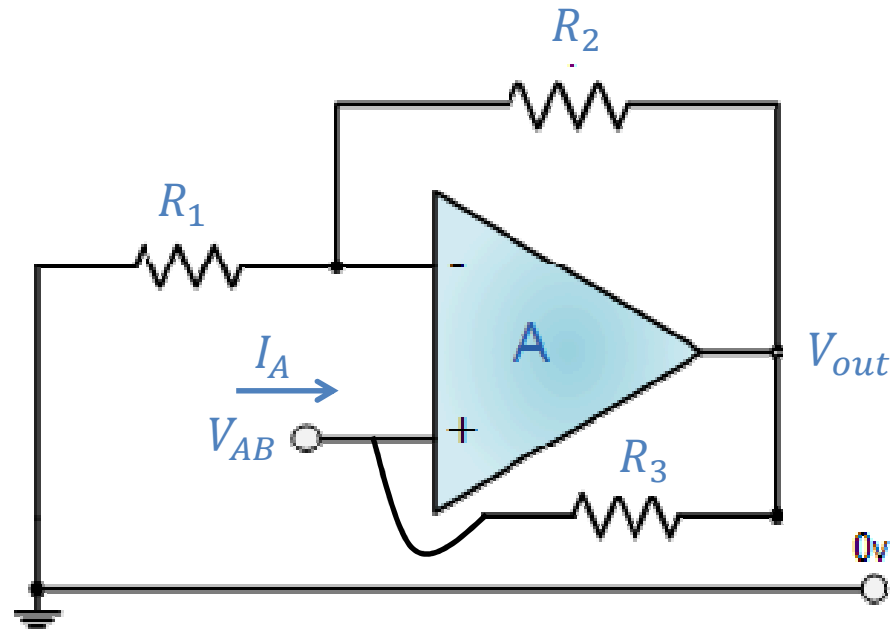

- Equating our 2 expressions for  $V_{out}$ :

$$V_{out} = V_{AB} - I_A R_3 = V_{AB} + V_{AB} R_2 / R_1$$


$$-I_A R_3 = \frac{V_{AB} R_2}{R_1}$$

- Comparing with Thevenin circuit equation  $V_{AB} = R_{th} I_A + V_{oc}$  yields:


$$V_{oc} = 0; R_{th} = -\frac{R_1 R_3}{R_2}$$
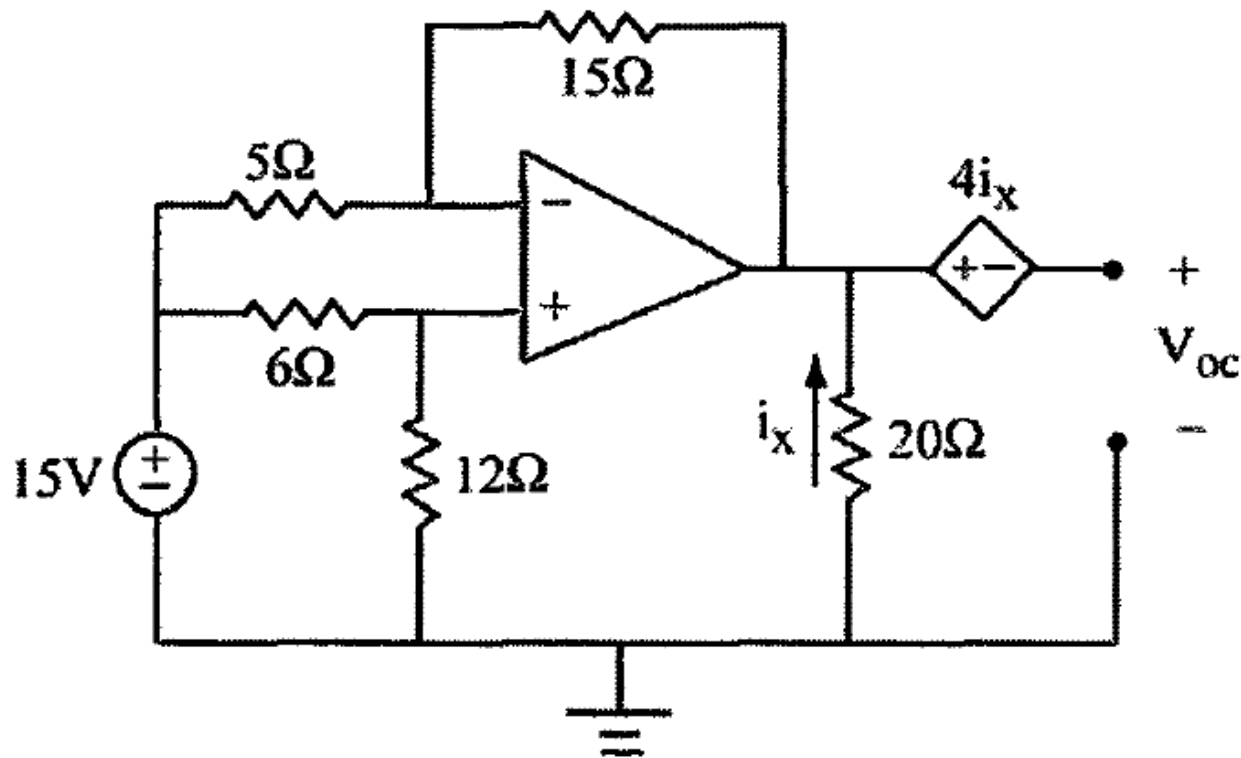
# Example

- What is the Thevenin equivalent of this op-amp circuit, containing a dependent source?




# Solution

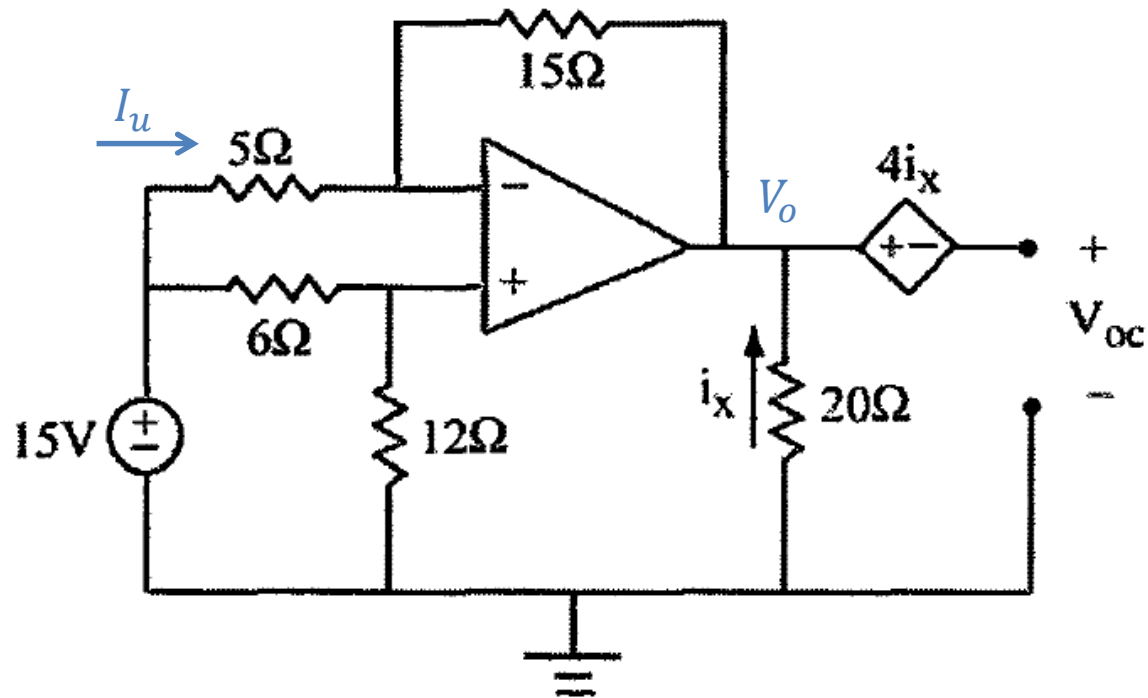

- By voltage division:  $V_+ = \frac{12}{6+12} \cdot 15 \text{ V} = 10 \text{ V}$
- Thus,  $I_u = \frac{15-10 \text{ V}}{5 \Omega} = 1 \text{ A}$ ;  $V_o = 10 - I_u \cdot (15 \Omega) = -5 \text{ V}$

# Solution

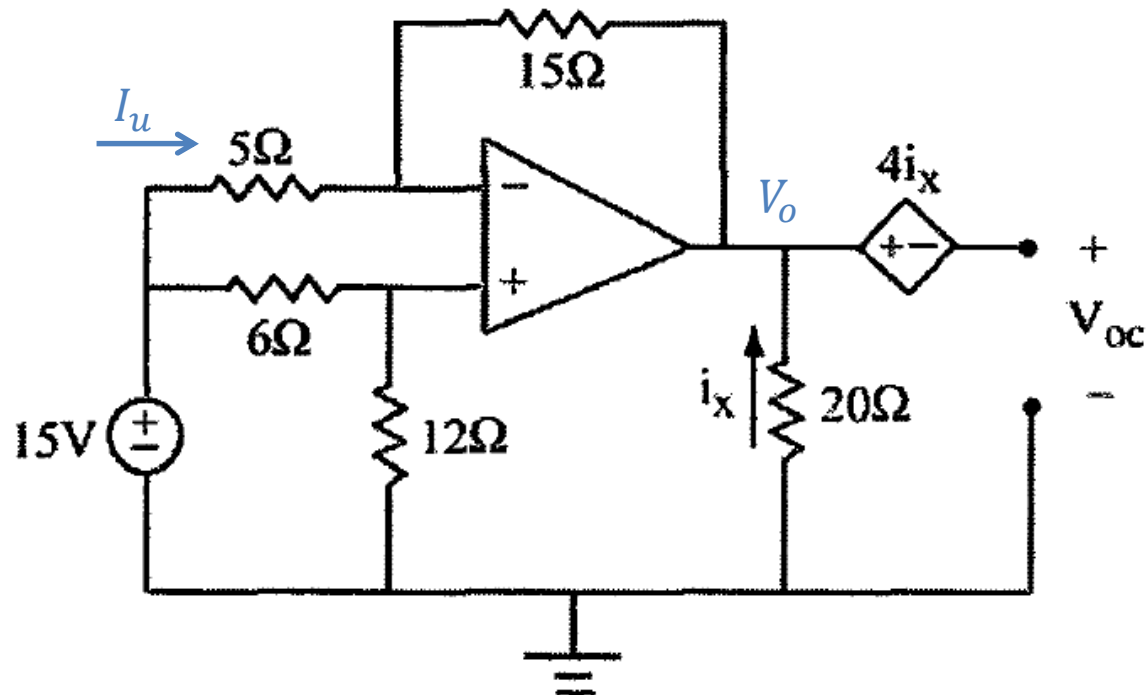

- By Ohm's law:  $I_x = \frac{0 - V_o}{20 \Omega} = -\frac{V_o}{20}$
- By KVL:  $V_{AB} = V_o - 4I_x = -5 - 4 \cdot \left(-\frac{V_o}{20}\right) = -5 + \frac{V_o}{5} = -6 \text{ V}$
- Thus,  $V_{oc} = -6 \text{ V}$ , and  $R_{th} = 0 \Omega$

# Homework

- HW #26 due today by 4:30 pm in EE 325B
- HW #27 due Wed.: DeCarlo & Lin, Chapter 4:
  - Problem 9
  - Problem 11