

# ECE 201, Section 3

## Lecture 28

Prof. Peter Bermel


October 31, 2012

# General Procedure to Solve Op-Amp Problems with Feedback


- Find  $V_+$  or  $V_-$  with golden rule,  $I_+ = I_- = 0$  (usually easiest for input unconnected to output)
- Find other voltage with golden rule:  $V_+ = V_-$
- Apply KCL to input terminal connected to output to find residual current and output voltage
- If necessary, apply KCL at output node
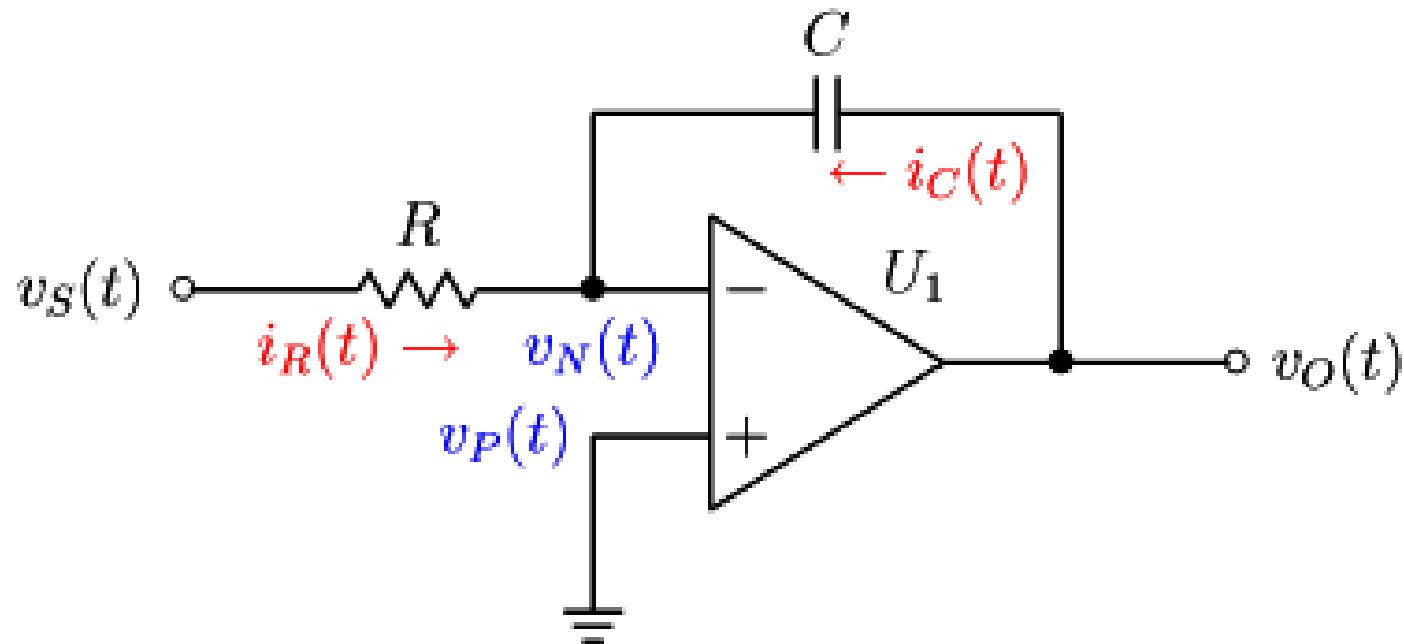
# Example

What is the output of this circuit? How would you describe it?




# Solution

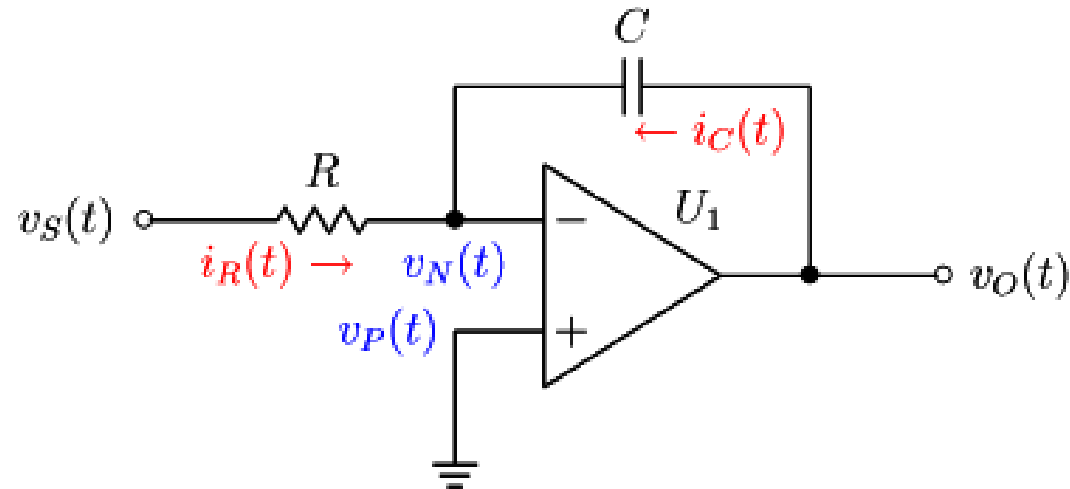

$$i_R(t) + i_C(t) = 0 \quad \Rightarrow \quad \frac{v_S(t) - v_N(t)}{R} + C \frac{d[v_O(t) - v_N(t)]}{dt} = 0.$$

$$\frac{v_S(t)}{R} + C \frac{dv_O(t)}{dt} = 0 \quad \Rightarrow \quad \frac{dv_O(t)}{dt} = -\frac{1}{RC} v_S(t).$$


# Solution

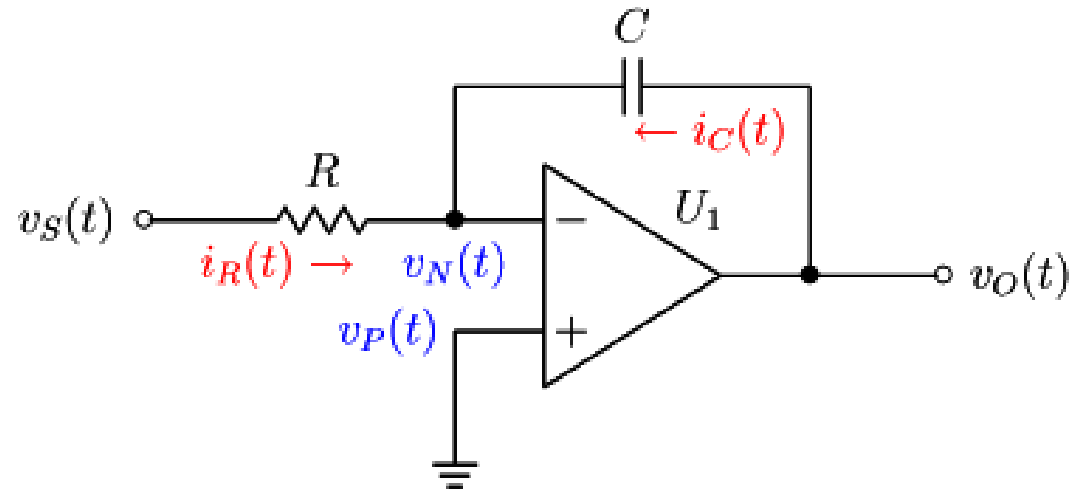

$$v_O(t) = -\frac{1}{RC} \int_{-\infty}^t v_S(\tau) d\tau = -\frac{1}{RC} \int_{t_0}^t v_S(\tau) d\tau + v_O(t_0) .$$

Integrating circuit; problem is: what if it reaches saturation for low-frequency signals?



# Solution

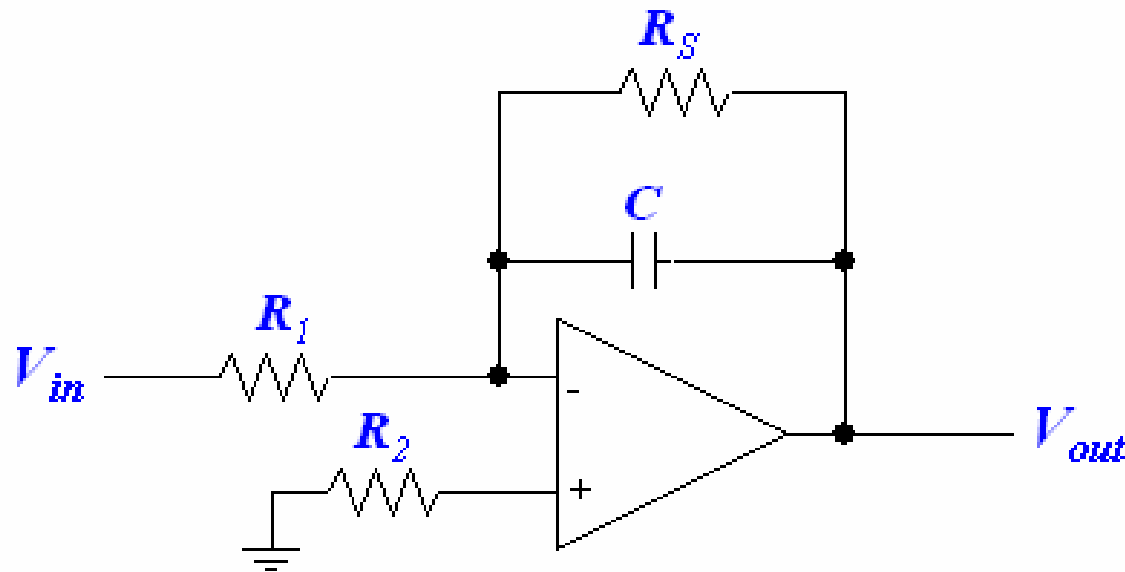

Revised integrating circuit provides shunt resistor to prevent charge storage, plus  $R_2$  to prevent input DC bias current

# Solution


## Assumed input waveform

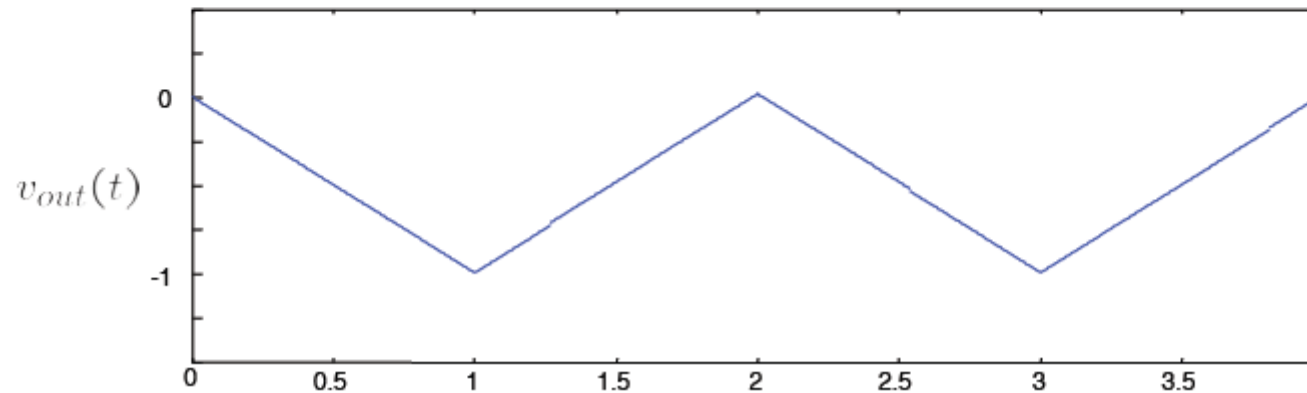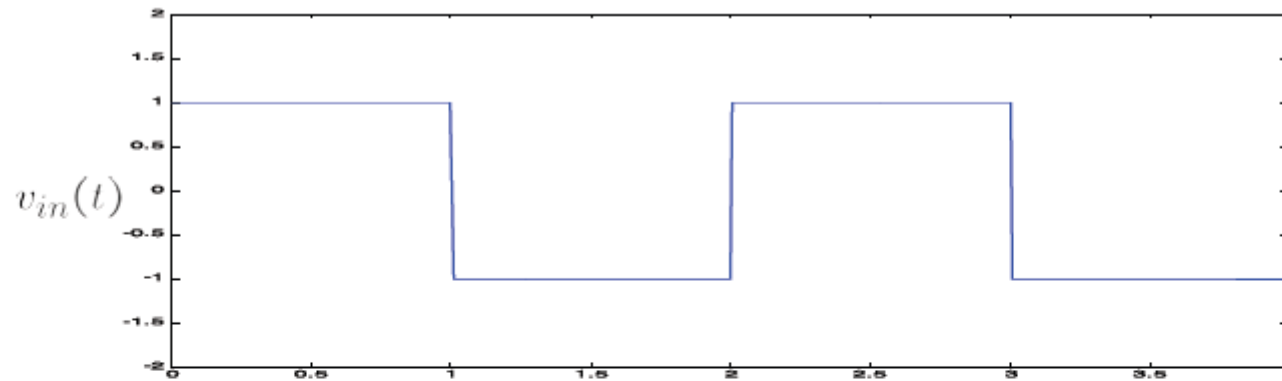

## Integrated output waveform

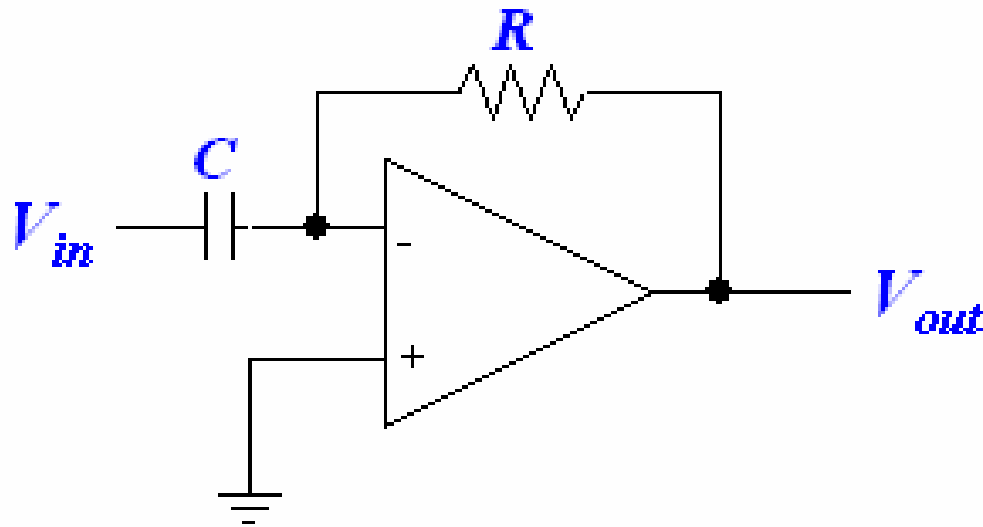
# Example

What is the output of this circuit? How would you describe it?






# Solution

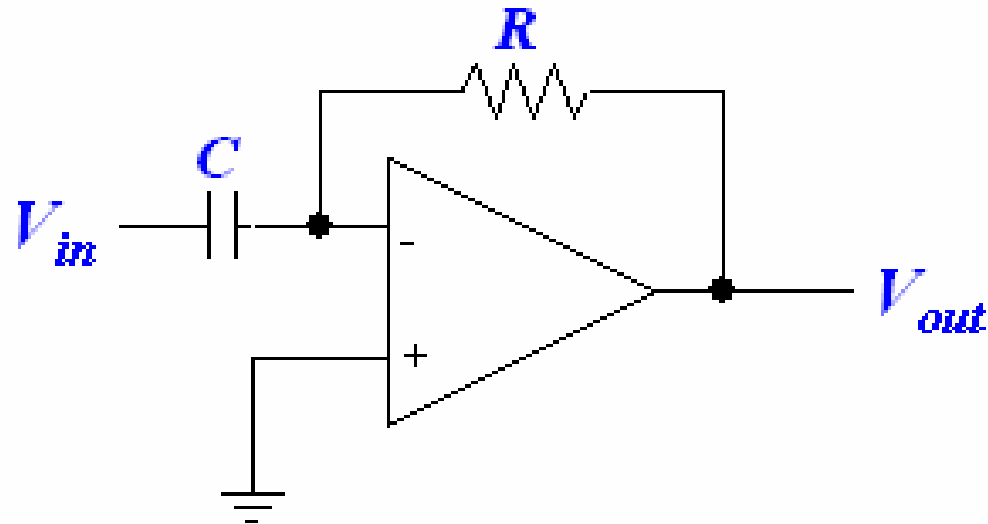

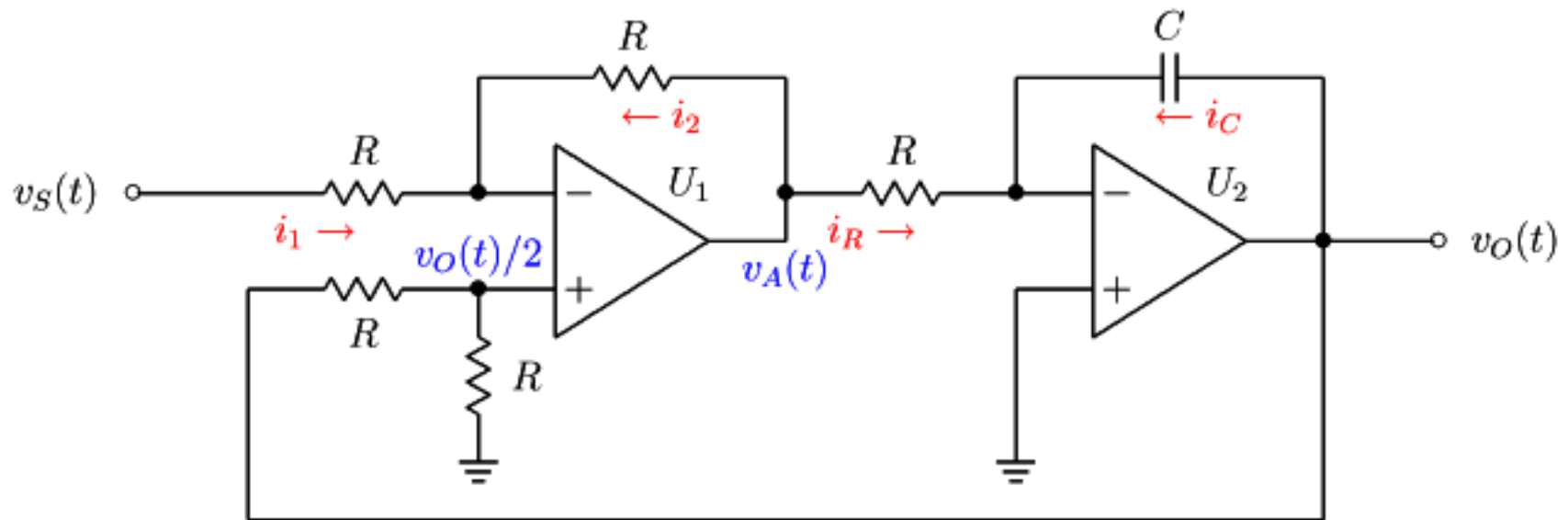
# Example

What is the output of this circuit? How would you describe it?



# Solution

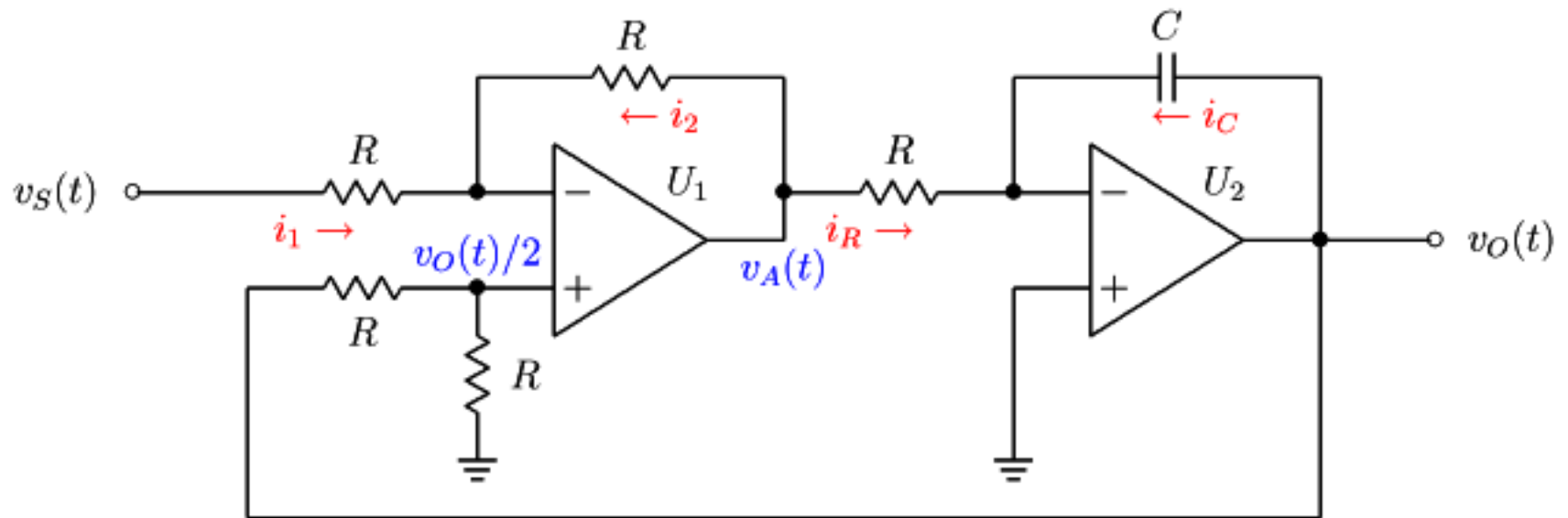


$$i_R(t) + i_C(t) = 0 \quad \Rightarrow \quad \frac{v_A(t)}{R} + C \frac{dv_O(t)}{dt} = 0 \quad \Rightarrow \quad v_A(t) = -RC \frac{dv_O(t)}{dt}.$$

$$i_1(t) + i_2(t) = 0 \quad \Rightarrow \quad \frac{2v_S(t) - v_O(t)}{2R} + \frac{2v_A(t) - v_O(t)}{2R} = 0 \quad \Rightarrow \quad v_S(t) = v_O(t) - v_A(t).$$

$$v_S(t) = v_O(t) + RC \frac{dv_O(t)}{dt}.$$


# Example

## Electronic stethoscope

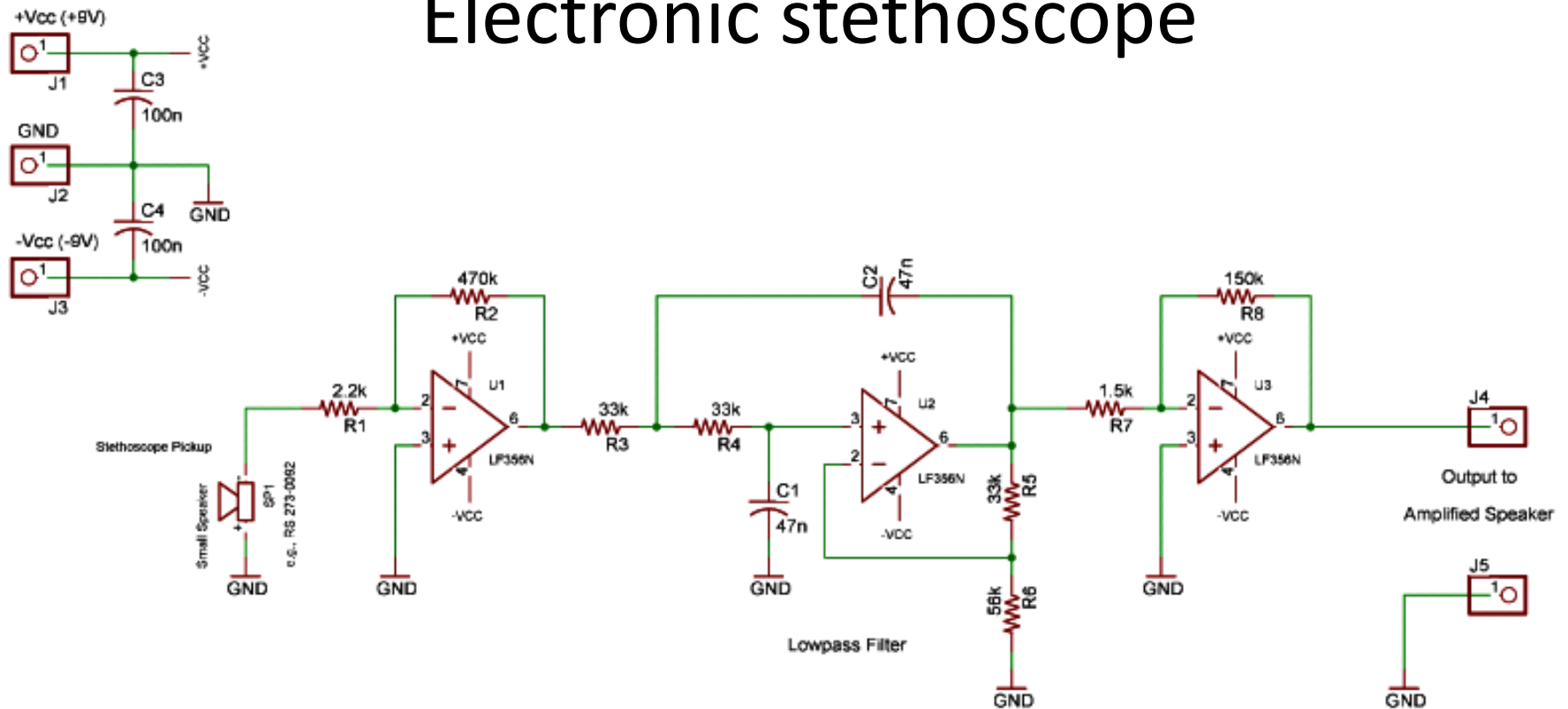

# Example

## Electronic stethoscope

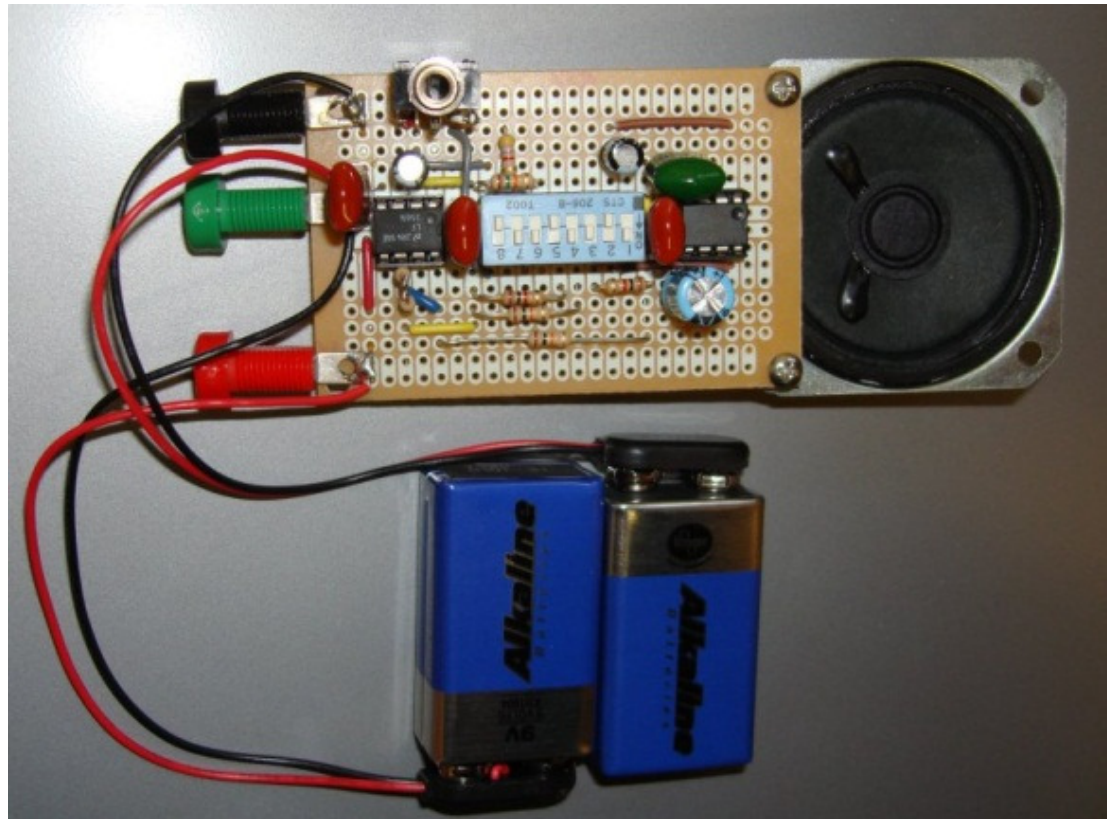


# Putting it All Together



- Making a stormtrooper helmet!

# Example

## Fully differential amplifier

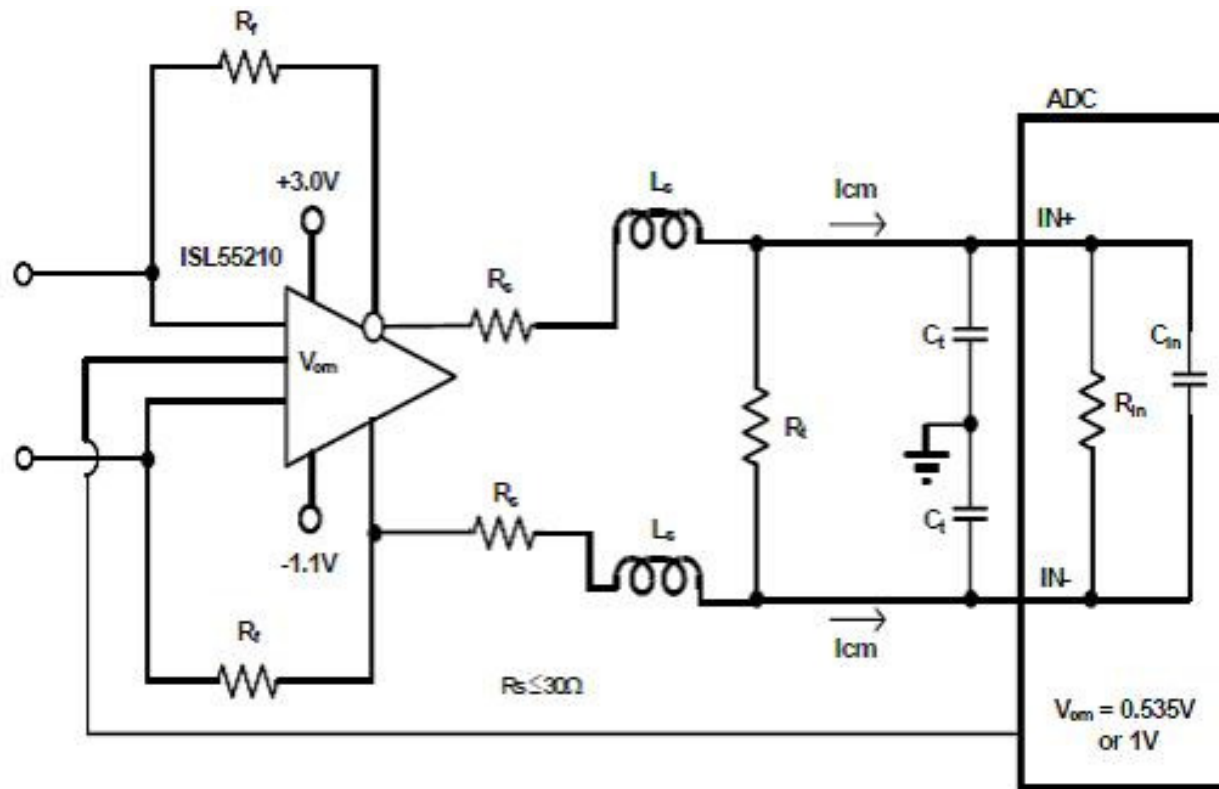

# Solution

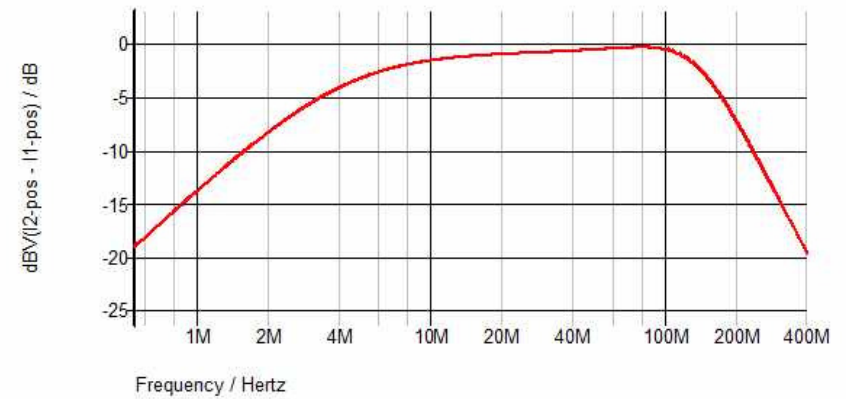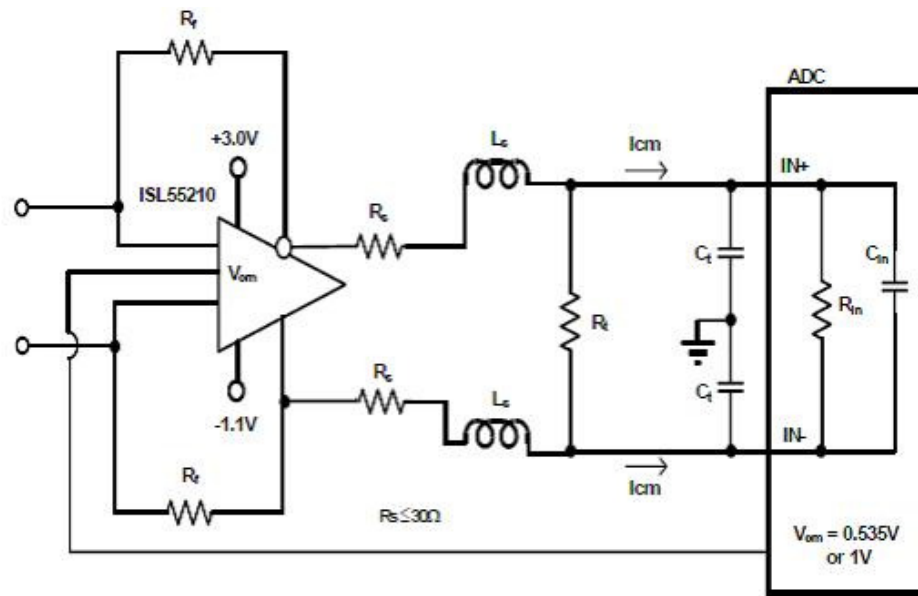



# Homework

- HW #27 due today by 4:30 pm in EE 325B
- HW #28 due Fri.: DeCarlo & Lin, Chapter 6:
  - Problem 31
  - Problem 32