

ECE 201, Section 4

Lecture 3


Prof. Peter Bermel

August 24, 2012

Homework Changes

- HW solution #1 posted

Ohm's Law

- Ohm's Law: $V=IR$ 
- Power $P(t)=I(t)V(t)$, thus:
$$P(t)=[I(t)]^2R$$
$$P(t)=[V(t)]^2/R$$
- Dissipated power given off as heat

Resistance


- Physical property of material: resistivity ρ ($\Omega \cdot \text{m}$)
- Resistance for cylinder: $R = \rho L / A$ (Ω)

Conductance

- Physical property of material: conductivity σ (S/m)
- Conductance for cylinder $G = \sigma A / L$ (S or Ω^{-1})

Example 1

- Find the resistance of a carbon rod with $L=1\text{ cm}$ and $A=0.1\text{ cm}^2$
- Find the current flow and power dissipated through the carbon rod when connected to a 1.5 V battery:

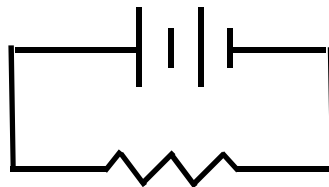

Example 1: Solution

- Find the resistance of a carbon rod with $L=1$ cm and $r=0.02$ cm:

$$\rho = 2400 \cdot (17 \text{ n}\Omega \cdot \text{m}) = 40.8 \text{ }\mu\Omega \cdot \text{m}$$


$$R = \rho L / A = (40.8 \text{ }\mu\Omega \cdot \text{m})(1 \text{ cm}) / \pi (0.02 \text{ cm})^2 = 3.25 \text{ }\Omega$$

- Find the current flow through the carbon rod when connected to a 1.5 V battery:

$$I = V / R = (1.5 \text{ V}) / (3.25 \text{ }\Omega) = 0.46 \text{ A}$$

- Find the power dissipated:

$$P = IV = (0.46 \text{ A})(1.5 \text{ V}) = 0.69 \text{ W}$$

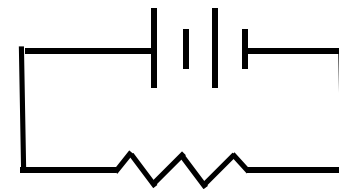


Example 2: Series Circuits

- Calculate the effective resistance of 3 resistors in series with resistances $2\ \Omega$, $3\ \Omega$, and $5\ \Omega$:



- Calculate the current generated when powered by a $9\ \text{V}$ battery:

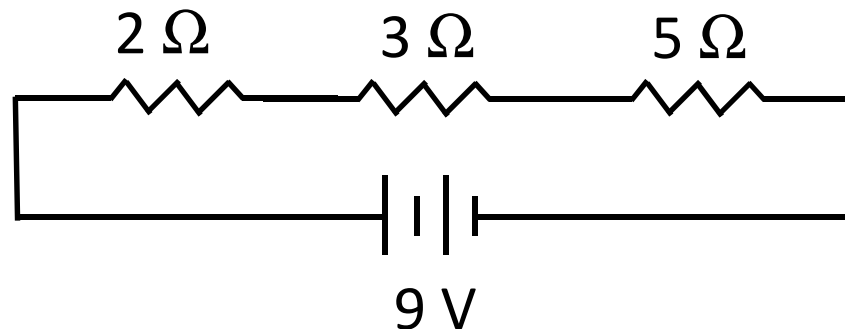

Example 2: Solution


- Calculate the effective resistance of 3 resistors in series with resistances $2\ \Omega$, $3\ \Omega$, and $5\ \Omega$:



$$R_{\text{eff}} = \sum_{i=1}^3 R_i = 2\ \Omega + 3\ \Omega + 5\ \Omega = 10\ \Omega$$

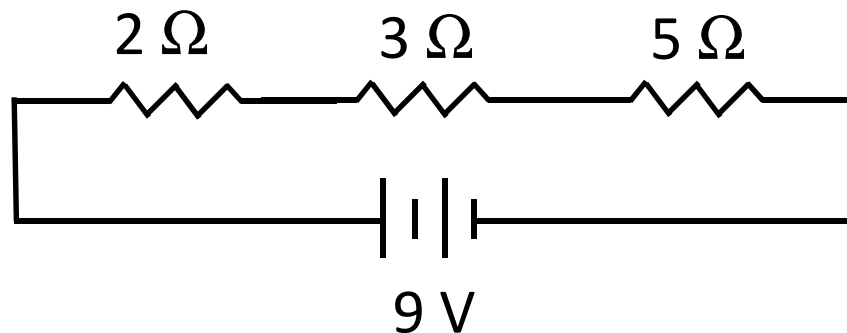Example 2: Solution Cont'd


- Calculate the current generated when powered by a 9 V battery:



$$I = V / R_{\text{eff}} = (9 \text{ V}) / (10 \text{ } \Omega) = 0.9 \text{ A}$$

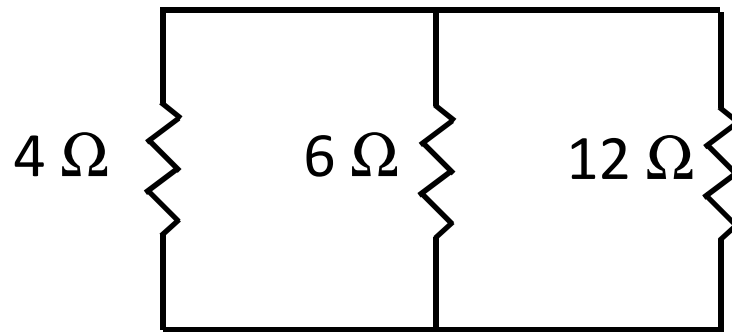Example 3: Parallel Circuits


- Calculate effective resistance of 3 resistors of resistances 4, 6, and 12 Ω :



- Calculate current when connected to two 1.5 V batteries in series:

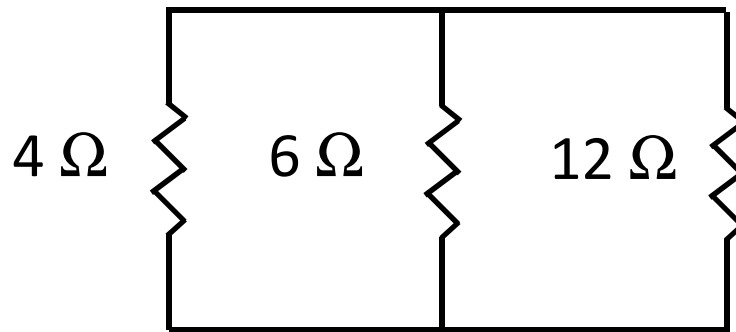Example 3: Solution

- Calculate effective resistance of 3 resistors of resistances 4, 6, and 12 Ω :




$$R_{\text{eff}}^{-1} = \sum_{i=1}^3 R_i^{-1}$$

$$R_{\text{eff}}^{-1} = \frac{1}{4} + \frac{1}{6} + \frac{1}{12} = 0.5 \text{ S}$$

$$R_{\text{eff}} = 2 \Omega$$

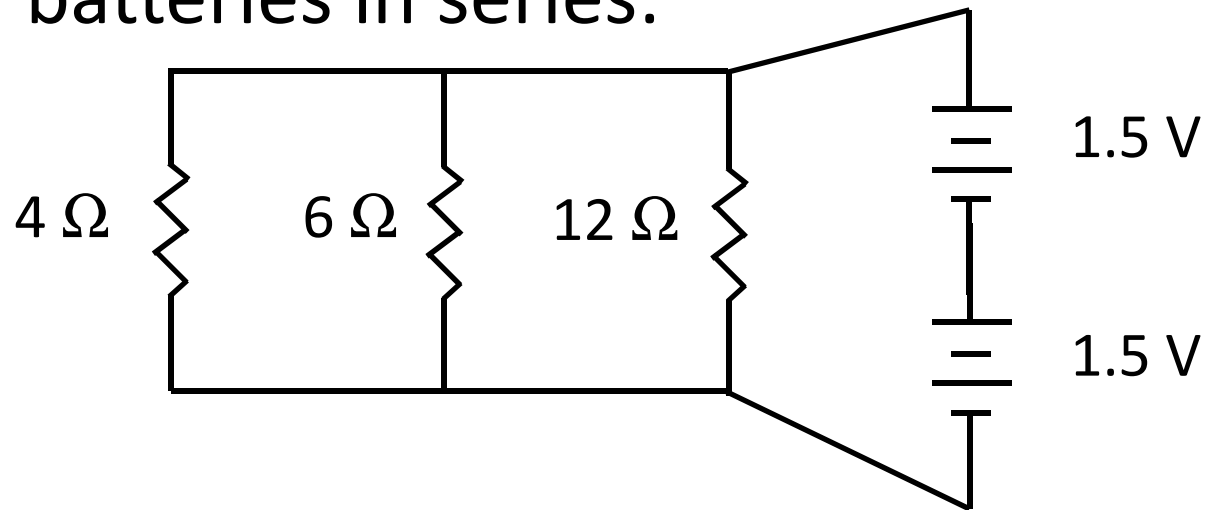Example 3: Parallel Circuits


- Calculate current when connected to two 1.5 V batteries in series:




$$I = V_{\text{eff}}/R_{\text{eff}} = (1.5 + 1.5\ \text{V})/2\ \Omega = 1.5\ \text{A}$$

Current-Voltage Relations


- Resistor

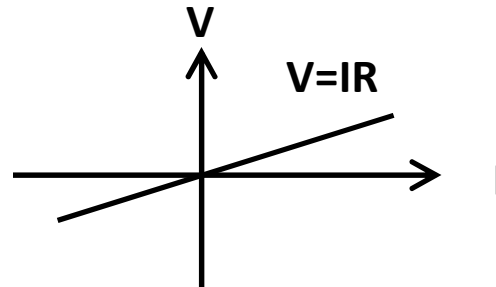

- Ideal voltage source

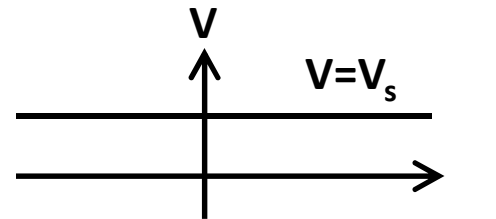



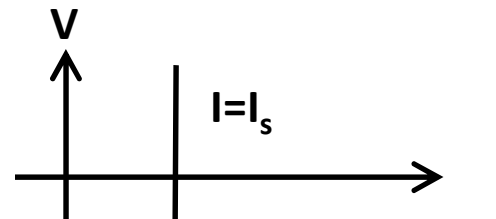

- Ideal current source



Controlled Ideal Sources

- Can use current or voltage to control output current or voltage

		Control type	
		Voltage	Current
Output type	Voltage	VCVS $V = \mu v_x$ 	CCVS $V = IR$ 
	Current	VCCS $I = gV$ 	CCCS $I = \beta I_x$ 

Homework #3 for Monday

- DeCarlo & Lin, 3rd Edition, Chapter 1
 - Problem 23
 - Problem 28
 - Problem 38
- All homework posted on Blackboard