

ECE 201, Section 3

Lecture 30

Prof. Peter Bermel

November 5, 2012

Recap From Last Time

- Solving first AC circuits – solution comprised of two parts:
 - Transient (exponentially decaying) solution
 - Sinusoidal steady state solution, tracking source frequency
- Best to treat everything in terms of complex exponentials; can be represented and manipulated in Cartesian and polar coordinates

Phasors

- Shorthand for writing complex numbers
- Closely connected with polar representation
- General form:

$$\mathbf{V} = V_m \angle \phi = V_m e^{j(\omega t + \phi)}$$

- Example: for a voltage source given by $5 \cos(\omega t + 30^\circ)$, the phasor $\mathbf{V} = 5 \angle 30^\circ$


KCL for Phasors

- Generalization of KCL from before
- At each current junction or Gaussian surface:


$$\sum_{k=1}^N \mathbf{I}_k(t) = \sum_{k=1}^N I_{km} \angle \phi_k = 0$$

Phasor KCL Example

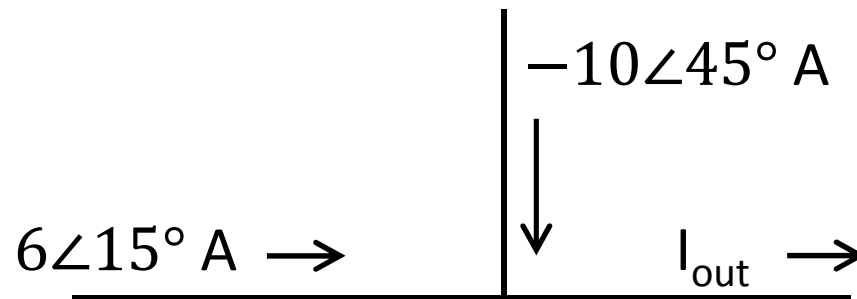- Consider 2 input currents with phasors given by $6\angle 15^\circ$ A and $-10\angle 45^\circ$ A. What is the total output current?



Phasor KCL Solution

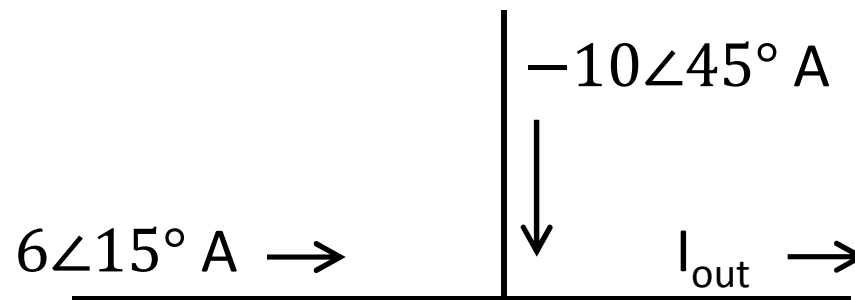

- Assuming $\omega t=0$, we can convert to Cartesian coordinates with $x = r \cos \phi$ and $y = r \sin \phi$:

$$6\angle 15^\circ = 6 \cos 15^\circ + j \cdot 6 \sin 15^\circ = 5.80 + 1.55j$$

$$-10\angle 45^\circ = -10 \cos 45^\circ + j \cdot (-10) \sin 45^\circ = -7.07 - 7.07j$$

$$6\angle 15^\circ + -10\angle 45^\circ = (5.80 - 7.07) + (1.55 - 7.07)j$$

$$6\angle 15^\circ + -10\angle 45^\circ = -1.27 - 5.52j$$

- We can convert back with $r = \sqrt{x^2 + y^2}$ and $\phi = \tan^{-1} y/x$:


$$6\angle 15^\circ + -10\angle 45^\circ = 5.66\angle -103^\circ = -5.66\angle 77^\circ$$

KVL for Phasors


- Generalization of KVL from before to phasors:
 - Voltage difference phasor V_{AB} between points A and B is the same, regardless of the path taken
 - The voltage difference is directionally sensitive, i.e., $V_{AB} = -V_{BA}$
 - The voltage difference over a closed loop is zero (otherwise, voltage would be non-unique)

Phasor KVL Example

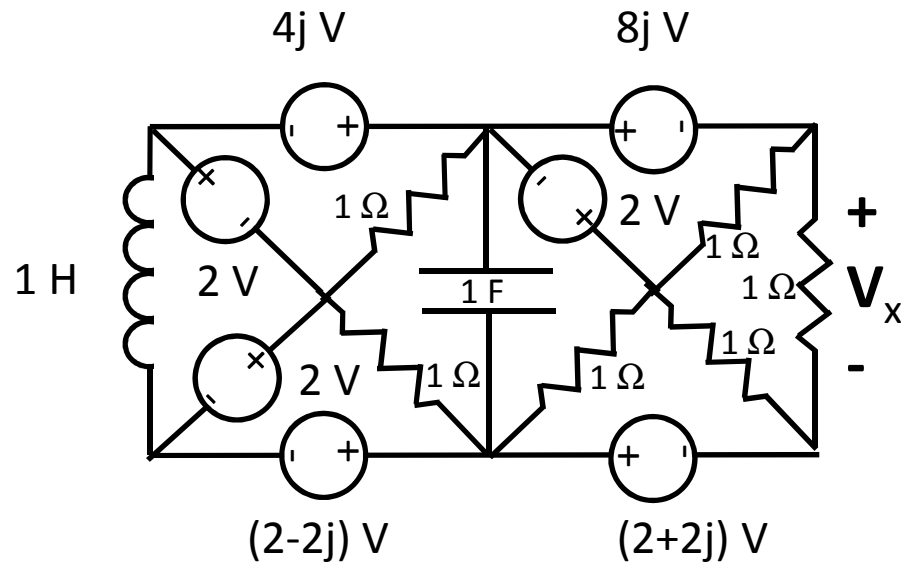- What is the phasor voltage V_x in this circuit?



Phasor KVL Solution

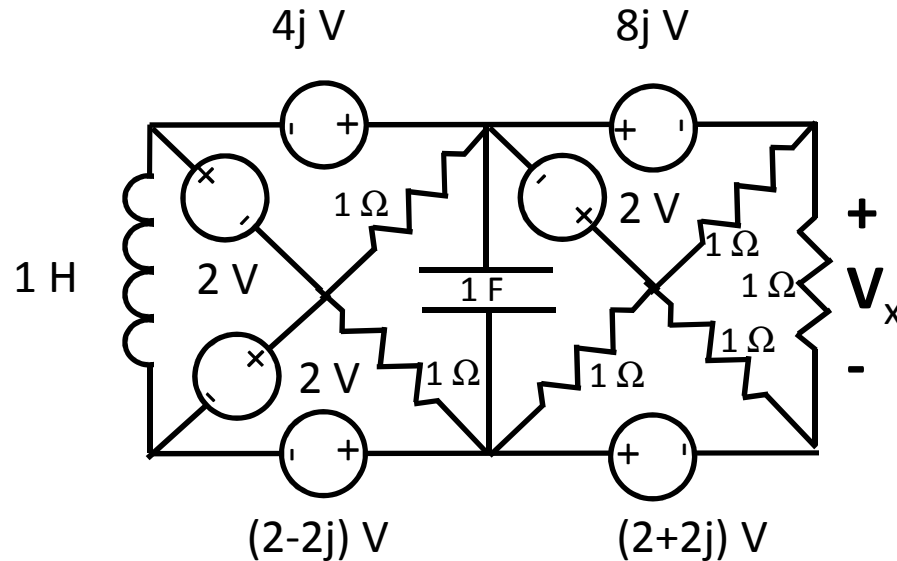

- Assign - terminal of V_x to ground
- Find path leading to + terminal of V_x
- Keeping track of signs:

$$V_x = (2 + 2j) - (2 - 2j) + 2 + 2 + 4j - 8j = 4 \text{ V}$$

Phasor Impedance

- Basic concept: generalize resistance to the concept of impedance for phasors, such that:

$$\mathbf{V} = \mathbf{Z}(j\omega)\mathbf{I}$$

- For resistor, no conservation rules mean no lag and simple relation between impedance and resistance:

$$\mathbf{Z}(j\omega) = R, \quad \text{for all } \omega$$

Phasor Impedance: Inductors

- Given that we have impedance given by:

$$\mathbf{V} = Z(j\omega)\mathbf{I}$$

- For inductors, we have:

$$V = L \frac{dI}{dt}$$

- Assuming an input current source $I = Ae^{j(\omega t + \phi)}$:

$$V = (Lj\omega)Ae^{j(\omega t + \phi)} = j\omega LI$$

- Comparing the first & third expressions yields:

$$Z(j\omega) = j\omega L, \quad \text{for all } \omega$$

- Thus, voltage leads current by 90°

Phasor Impedance: Capacitors

- Given that we have impedance given by:

$$V = Z(j\omega)I$$

- For capacitors, we have:

$$I = C \frac{dV}{dt}$$

- Assuming an input voltage source $V = Ae^{j(\omega t + \phi)}$:

$$I = (Cj\omega)Ae^{j(\omega t + \phi)} = j\omega CV$$




- Comparing the first & third expressions yields:

$$Z(j\omega) = \frac{1}{j\omega C}, \quad \text{for all } \omega$$

- Thus, current leads voltage by 90°

Phasor Admittance

- Inverse of impedance
- Symbolized by $Y(j\omega) = 1/Z(j\omega)$

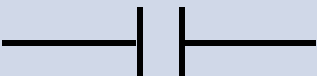Circuit Element	Impedance	Admittance
	$Z(j\omega) = R$	$Y(j\omega) = \frac{1}{R}$
	$Z(j\omega) = j\omega L$	$Y(j\omega) = \frac{1}{j\omega L}$
	$Z(j\omega) = \frac{1}{j\omega C}$	$Y(j\omega) = j\omega C$

Impedance Properties

- For general linear networks:
 - Resistance $R = \operatorname{Re} Z(j\omega)$ (from resistors)
 - Reactance $X = \operatorname{Im} Z(j\omega)$ (from inductors, capacitors)
- Impedances add in series:

$$Z_{eq}(j\omega) = \sum_{k=1}^N Z_k(j\omega)$$

- Admittances add in parallel:

$$Y_{eq}(j\omega) = \sum_{k=1}^N Y_k(j\omega)$$

Impedance Properties

- For circuit elements in series, voltage division rule becomes:


$$V_k = \frac{Z_k}{Z_{eq}} V_{tot}$$

- For circuit elements in parallel, current division rule becomes:


$$I_k = \frac{Y_k}{Y_{eq}} I_{tot}$$

Impedance Example

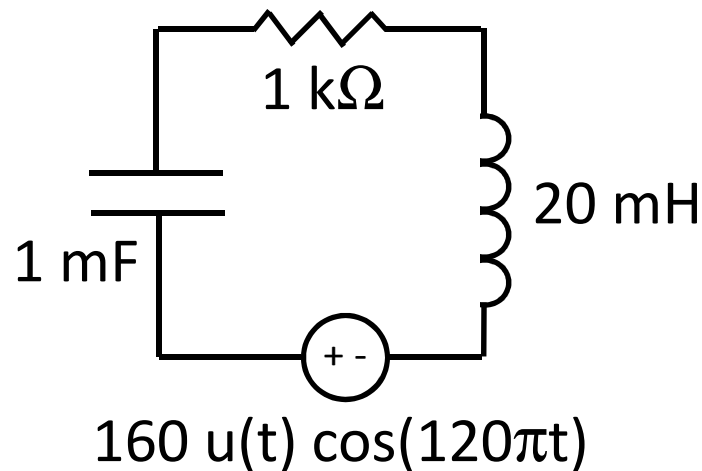- What is the impedance across the source terminals of this circuit? After the source is turned on, what is its steady-state response?



Impedance Solution

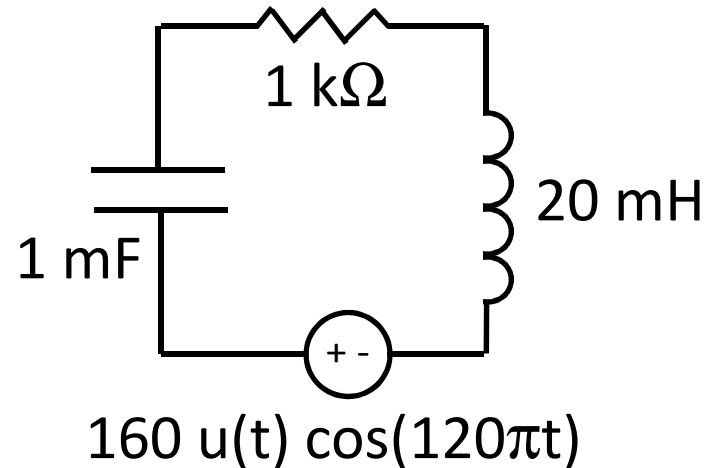

- Since impedances add in series, we get:


$$Z_{eq} = 1 \text{ k}\Omega + j\omega(20 \text{ mH}) + 1/[j\omega(1 \text{ mF})]$$

- If $\omega = 120\pi$, we get:

$$Z_{eq} = 1 \text{ k}\Omega + j120\pi(20 \text{ mH}) + 1/[j120\pi(1 \text{ mF})]$$

$$Z_{eq} = 10^3 + 4.887j \text{ }\Omega$$

Impedance Solution

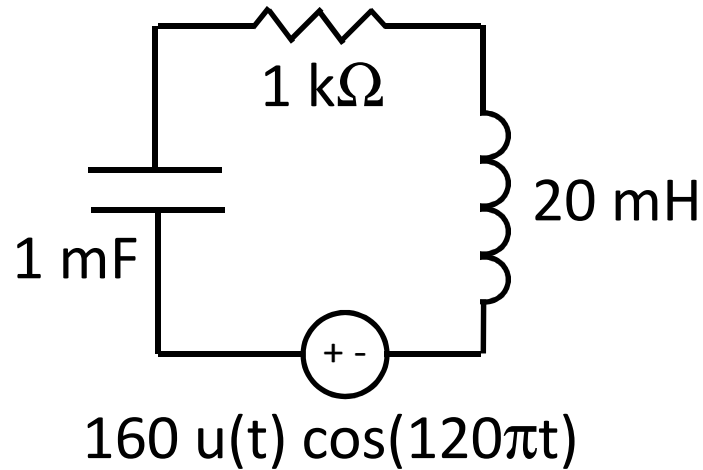

- Given that:

$$Z_{eq} = 10^3 + 4.887j \, \Omega$$

- Applying the definition of impedance:

$$I = \frac{V}{Z_{eq}} = \frac{160e^{j120\pi t}}{10^3 + 4.887j}$$

$$I = 0.160e^{j(120\pi t - 0.28^\circ)} = 0.16 \angle -0.28^\circ$$

Homework

- HW #29 due today by 4:30 pm in EE 325B
- HW #30 due Wed:
 1. Add the complex numbers $z_1 = 8e^{-j\pi/6}$ and $z_2 = -5e^{j5\pi/8}$. Express your answer (a) in real and imaginary parts, and (b) as a magnitude and phase. Draw z_1 , z_2 and $z_1 + z_2$ on the complex plane. Label the real part, the imaginary part, and magnitude and the phase of $z_1 + z_2$.
 2. Multiply the complex numbers $z_1 = 2-4j$ and $z_2 = -4+3j$. Express your answer (a) in real and imaginary parts, and (b) as a magnitude and phase. (c) Compare $|z_1| |z_2|$ to $|z_1 z_2|$. (d) What is the relationship between the phase of z_1 , the phase of z_2 , and the phase of $z_1 z_2$?
 3. For z_1 and z_2 given in problem 2, determine z_1/z_2 . Express your answer (a) in real and imaginary parts, and (b) as a magnitude and phase. (c) Compare $|z_1|$ and $|z_2|$ to $|z_1 / z_2|$. (d) What is the relationship between the phase of z_1 , the phase of z_2 , and the phase of z_1/z_2 ?