

ECE 201, Section 3

Lecture 31

Prof. Peter Bermel

November 7, 2012




Phasor Review

- Shorthand for writing complex numbers:

$$\mathbf{V} = V_m \angle \phi = V_m e^{j(\omega t + \phi)}$$

- Ohm's law with phasors:

$$\mathbf{V} = Z(j\omega)\mathbf{I}$$

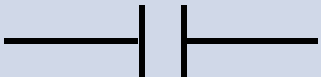Circuit Element	Impedance	Admittance
	$Z(j\omega) = R$	$Y(j\omega) = \frac{1}{R}$
	$Z(j\omega) = j\omega L$	$Y(j\omega) = \frac{1}{j\omega L}$
	$Z(j\omega) = \frac{1}{j\omega C}$	$Y(j\omega) = j\omega C$

Impedance Properties

- For circuit elements in series, voltage division rule becomes:


$$V_k = \frac{Z_k}{Z_{eq}} V_{tot}$$

- For circuit elements in parallel, current division rule becomes:


$$I_k = \frac{Y_k}{Y_{eq}} I_{tot}$$

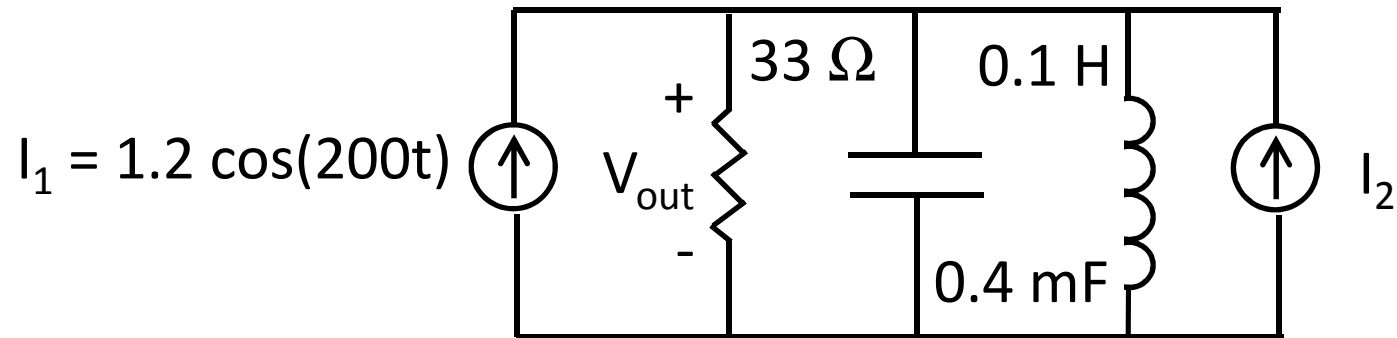Example #1

- If $V_{\text{out}} = 40 \sin(200t)$, what are I_1 and V_{out} ? What is the phasor I_2 ?



Solution

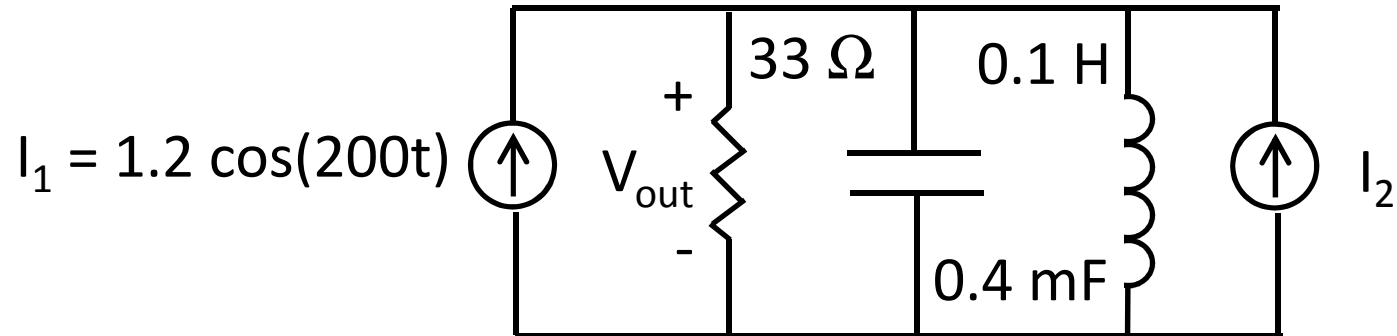


- Phasors given by:

$$I_1 = 1.2 \angle 0^\circ$$
$$V_{out} = 40 \angle -90^\circ$$

- Calculate admittance:

$$Y = \frac{1}{33} + 0.0004 \cdot 200j + \frac{1}{0.1 \cdot 200j} \approx 0.03 - 0.03j$$

Solution

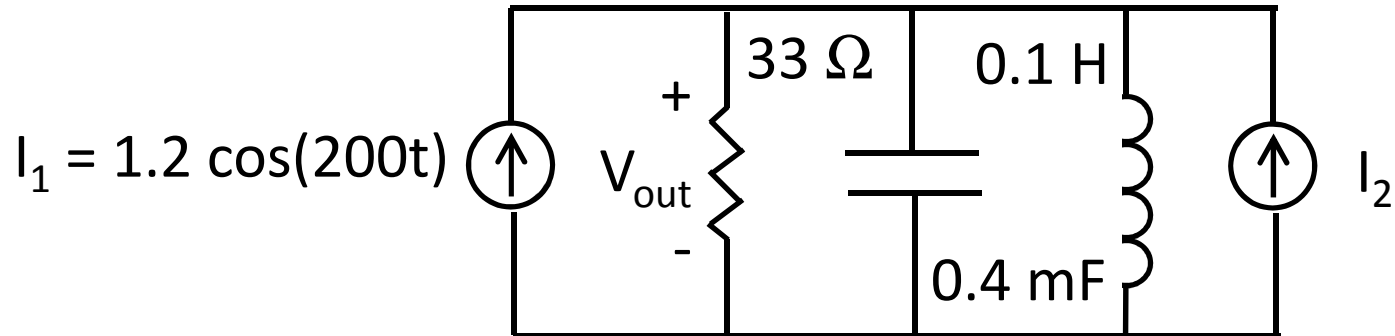

- Total current given by:

$$I = YV = 0.0424e^{-j45^\circ} \cdot 40e^{j(200t-90^\circ)}$$

$$I = YV = 1.696e^{j(200t-135^\circ)} = 1.696\angle -135^\circ$$

- Current on the right is given by:


$$I_2 = I + I_1$$

$$I_2 = 1.696 \cos(-135^\circ) + j1.696 \sin(-135^\circ) + 1.2$$


$$I_2 = -1.2j = 1.2\angle -90^\circ$$

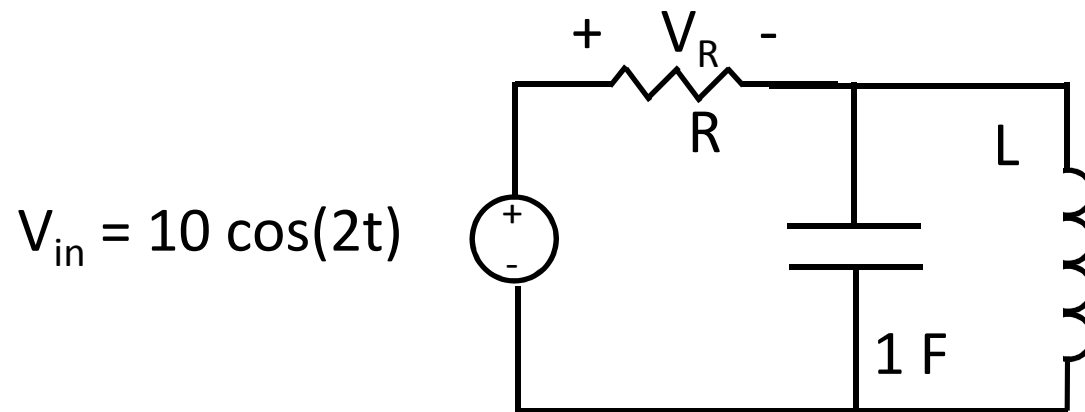Example #2

- If $Z(2j) = 4 + 2j$, what are R and L ? What is the voltage phasor across the resistor?



Solution

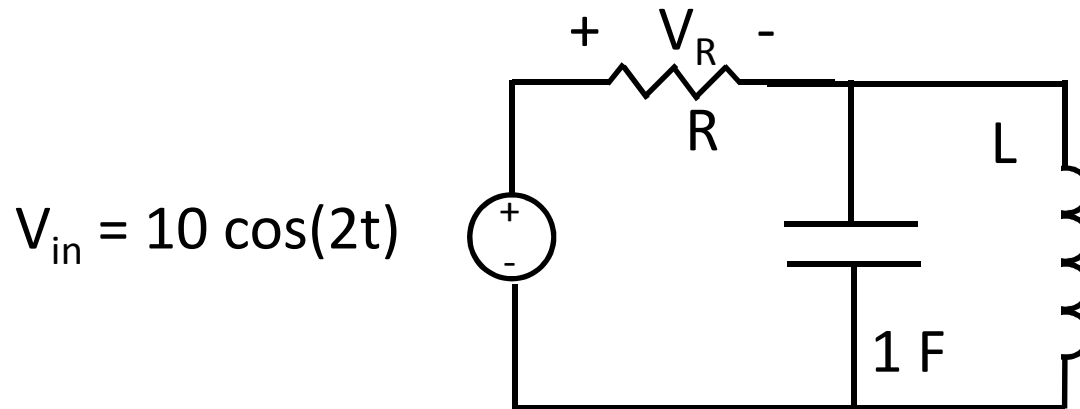

- Impedance here is given by:

$$Z(j\omega) = R + \left[j\omega C + \frac{1}{j\omega L} \right]^{-1}$$

- Setting equal to our target impedance at $\omega=2$:


$$Z(2j) = R + \left[2j + \frac{1}{2jL} \right]^{-1} = 4 + 2j$$

- Equating real and imaginary parts yields $R=4 \Omega$ and:

$$\frac{1}{2j} = 2j + \frac{1}{2jL}$$

$$2jL = \frac{1}{\frac{1}{2j} - 2j} = \frac{2j}{5}; \text{ thus, } L=0.2 \text{ H}$$

Solution

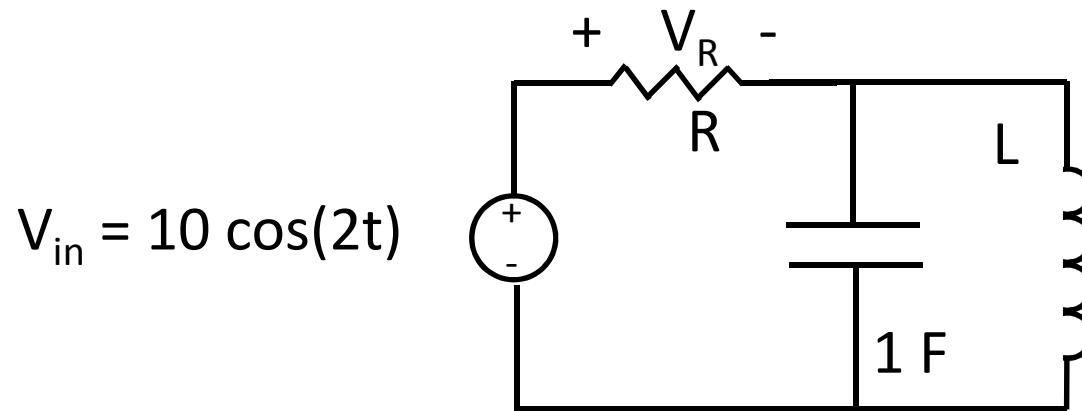

- Using the voltage division rules:

$$V_R = \frac{R}{Z(2j)} V_{in}$$

- Substituting the values found before:


$$V_R = \frac{4}{4 + 2j} 10e^{j2t}$$

$$V_R = \frac{40e^{j2t}}{\sqrt{4^2 + 2^2} e^{j \tan^{-1} 2/4}}$$


$$V_R = 8.94e^{j(2t-26.6^\circ)}$$

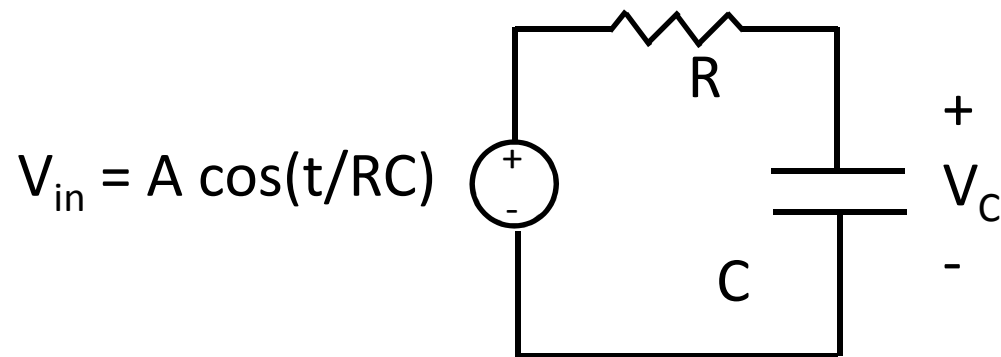Example #3

- What is the voltage across the capacitor as a function of time, with a source $A \cos(t/RC)$?



Solution

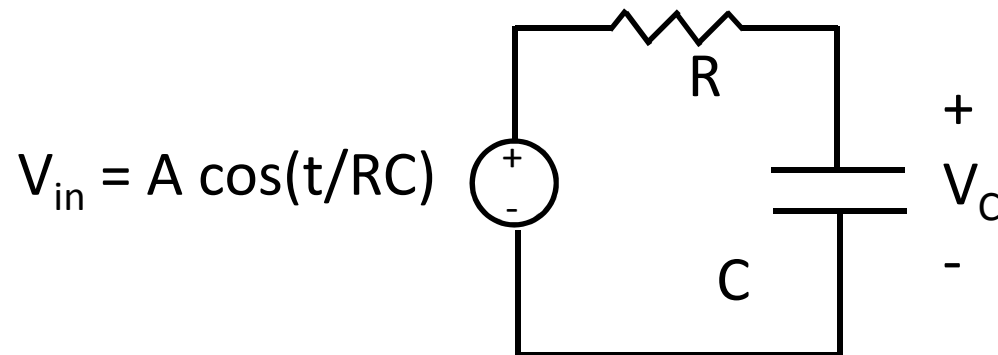


- From the voltage division rule:

$$V_C = \frac{-jRC/C}{R - jRC/C} A e^{jt/RC}$$


$$V_C = \frac{A}{\sqrt{2}} e^{j(\frac{t}{RC} - 90^\circ + 45^\circ)}$$

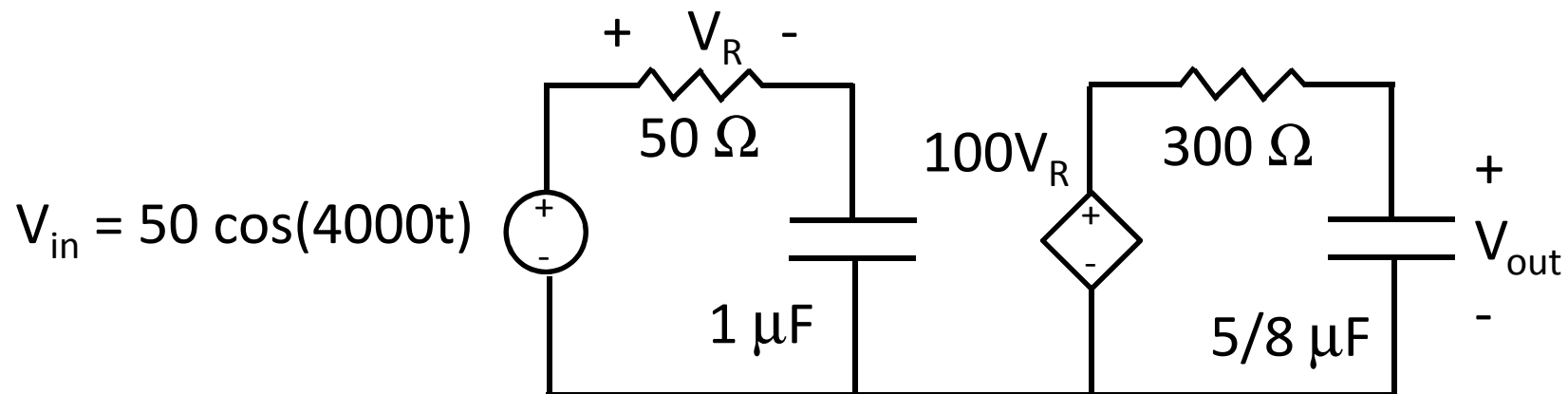Example #4

- What is the voltage across the right capacitor V_{out} as a function of time?



Solution

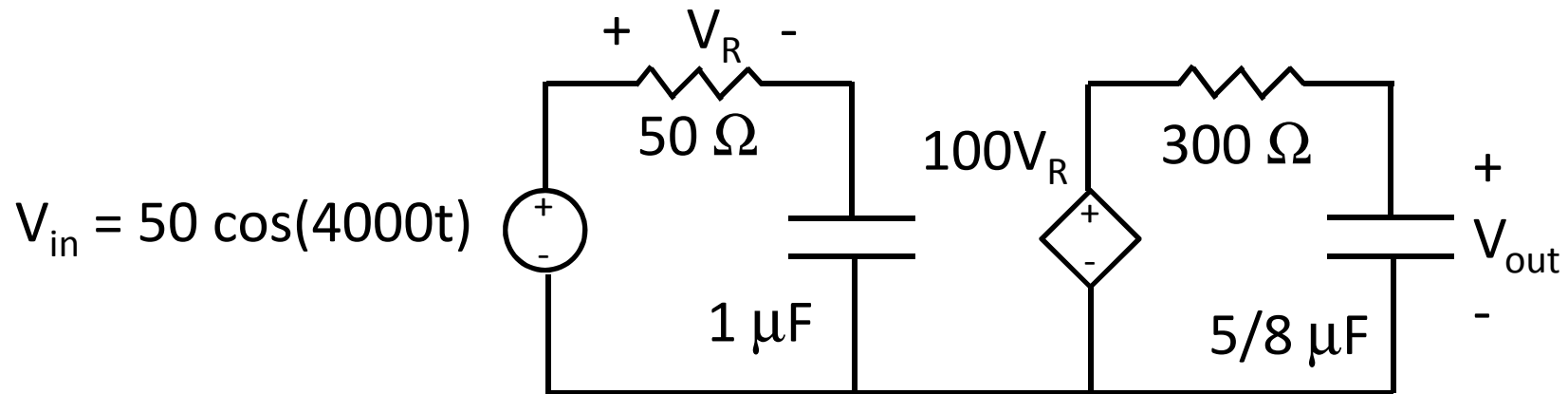

- On the left side, voltage division yields:


$$V_R = \frac{50 \cdot 50e^{j4000t}}{50 + 1/(10^{-6} \cdot 4000j)}$$

$$V_R = 9.806e^{j(4000t+78.69^\circ)}$$

- Thus, our VCVS has an output of:

$$V_S = 980.6e^{j(4000t+78.69^\circ)}$$

Solution

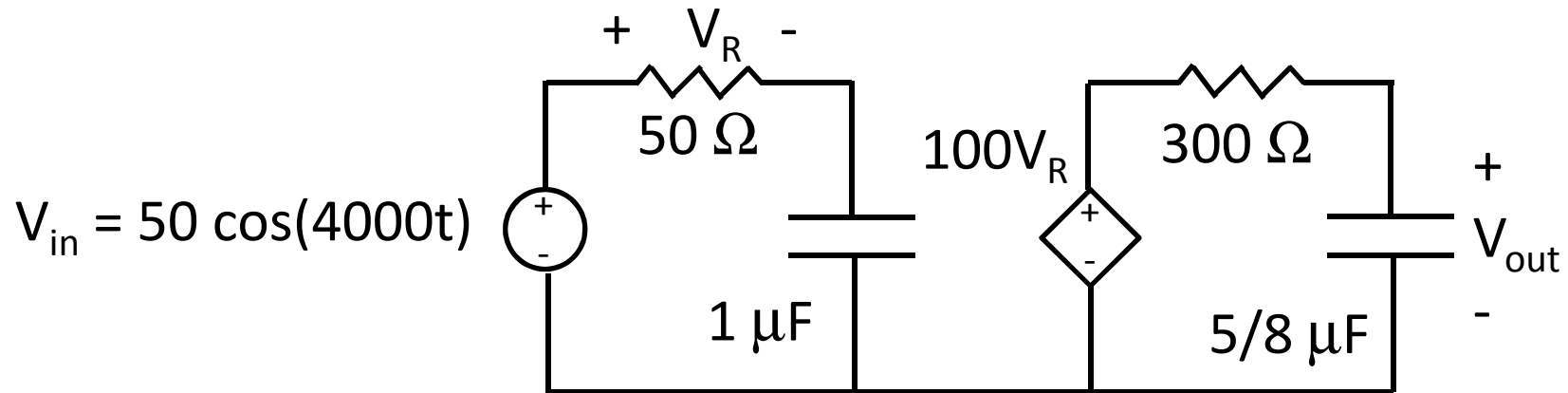

- Since our VCVS voltage is $980.6e^{j(4000t+78.69^\circ)}$
- Voltage division on the right-hand side yields:


$$V_{out} = \frac{980.6e^{j(4000t+78.69^\circ)} / (j4000 \cdot 5/8 \cdot 10^{-6})}{300 + 1/(j4000 \cdot 5/8 \cdot 10^{-6})}$$

$$V_{out} = 784.5e^{j(4000t+78.69^\circ-90^\circ+53.13^\circ)}$$


$$V_{out} = 784.5e^{j(4000t+41.82^\circ)}$$

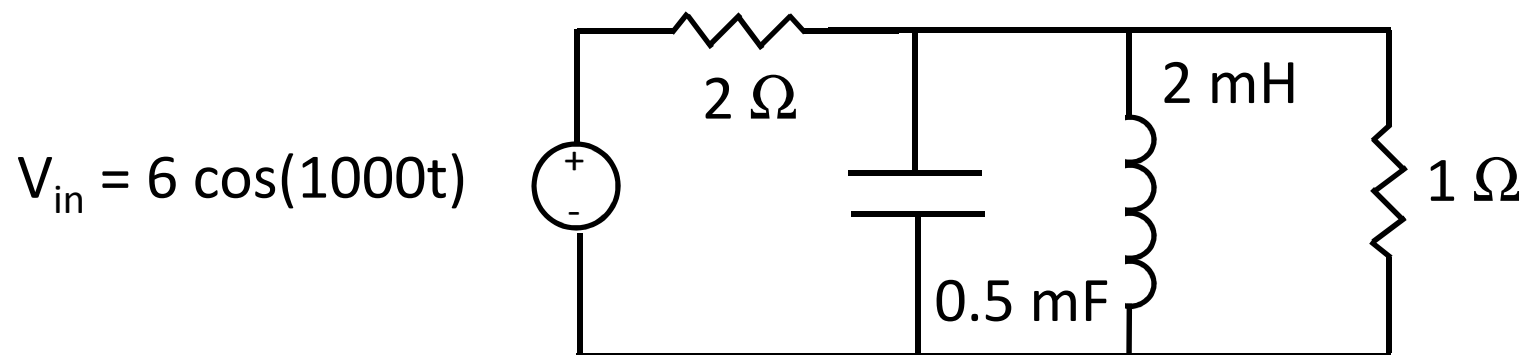Example #5

- What total current flows through this circuit, and how much flows through the inductor?



Solution

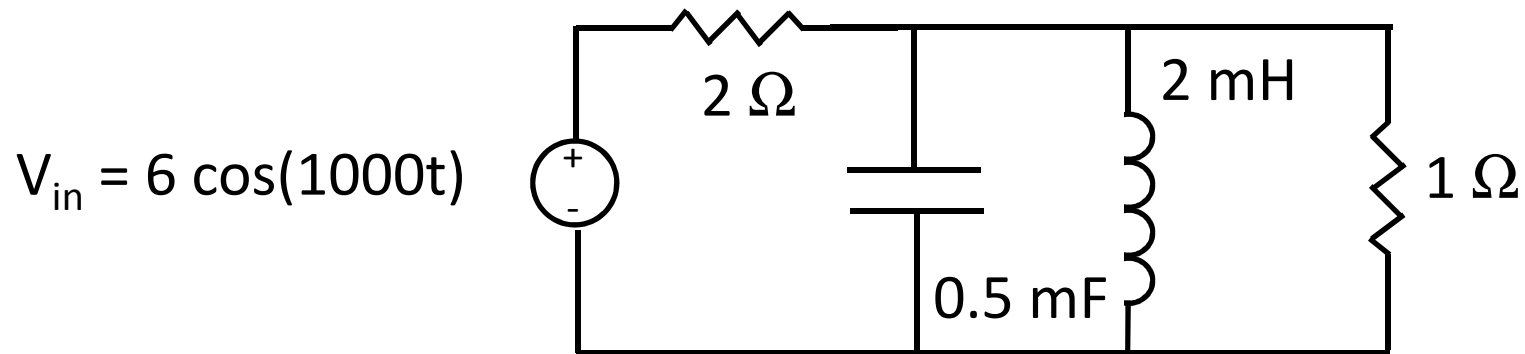

- The impedance is given by:


$$Z = 2 + \left[1 + j \cdot 10^3 \cdot 5 \cdot 10^{-4} + \frac{1}{j \cdot 10^3 \cdot 2 \cdot 10^{-3}} \right]^{-1}$$

$$Z = 3 \Omega$$

- The total current is thus given by:

$$I_{tot} = \frac{V}{Z} = \frac{6e^{j1000t}}{3} = 2e^{j1000t}$$

Solution

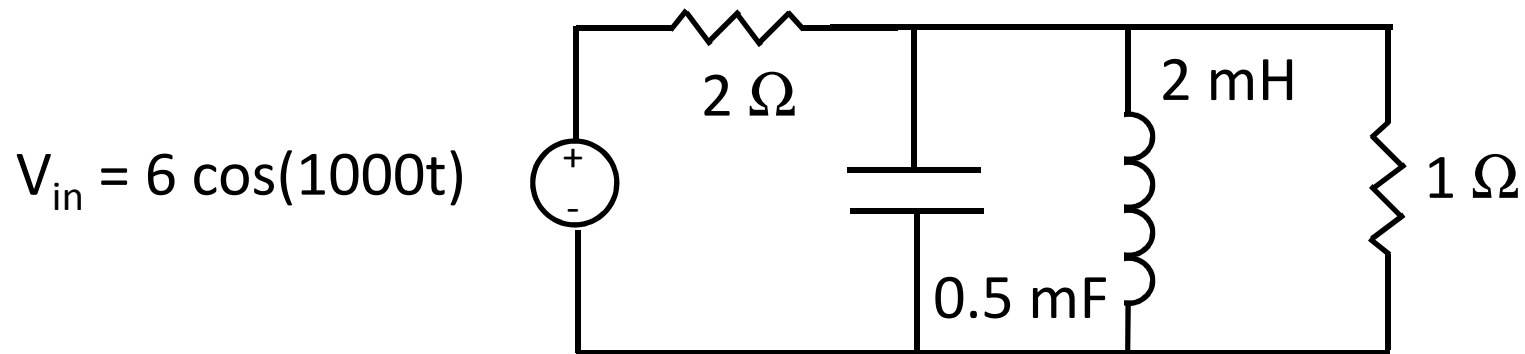

- Applying the current division rule:

$$I_L = \frac{Y_L}{Y} I_{tot}$$
$$I_L = \frac{-0.5j}{1} 2e^{j1000t} = e^{j(1000t-90^\circ)}$$

Homework

- HW #30 due today by 4:30 pm in EE 325B
- HW #31 due Fri.: DeCarlo & Lin, Chapter 10:
 - Problem 7
 - Problem 8
 - Problem 10 [Correction: In ANSWER, the phase angle of V_x is 71.56°]