


# ECE 201, Section 3

## Lecture 33

Prof. Peter Bermel

November 12, 2012

# Second Order Circuit Overview

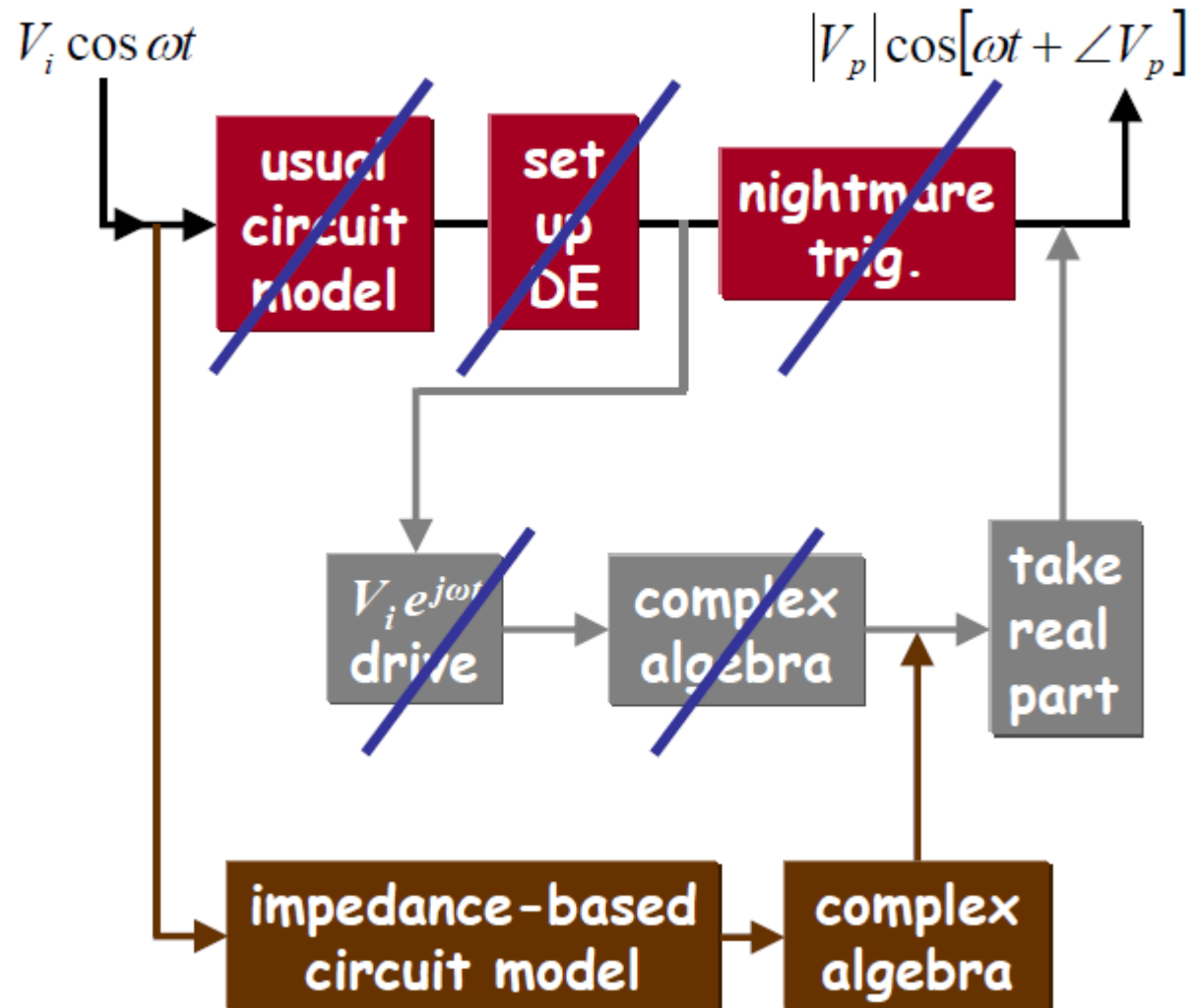


Adapted from A. Agarwal & J. Lang, Course Materials for MIT 6.002, Spring 2007

# Frequency Response


- Frequency response: the ratio of phasor output to phasor input as a function of frequency
- Consists of two plots:
  - Magnitude of phasor ratio:  $\left| \frac{V_p}{V_i} \right|$
  - Phase of the phasor ratio:  $\angle V_p - \angle V_i$
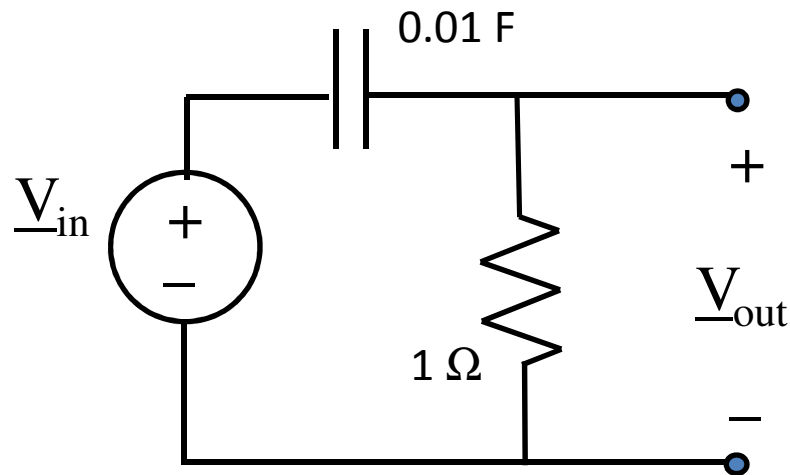
# Example #1

- Plot the frequency response of the circuit below:




# Solution

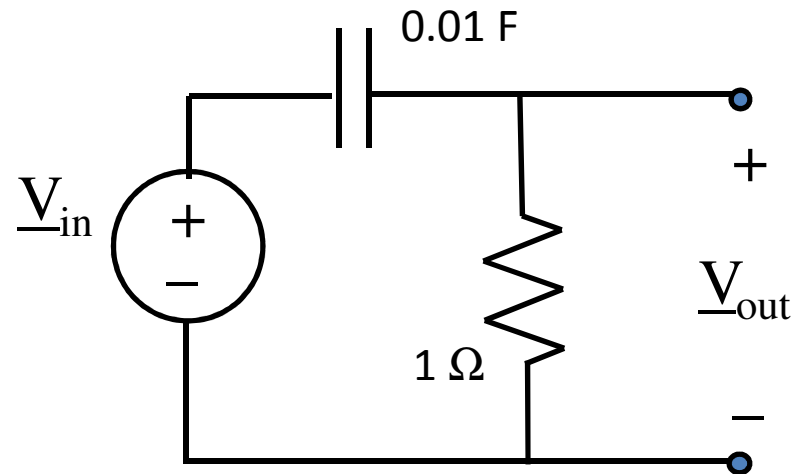

Step 1: Find impedance of the capacitor and resistor pair.

$$Z_{in} = R + (1/j\omega C) = 1 + (1/j0.01\omega)$$



# Solution

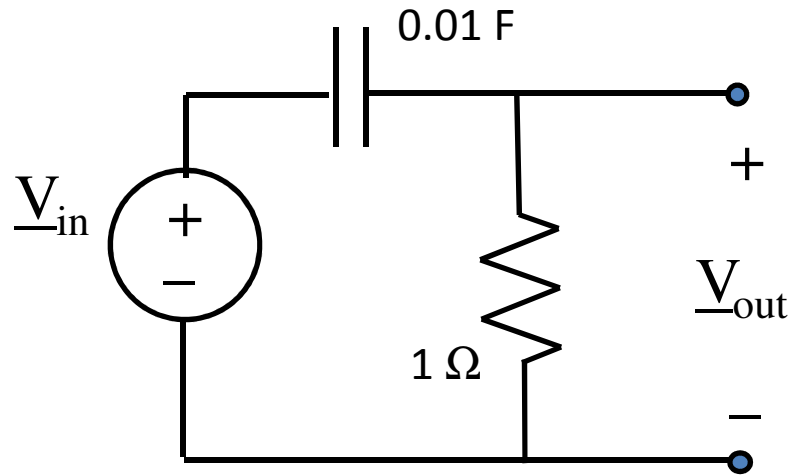

Step 2: Use voltage division to establish output to input ratio.

$$\frac{\underline{V}_{\text{out}}}{\underline{V}_{\text{in}}} = \frac{1}{1 + (1/j0.01\omega)} = \frac{j0.01\omega}{1 + j0.01\omega} = H(j\omega)$$

# Frequency Response

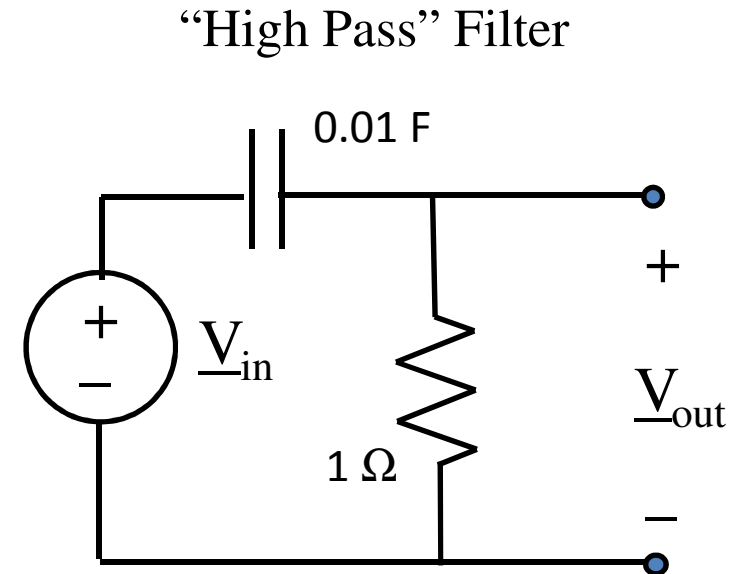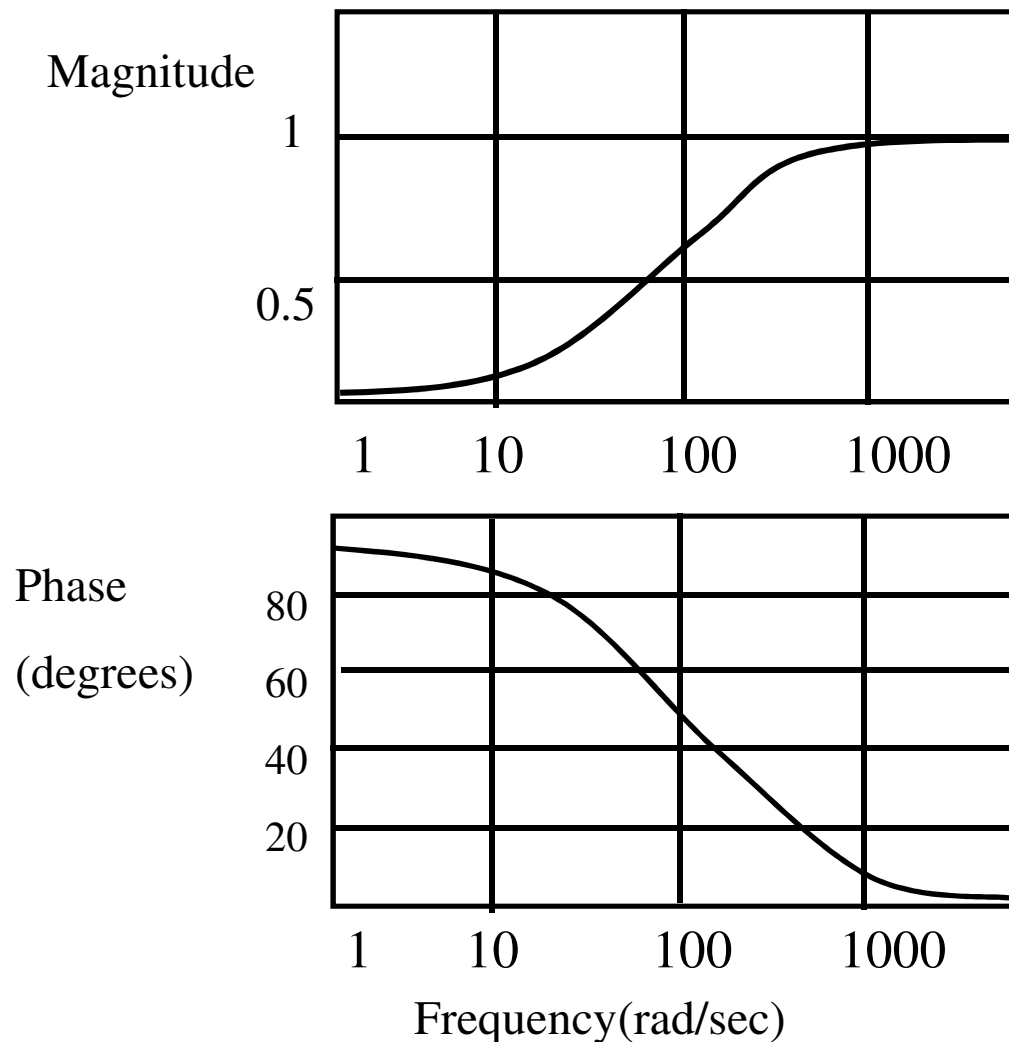

Two plots, one for magnitude and one for phase angle, are needed because  $H(j\omega)$  is a complex quantity.

# Limiting Frequency Responses

Important frequencies for RC circuits.

$$\omega = 0 \quad \text{and} \quad \omega = \infty$$

$$H(j0) = 0 \angle 90^\circ$$

$$H(j\infty) = 1 \angle 0^\circ$$

For magnitude:

$$|H(j\omega)| \longrightarrow 0 \quad \text{as} \quad \omega \longrightarrow 0$$

$$|H(j\omega)| \longrightarrow 1 \quad \text{as} \quad \omega \longrightarrow \infty$$

For phase:


$$\angle H(j\omega) \longrightarrow 0^\circ \quad \text{as} \quad \omega \longrightarrow \infty$$

$$\angle H(j\omega) \longrightarrow 90^\circ \quad \text{as} \quad \omega \longrightarrow 0$$



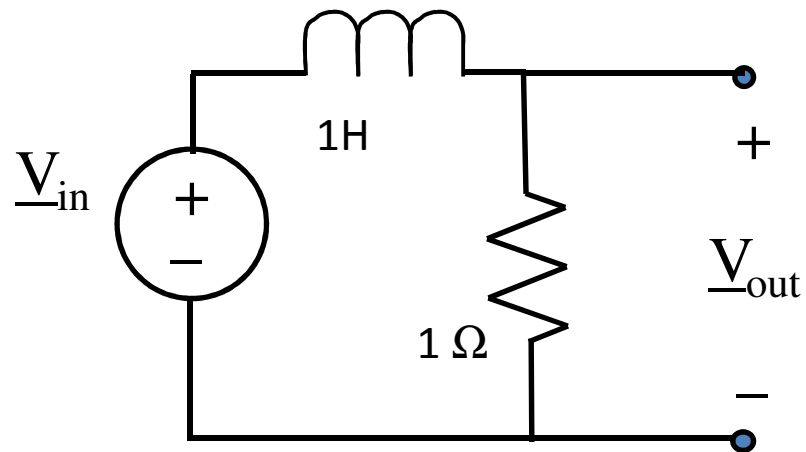
## Example #2

Plot the frequency response for the circuit below.




# Solution

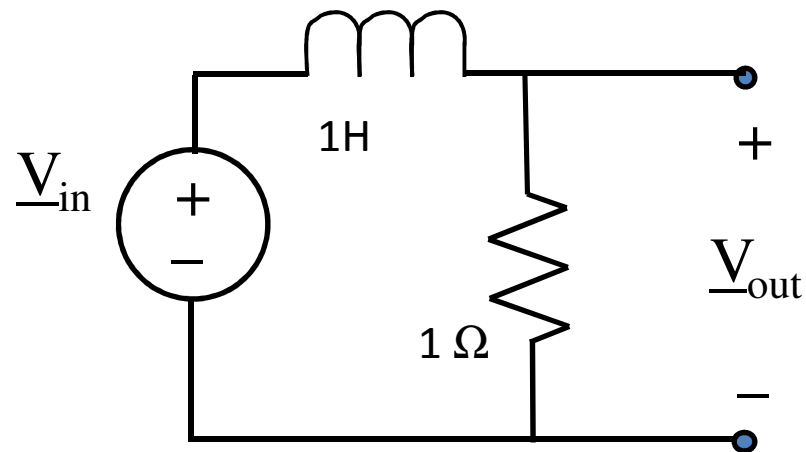

Step 1: Find the impedance of inductor and resistor pair.

$$Z_{in} = R + (j\omega L) = 1 + (j\omega)$$


# Solution

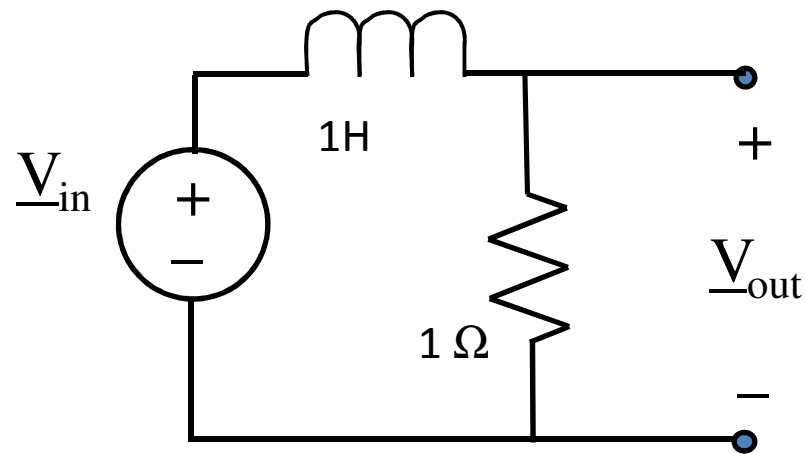


Step 2: Use voltage division to establish output to input ratio.

$$\frac{\underline{V}_{out}}{\underline{V}_{in}} = \frac{R}{R+j\omega L} = \frac{1}{1+j\omega} = H(j\omega)$$

# Frequency Response

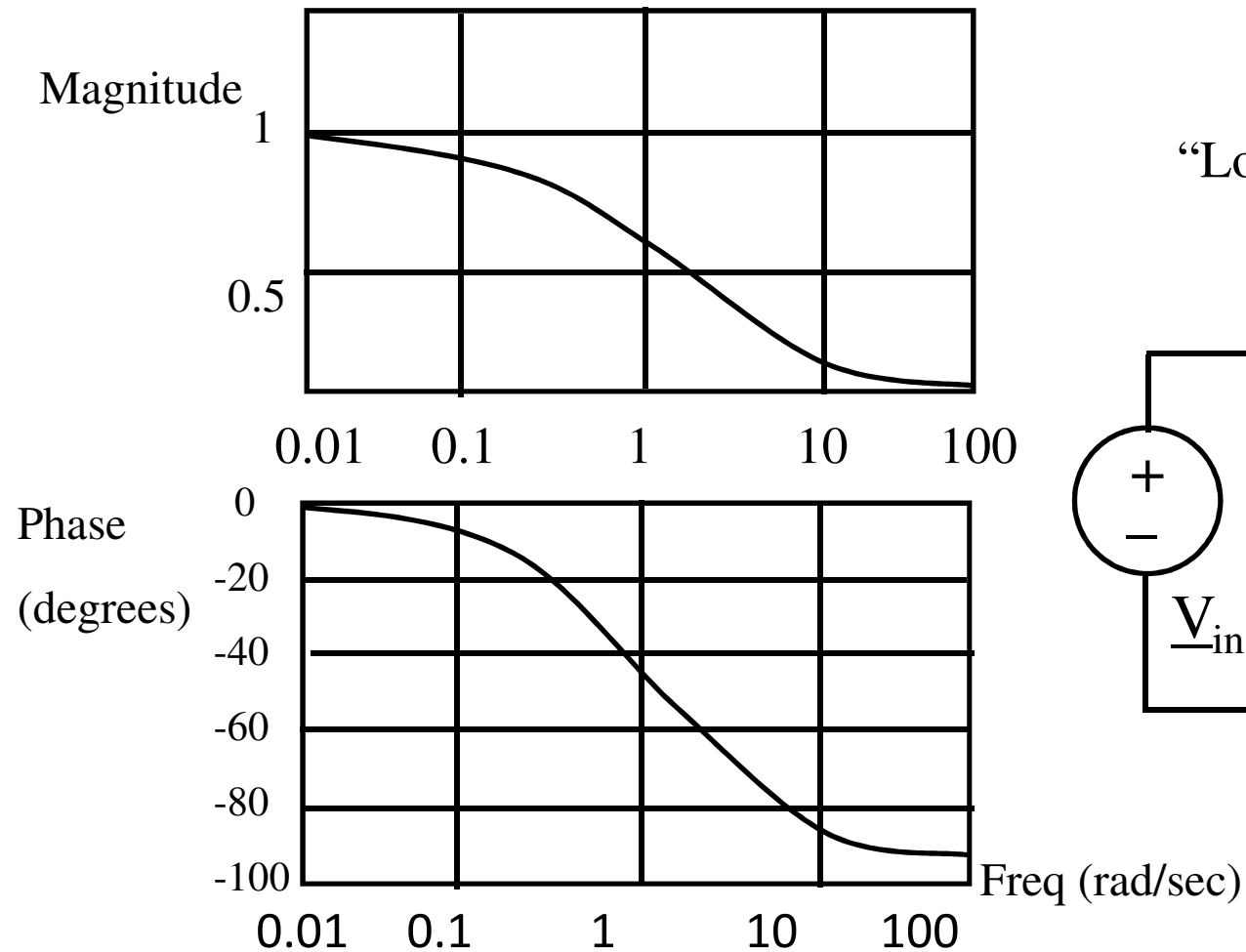

“Low Pass” Filter

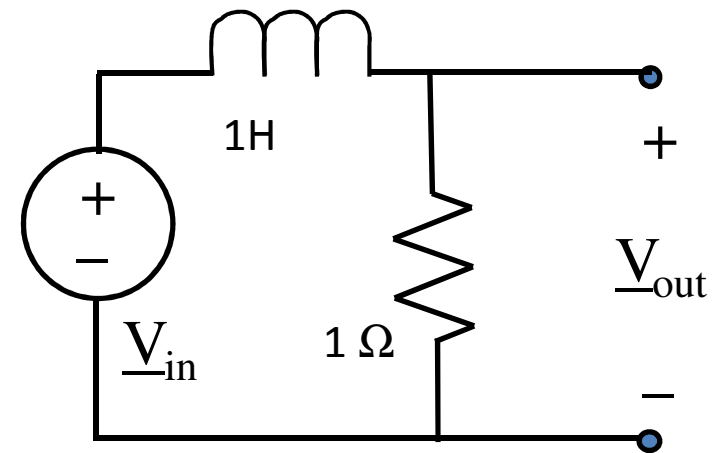

# Limiting Frequency Responses

Important frequencies for RL circuits:

$$\omega = 0 \quad \text{and} \quad \omega = \infty$$

$$H(j0) = 1 \angle 0^\circ$$

$$H(j\infty) = 0 \angle -90^\circ$$

For magnitude:

$$|H(j\omega)| \longrightarrow 1 \quad \text{as} \quad \omega \longrightarrow 0$$

$$|H(j\omega)| \longrightarrow 0 \quad \text{as} \quad \omega \longrightarrow \infty$$


For phase:

$$\angle H(j\omega) \longrightarrow 0^\circ \quad \text{as} \quad \omega \longrightarrow 0$$


$$\angle H(j\omega) \longrightarrow -90^\circ \quad \text{as} \quad \omega \longrightarrow \infty$$
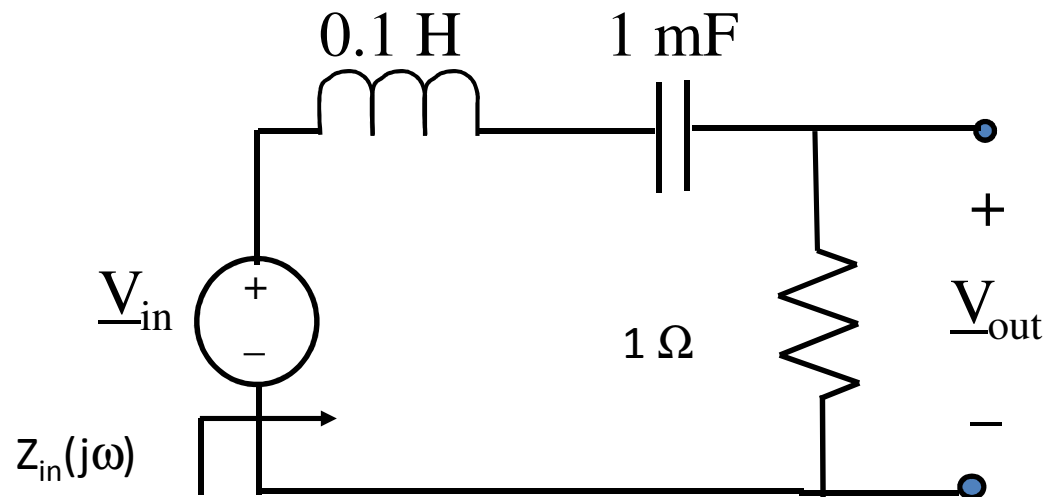
## Example #3

- Find the frequency response across the resistor of this series RLC circuit



# Solution

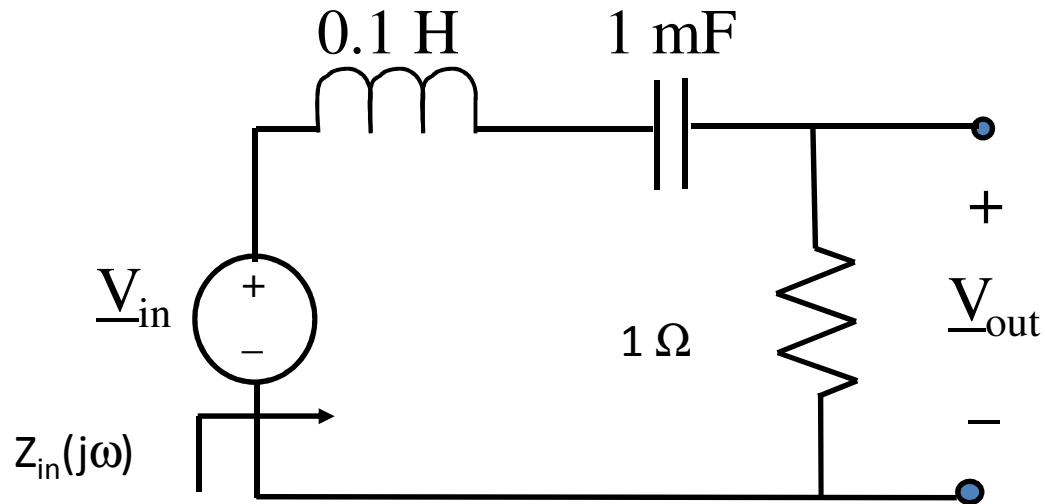

Find ratio of phasor output to input

$$Z_{in} = R + j\omega L + (1/j\omega C) = 1 + j0.1\omega + (1/j0.01\omega)$$

By voltage division

$$\frac{\underline{V}_{out}}{\underline{V}_{in}} = \frac{R}{R + j\omega L + (1/j\omega C)} = \frac{1}{1 + j0.01\omega + (1/j0.001\omega)}$$

# Limiting Frequency Responses

$$|H(j\omega)| \longrightarrow 0 \text{ as } \omega \longrightarrow \infty$$

$$|H(j\omega)| \longrightarrow 0 \text{ as } \omega \longrightarrow 0$$

$$\angle H(j\omega) \longrightarrow -90^\circ \text{ as } \omega \longrightarrow \infty$$

$$\angle H(j\omega) \longrightarrow 90^\circ \text{ as } \omega \longrightarrow 0$$

Look at other frequencies


$$|H(j\omega)| \longrightarrow 0.01 \text{ as } \omega \longrightarrow 10 \text{ rad/sec}$$

$$|H(j\omega)| \longrightarrow 1 \text{ as } \omega \longrightarrow 100 \text{ rad/sec}$$


$$|H(j\omega)| \longrightarrow 0.01 \text{ as } \omega \longrightarrow 1000 \text{ rad/sec}$$



# Frequency Response

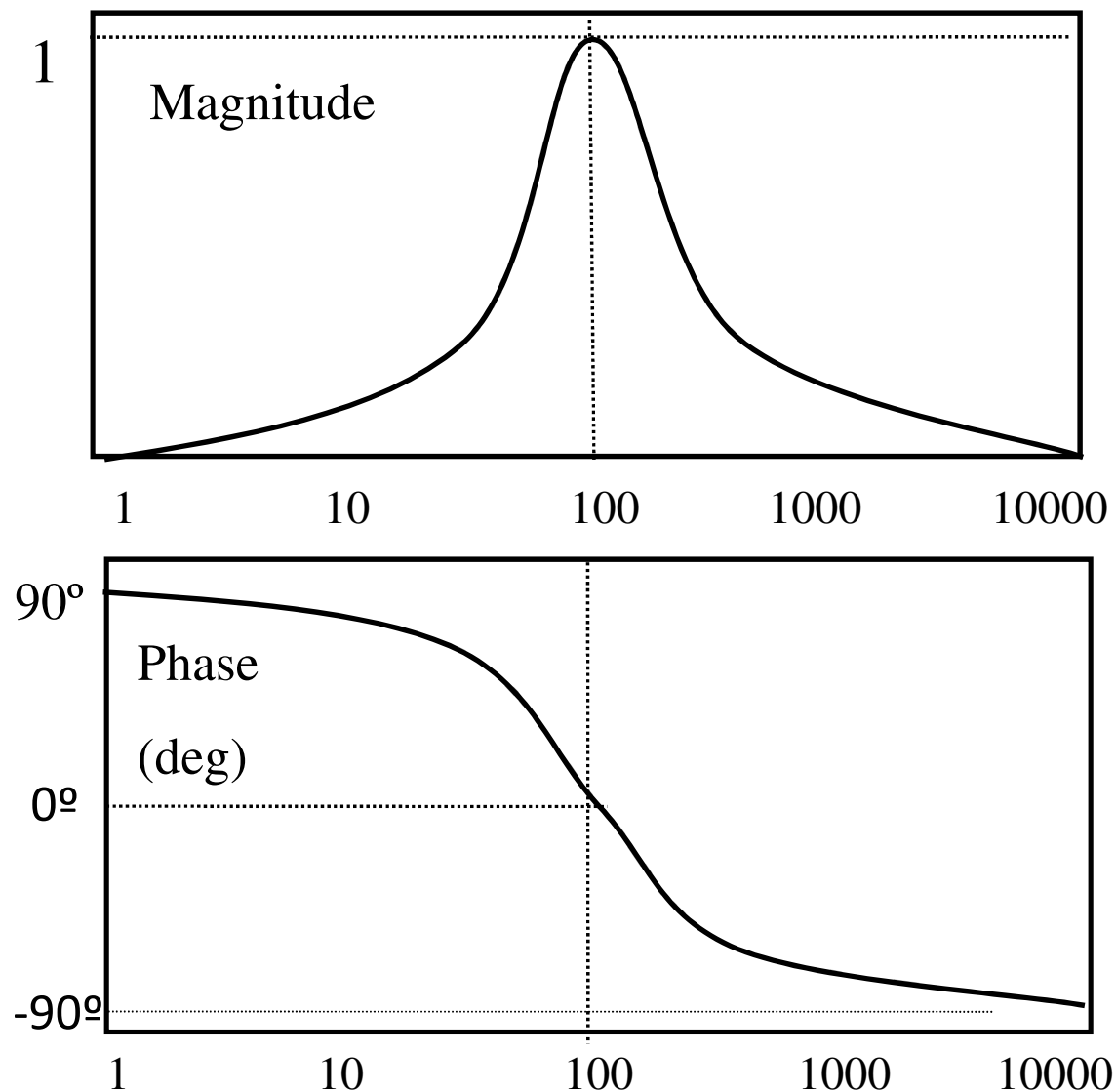

“Band Pass” Response

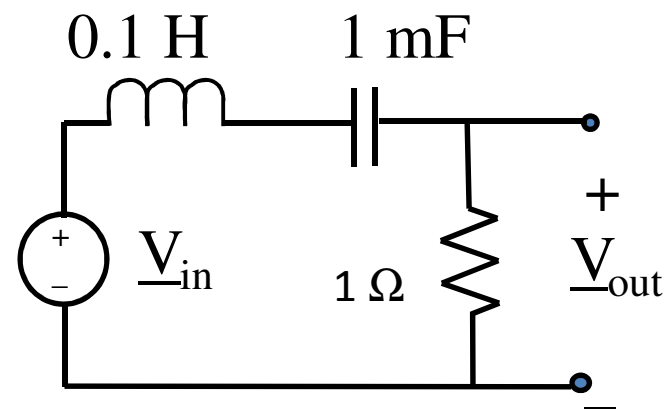

# Homework

- HW #32 due today by 4 pm in EE 325B
- HW #33 due Wed.: DeCarlo & Lin, Chapter 10:
  - Problem 52
  - Problem 55