

ECE 201, Section 3

Lecture 34

Prof. Peter Bermel

November 14, 2012


Exam #3

- Thurs., Nov. 15 at 6:30 pm in LILY 1105
- No class or HW next week (Nov. 19-23)!
- Covers Lectures 22-32, with 3 major topics:
 - Second-order circuits (primarily RLC)
 - Op-amps
 - Sinusoidal steady state
- Posted 7 sample exams with answers for Spring 2009, 2010, and 2011, and full solutions for '09 and '11


General Solutions: RC & RL Circuits

$$X(t) = X_{\infty} + [X(t_o^+) - X_{\infty}]e^{-(t-t_o)/\tau}$$

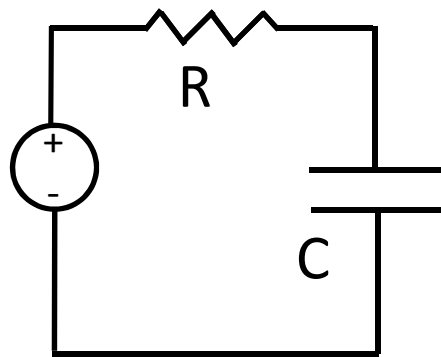- Where $X(t)$ is current or voltage at time t
- Voltages are continuous across capacitors; currents are continuous through inductors
- Capacitor currents and inductor voltages can jump discontinuously



RC Circuit

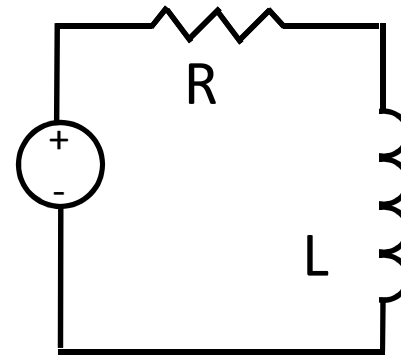


RL Circuit

Driven Series RLC Circuits

From KVL:

$$\frac{d^2 Q}{dt^2} + \frac{R}{L} \frac{dQ}{dt} + \frac{1}{LC} Q = \frac{V_s}{L}$$
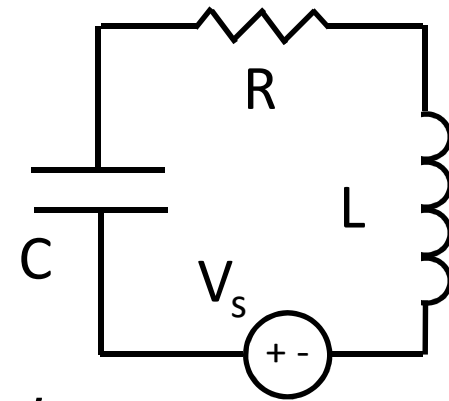
$$\frac{d^2 V_C}{dt^2} + 2\Gamma \frac{dV_C}{dt} + \omega_o^2 V_C = \omega_o^2 V_s$$



$$\Gamma = R/2L; \omega_o = 1/\sqrt{LC}; \omega' = \sqrt{\omega_o^2 - \Gamma^2} = -i\Gamma'$$


Regime	Range	Solution	Behavior
Under-damped	$\Gamma < \omega_o$	$V_C(t) = V_o e^{-\Gamma t} \cos(\omega' t + \phi) + V_s$	Oscillate & decay
Critically damped	$\Gamma = \omega_o$	$V_C(t) = e^{-\Gamma t} (A_1 + A_2 t) + V_s$	Decay
Over-damped	$\Gamma > \omega_o$	$V_C(t) = e^{-\Gamma t} (A_+ e^{\Gamma' t} + A_- e^{-\Gamma' t}) + V_s$	Decay

Driven Parallel RLC Circuits

From KCL:

$$\frac{d^2 I_L}{dt^2} + \frac{1}{RC} \frac{dI_L}{dt} + \frac{1}{LC} I_L = \frac{I_s}{LC}$$
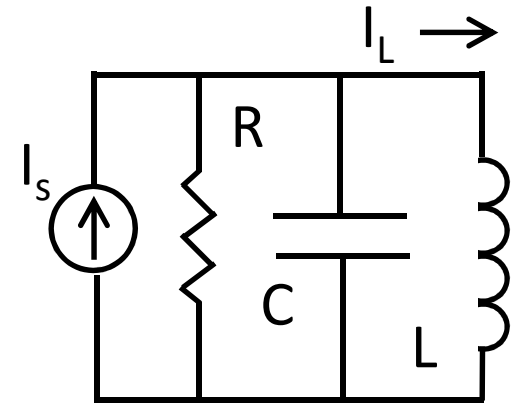
$$\frac{d^2 I_L}{dt^2} + 2\Gamma \frac{dI_L}{dt} + \omega_o^2 I_L = \omega_o^2 I_s$$



$$\Gamma = 1/(2RC); \omega_o = 1/\sqrt{LC}; \omega' = \sqrt{\omega_o^2 - \Gamma^2} = -i\Gamma'$$

Regime	Range	Solution	Behavior
Under-damped	$\Gamma < \omega_o$	$I_L(t) = I_o e^{-\Gamma t} \cos(\omega' t + \phi) + I_s$	Oscillate & decay
Critically damped	$\Gamma = \omega_o$	$I_L(t) = e^{-\Gamma t} (A_1 + A_2 t) + I_s$	Decay
Over-damped	$\Gamma > \omega_o$	$I_L(t) = e^{-\Gamma t} (A_+ e^{\Gamma' t} + A_- e^{-\Gamma' t}) + I_s$	Decay

Phasor Review




- Shorthand for writing complex numbers:

$$\mathbf{V} = V_m \angle \phi = V_m e^{j(\omega t + \phi)}$$

- Ohm's law with phasors:

$$\mathbf{V} = \mathbf{Z}(j\omega)\mathbf{I}$$

$$\mathbf{I} = \mathbf{Y}(j\omega)\mathbf{V}$$

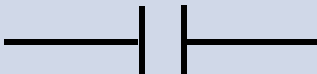Circuit Element	Impedance	Admittance
	$Z(j\omega) = R$	$Y(j\omega) = \frac{1}{R}$
	$Z(j\omega) = j\omega L$	$Y(j\omega) = \frac{1}{j\omega L}$
	$Z(j\omega) = \frac{1}{j\omega C}$	$Y(j\omega) = j\omega C$

Impedance Properties


- For circuit elements in series, voltage division rule becomes:

$$V_k = \frac{Z_k}{Z_{eq}} V_{tot}$$

- For circuit elements in parallel, current division rule becomes:


$$I_k = \frac{Y_k}{Y_{eq}} I_{tot}$$

Second Order Circuit Overview

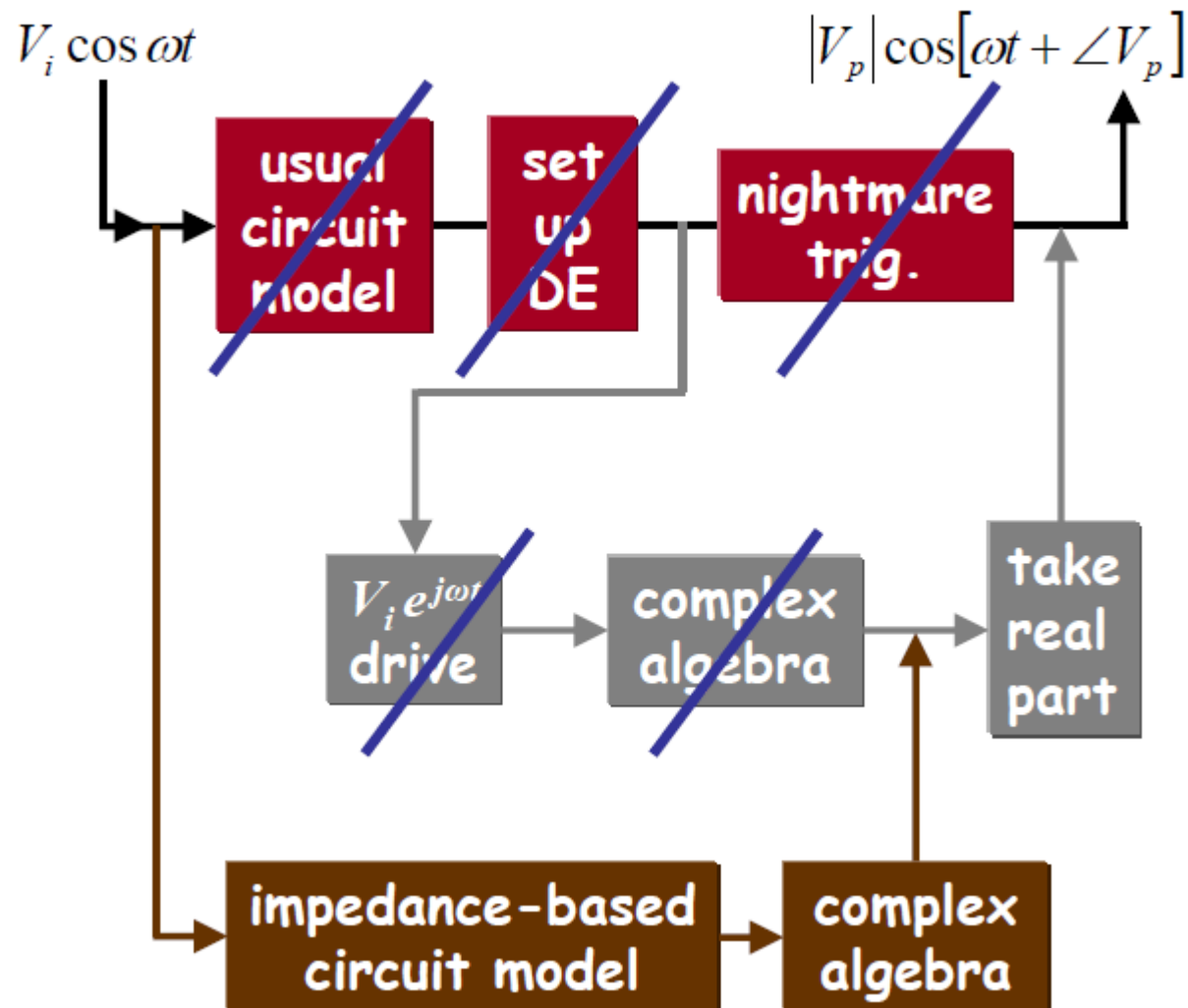


Ideal Op-Amps

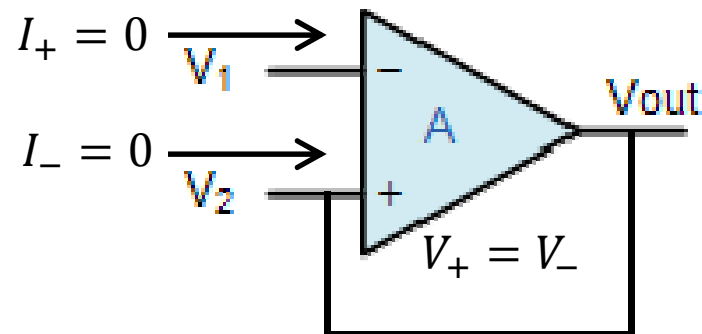- Golden rules:
 - Both input currents are zero
 - For closed loops: both input voltages are equal



Exam 3 Spring 2010

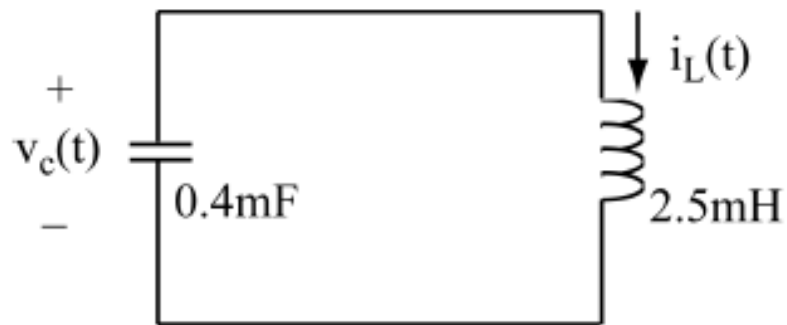
1. At $t = 0$ sec, the inductor current is $i_L(0^+) = 5\text{A}$ and the capacitor voltage is $v_c(0^+) = 0\text{V}$. Find $v_c(t)$ for $t \geq 0$ s (in V).



- | | |
|--|--|
| (1) $v_c(t) = 25 \cos(10^6 t) + 25 \sin(10^6 t)$ | (2) $v_c(t) = 25 \cos(10^6 t)$ |
| (3) $v_c(t) = 25 \sin(10^6 t)$ | (4) $v_c(t) = 12.5 \cos(10^3 t) + 12.5 \sin(10^3 t)$ |
| (5) $v_c(t) = 12.5 \cos(10^3 t)$ | (6) $v_c(t) = -12.5 \sin(10^3 t)$ |
| (7) $v_c(t) = 0$ | |

Exam 3 Spring 2010

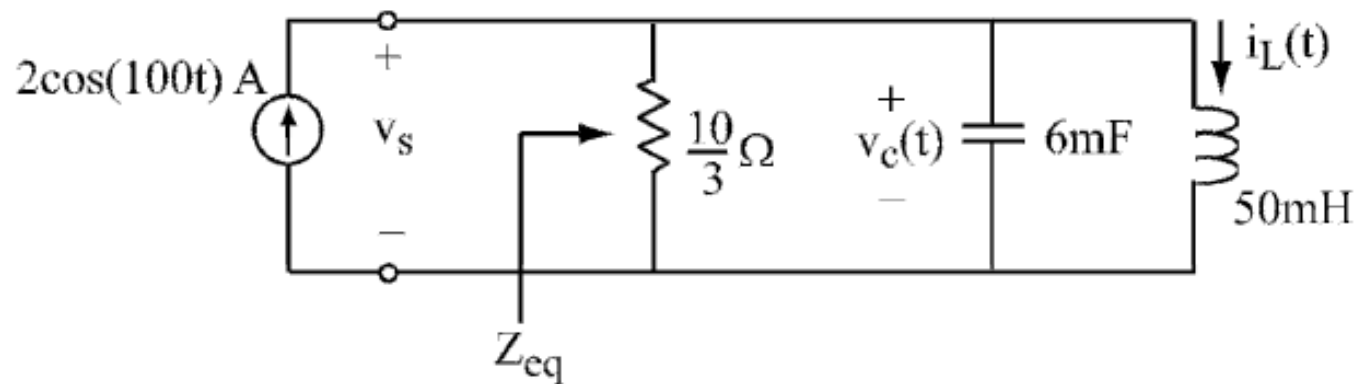11. Calculate the equivalent impedance, Z_{eq} (in Ω), for the circuit below.



(1) $2 \angle 53.13^\circ$

(2) $2 \angle -53.13^\circ$

(3) $2 \angle 36.7^\circ$

(4) $2 \angle -36.7^\circ$


(5) $1 \angle 40^\circ$

(6) $1 \angle -40^\circ$

(7) $1 \angle 45^\circ$

Exam 3 Spring 2010

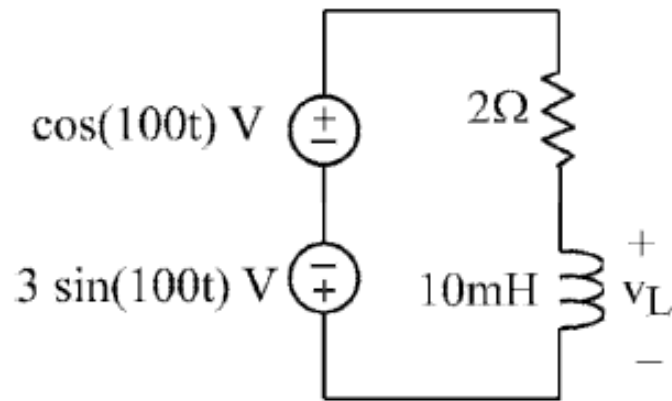13. The circuit shown below is in steady state. Find $v_L(t)$.



(1) $v_L(t) = \sqrt{2} \cos(100t + 90^\circ)$

(3) $v_L(t) = \sqrt{2} \cos(100t + 135^\circ)$

(5) $v_L(t) = \sqrt{2} \cos(100t + 170^\circ)$

(7) $v_L(t) = \sqrt{2} \cos(200t + 170^\circ)$

(2) $v_L(t) = 2 \cos(100t + 90^\circ)$

(4) $v_L(t) = 2 \cos(100t + 135^\circ)$

(6) $v_L(t) = 2 \cos(100t + 170^\circ)$

Equation Sheet for Exam

$$I = dQ/dt$$

$$V = IR \text{ or } V = IZ; I = GV \text{ or } I = YV$$

$$Q = CV \text{ and } V = L \, di/dt$$

In series:

$$Z_{eq} = \sum_k Z_k$$

$$V_k = V Z_k / Z_{eq}$$

In parallel:

$$Y_{eq} = \sum_k Y_k$$

$$I_k = V Y_k = I Y_k / Y_{eq}$$

$$P = IV$$

For first-order circuits:

$$X = X_{\infty} + (X_o - X_{\infty}) e^{-(t-t_o)/\tau}$$

For RL circuits: $\tau = L/R$

For RC circuits: $\tau = RC$

For second-order (RLC) circuits:

$$X(t) = A e^{-\Gamma t} \cos(\omega' t + \phi) + X_s$$

$$X(t) = (A_1 + A_2 t) e^{-\Gamma t} + X_s$$

$$X(t) = e^{-\Gamma t} (A_+ e^{\Gamma' t} + A_- e^{-\Gamma' t}) + X_s$$

where: $\Gamma = R/2L$ (series) or $\Gamma = 1/(2RC)$ (parallel);

$$\omega_o = 1/\sqrt{LC}; \omega' = \sqrt{\omega_o^2 - \Gamma^2}; \text{ and } \Gamma' = \sqrt{\Gamma^2 - \omega_o^2}$$

Homework

- HW #33 due today by 4:30 pm in EE 325B
- HW #34 due Fri. – DeCarlo & Lin, Chapter 10:
 - Problem 58
 - Problem 62