

ECE 201, Section 3

Lecture 35

Prof. Peter Bermel

November 16, 2012

Real-World Significance of Power

- Energy used in homes, vehicles
- Battery life in mobile devices
- Safety in electrical wiring

Instantaneous and Average Power

- Instantaneous power given by:

$$P(t) = I(t) V(t)$$

- Average power over time interval $[t_1, t_2]$ given by:

$$P_{ave} = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} dt P(t)$$

Average Power for SSS

- Generally, currents and voltages driven at the same frequency ω – assume:

$$I(t) = I_o \cos \omega t$$


$$V(t) = V_o \cos(\omega t + \phi)$$

- Instantaneous power then given by:

$$P(t) = I_o V_o \cos \omega t \cos(\omega t + \phi)$$

$$P(t) = \frac{I_o V_o}{2} [\cos \phi + \cos(2\omega t + \phi)]$$

Average Power for SSS

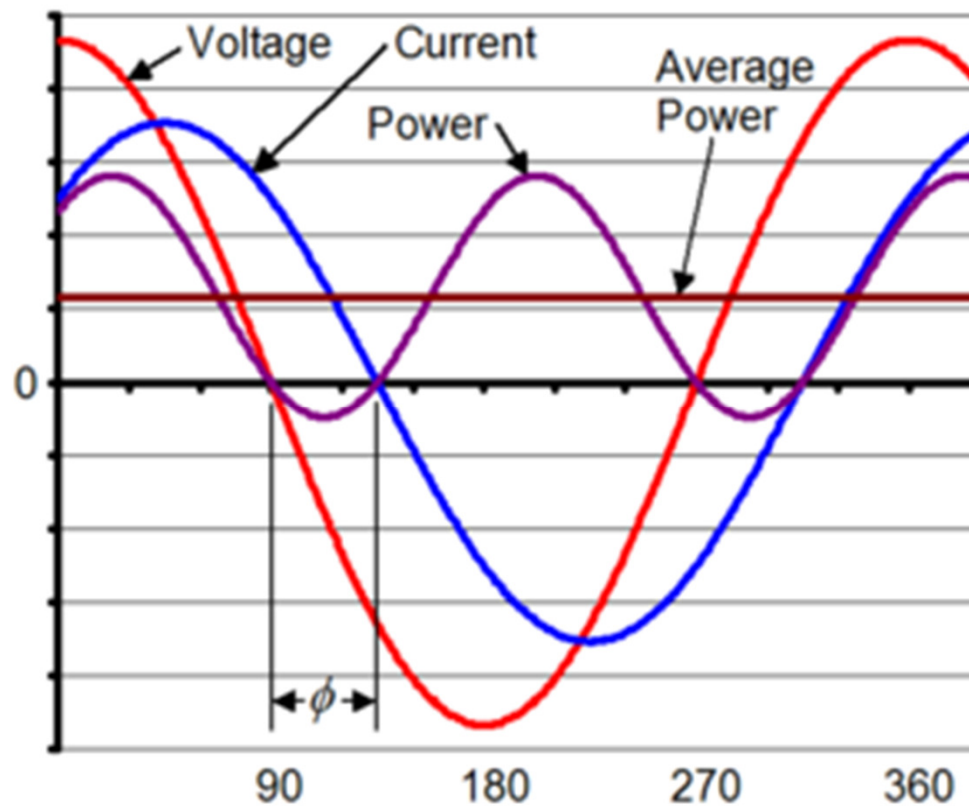

Over half-integer periods, only the first term contributes, so that:


$$P_{ave} = \frac{1}{2} I_o V_o \cos \phi$$

Demonstration


- [RLC circuit with storage](#)

Superposition of Average Power

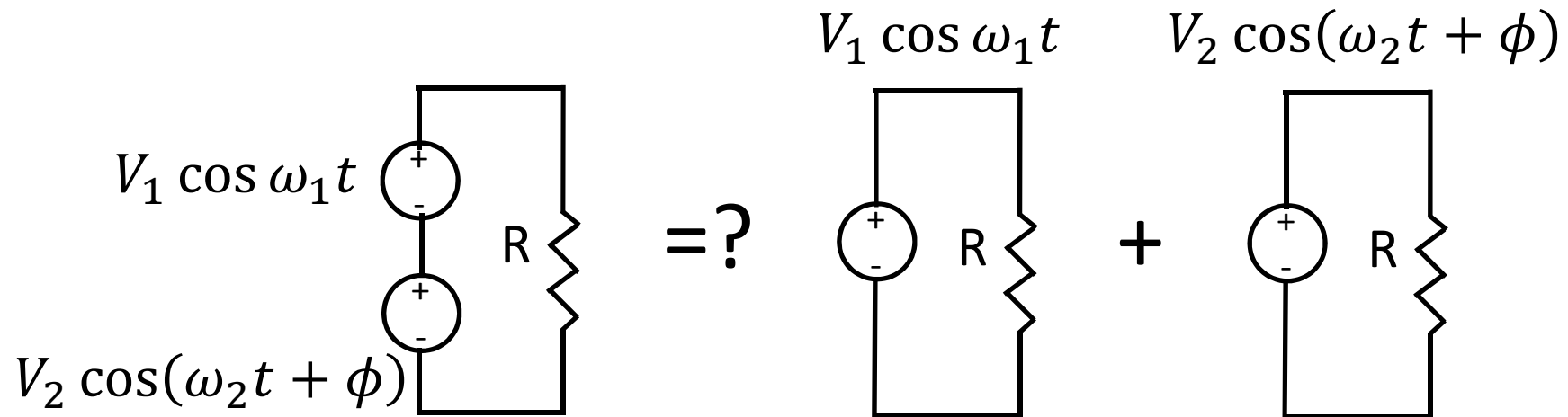- Example: how does the average power of 2 AC sources connected to a resistor compare to the average power of each one alone?



Superposition of Average Power

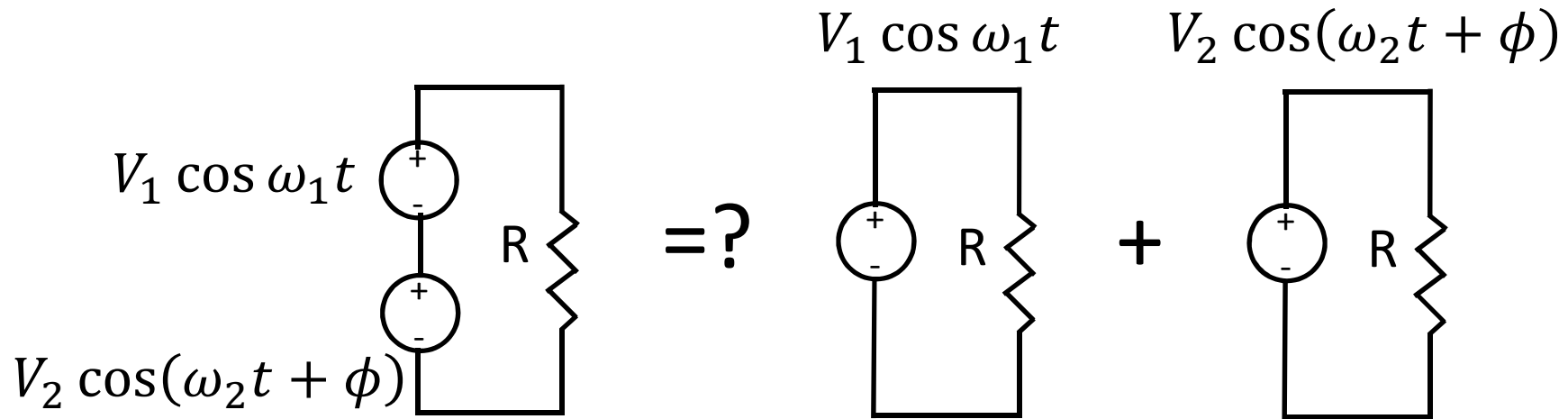

- By linearity:

$$P(t) = \frac{1}{R} [V_1 \cos \omega_1 t + V_2 \cos(\omega_2 t + \phi)]^2$$

$$P(t) = P_1 + P_2 + \frac{2V_1 V_2}{R} \cos \omega_1 t \cdot \cos(\omega_2 t + \phi)$$

Superposition of Average Power

- 3 important cases:
 - $\omega_1 \neq \omega_2$, integer periods: superposition holds
 - $\omega_1 = \omega_2$, $\cos \phi = 0$, integer periods: superposition holds
 - Otherwise: superposition fails

Effective Values

- We can generally define effective values for periodic signals, $f(t + T) = f(t)$, such that:

$$F_{eff} = \sqrt{\frac{1}{T} \int_{t_o}^{t_o+T} dt [f(t)]^2}$$

- Also known as root-mean-square (rms) value

Effective Values

- For an AC signal given by:

$$f(t) = f_o \cos(\omega_o t + \phi)$$

- Plugging into our formula yields:

$$F_{eff} = \sqrt{\frac{1}{T} \int_{t_o}^{t_o+T} dt [f_o \cos(\omega_o t + \phi)]^2}$$
$$F_{eff}^2 = \frac{f_o^2}{T} \int_{t_o}^{t_o+T} dt \frac{1}{2} [1 + \cos(\omega_o t + \phi)]$$
$$F_{eff}^2 = \frac{f_o^2}{T} \frac{T}{2} = \frac{f_o^2}{2}$$
$$F_{eff} = \frac{f_o}{\sqrt{2}}$$

Power from Effective Values

- Revisiting our calculation from last time:

$$P_{ave} = \frac{1}{2} I_o V_o \cos \phi$$

- Rewriting in our new notation:


$$P_{ave} = I_{eff} V_{eff} \cos \phi$$

- In electrical engineering, drop the effective subscripts and write:

$$P_{ave} = IV \cos \phi$$


Effective Values Example

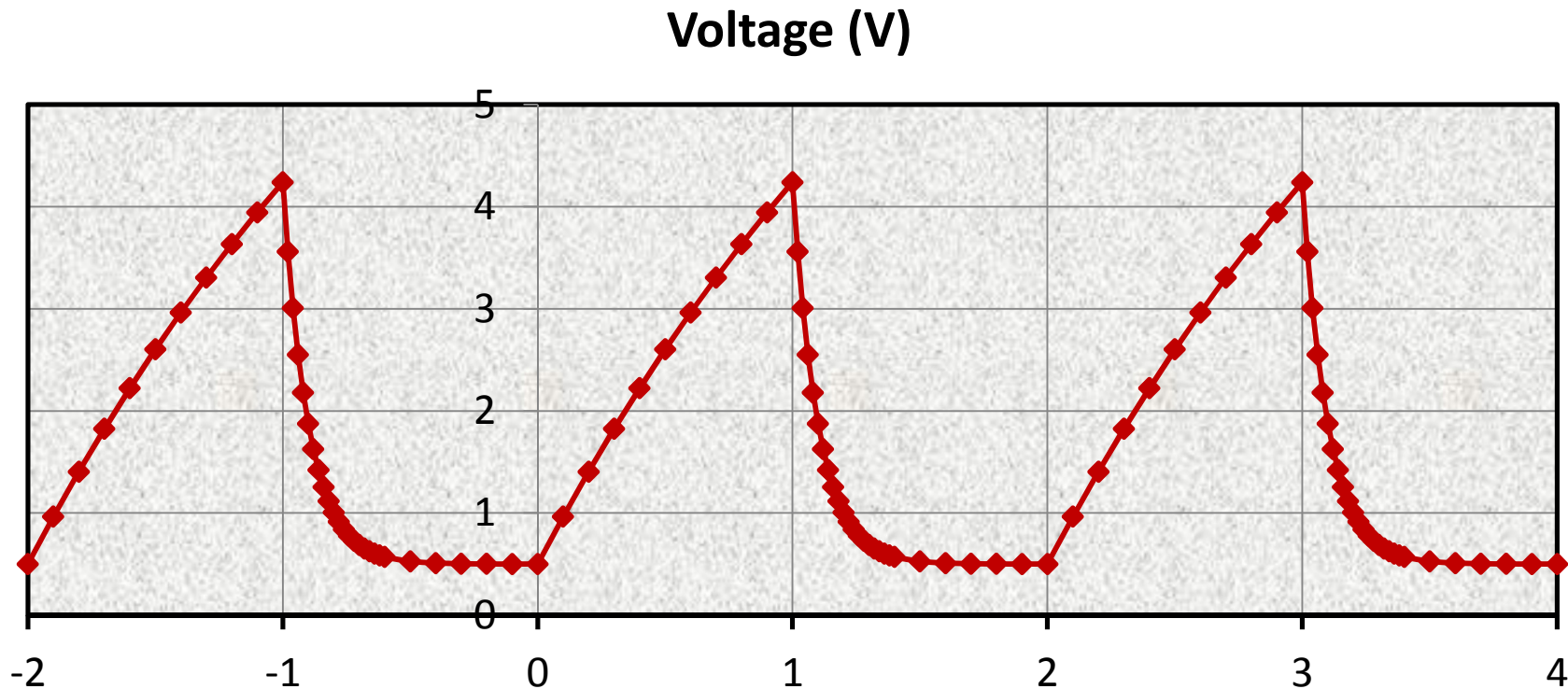- What is the effective voltage of this waveform?
How much power is dissipated by a $2\ \Omega$ resistor?



Effective Values Example

Voltage (V)

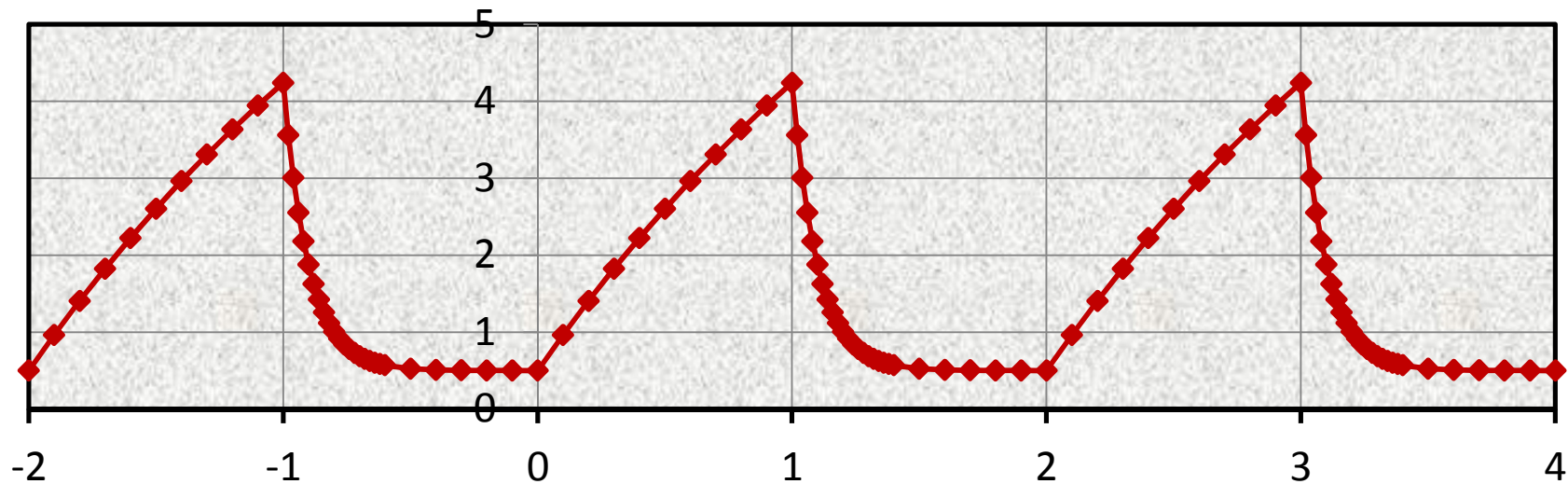

$$V_{eff}^2 = \frac{1}{2} \int_0^2 dt [0.5^2 + (3.8t + 0.5)^2 u(1-t) + [0.5 + 3.8(6-5t)]^2 u(t-1)u(6-5t)]$$

$$V_{eff}^2 \approx \frac{1}{2} \left[0.25 \cdot 0.8 + \frac{4.3^3 - 0.5^3}{3 \cdot 3.8} + \frac{4.3^3 - 0.5^3}{3 \cdot 19} \right] = 4.28 \text{ V}^2$$

$$P_{ave} = \frac{V_{eff}^2}{R} = \frac{4.28}{2} = 2.14 \text{ W}$$

Complex Power

- Complex power is defined as:

$$\mathbf{S} = \mathbf{I}^* \mathbf{V}$$

- For AC signals:


$$\mathbf{S} = I_o e^{-j\omega t} V_o e^{j(\omega t + \phi)}$$

$$\mathbf{S} = I_o V_o e^{j\phi} = I_o V_o (\cos \phi + j \sin \phi)$$


- Key definitions:
 - Re \mathbf{S} – average power (dissipated)
 - Im \mathbf{S} – reactive power (stored)
 - $|\mathbf{S}|$ – apparent power

Complex Power Example

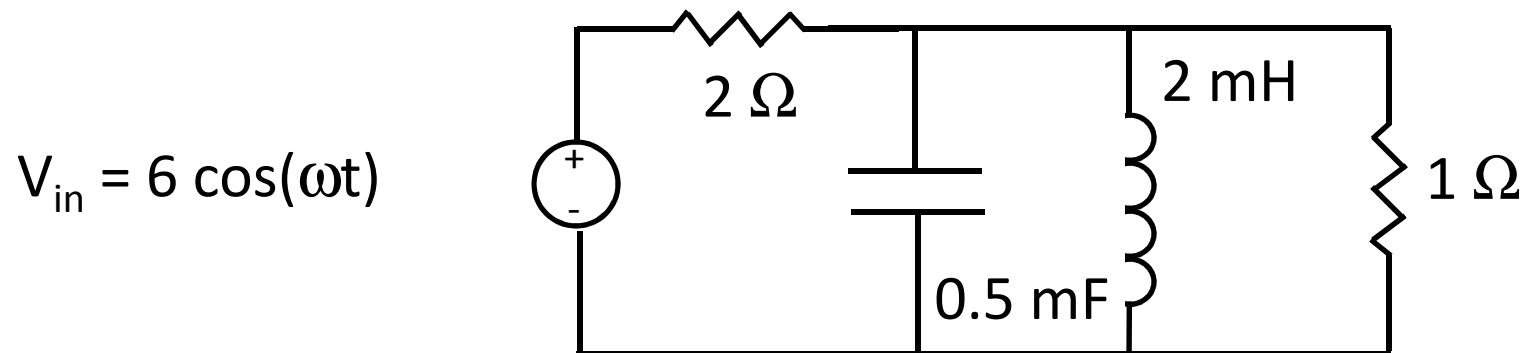- What is the current and complex power dissipated by this circuit?



Complex Power: Solution

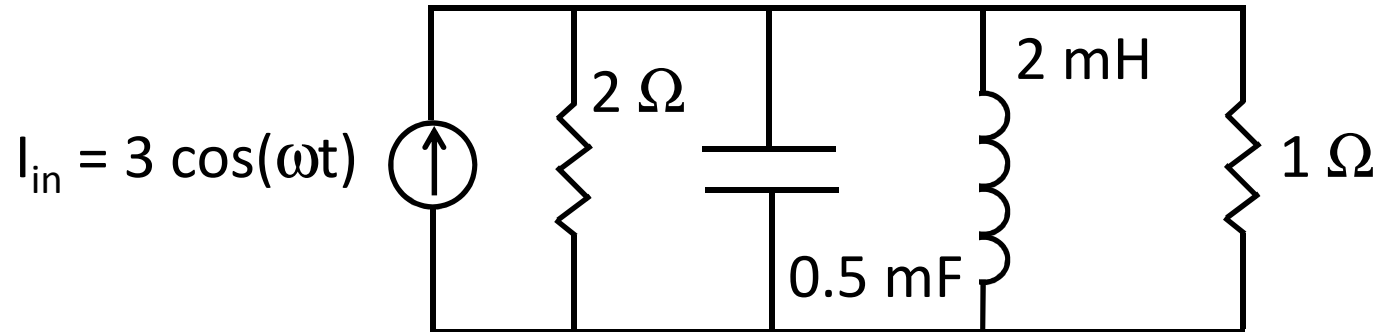

- The impedance is given by:

$$Z = \left[\frac{3}{2} + j\omega \cdot 5 \cdot 10^{-4} + \frac{1}{j\omega \cdot 2 \cdot 10^{-3}} \right]^{-1}$$

- The voltage drop is thus given by:

$$V = IZ = \frac{3e^{j\omega t}}{\frac{3}{2} + j \cdot (\omega/2000 - 500/\omega)}$$

$$V = \frac{2e^{j[\omega t - \tan^{-1}(\frac{\omega}{3000} - \frac{1000}{3\omega})]}}{\left[1 + \left(\frac{\omega}{3000} - \frac{1000}{3\omega} \right)^2 \right]^{1/2}}$$

Complex Power: Solution

- Applying the current division rule:


$$I_L = \frac{Y_L}{Y} I_{tot}$$

$$I_L = \frac{(500/j\omega)3e^{j\omega t}}{\frac{3}{2} + j \cdot (\omega/2000 - 500/\omega)} = \frac{1000e^{j\omega t}}{j\omega + \frac{1000}{3} - \frac{\omega^2}{3000}}$$

$$I_L = \frac{1000e^{j[\omega t - \tan^{-1}(\omega/(333 - \omega^2/3000))]}}{\left[\omega^2 + \left(\frac{1000}{3} - \frac{\omega^2}{3000} \right)^2 \right]^{1/2}}$$

Solution

Inductor Current Amplitude (A)

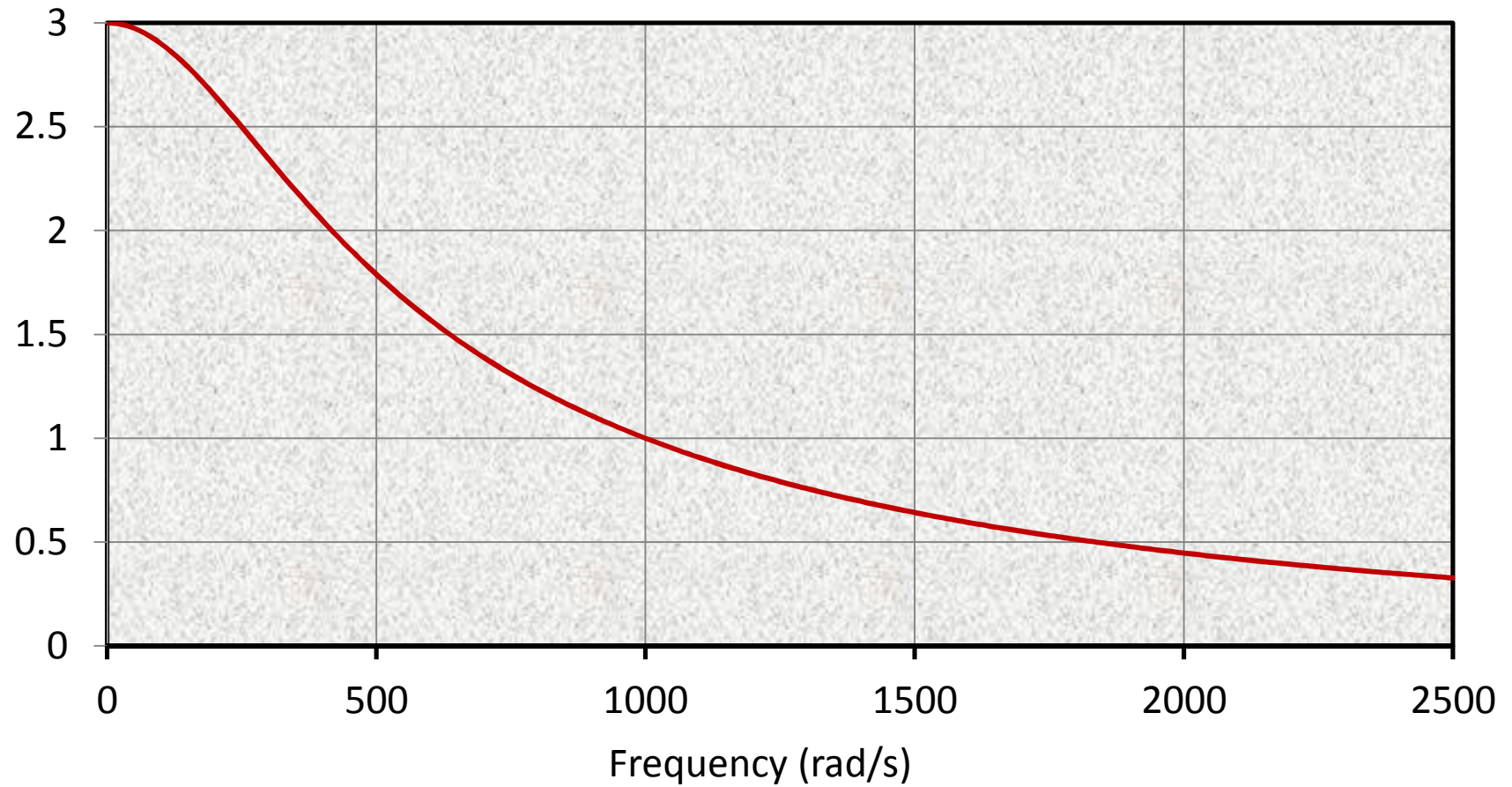

Complex Power: Solution

- From our earlier definitions:


$$\mathbf{S} = \mathbf{I}^* \mathbf{V}$$

- Substitution yields:

$$\mathbf{S} = \frac{1000e^{-j[\omega t - \tan^{-1}(\omega/(333 - \omega^2/3000))]} }{\left[\omega^2 + \left(\frac{1000}{3} - \frac{\omega^2}{3000} \right)^2 \right]^{1/2}} \cdot 6e^{j\omega t}$$
$$\mathbf{S} = 6000 \cdot \frac{333 - \frac{\omega^2}{3000} + j\omega}{\left[\omega^2 + \left(\frac{1000}{3} - \frac{\omega^2}{3000} \right)^2 \right]^{3/2}}$$

Solution

Average Power (mW)

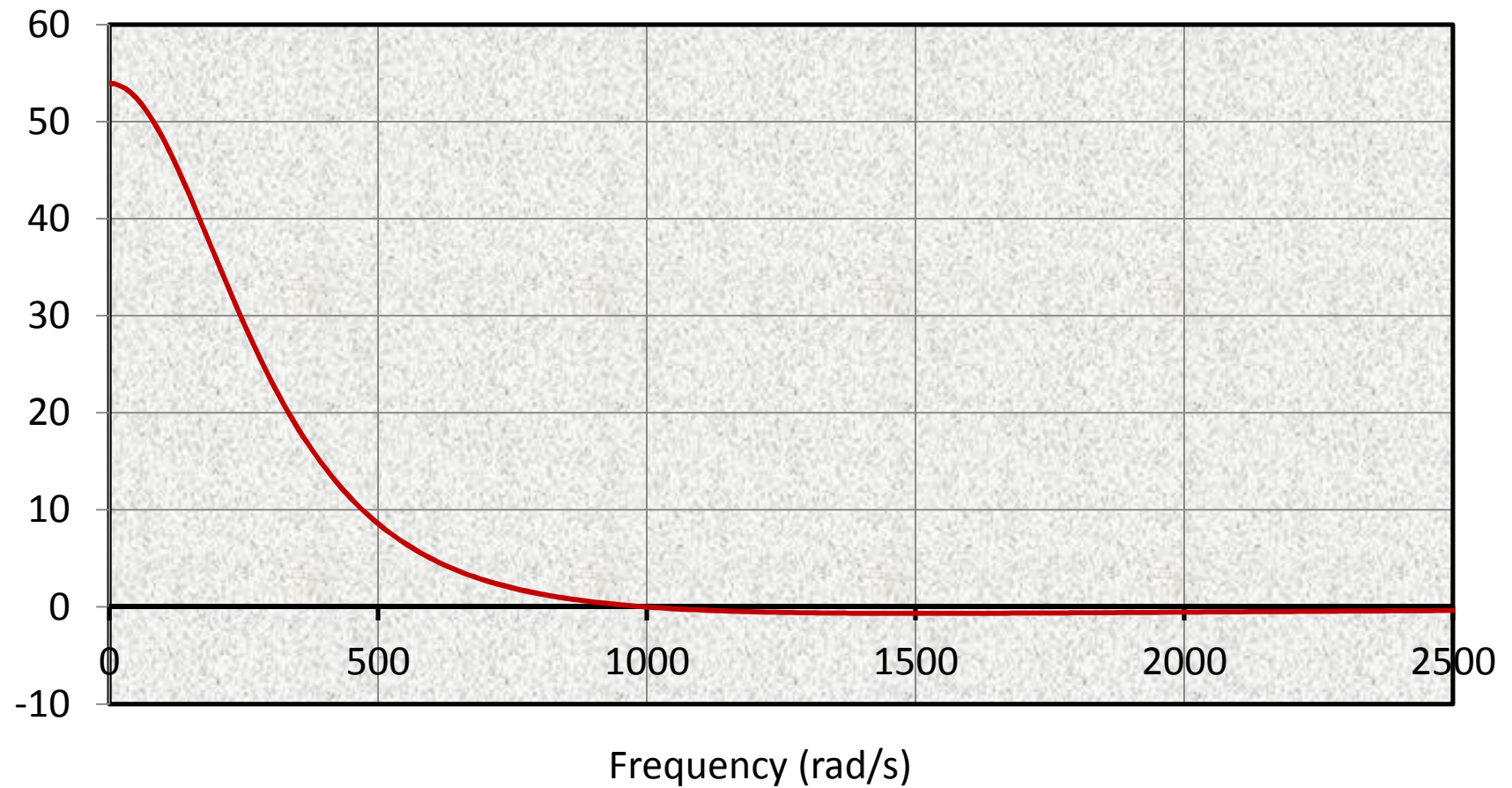

Homework

- HW #34 due today by 4:30 pm in EE 325B
- HW #35 due Mon. Nov. 26: DeCarlo & Lin, Chapter 10:
 - Problem 64 [Correction: Delete “and determine the frequency ... of its maximum value.” Also, either a plot from MATLAB or a sketch from an analytical formula is fine.]
 - Problem 66