

ECE 201, Section 3

Lecture 36


Prof. Peter Bermel

November 26, 2012

Exam #3

- Out of 158 exams taken: $\mu=53\%$, $\sigma=17\%$
- Much more challenging than last time

of students

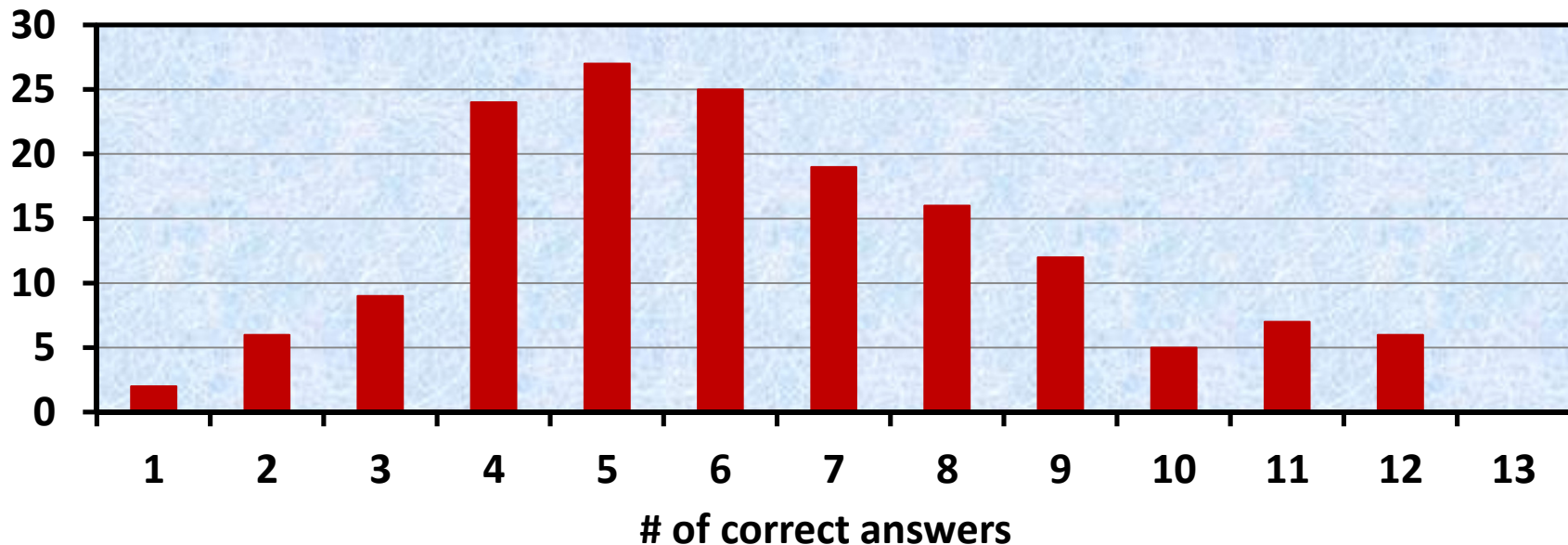

Exam Z-Scores

- Z-scores calculated from your score s by:


$$Z = \frac{s - \mu}{\sigma}$$

- General scale:

Z-score range	Approximate Letter Grade
$Z > 1$	A/A-
$Z > 0$	B+/B/B-
$Z > -0.6$	C+/C/C-
$Z > -1$	D
$Z < -1$	F


Exam #3

of students

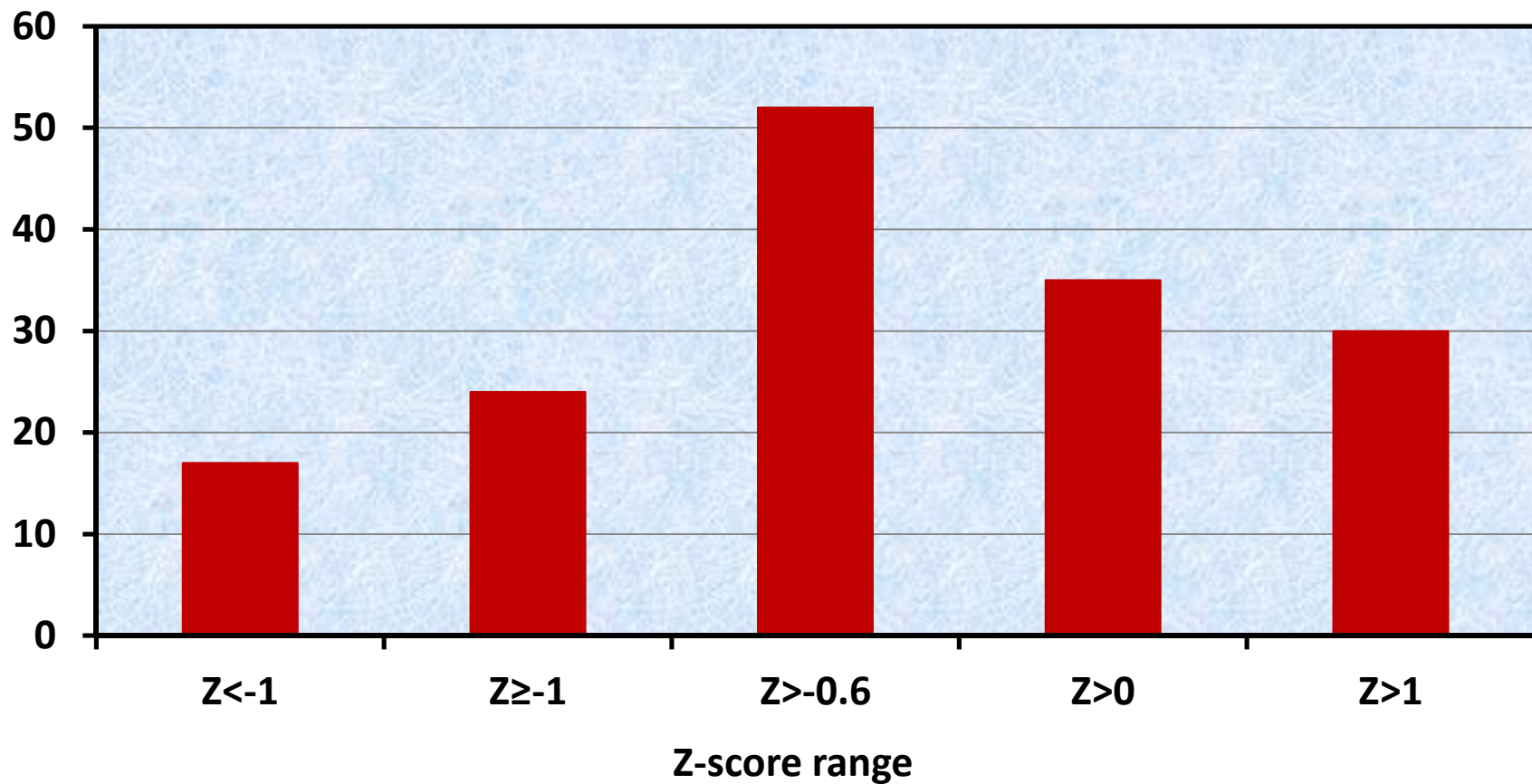

Exam #3

% correct for each question

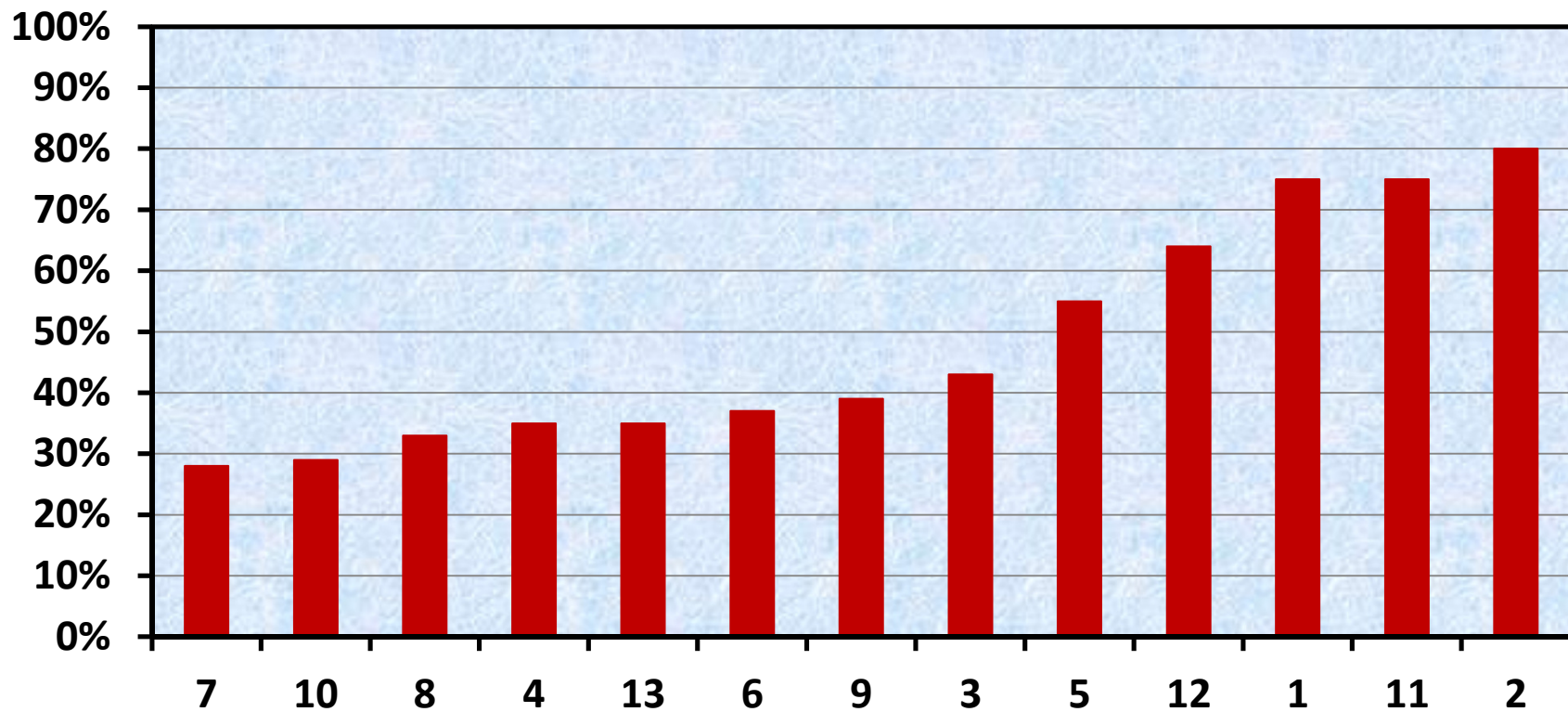


Solutions for Exam #3

- Posted original exam, answer key, and full solutions under “Fall 2012 Exams” folder
- Will review the following problems today: 3, 4, 6, 7, 8, 9, 10, 13

Exam #3

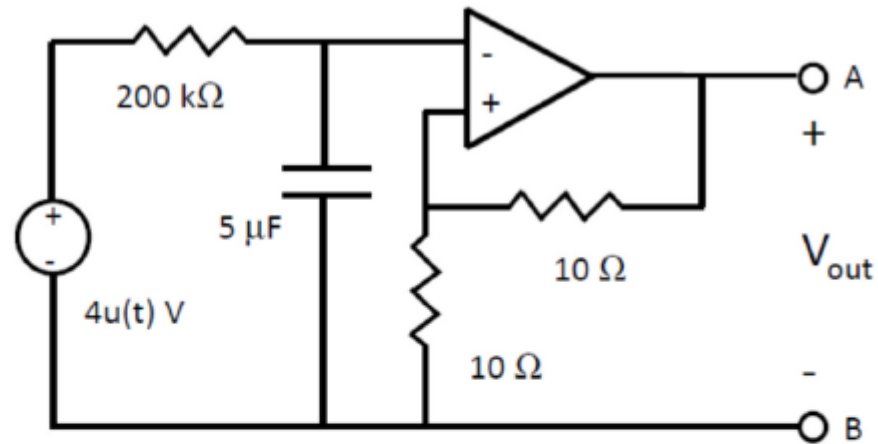3. For the circuit below, what is the output voltage $V_{out}(t)$ (in V), for $t \geq 0$?




Answers:

- (1) $2e^{-t}$
- (2) $2e^{-10t}$
- (3) $4e^{-10t}$
- (4) $4(1-e^{-t})$
- (5) $8e^{-t}$
- (6) $8(1-e^{-t})$
- (7) $16e^{-10t}$
- (8) None of the above

Exam #3

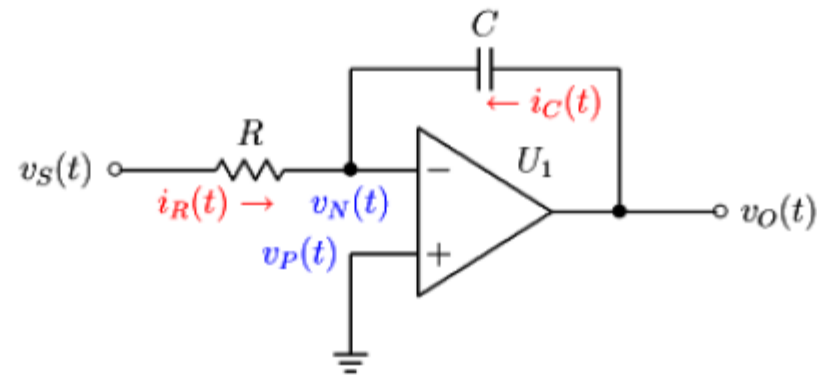4. Given that $R=2\ \Omega$, $C=50\ \text{mF}$, and input voltage $v_s(t)=20u(t)\sin(40t)\ \text{V}$ for the circuit below, what is the output voltage $v_o(t)$ (in V) for $t\geq 0$?




Answers:

- (1) $\sin(40t)$
- (2) $1-\cos(40t)$
- (3) $5\sin(40t)$
- (4) $5[\cos(40t)-1]$
- (5) $10\sin(40t)$
- (6) $10[1-\cos(40t)]$
- (7) $20\sin(40t)$
- (8) None of the above

Exam #3

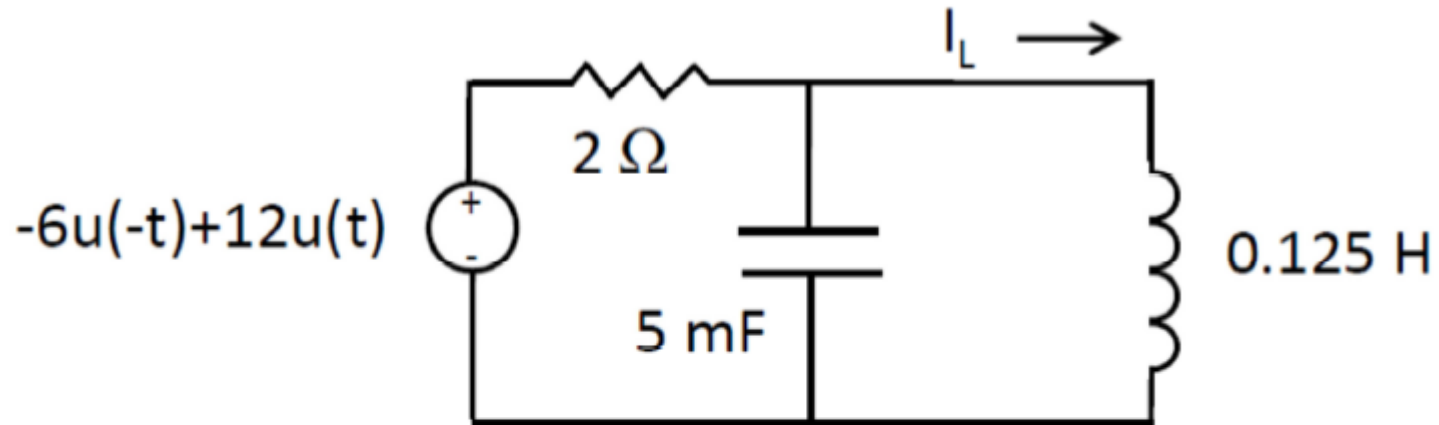6. For the circuit below, what is the inductor current $I_L(t)$ (in A) for $t \geq 0$?




Answers:

- (1) $-3e^{-40t} \cos(50t)$
- (2) $6e^{-40t} \cos(30t)$
- (3) $(-3+6t)e^{-50t}$
- (4) $-3 + 12e^{-20t} - 12e^{-80t}$
- (5) $3 - 6e^{-40t} \cos(50t)$
- (6) $6 + (18t-9)e^{-50t}$
- (7) $6 - 12e^{-20t} + 3e^{-80t}$
- (8) None of the above

Exam #3

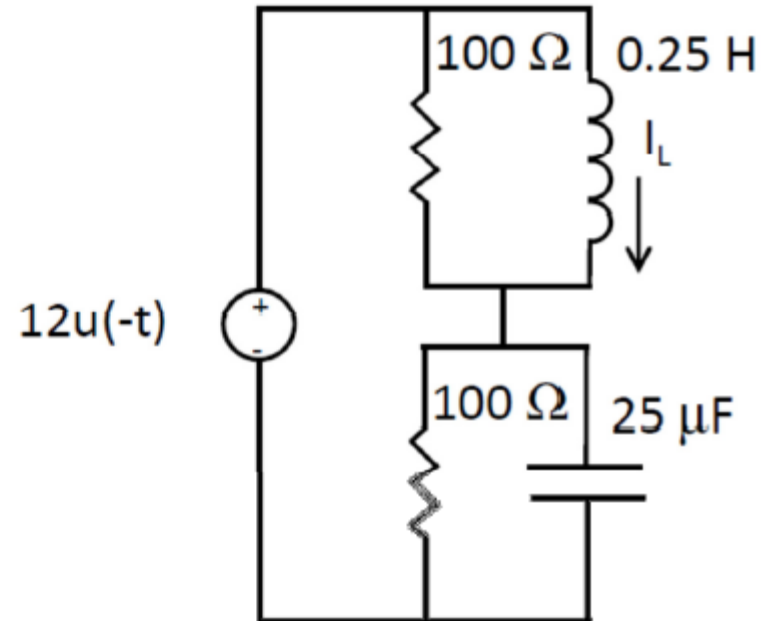7. For the circuit below, find the inductor current $I_L(t)$ (in A) for $t \geq 0$:




Answers:

- (1) $0.06e^{-400t}$
- (2) $0.12 \cos(400t)$
- (3) $(0.12+48t)e^{-400t}$
- (4) $0.12e^{-400t}$
- (5) $0.18e^{-400t}-0.06e^{-1200t}$
- (6) $0.24 \cos(400t)$
- (7) $0.24 e^{-400t}$
- (8) None of the above

Exam #3

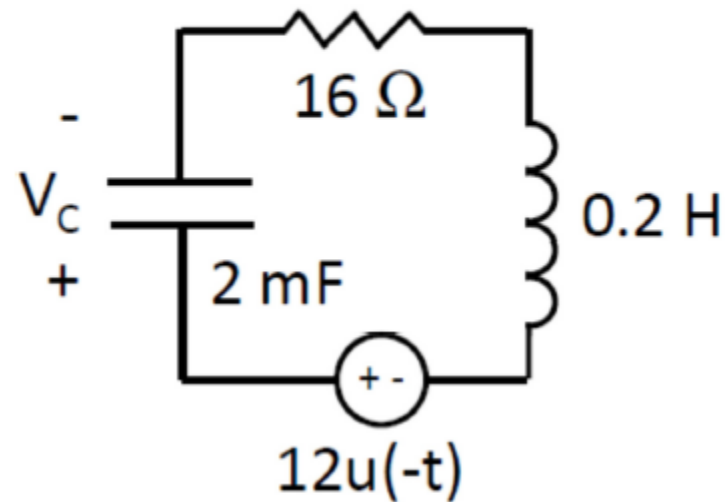8. For the circuit below, what is $V_c(t)$ (in V) for $t \geq 0$?




Answers:

- (1) $12 \cos(30t)$
- (2) $12 \cos(40t)$
- (3) $12e^{-40t} \cos(30t - 53.13^\circ)$
- (4) $20e^{-30t} \cos(40t + 36.87^\circ)$
- (5) $20e^{-40t} \cos(30t - 53.13^\circ)$
- (6) $20e^{-30t} \cos(50t + 36.87^\circ)$
- (7) $(12 + 24t) e^{-50t}$
- (8) None of the above

Exam #3

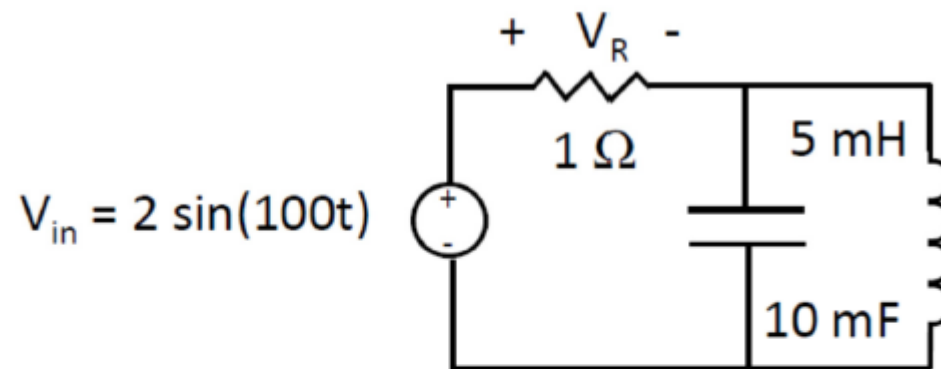9. For the circuit below, what is the resistor voltage $V_R(t)$ (in V) in the sinusoidal steady state?




Answers:

- (1) $0.5 \cos(100t+45^\circ)$
- (2) $0.5 \cos(100t-135^\circ)$
- (3) $2^{-1/2} \cos(100t-135^\circ)$
- (4) $\cos(100t-90^\circ)$
- (5) $\cos(100t)$
- (6) $2^{1/2} \cos(100t+45^\circ)$
- (7) $2^{1/2} \cos(100t-135^\circ)$
- (8) None of the above

Exam #3

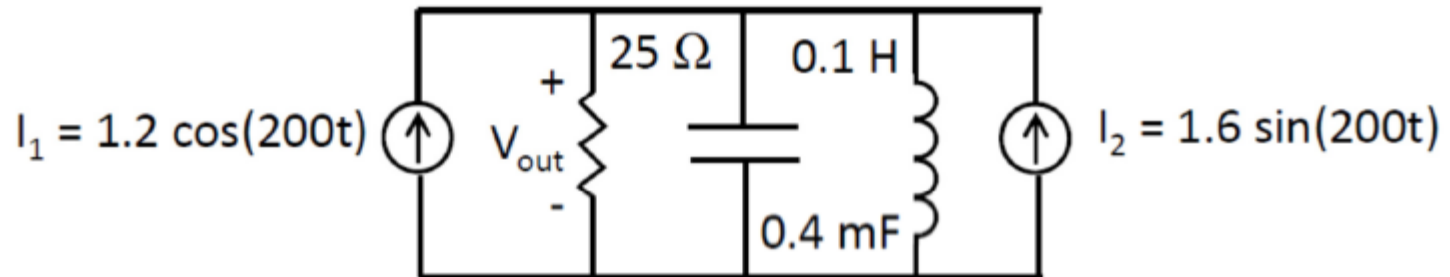10. What is the output voltage V_{out} (in V) for the circuit below, in the sinusoidal steady state?




Answers:

- (1) $20 \cos(200t)$
- (2) $20 \sin(200t)$
- (3) $40 \cos(200t)$
- (4) $40 \sin(200t)$
- (5) $56 \cos(200t)$
- (6) $70 \cos(200t)$
- (7) $70 \sin(200t)$
- (8) None of the above

Exam #3

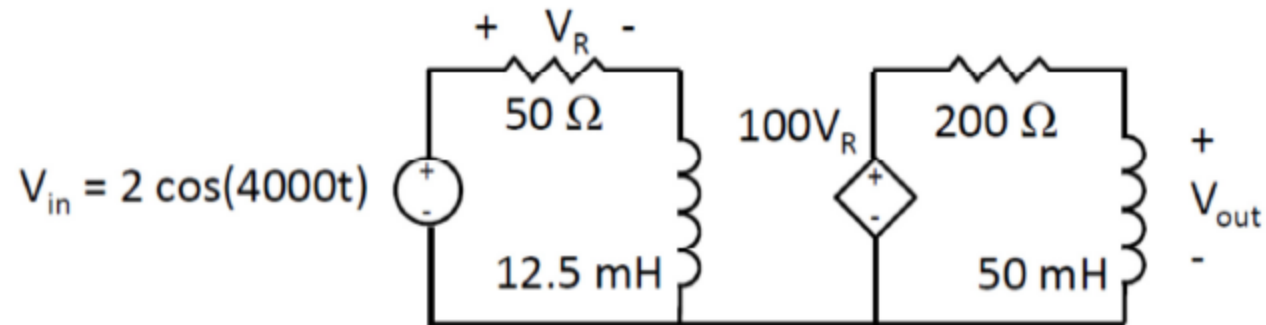
13. For the circuit below in the sinusoidal steady state, what is V_{out} (in V)?



Answers:

- (1) $50 \sin(4000t)$
- (2) $50 \cos(4000t-45^\circ)$
- (3) $50 \cos(4000t)$
- (4) $100 \sin(4000t)$
- (5) $100 \cos(4000t-45^\circ)$
- (6) $100 \cos(4000t)$
- (7) $100 \cos(4000t+45^\circ)$
- (8) None of the above

Average Power for SSS

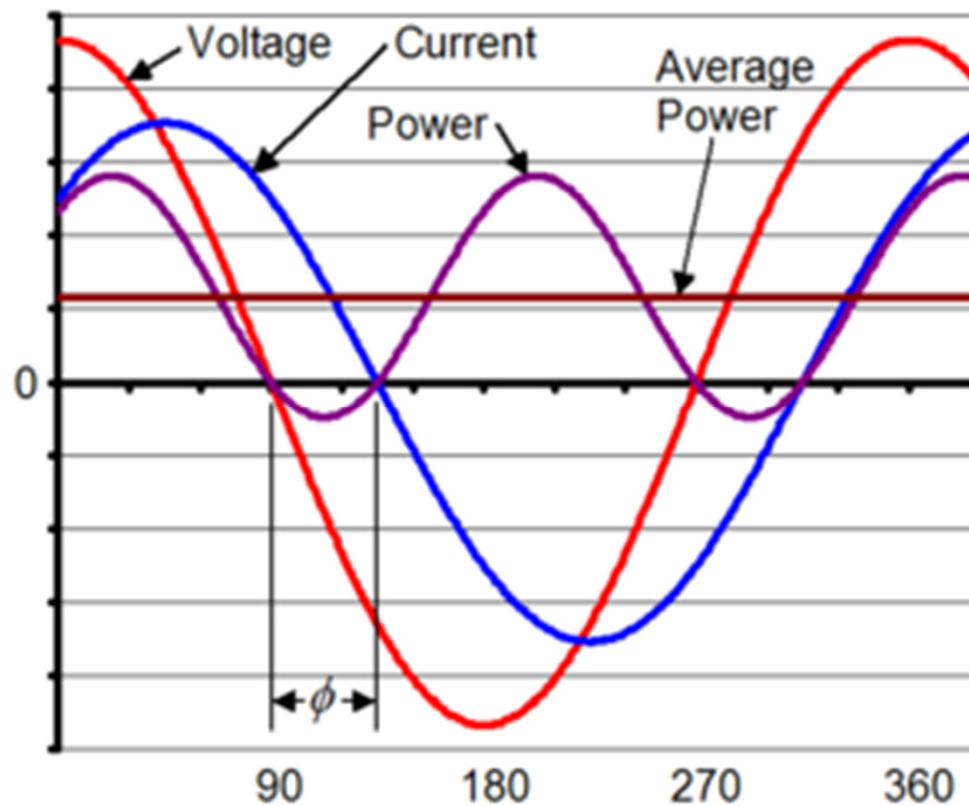

Over half-integer periods, only the first term contributes, so that

$$P_{ave} = \frac{1}{2} I_o V_o \cos \phi$$

Effective Values

- We can generally define effective values for periodic signals, $f(t + T) = f(t)$, such that:

$$F_{eff} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} dt [f(t)]^2}$$

- Also known as root-mean-square (rms) value
- For AC signals, $F_{eff} = \frac{f_o}{\sqrt{2}}$

Power from Effective Values

- Revisiting our calculation from last time:

$$P_{ave} = \frac{1}{2} I_o V_o \cos \phi$$

Rewriting in our new notation:

$$P_{ave} = I_{eff} V_{eff} \cos \phi$$

In electrical engineering, drop the effective subscripts and write:

$$P_{ave} = IV \cos \phi$$

Complex Power

- Complex power is defined as:

$$\mathbf{S} = \mathbf{I}^* \mathbf{V}$$

- For AC signals:


$$\mathbf{S} = I_o e^{-j\omega t} V_o e^{j(\omega t + \phi)}$$

$$\mathbf{S} = I_o V_o e^{j\phi} = I_o V_o (\cos \phi + j \sin \phi)$$


- Key definitions:
 - Re \mathbf{S} – average power
 - Im \mathbf{S} – reactive power
 - $|\mathbf{S}|$ – complex power

Complex Power Example

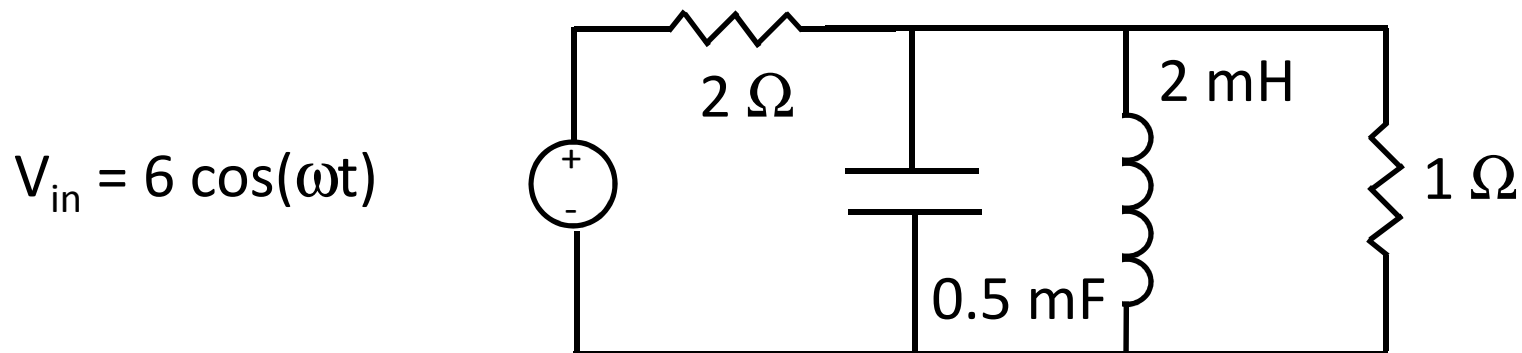- What is the current and complex power dissipated by this circuit?



Complex Power: Solution

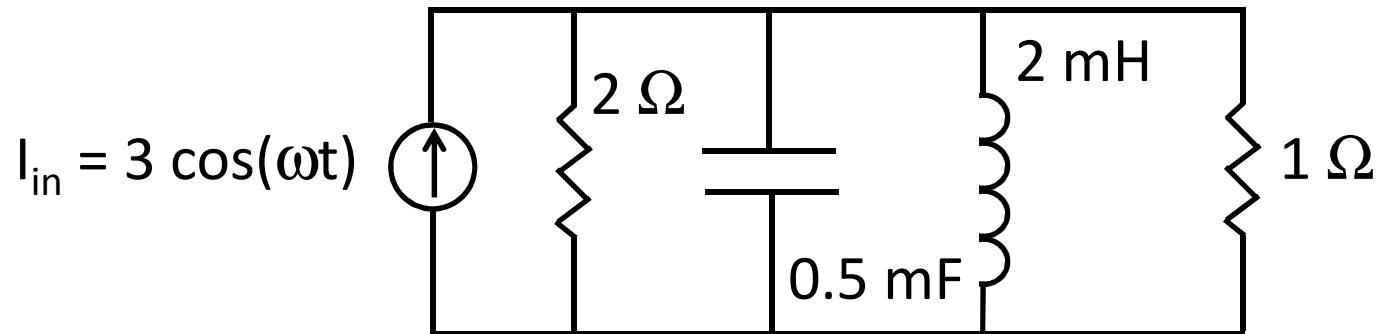

- The impedance is given by:

$$Z = \left[\frac{3}{2} + j\omega \cdot 5 \cdot 10^{-4} + \frac{1}{j\omega \cdot 2 \cdot 10^{-3}} \right]^{-1}$$

- The voltage drop is thus given by:

$$V = IZ = \frac{3e^{j\omega t}}{\frac{3}{2} + j \cdot (\omega/2000 - 500/\omega)}$$

$$V = \frac{2e^{j[\omega t - \tan^{-1}(\frac{\omega}{3000} - \frac{1000}{3\omega})]}}{\left[1 + \left(\frac{\omega}{3000} - \frac{1000}{3\omega} \right)^2 \right]^{1/2}}$$

Complex Power: Solution

- Applying the current division rule:


$$I_L = \frac{Y_L}{Y} I_{tot}$$

$$I_L = \frac{(500/j\omega)3e^{j\omega t}}{\frac{3}{2} + j \cdot (\omega/2000 - 500/\omega)} = \frac{1000e^{j\omega t}}{j\omega + \frac{1000}{3} - \frac{\omega^2}{3000}}$$

$$I_L = \frac{1000e^{j[\omega t - \tan^{-1}(\omega/(333 - \omega^2/3000))]}}{\left[\omega^2 + \left(\frac{1000}{3} - \frac{\omega^2}{3000} \right)^2 \right]^{1/2}}$$

Solution

Inductor Current Amplitude (A)

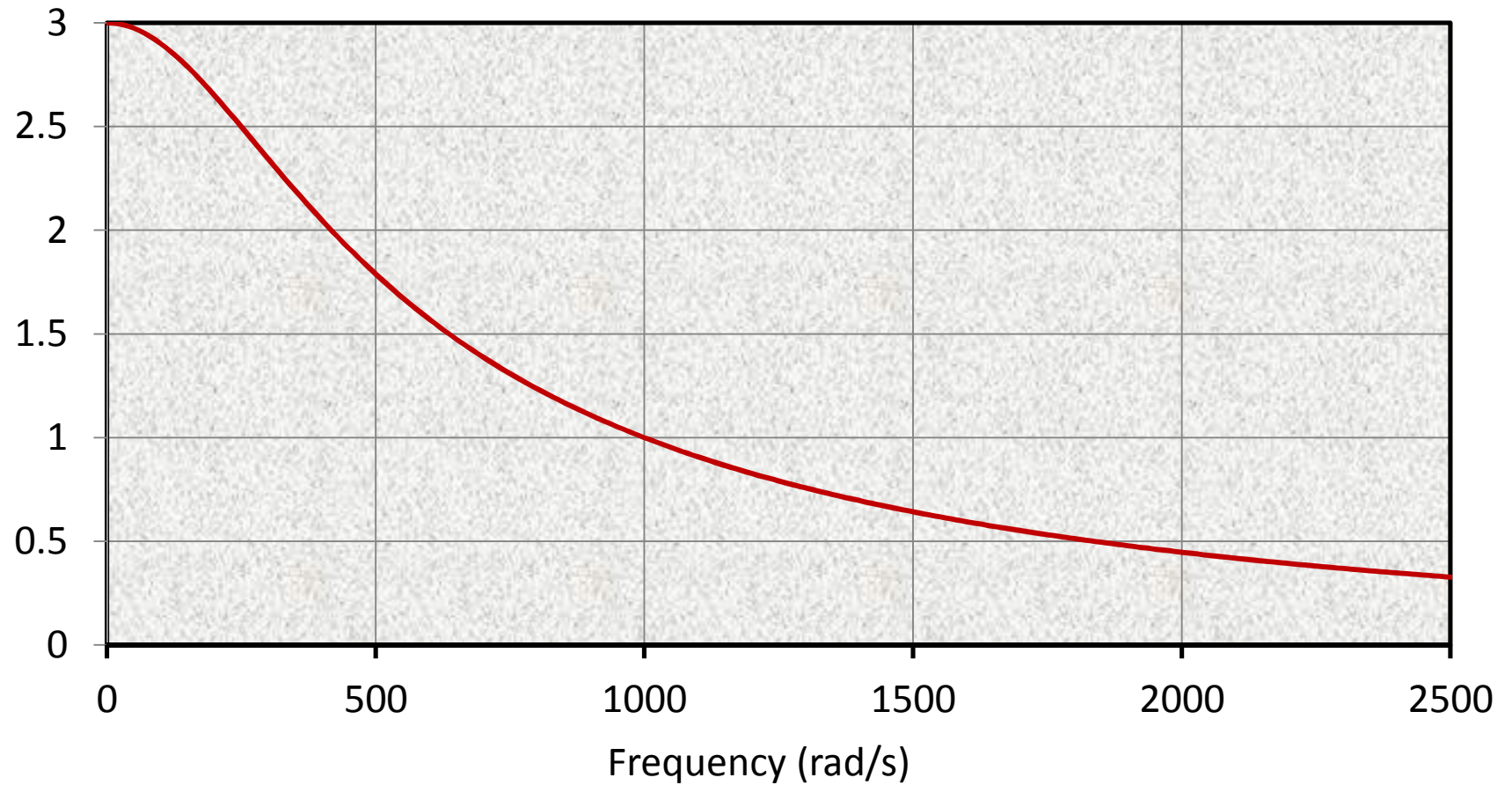

Complex Power: Solution

- From our earlier definitions:


$$\mathbf{S} = \mathbf{I}^* \mathbf{V}$$

- Substitution yields:

$$\mathbf{S} = \frac{1000e^{-j[\omega t - \tan^{-1}(\omega/(333 - \omega^2/3000))]}{\left[\omega^2 + \left(\frac{1000}{3} - \frac{\omega^2}{3000} \right)^2 \right]^{1/2}} \cdot 6e^{j\omega t}$$
$$\mathbf{S} = 6000 \cdot \frac{333 - \frac{\omega^2}{3000} + j\omega}{\left[\omega^2 + \left(\frac{1000}{3} - \frac{\omega^2}{3000} \right)^2 \right]^{3/2}}$$

Solution

Average Power (mW)

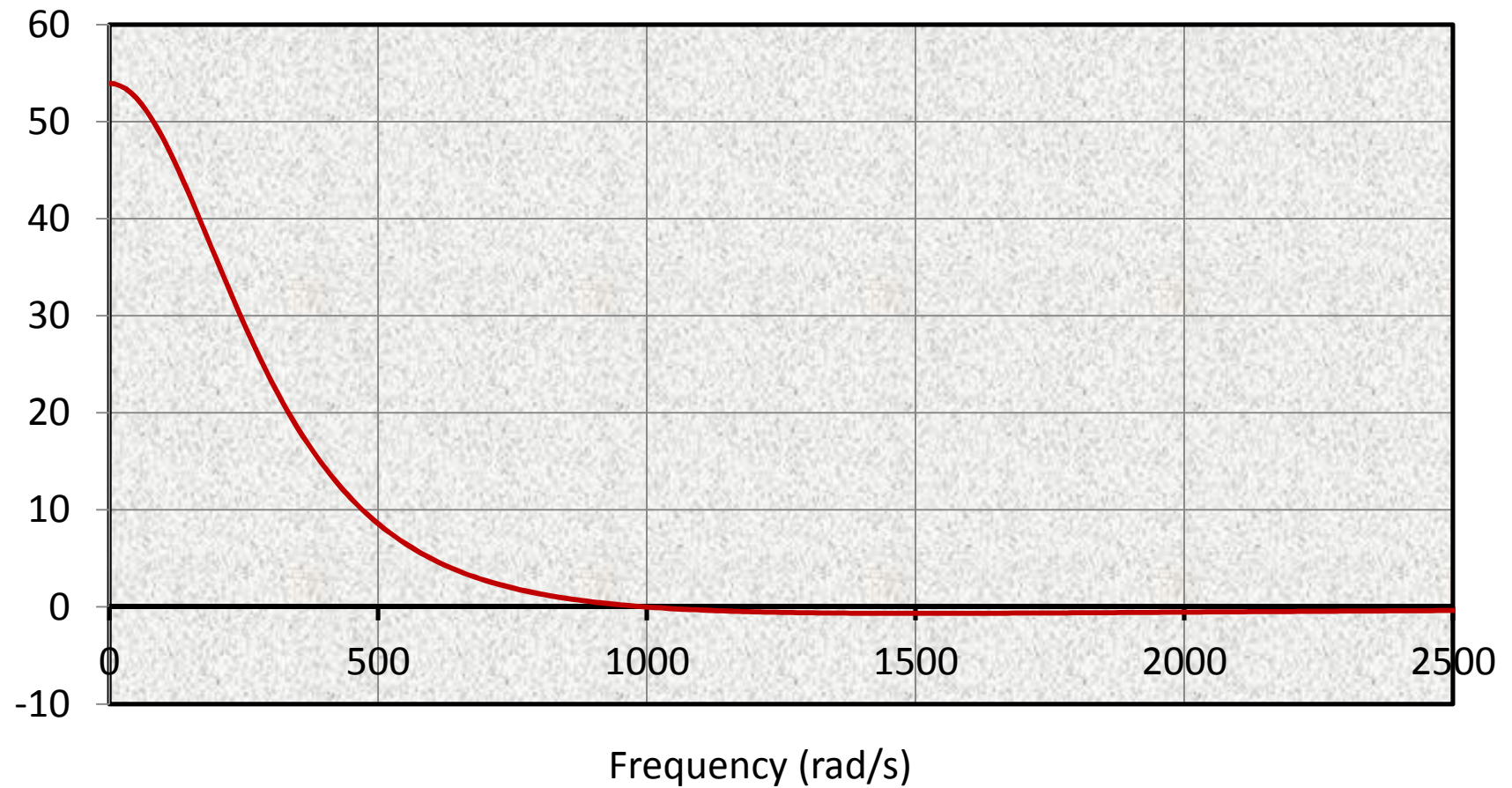

Homework

- HW #35 and extra credit assignment due today by 4:30 pm in EE 325B
- HW #36 due Wed.: DeCarlo & Lin, Chapter 11:
 - Problem 1
 - Problem 3