


ECE 201, Section 3

Lecture 37

Prof. Peter Bermel

November 28, 2012

Average Power for SSS

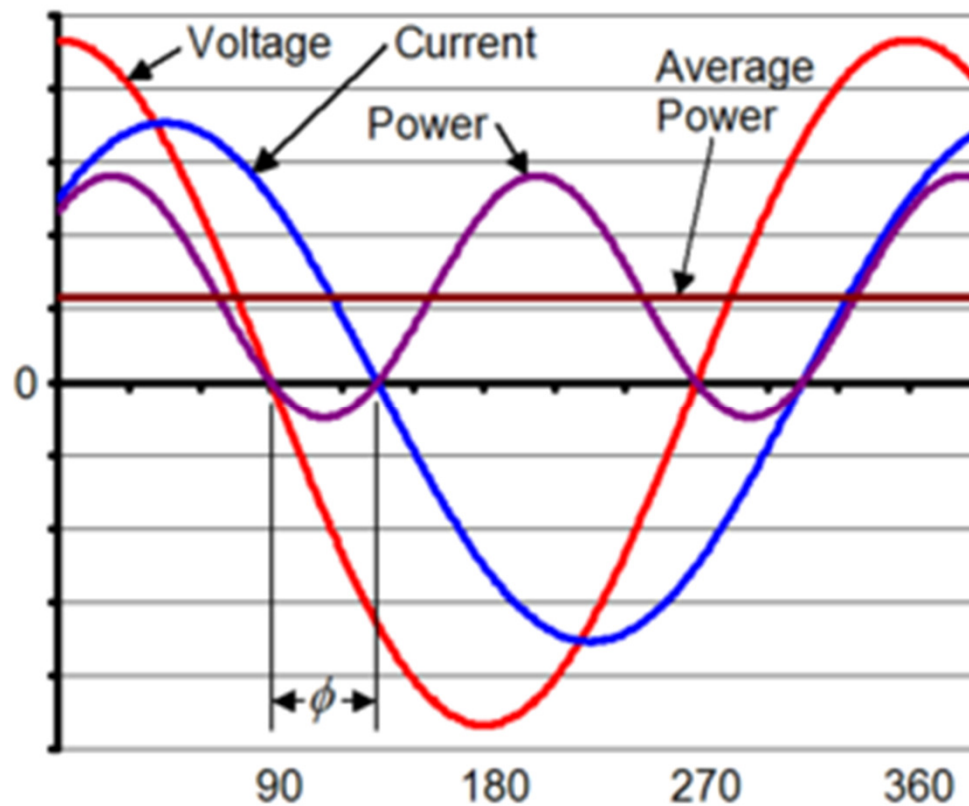

Over half-integer periods, only the first term contributes, so that:

$$P_{ave} = IV \cos \phi$$

Complex Power

- Complex power is defined as:

$$\mathbf{S} = \mathbf{I}^* \mathbf{V}$$

- For AC signals:


$$\mathbf{S} = I e^{-j\omega t} V e^{j(\omega t + \phi)}$$

$$\mathbf{S} = IV e^{j\phi} = IV (\cos \phi + j \sin \phi)$$


- Key definitions:
 - Re \mathbf{S} – average power
 - Im \mathbf{S} – reactive power
 - $|\mathbf{S}|$ – complex power

Complex Power Example #1

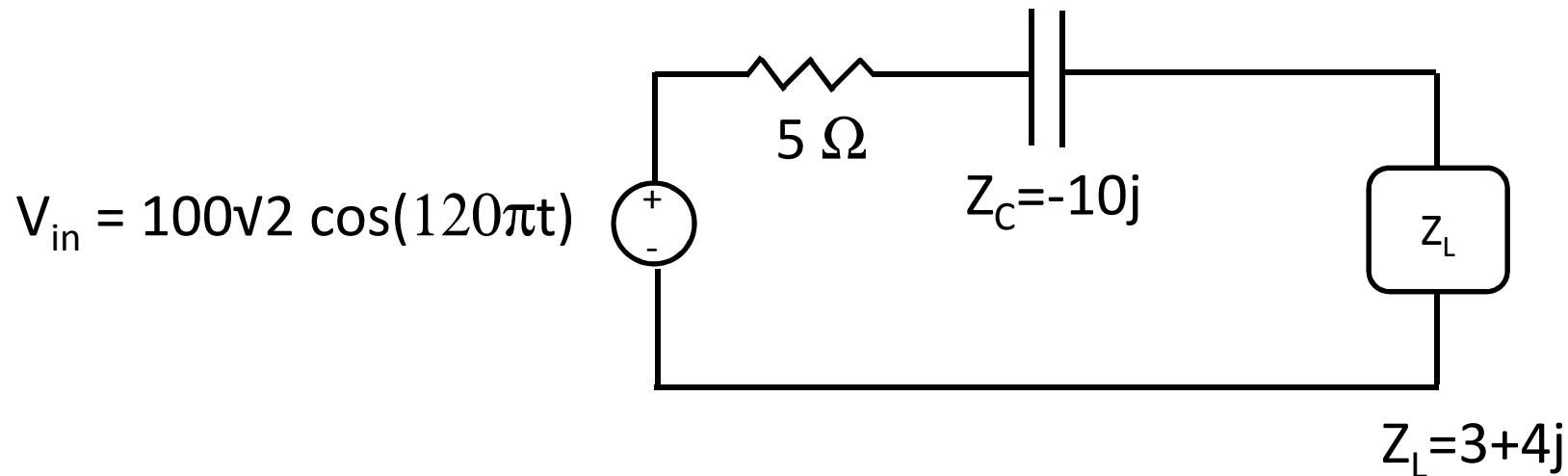- Find the complex power and its components at the load in this circuit




Solution

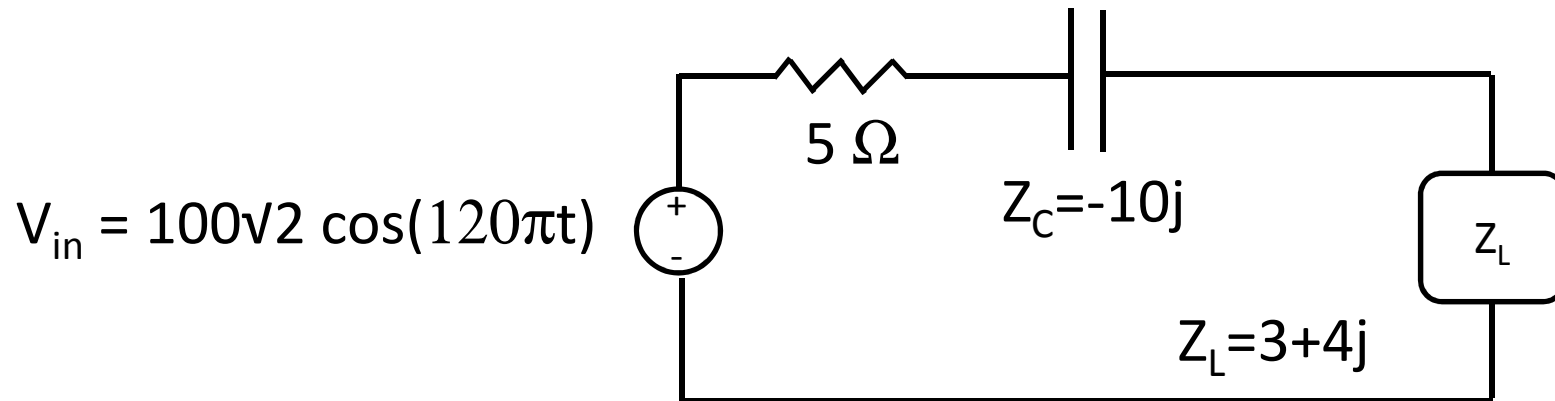

- Using Ohm's law for phasors:

$$I = \frac{V_{in}}{Z_{eq}} = \frac{100\sqrt{2}e^{j120\pi t}}{5 - 10j + 3 + 4j} = \frac{100\sqrt{2}e^{j120\pi t}}{8 - 6j}$$
$$I = 10\sqrt{2}e^{j(120\pi t + 37^\circ)}$$


Solution

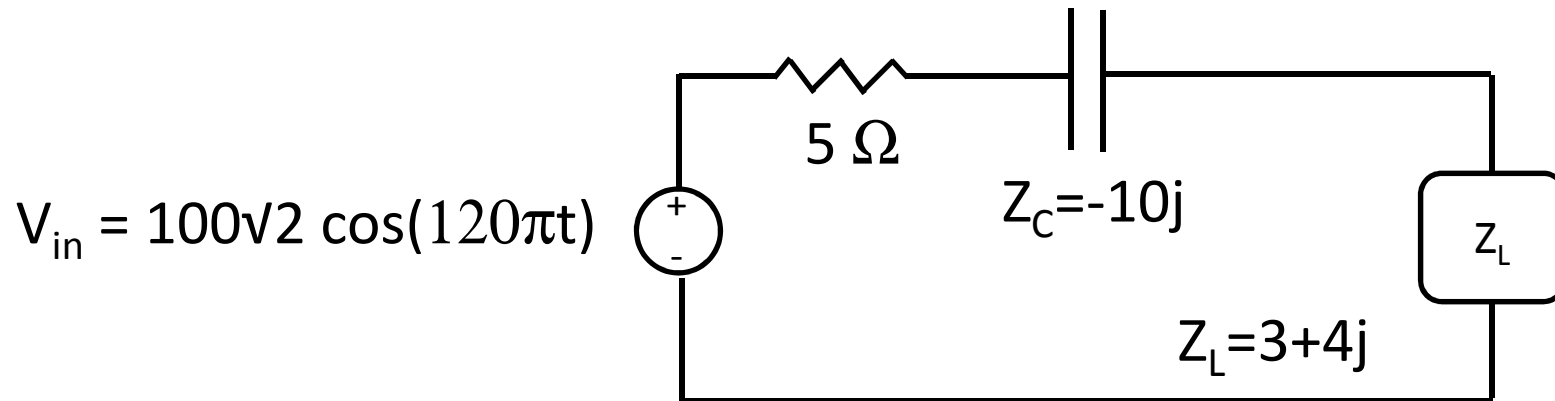

- Using voltage division for phasors:

$$V_L = \frac{Z_L}{Z_{eq}} V_{in} = \frac{3 + 4j}{8 - 6j} 100\sqrt{2} e^{j120\pi t}$$
$$V_L = 50\sqrt{2} e^{j(120\pi t + 90^\circ)}$$

Solution

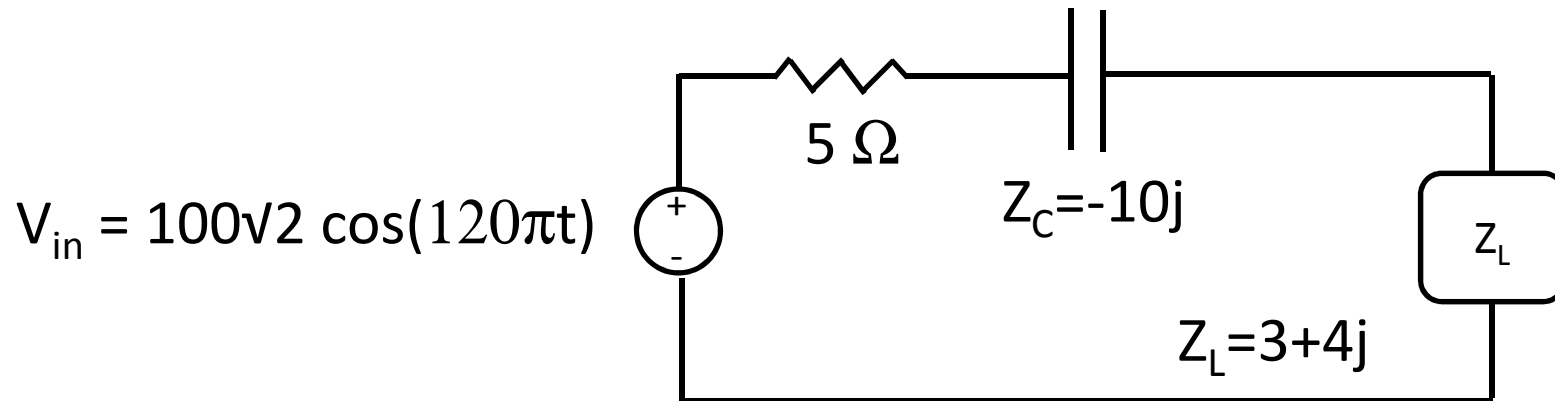


- Putting those results together:

$$\begin{aligned} S_L &= I_{L,eff}^* V_{L,eff} \\ S_L &= 10e^{-j(120\pi t + 37^\circ)} 50e^{j(120\pi t + 90^\circ)} \\ S_L &= 500e^{j53^\circ} = 300 + 400j \end{aligned}$$


Complex Power Example #2

- What is the current and complex power for the inductor contained within this circuit?

$$V_{\text{in}} = 6 \cos(\omega t)$$

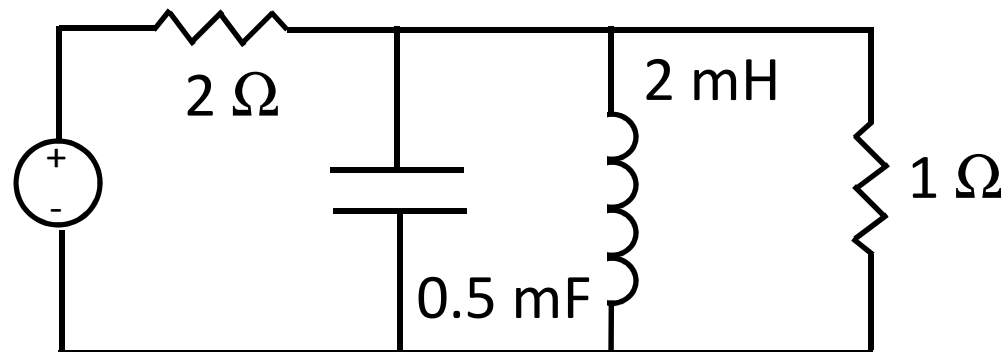

Complex Power: Solution

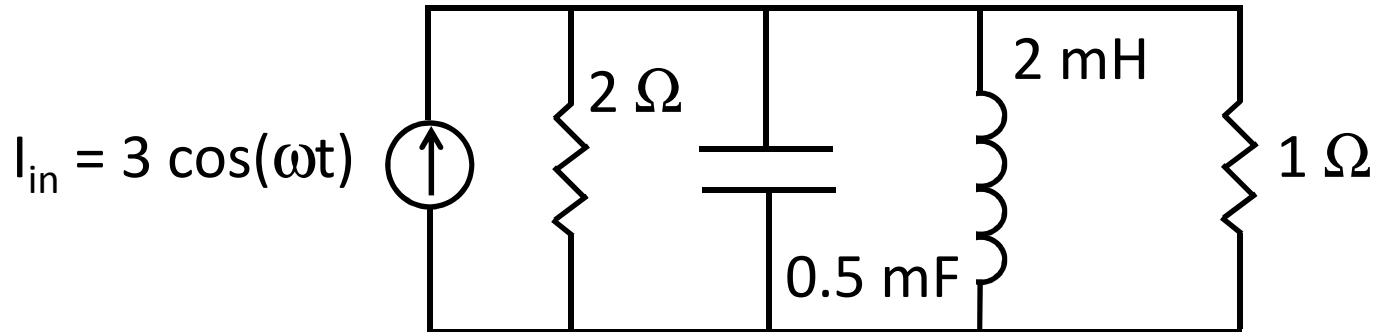

- The impedance is given by:

$$Z = \left[\frac{3}{2} + j\omega \cdot 5 \cdot 10^{-4} + \frac{1}{j\omega \cdot 2 \cdot 10^{-3}} \right]^{-1}$$

- The voltage drop is thus given by:

$$V = IZ = \frac{3e^{j\omega t}}{\frac{3}{2} + j \cdot (\omega/2000 - 500/\omega)}$$

$$V = \frac{2e^{j[\omega t - \tan^{-1}(\frac{\omega}{3000} - \frac{1000}{3\omega})]}}{\left[1 + \left(\frac{\omega}{3000} - \frac{1000}{3\omega} \right)^2 \right]^{1/2}}$$

Complex Power: Solution

- Applying the current division rule:


$$I_L = \frac{Y_L}{Y} I_{tot}$$

$$I_L = \frac{(500/j\omega)3e^{j\omega t}}{\frac{3}{2} + j \cdot (\omega/2000 - 500/\omega)} = \frac{1000e^{j\omega t}}{j\omega + \frac{1000}{3} - \frac{\omega^2}{3000}}$$

$$I_L = \frac{1000e^{j[\omega t - \tan^{-1}(\omega/(333 - \omega^2/3000))]}}{\left[\omega^2 + \left(\frac{1000}{3} - \frac{\omega^2}{3000} \right)^2 \right]^{1/2}}$$

Solution

Inductor Current Amplitude (A)

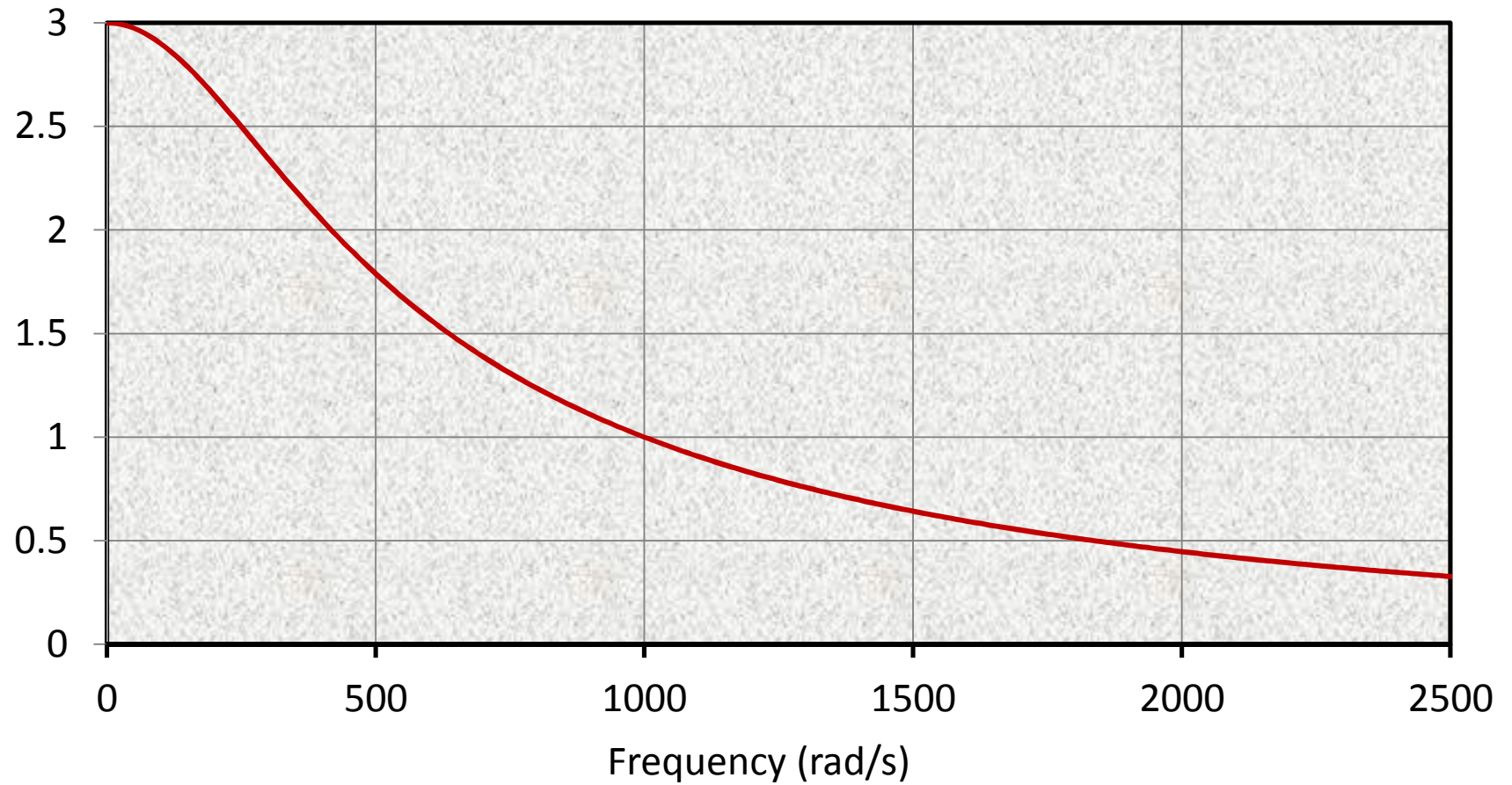

Complex Power: Solution

- From our earlier definitions:

$$\mathbf{S}_L = \mathbf{I}_{L,eff}^* \mathbf{V}_{L,eff}$$


- Substitution yields:

$$\mathbf{S} = \frac{1000e^{-j[\omega t - \tan^{-1}(\omega/(333 - \omega^2/3000))]} }{\left[\omega^2 + \left(\frac{1000}{3} - \frac{\omega^2}{3000} \right)^2 \right]^{1/2}} \cdot 6e^{j\omega t}$$

$$\mathbf{S} = 6000 \cdot \frac{333 - \frac{\omega^2}{3000} + j\omega}{\left[\omega^2 + \left(\frac{1000}{3} - \frac{\omega^2}{3000} \right)^2 \right]^{3/2}}$$

Solution

Average Power (mW)

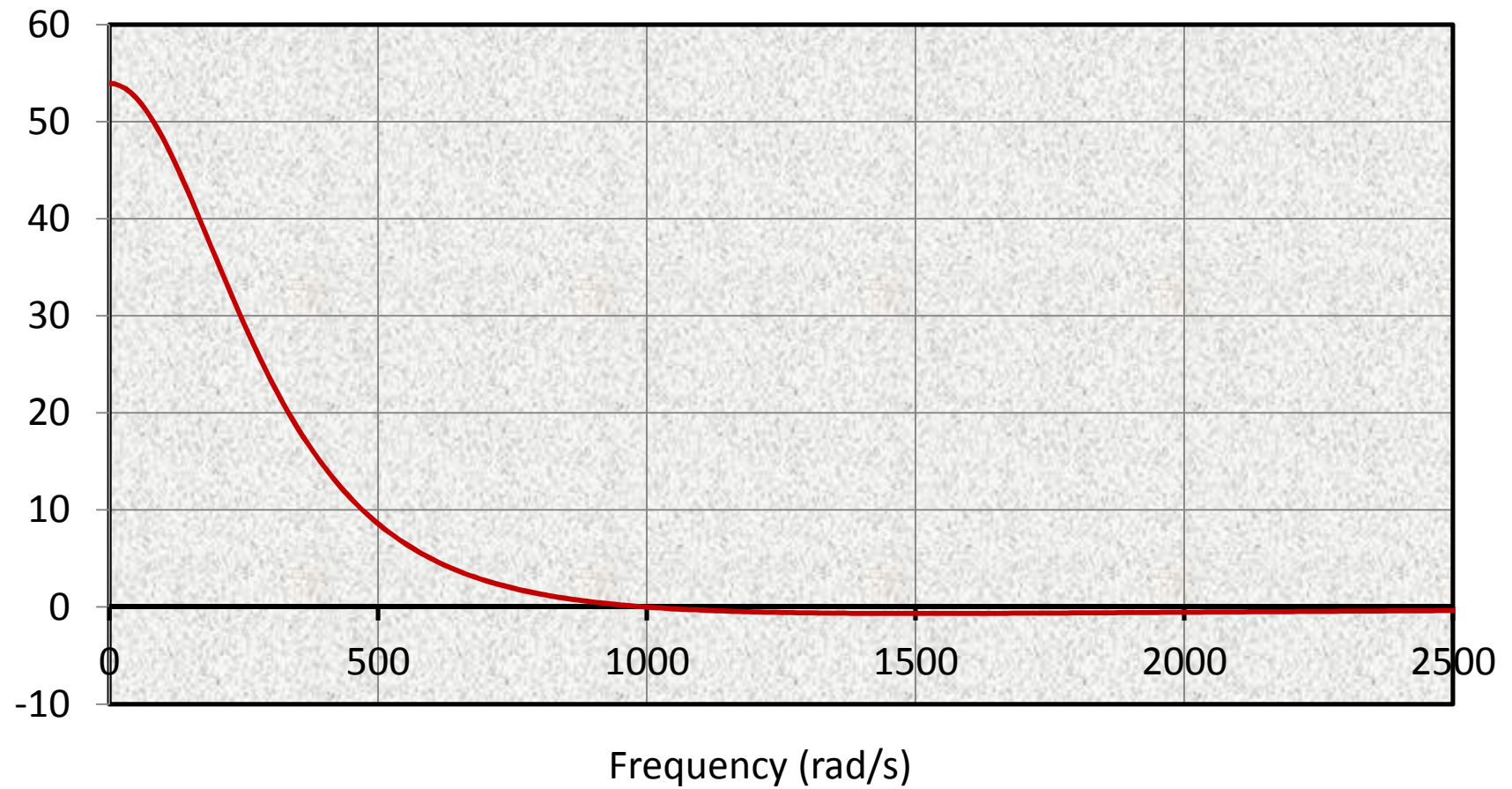


Conservation of Complex Power


- In SSS circuits, complex power is conserved:
 - Average power generated = average power dissipated
 - Reactive power accumulated = reactive power spent
- Direct extension of previous power conservation law
- Implies conservation of energy, as well

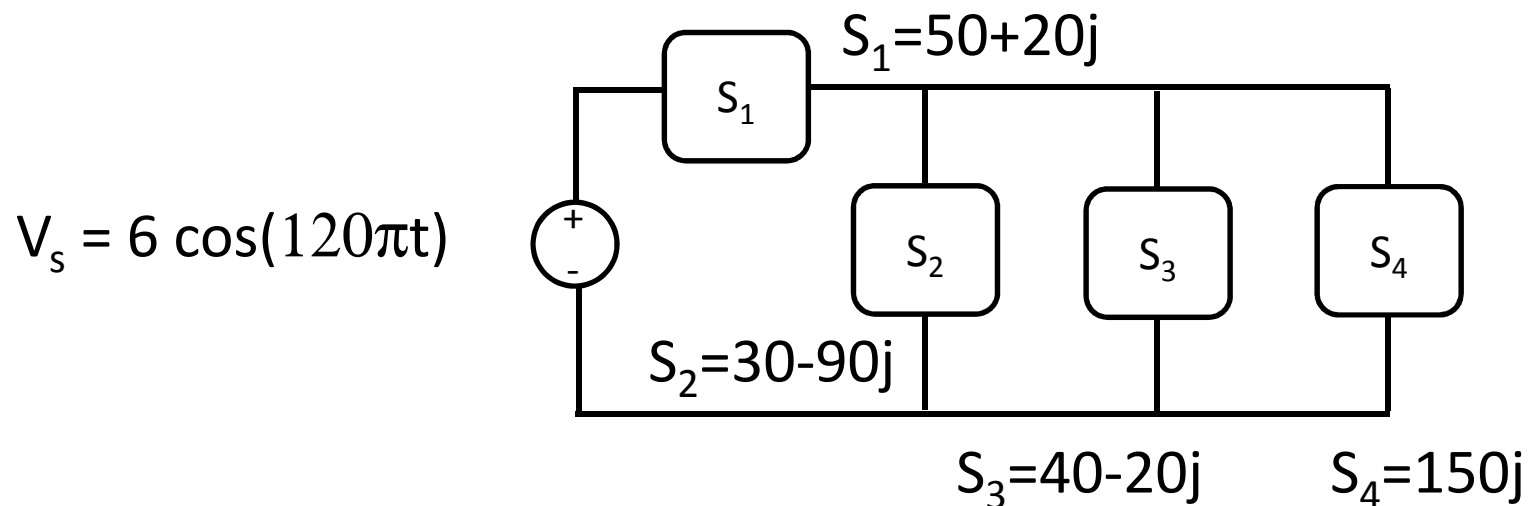Example

- What complex power and current is supplied by this voltage source V_s ?



Solution

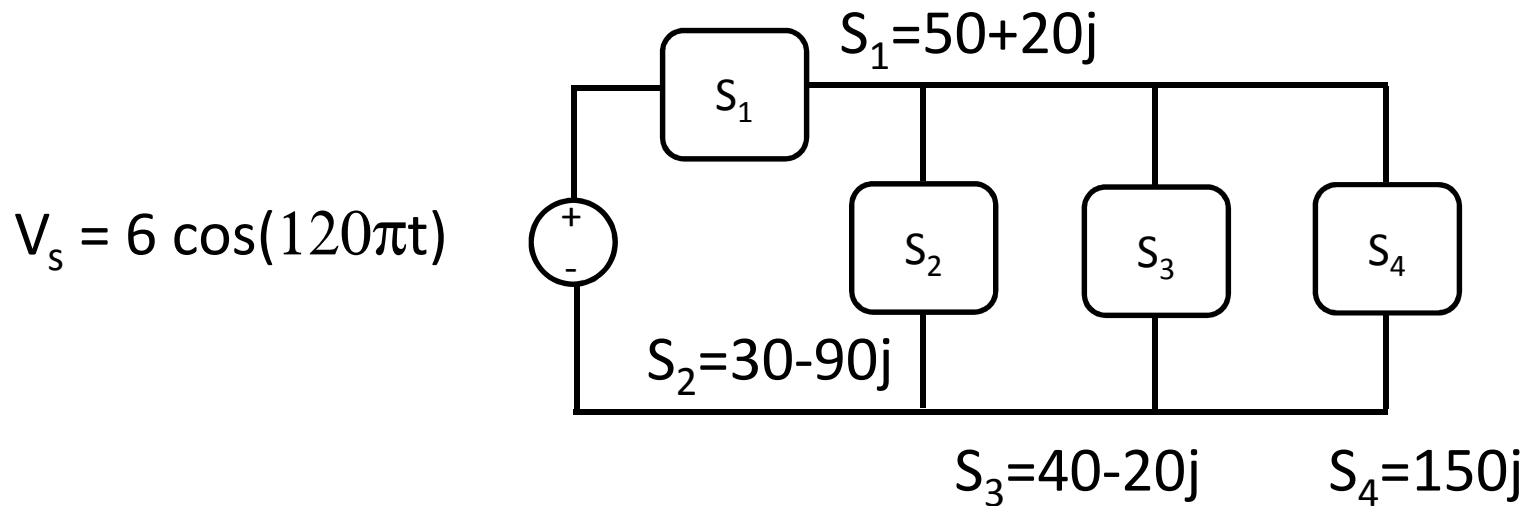

By conservation of complex power:

$$\mathbf{S}_v + \mathbf{S}_1 + \mathbf{S}_2 + \mathbf{S}_3 + \mathbf{S}_4 = 0$$

$$\mathbf{S}_v = -[50 + 20j + 30 - 90j + 40 - 20j + 150j]$$

$$\mathbf{S}_v = -120 - 60j$$

$$I^* = \frac{\mathbf{S}_v}{V_{eff}} = -20 - 10j$$

Power Factor

- Power factor is given by:

$$pf = \frac{P_{ave}}{|S|}$$

- For AC circuits in SSS:

$$pf = \cos \phi$$

- Usually give values like 0.9, lagging (for circuits with finite inductance)

Power Factor Values

| Type of Load | Power factor (lagging) |
|---|------------------------|
| Incandescent lighting | 1.0 |
| Fluorescent lighting (with ballast) | 0.93 |
| One-phase arc welder | 0.5 |
| Three-phase 2 hp motor, fully loaded | 0.84 |

Homework

- HW #36 due today by 4:30 pm in EE 325B
- HW #37 due Fri.: DeCarlo & Lin, Chapter 11:
 - Problem 6
 - Problem 9