

ECE 201, Section 3

Lecture 39

Prof. Peter Bermel

pbermel@purdue.edu

December 3, 2012

Final Exam

- Friday, December 14 from 3:30-5:30 pm in EE 129
- Review sessions:
 - Fri., Dec. 7 from 6:30-7:30 pm in MATH 175
 - Wed., Dec. 12 from 4:30-5:30 pm in ARMS 1010
- Office hours will be held MWF 12:30-1:30 pm (including Dec. 14) in EE 331A & by appointment
- TA office hours will be M-F, 8:30 am-4:30 pm, including December 14 (until 2:30 pm)

Final Exam

- Key Concepts (from course outcomes):
 - Basic concepts: current, voltage, charge, Ohm's law, KCL, KVL, current & voltage division
 - Resistor networks: node, supernode, loop analysis
 - Combining resistors, inductors, and capacitors
 - Source transformation; Thévenin & Norton equivalents
 - Op-amps
 - First and second order circuits: DC with stepped sources, AC in sinusoidal steady state
 - Phasor analysis, including complex power
 - Maximum power transfer for 'realistic' sources

Basic Concepts

- Current I represents the flow of charge:

$$I = \frac{dq}{dt}$$

- Voltage V creates potential energy U for charges:

$$U = qV$$

- Power dissipated (passive sign convention):

$$P = IV$$

- Ohm's Law for resistors:

$$V = IR$$

Basic Concepts: Kirchhoff's Laws

Kirchoff's Current Law (KCL)

- Sum of all currents entering a node or Gaussian surface is zero at all times:

$$\sum_{k=1}^N I_k(t) = 0, \text{ for all } t$$

Kirchoff's Voltage Law (KVL)

- Voltage drop between any two nodes is direction-dependent and path-independent (i.e., $V_{AB} = V_A - V_B$)
- Sum of voltage drops over any closed loop is zero

Voltage and Current Division in Resistors; Resistor Networks

- Series resistors:

$$R_{eq} = \sum R_l$$

$$V_k = VR_k/R_{eq}; \text{ currents equal}$$

- Parallel resistors

$$G_{eq} = \sum G_l$$

$$I_k = IR_{eq}/R_k; \text{ voltages equal}$$

- Series-parallel circuits
 - Analyzed iteratively


Resistor Network Analysis Approaches

- **Nodal analysis**
- Modified nodal analysis
- Nodal analysis with floating voltage sources
- **Loop analysis**
- All approaches should generally yield the same physical results
- Best choice generally involves least number of unknowns, and will depend on details of problem


General Solutions: RC & RL Circuits

$$X = X_{\infty} + (X_o - X_{\infty})e^{-(t-t_o)/\tau}$$

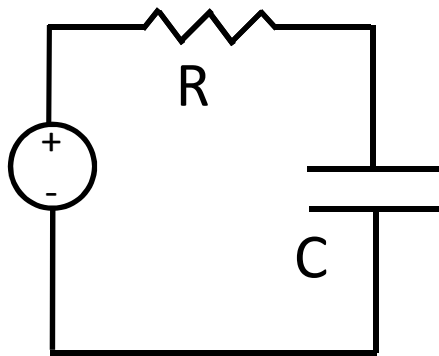- Solution steps:
 - Choose X : RC circuits: $X=Q$ or $X=V$; LR circuits: $X=I$
 - Find X_o (simplifying diagram)
 - Find X_{∞} (simplifying diagram)
 - Find R_{th} (for inductor/capacitor)
 - Find τ : RC circuits: $\tau = R_{th}C$; LR circuits: $\tau = L/R_{th}$
 - If circuit changes at t_1 , use $X(t_1)$ from prior solution for initial values



RC Circuit

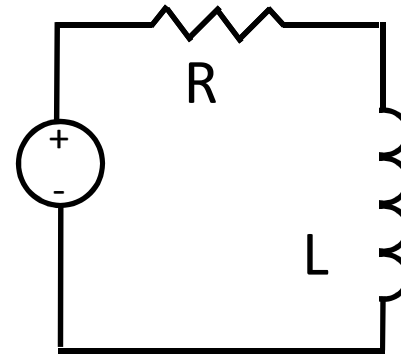


RL Circuit

Driven Series RLC Circuits

From KVL:

$$\frac{d^2 Q}{dt^2} + \frac{R}{L} \frac{dQ}{dt} + \frac{1}{LC} Q = \frac{V_s}{L}$$
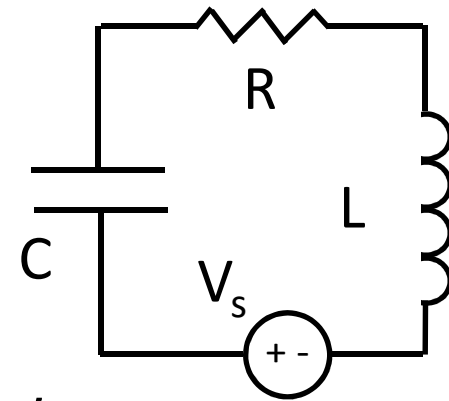
$$\frac{d^2 V_C}{dt^2} + 2\Gamma \frac{dV_C}{dt} + \omega_o^2 V_C = \omega_o^2 V_s$$



$$\Gamma = R/2L; \omega_o = 1/\sqrt{LC}; \omega' = \sqrt{\omega_o^2 - \Gamma^2} = -i\Gamma'$$


Regime	Range	Solution	Behavior
Under-damped	$\Gamma < \omega_o$	$V_C(t) = V_o e^{-\Gamma t} \cos(\omega' t + \phi) + V_s$	Oscillate & decay
Critically damped	$\Gamma = \omega_o$	$V_C(t) = e^{-\Gamma t} (A_1 + A_2 t) + V_s$	Decay
Over-damped	$\Gamma > \omega_o$	$V_C(t) = e^{-\Gamma t} (A_+ e^{\Gamma' t} + A_- e^{-\Gamma' t}) + V_s$	Decay

Driven Parallel RLC Circuits

From KCL:

$$\frac{d^2 I_L}{dt^2} + \frac{1}{RC} \frac{dI_L}{dt} + \frac{1}{LC} I_L = \frac{I_s}{LC}$$
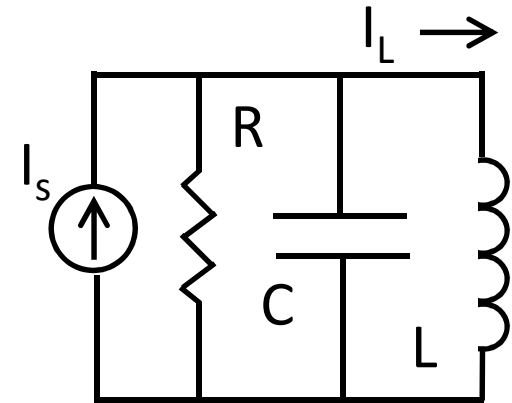
$$\frac{d^2 I_L}{dt^2} + 2\Gamma \frac{dI_L}{dt} + \omega_o^2 I_L = \omega_o^2 I_s$$




$$\Gamma = 1/(2RC); \omega_o = 1/\sqrt{LC}; \omega' = \sqrt{\omega_o^2 - \Gamma^2} = -i\Gamma'$$

Regime	Range	Solution	Behavior
Under-damped	$\Gamma < \omega_o$	$I_L(t) = I_o e^{-\Gamma t} \cos(\omega' t + \phi) + I_s$	Oscillate & decay
Critically damped	$\Gamma = \omega_o$	$I_L(t) = e^{-\Gamma t} (A_1 + A_2 t) + I_s$	Decay
Over-damped	$\Gamma > \omega_o$	$I_L(t) = e^{-\Gamma t} (A_+ e^{\Gamma' t} + A_- e^{-\Gamma' t}) + I_s$	Decay

Complex Numbers (for Phasors)

- Representations
 - Cartesian: $z = x + jy = r(\cos \theta + j \sin \theta)$
 - Polar: $z = re^{j\theta} = \sqrt{x^2 + y^2} e^{j \tan^{-1} \frac{y}{x}}$
- Complex math
 - Absolute value: $|z| = r = \sqrt{x^2 + y^2}$
 - Complex conjugation: $z^* = x - jy = re^{-j\theta}$
 - Natural log: $\ln z = \ln r + j\theta$
 - Multiplication: $z_1 z_2 = r_1 r_2 e^{j(\theta_1 + \theta_2)}$
 - Division: $\frac{z_1}{z_2} = \frac{r_1}{r_2} e^{j(\theta_1 - \theta_2)} = \frac{(x_1 + jy_1)(x_2 - jy_2)}{x_2^2 + y_2^2}$
- Complex exponential properties:
 - Euler's equation: $e^{j\omega t} = \cos \omega t + j \sin \omega t$
 - Converting to phasors:
 - $\cos \omega t \rightarrow e^{j\omega t}$
 - $\sin \omega t \rightarrow e^{j(\omega t - 90^\circ)}$

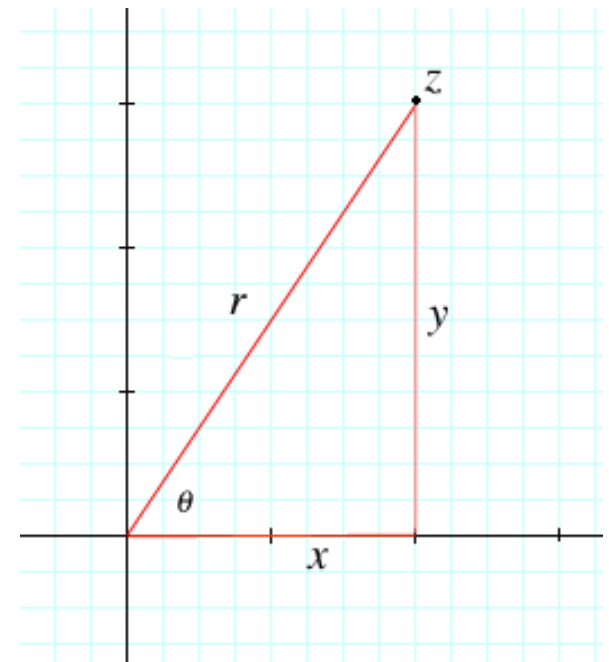

Phasor Review




- Shorthand for writing complex numbers:

$$\mathbf{V} = V_m \angle \phi = V_m e^{j(\omega t + \phi)}$$

- Ohm's law with phasors:

$$\mathbf{V} = \mathbf{Z}(j\omega)\mathbf{I}$$

$$\mathbf{I} = \mathbf{Y}(j\omega)\mathbf{V}$$

Circuit Element	Impedance	Admittance
	$Z(j\omega) = R$	$Y(j\omega) = \frac{1}{R}$
	$Z(j\omega) = j\omega L$	$Y(j\omega) = \frac{1}{j\omega L}$
	$Z(j\omega) = \frac{1}{j\omega C}$	$Y(j\omega) = j\omega C$

Impedance Properties

- For circuit elements in series, voltage division rule becomes:


$$V_k = \frac{Z_k}{Z_{eq}} V_{tot}$$

- For circuit elements in parallel, current division rule becomes:

$$I_k = \frac{Y_k}{Y_{eq}} I_{tot}$$

Ideal Op-Amps

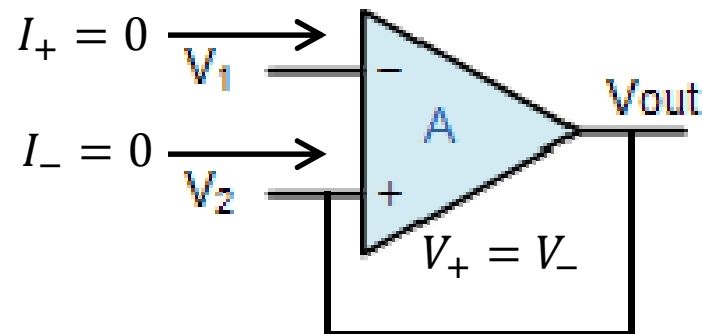- Golden rules:
 - Both input currents are zero
 - For closed loops: both input voltages are equal




Effective Values

- We can generally define effective values for periodic signals, $f(t + T) = f(t)$, such that:

$$F_{eff} = \sqrt{\frac{1}{T} \int_{t_o}^{t_o+T} dt [f(t)]^2}$$

- Also known as root-mean-square (rms) value
- For AC signals, $F_{eff} = \frac{f_o}{\sqrt{2}}$

Average Power for SSS

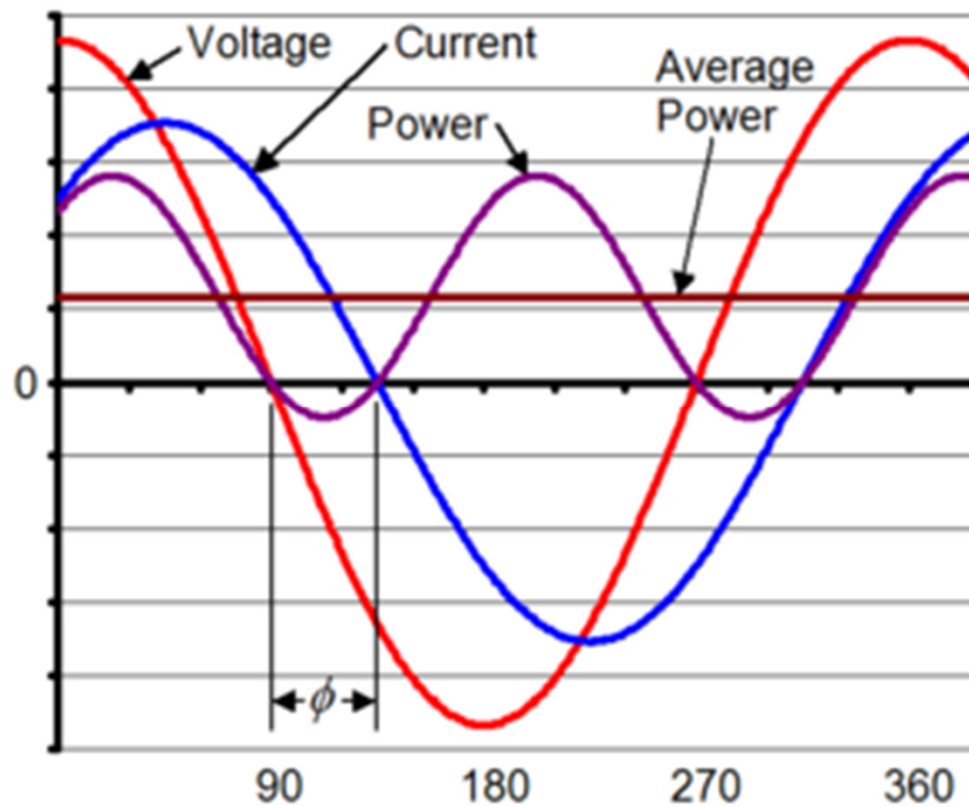

Over half-integer periods, only the first term contributes, so that:

$$P_{ave} = IV \cos \phi$$

Complex Power

- Complex power is defined as:

$$\mathbf{S} = \mathbf{I}^* \mathbf{V}$$


- For AC signals:

$$\mathbf{S} = I e^{-j\omega t} V e^{j(\omega t + \phi)}$$

$$\mathbf{S} = IV e^{j\phi} = IV (\cos \phi + j \sin \phi)$$

- Key definitions:
 - Re \mathbf{S} – average power
 - Im \mathbf{S} – reactive power
 - $|\mathbf{S}|$ – apparent power
 - $\cos \phi$ – power factor

Maximum Power Transfer

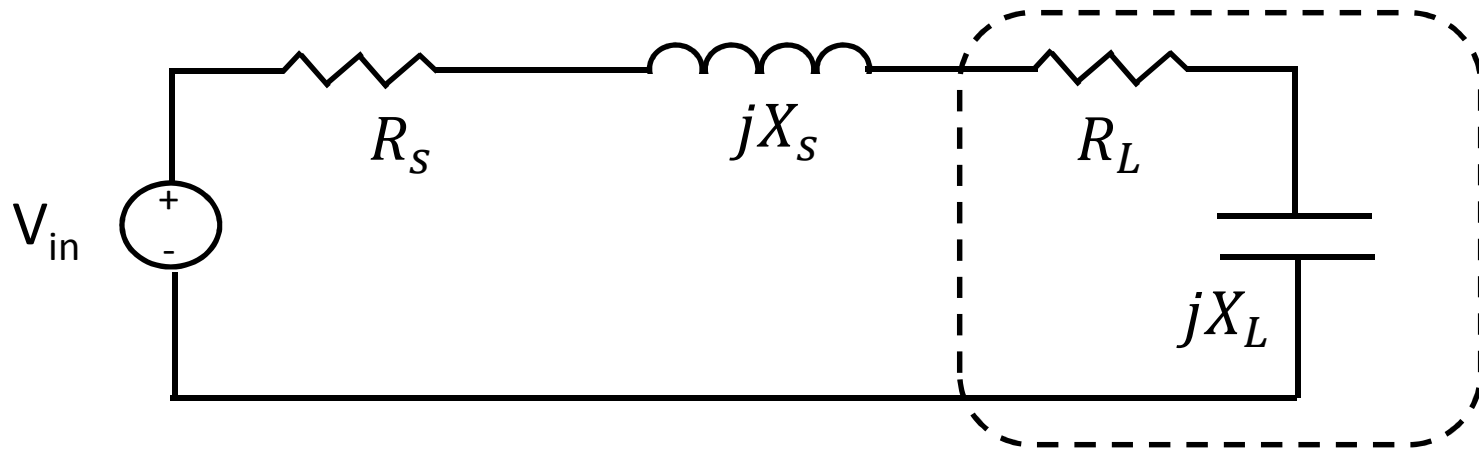

- For a source with impedance $Z_S = R_S + jX_S$, maximum power is transferred when load impedance $Z_L = Z_S^*$
 - Resistances are equal: $R_L = R_S$
 - Reactances are opposite: $X_L = -X_S$
- Magnitude of maximum power transfer:

$$P_{max} = \frac{V_{s,eff}^2}{4R_S}$$

Homework

- HW #38 due today at 4:30 pm in EE 325B
- HW #39 due Wed.: DeCarlo & Lin, Chapter 11:
 - Problem 24
 - Problem 26 [Correction: the power factor is 0.866.]