

ECE 201, Section 3

Lecture 4

Prof. Peter Bermel

August 27, 2012

Definitions

- **Node** – a connecting point between two or more circuit elements
- **Branch** – part of a circuit; one or more circuit elements with two terminals
- **Gaussian surface** – enclosed surface where charge & electromagnetic flux is calculated
- **Parallel circuit** – two or more branches linked by two nodes
- **Series circuit** – two or more branches linked by one node

Definitions

- **Closed path** – series of connected nodes with the same beginning & end
- **Closed node sequence** – series of nodes where the same beginning & end
- **Connected circuit** – a circuit in which all nodes are connected to each other via a path of circuit elements

Kirchoff's Current Law

- Sum of all currents entering a node or Gaussian surface is zero at all times
- From the conservation of charge:


$$Q(t) = \int_0^t \sum_{k=1}^N dQ_k = 0, \text{ for all } t$$

$$Q(t) = \int_0^t dt \sum_{k=1}^N I_k(t) = 0, \text{ for all } t$$

$$\sum_{k=1}^N I_k(t) = 0, \text{ for all } t$$

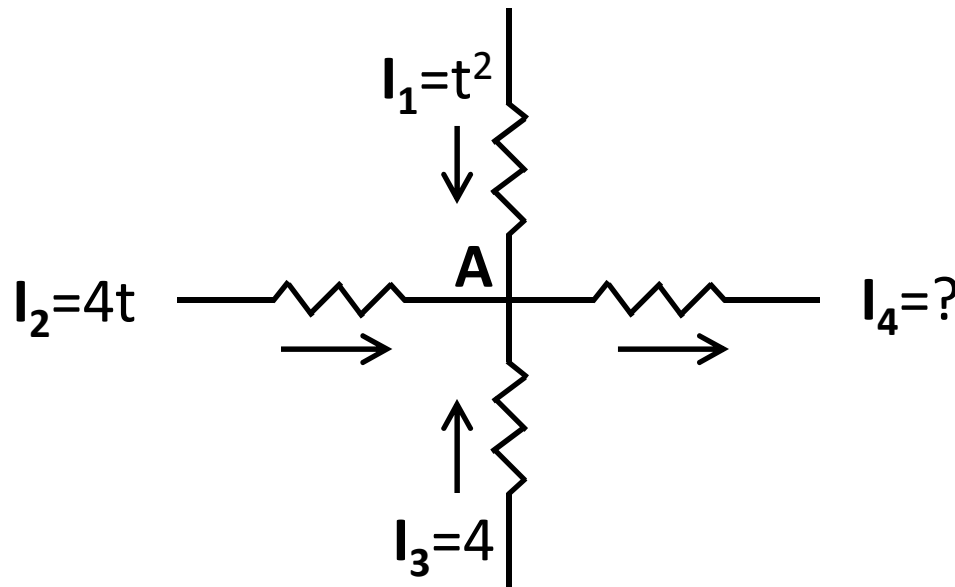Example 1


- At node A, input currents look like this:



What is the output current I_4 ?

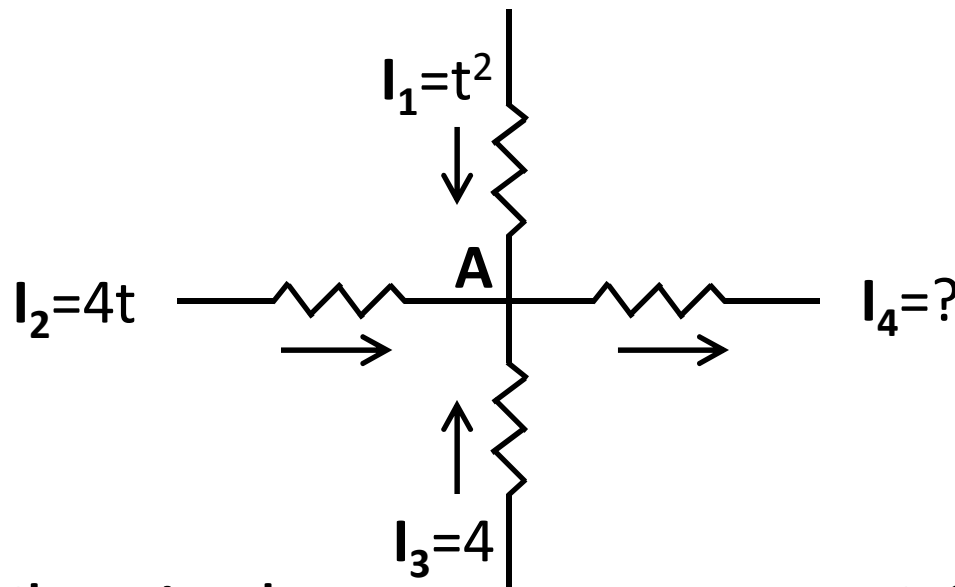Example 1: Solution

- At node A, input currents look like this:




What is the output current I_4 ?

$$I_4 = t^2 + 4t + 4 = (t+2)^2$$

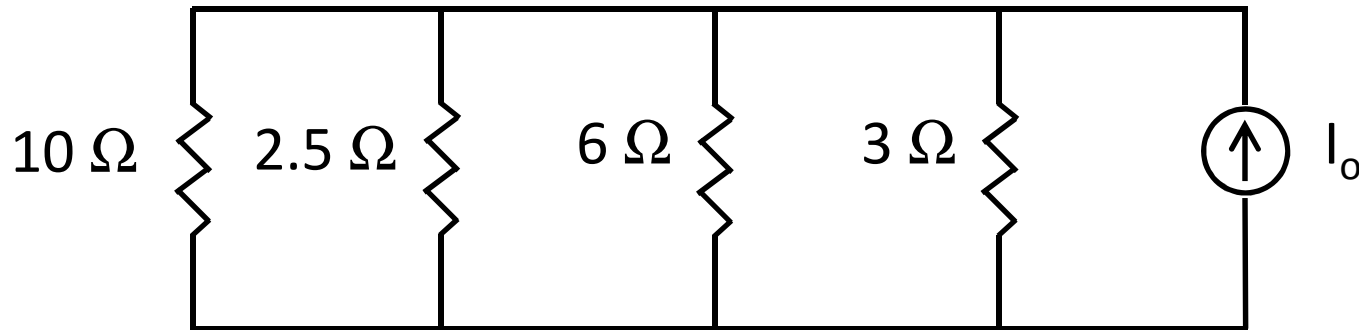Example 2


- Given an ideal current source I_o connected to 4 parallel resistors, how is the current divided?



- What if 2 identical ICS's are connected in parallel? In series? What if only one has its current doubled?

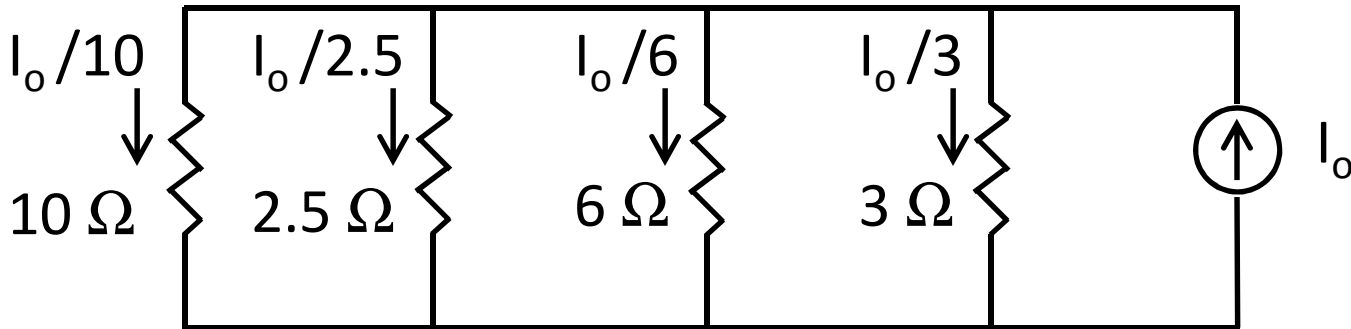Example 2: Solution


- Given an ideal current source I_o connected to 4 parallel resistors, how is the current divided?



- Equal voltage drop across every resistor implies:

$$I_k = \frac{V}{R_k} = \frac{I_o}{R_k} \sum_{l=1}^N \frac{1}{R_l}$$

Example 2: Solution, Cont'd

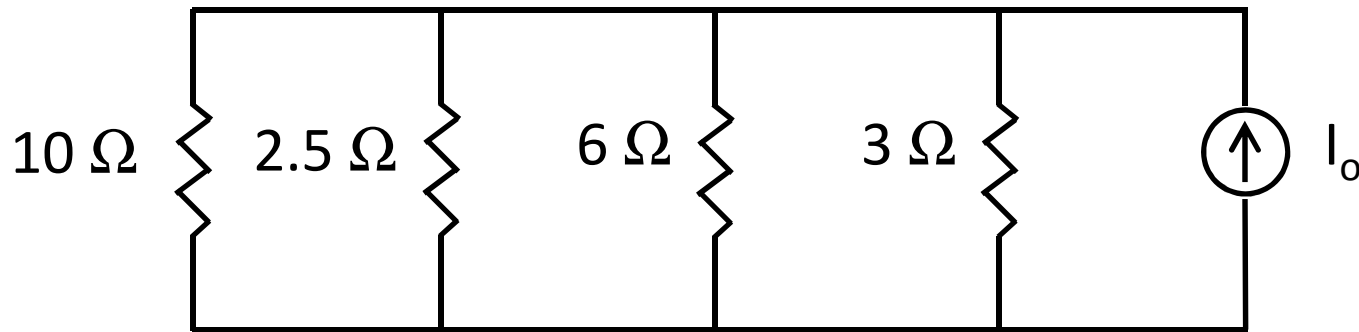

- What if 2 identical ICS's are connected in parallel?
 - All currents in resistors double
- In series?
 - No change
- What if only one has its current doubled?
 - Currents triple in parallel; unphysical in series


Kirchoff's Voltage Law

- Since voltage is a unique quantity at a given place and time (see Lecture 2):
 - Voltage drop between any two nodes is given by the difference of their voltages, independent of path (i.e., $V_{AB} = V_A - V_B$)
 - It is directionally dependent (e.g., $V_{AB} = -V_{BA}$, since $V_A - V_B = -(V_B - V_A)$)
 - Sum of voltage drops over any closed loop is zero (otherwise, voltage would be non-unique)

Kirchoff's Voltage Law


- Alternative statements:
 - For connected circuits and any node sequence, the voltage difference between the end points equals the sum of the voltage drops across each element: e.g., $V_{AD} = V_{AB} + V_{BC} + V_{CD}$, since $V_{AB} + V_{BC} + V_{CD} = V_A - V_B + V_B - V_C + V_C - V_D = V_A - V_D$
 - For connected circuits, the sum of node-to-node voltages over any closed node sequence is always zero (a special case of the last rule)

Example 3

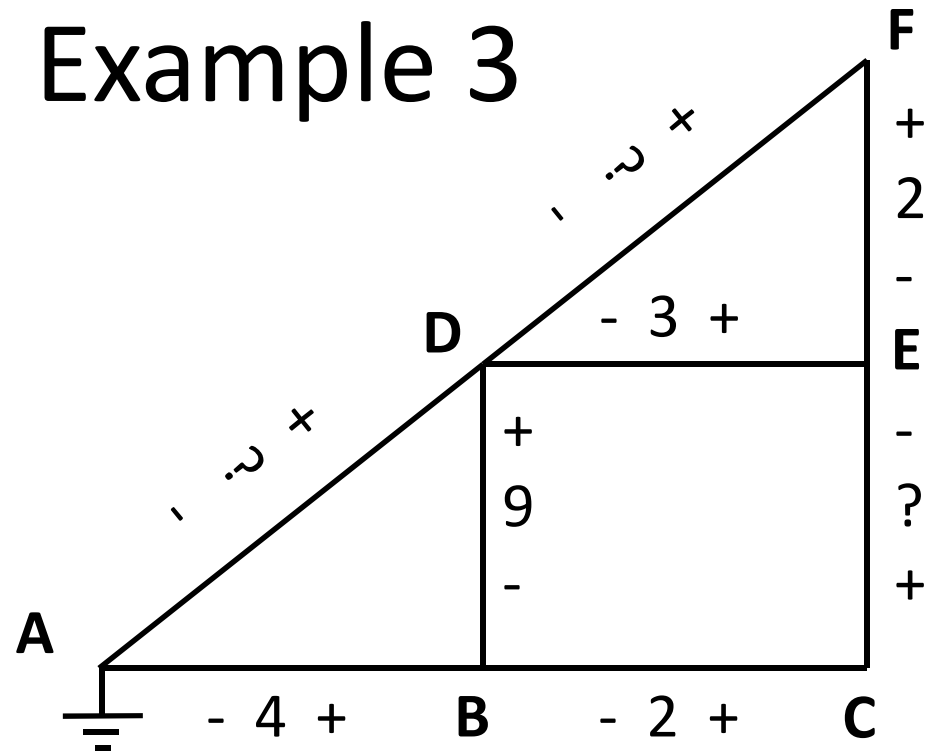

- What are V_{DA} , V_{FD} , and V_{EC} ?

Example 3: Solution

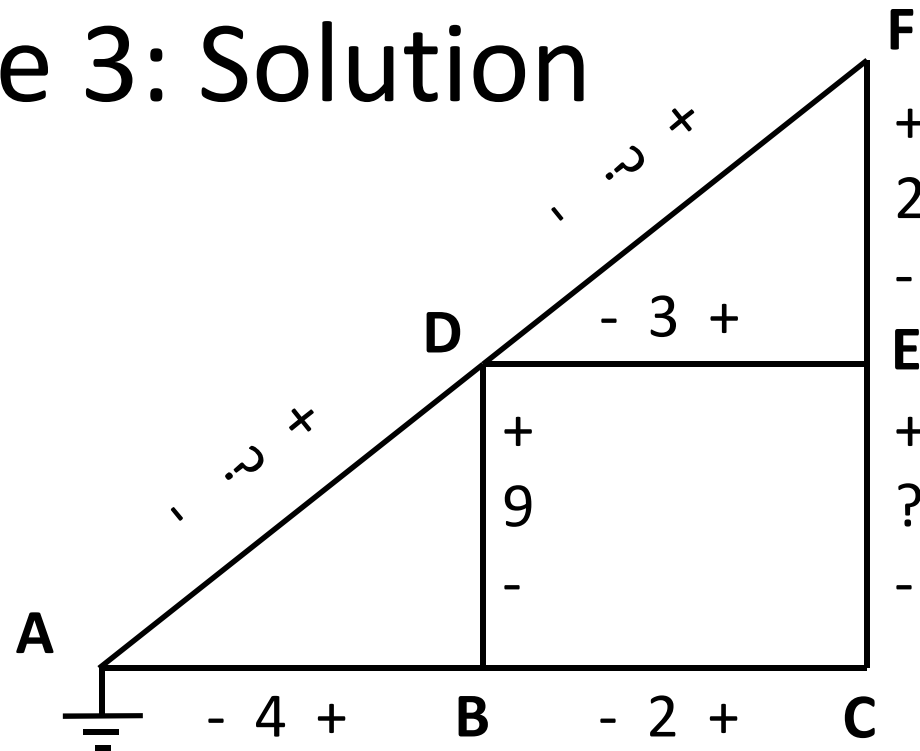

- What are V_{DA} , V_{FD} , and V_{EC} ?
 - $V_{DA} = V_{DB} + V_{BA} = 9\text{ V} + 4\text{ V} = 13\text{ V}$
 - $V_{FD} = V_{FE} + V_{ED} = 2\text{ V} + 3\text{ V} = 5\text{ V}$
 - $V_{EC} = V_{ED} + V_{DB} + V_{BC} = 3\text{ V} + 9\text{ V} - 2\text{ V} = 10\text{ V}$

Homework

- HW #2 solution posting this morning
- HW #3 due today by 4:30 pm in EE 325B
- HW #4 due Wed. – DeCarlo & Lin, **Chapter 2:**
 - Problem 2(a)
 - Problem 3
 - Problem 6
 - Problem 12