

ECE 201, Section 3

Lecture 5

Prof. Peter Bermel

August 29, 2012

Recap from Monday

Kirchoff's Current Law (KCL)

- Sum of all currents entering a node or Gaussian surface is zero at all times:


$$\sum_{k=1}^N I_k(t) = 0, \text{ for all } t$$

Kirchoff's Voltage Law (KVL)

- Voltage drop between any two nodes is direction-dependent and path-independent (i.e., $V_{AB} = V_A - V_B$)
- Sum of voltage drops over any closed loop is zero


Gaussian Surfaces

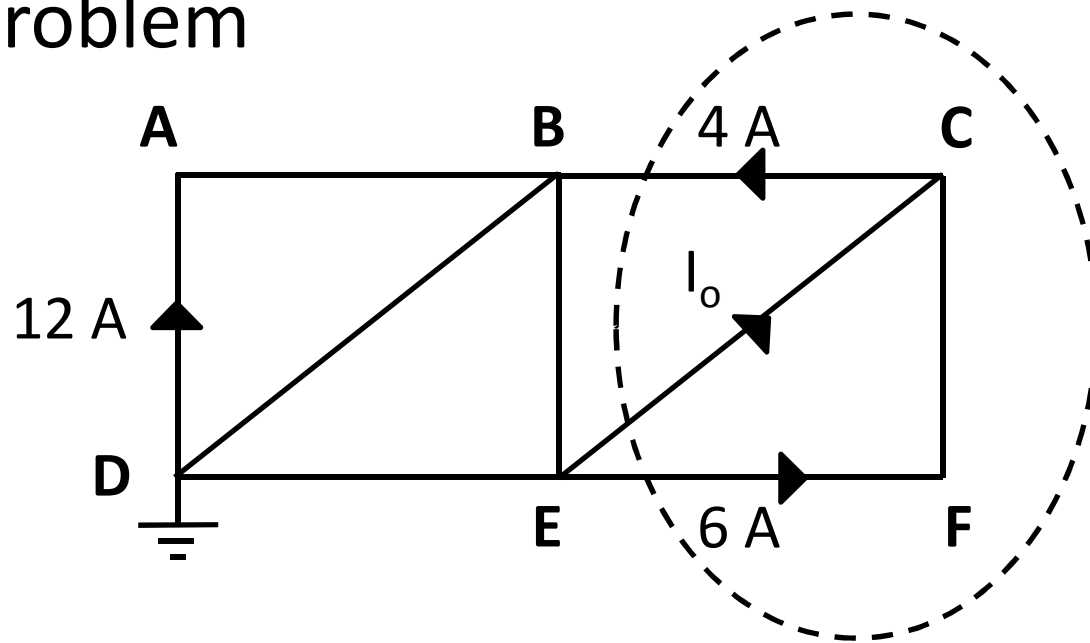- Hypothetical surface through which sum of currents must always be zero
- Clever choice of Gaussian surface can vastly simplify problem
- Example:



Series Resistive Circuits

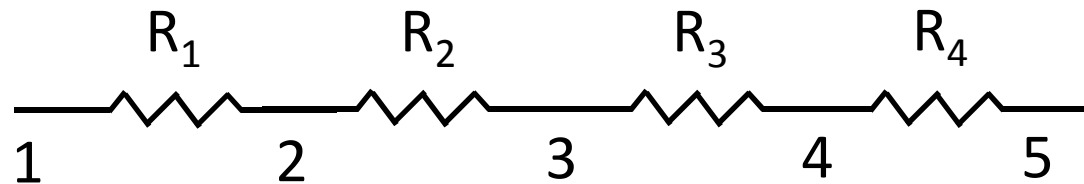- Calculate the effective resistance of N resistors in series:



- According to KVL:

$$V_{N+1,1} = \sum_{l=1}^N V_{l+1,l}$$
$$IR_{eq} = \sum_{l=1}^N IR_l$$
$$R_{eq} = \sum_{l=1}^N R_l$$

Series Resistive Circuits

- Calculate the power dissipated by N resistors in series

- For each element:

$$P_k = I^2 R_k$$


- For the circuit as a whole:

$$P = \sum_{l=1}^N I^2 R_l = I^2 \sum_{l=1}^N R_l$$

$$P = I^2 R_{eq}$$

Parallel Resistive Circuits

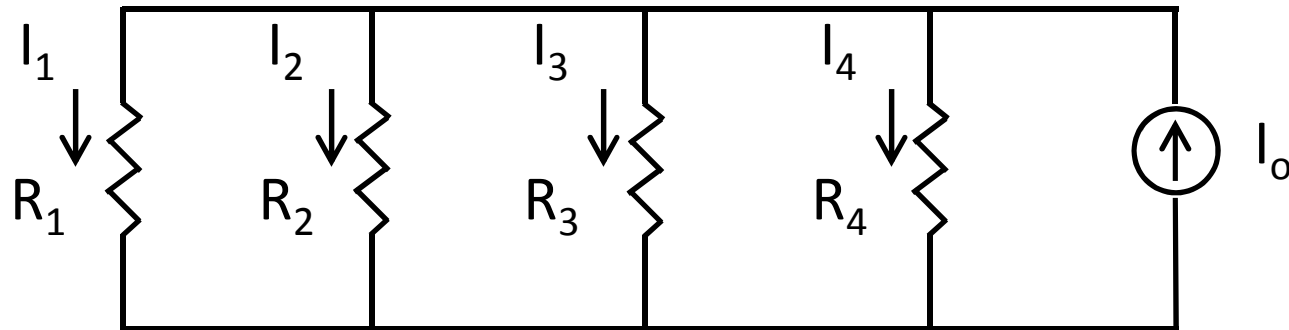- Given a current source I_o connected to N parallel resistors, what is the equivalent resistance?



- Equal voltage drop across every resistor implies:

$$V = I_k R_k = I_o R_{eq}$$

- Kirchoff's current law tells us that:

$$I_o = \sum_{l=1}^N I_l$$
$$\frac{V}{R_{eq}} = \sum_{l=1}^N \frac{V}{R_l}$$
$$G_{eq} = \sum_{l=1}^N G_l$$

Parallel Resistive Circuits

- Calculate the power dissipated by N resistors in parallel
 - For each element:

$$P_k = I_k^2 R_k$$

- For the circuit as a whole:

$$P = \sum_{l=1}^N I_l^2 R_l = V \sum_{l=1}^N I_l$$


$$P = I_o^2 R_{eq}$$

Series-Parallel Circuits

- Combines features of series and parallel circuits
- Depend on two reference points
- Solve iteratively with previous equations

Series-Parallel Circuits

- Example:

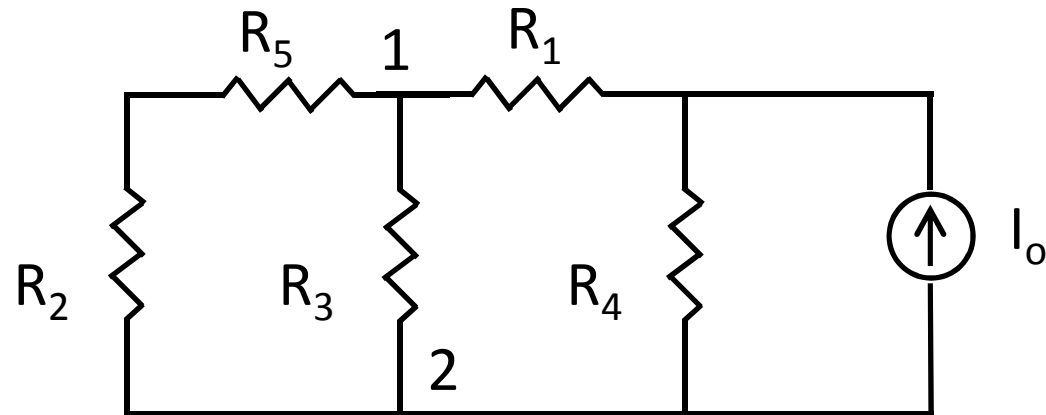

Equivalent resistance across source terminals:

$$\frac{1}{R_{12}} = \frac{1}{R_3} + \frac{1}{R_2 + R_5}$$
$$\frac{1}{R_{eq}} = \frac{1}{R_4} + \frac{1}{R_1 + R_{12}}$$

Summary

- Series resistors:

$$R_{eq} = \sum R_l$$

$$V_k = VR_k/R_{eq}; \text{ currents equal}$$

- Parallel resistors


$$G_{eq} = \sum G_l$$

$$I_k = IR_{eq}/R_k; \text{ voltages equal}$$

- Series-parallel circuits
 - Analyzed iteratively


Loading Effect

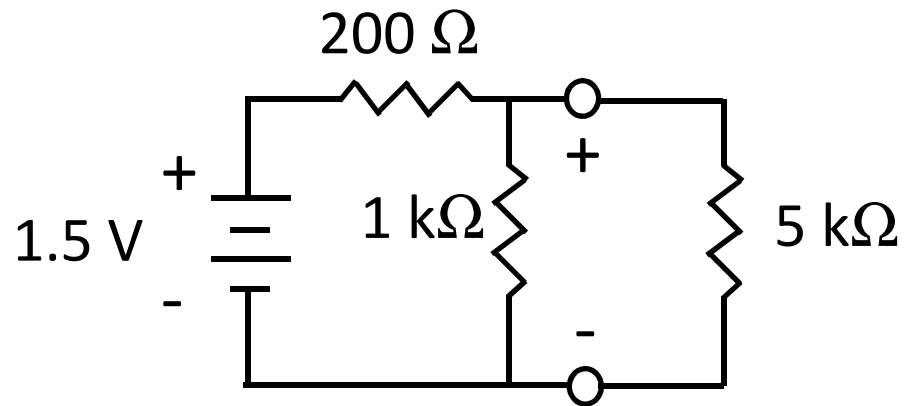- Measuring voltage requires using a large but finite resistance
- Example:
 - 1.25 V nominal
 - 1.21 V measured




Internal Resistance

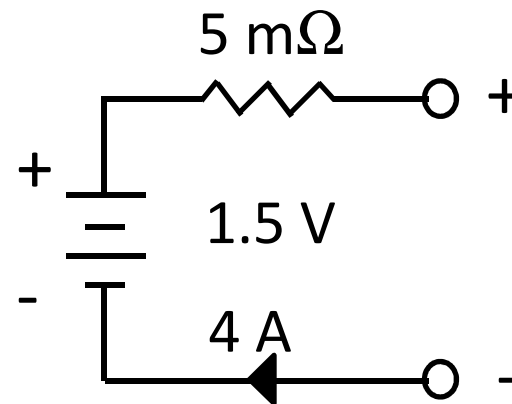- Internal resistance distinguishes real battery from ideal battery
- Would like internal resistance to be as low as possible
- Example:
 - 1.5 V nominal
 - 1.48 V measured
 - 80 mW heat loss





Internal Resistance

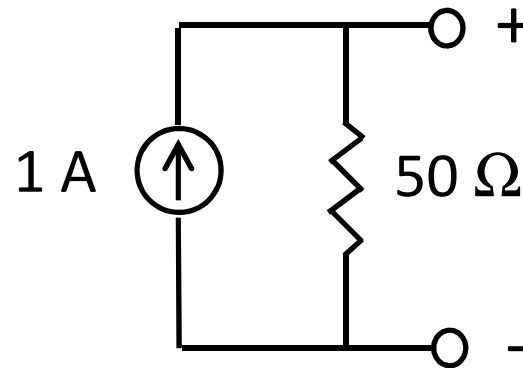- Another example:
 - Current source
 - 1.5 V load
 - 1 A nominal
 - 0.97 A measured
 - 45 mW heat loss





Voltage Sources

- Ideal voltage source:

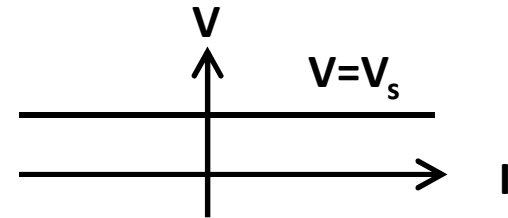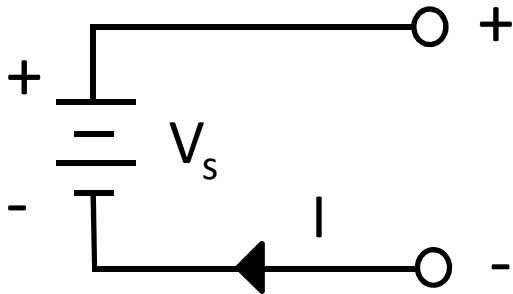



- Non-ideal voltage source:

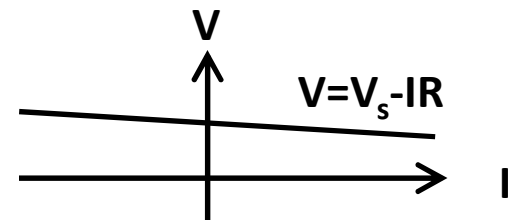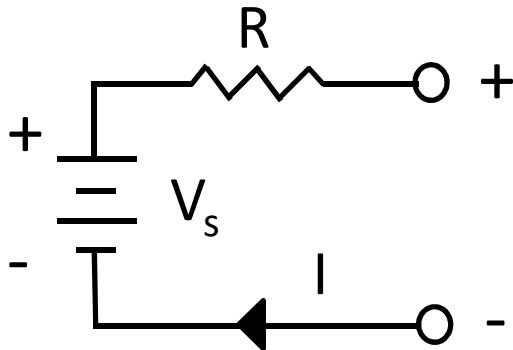



Note: R is generally small

Ideal Current Sources

- Ideal current source

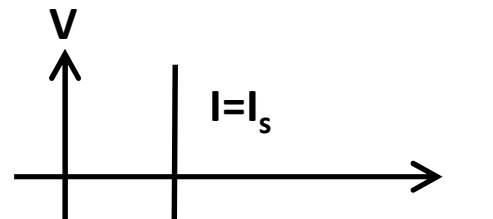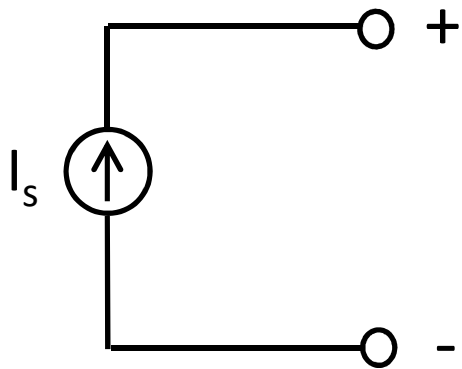

- Non-ideal current source:

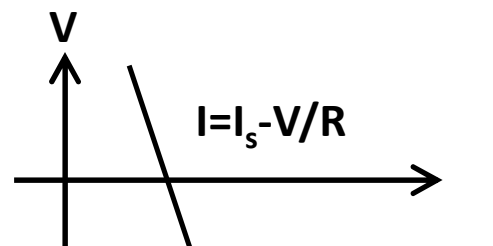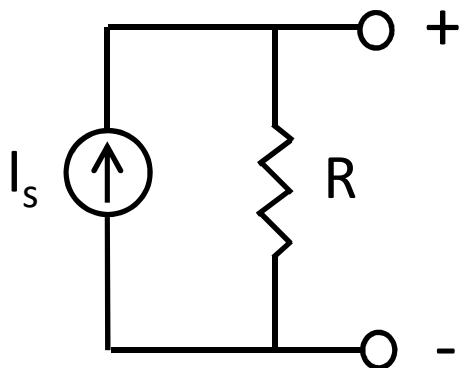

Note: R is generally large

Homework

- HW #3 solution now posted
- HW #4 due today by 4:30 pm in EE 325B
- HW #5 due Friday: DeCarlo & Lin, Chapter 2:
 - Problem 25
 - Problem 32(b)
 - Problem 35
 - Problem 41