

ECE 201, Section 3

Lecture 7

Prof. Peter Bermel

September 5, 2012

Nodal Analysis Recap

- For solving non-series-parallel circuits
- Uses KCL, $V=IR$, matrix algebra to calculate unknown voltages and currents
- Example of matrix for two unknowns:

$$\begin{bmatrix} G_1 + G_3 + G_4 & -G_3 \\ -G_3 & G_2 + G_3 + G_5 \end{bmatrix} \begin{bmatrix} V_b \\ V_c \end{bmatrix} = \begin{bmatrix} G_1 V_a \\ G_2 V_a \end{bmatrix}$$

- Solve with matrix inversion formula:

$$M^{-1} = \begin{bmatrix} a & b \\ c & d \end{bmatrix}^{-1} = \frac{1}{\det(M)} \begin{bmatrix} d & -b \\ -c & a \end{bmatrix}$$

Nodal Analysis Recap

- Using matrix inversion formula, we obtain:

$$\begin{bmatrix} V_b \\ V_c \end{bmatrix} = \frac{1}{(G_1 + G_3 + G_4)(G_2 + G_3 + G_5) - G_3^2} \begin{bmatrix} G_2 + G_3 + G_5 & G_3 \\ G_3 & G_1 + G_3 + G_4 \end{bmatrix} \begin{bmatrix} G_1 V_a \\ G_2 V_a \end{bmatrix}$$

- Introducing the shorthand notation:

$$G_{235} = G_2 + G_3 + G_5$$

$$G_{134} = G_1 + G_3 + G_4$$

- Yields the solutions:

$$V_b = \left[\frac{G_{235}G_1 + G_2G_3}{G_{134}G_{235} - G_3^2} \right] V_a$$
$$V_c = \left[\frac{G_{134}G_2 + G_1G_3}{G_{134}G_{235} - G_3^2} \right] V_a$$

Nodal Analysis: # of Variables

- Should always be able to solve problems with 2 unknowns using matrix inversion formula
- What about more than 2 unknowns?
 - Substitution/elimination methods
 - Adjoint method (calculate cofactor matrix, take transpose, divide by determinant)
 - Software techniques

Substitution Method

- Formulate N equations with N unknowns
- Rewrite 1 equation in terms of 1 unknown, then **substitute** into the other equations, and iterate

- Example:

$$\begin{aligned}(G_1 + G_3 + G_4)V_b - G_3V_c &= G_1V_a \\ -G_3V_b + (G_2 + G_3 + G_5)V_c &= G_2V_a\end{aligned}$$

- Rewrite:

$$V_c = (G_1 + G_3 + G_4)V_b/G_3 - G_1V_a/G_3$$

- Substitute:

$$\begin{aligned}-G_3V_b + (G_2 + G_3 + G_5)[(G_1 + G_3 + G_4)V_b/G_3 - G_1V_a/G_3] \\ = G_2V_a\end{aligned}$$

- Simplify:

$$[G_{235}G_{134} - G_3^2]V_b = [G_2G_3 + G_1G_{235}]V_a$$

Elimination Method

- Formulate N equations with N unknowns
- Add equations to each other to eliminate target variables
- For example, take:

$$(G_1 + G_3 + G_4)V_b - G_3V_c = G_1V_a$$

$$-G_3V_b + (G_2 + G_3 + G_5)V_c = G_2V_a$$

- Multiply each equation to eliminate V_c :

$$G_{235} [G_{134}V_b - G_3V_c = G_1V_a]$$

$$+ G_3 [-G_3V_b + G_{235}V_c = G_2V_a]$$

$$[G_{235}G_{134} - G_3^2]V_b = [G_2G_3 + G_1G_{235}]V_a$$

Free, Web-Enabled Software

- SPICE on nanoHUB:
<https://nanohub.org/tools/spice3f4>
- Falstad circuit simulator:
<http://www.falstad.com/circuit/index.html>

Current Source Example

- Using KCL and KVL:


$$I_o = I_4 + I_5$$

$$I_5 = I_2 + I_3 = I_s + I_3$$

- Using Ohm's Law:

$$I_o = G_4 V_a + G_5 V_b$$

$$G_5 V_b = I_s + G_3 (V_a - V_b)$$

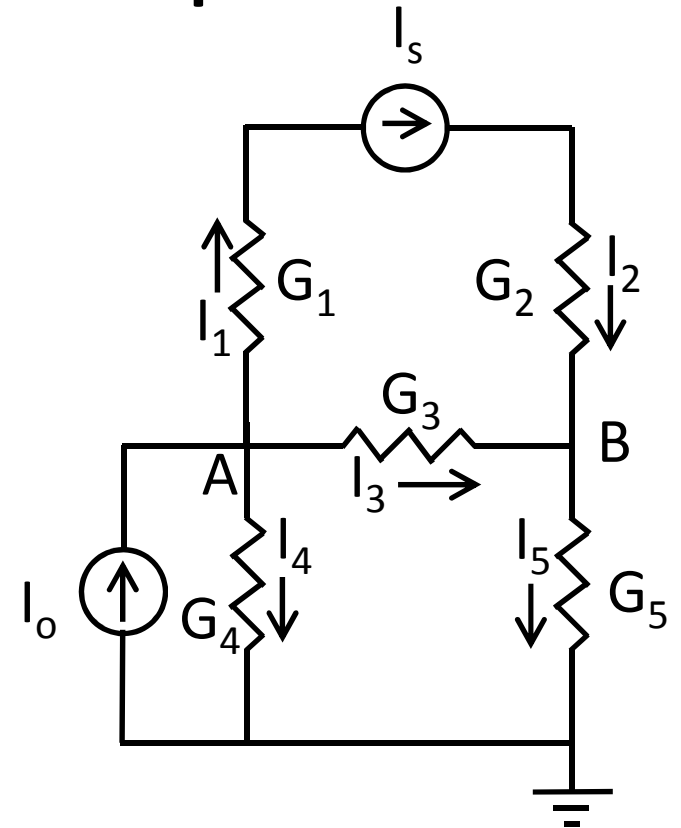

Current Source Example

- Combining & grouping terms:

$$\begin{aligned} -G_3 V_a + (G_3 + G_5) V_b &= I_s \\ G_4 V_a + G_5 V_b &= I_o \end{aligned}$$

- In matrix form:


$$\begin{bmatrix} -G_3 & G_3 + G_5 \\ G_4 & G_5 \end{bmatrix} \begin{bmatrix} V_a \\ V_b \end{bmatrix} = \begin{bmatrix} I_s \\ I_o \end{bmatrix}$$

- Solution:

$$\begin{bmatrix} V_a \\ V_b \end{bmatrix} = \frac{1}{G_3 G_5 + G_4 G_3} \begin{bmatrix} -G_5 & G_3 + G_5 \\ G_4 & G_3 \end{bmatrix} \begin{bmatrix} I_s \\ I_o \end{bmatrix}$$

- Why doesn't solution depend on G_1 or G_2 ?

Voltage vs. Source Current

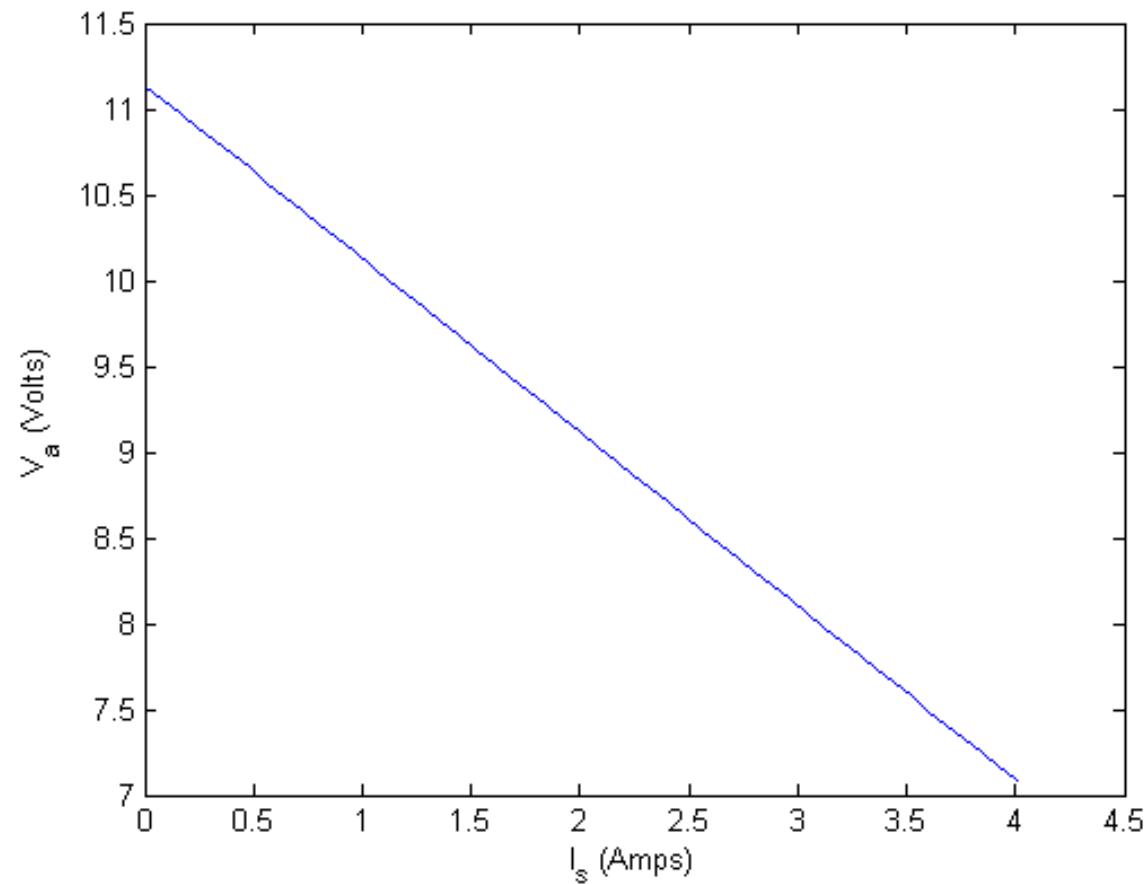

Controlled Sources

- Using KCL:

$$I_o = I_1 + I_3 + I_4$$

$$I_o = I_4 + I_5$$

$$I_1 + I_3 = I_5 = g_m(V_a - V_b)$$

- Using KVL:


$$V_a - V_b = I_1(R_1 + R_2) + R_n I_4$$

- Using Ohm's Law:

$$V_a - V_b = (I_o - I_3 - I_4)R_{12} + R_n G_4(V_a - V_c)$$

$$I_o = G_4(V_a - V_c) - G_5 V_c$$

$$g_m(V_a - V_b) = -G_5 V_c$$

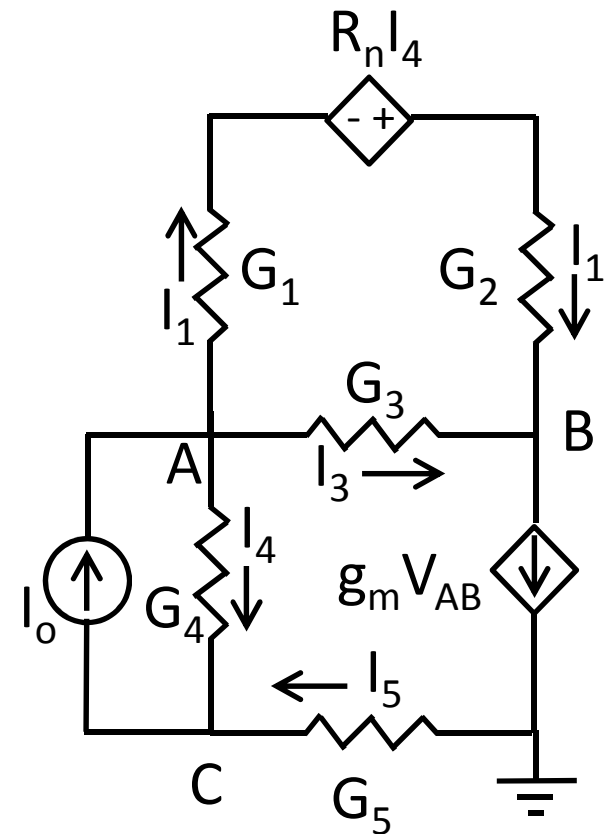

Controlled Sources

- Rearranging:

$$(G_{34}R_{12} + R_n G_4 + 1)V_a - (G_3 R_{12} + 1)V_b + (R_n - R_{12})G_4 V_c = I_o R_{12}$$


$$G_4 V_a - (G_4 + G_5)V_c = I_o$$

$$g_m V_a - g_m V_b + G_5 V_c = 0$$

- Which can be written as:

$$\begin{bmatrix} G_{34}R_{12} + R_n G_4 + 1 & -(G_3 R_{12} + 1) & (R_n - R_{12})G_4 \\ G_4 & 0 & -(G_4 + G_5) \\ g_m & -g_m & G_5 \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = \begin{bmatrix} I_o R_{12} \\ I_o \\ 0 \end{bmatrix}$$

Contour Plot of V_a

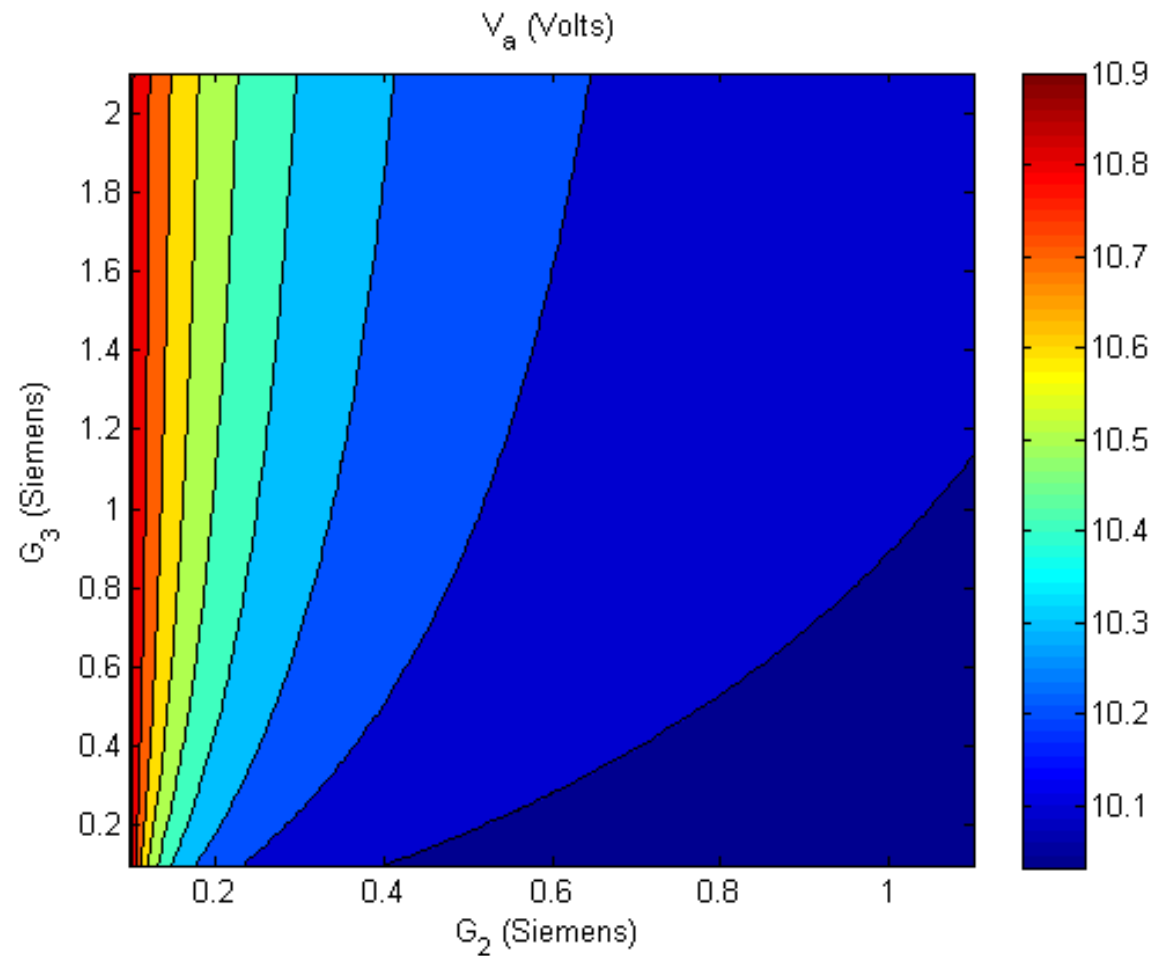

$$G = (0.5, G_2, G_3, 0.5, 0.8, 2.0, 1.0)$$

Homework

- HW #5 solution posted
- HW #6 due today by 4:30 pm in EE 325B
- HW #7 due Friday: DeCarlo & Lin, **Chapter 3**:
 - Problem 3
 - Problem 5
 - Problem 8(a),(b), and (c)