

# ECE 201, Section 3

## Lecture 9

Prof. Peter Bermel

September 10, 2012

# Exam #1: Thursday, Sep. 20

- Time: 6:30-7:30 pm
- Place: WTHR 200
- Review session: Mon., Sep. 17 from 6:30-7:30 pm (MATH 175)
- Posted 3 practice exams + solutions


# Loop Analysis

- Applying KVL around each loop:

$$R_4(I_1 + I_3) + R_2(I_1 - I_2) + R_1 I_1 = V_s$$

$$R_2(I_2 - I_1) + R_3 I_2 = V_r$$

$$R_4(I_3 + I_1) + R_5 I_3 = V_r$$

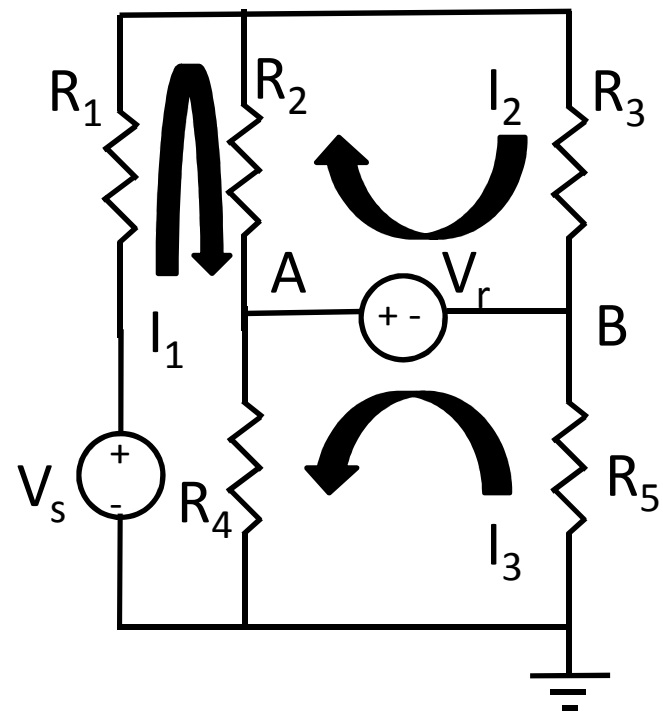


# Loop Analysis

- Rearranging as a matrix equation:

$$\begin{bmatrix} R_4 & 0 & R_4 + R_5 \\ -R_2 & R_2 + R_3 & 0 \\ R_{124} & -R_2 & R_4 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_r \\ V_r \\ V_s \end{bmatrix}$$

# MATLAB Code

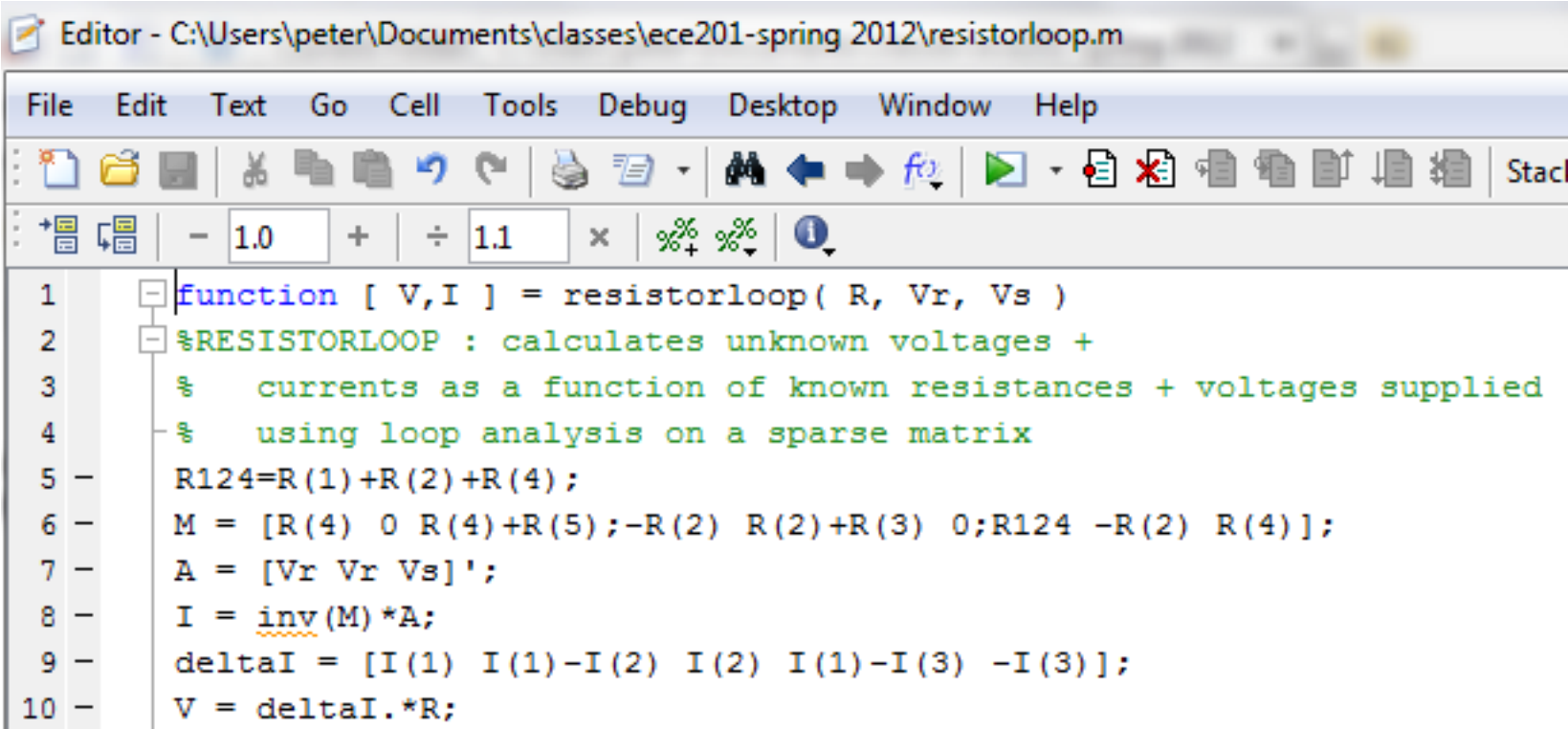

The image shows a MATLAB Editor window with the title bar "Editor - C:\Users\peter\Documents\classes\ece201-spring 2012\resistorloop.m". The window contains a menu bar (File, Edit, Text, Go, Cell, Tools, Debug, Desktop, Window, Help) and a toolbar with various icons. Below the toolbar is a numeric keypad with buttons for minus, 1.0, plus, divide, 1.1, multiply, percent, and a help icon. The main editor area displays the following MATLAB code:

```
1 function [ V,I ] = resistorloop( R, Vr, Vs )
2 %RESISTORLOOP : calculates unknown voltages +
3 %   currents as a function of known resistances + voltages supplied
4 %   using loop analysis on a sparse matrix
5 R124=R(1)+R(2)+R(4);
6 M = [R(4) 0 R(4)+R(5);-R(2) R(2)+R(3) 0;R124 -R(2) R(4)];
7 A = [Vr Vr Vs]';
8 I = inv(M)*A;
9 deltaI = [I(1) I(1)-I(2) I(2) I(1)-I(3) -I(3)];
10 V = deltaI.*R;
```

# Calling MATLAB Code

```
>> R=rand(1,5)
```

```
R =
```

```
    0.7577    0.7431    0.3922    0.6555    0.1712
```

```
>> [V,I]=resistorloop(R,4,6)
```

```
V =
```

```
    3.5881   -1.4025    2.5975    2.3932   -0.1856
```

```
I =
```

```
    4.7352
```

```
    6.6225
```

```
    1.0841
```

# Loop Analysis


- Applying KVL around each loop:

$$R_4(I_1 + I_3) + R_2(I_1 - I_2) + R_1 I_1 = V_s$$

$$R_2(I_2 - I_1) - v_1 = R_n I_1$$

$$R_4(I_3 + I_1) + R_5 I_3 = R_n I_1$$

$$I_2 = -I_s$$

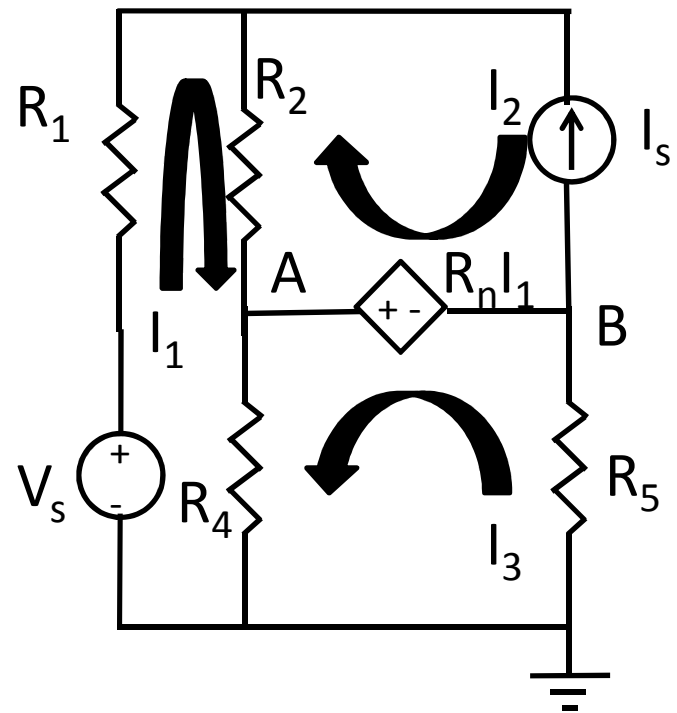


# Loop Analysis

- Combining KVL + constraints:

$$[R_1 + R_2 + R_4]I_1 + R_4I_3 = V_s - R_2I_s$$

$$(R_2 + R_n)I_1 + v_1 = -R_2I_s$$

$$(R_4 - R_n)I_1 + (R_4 + R_5)I_3 = 0$$

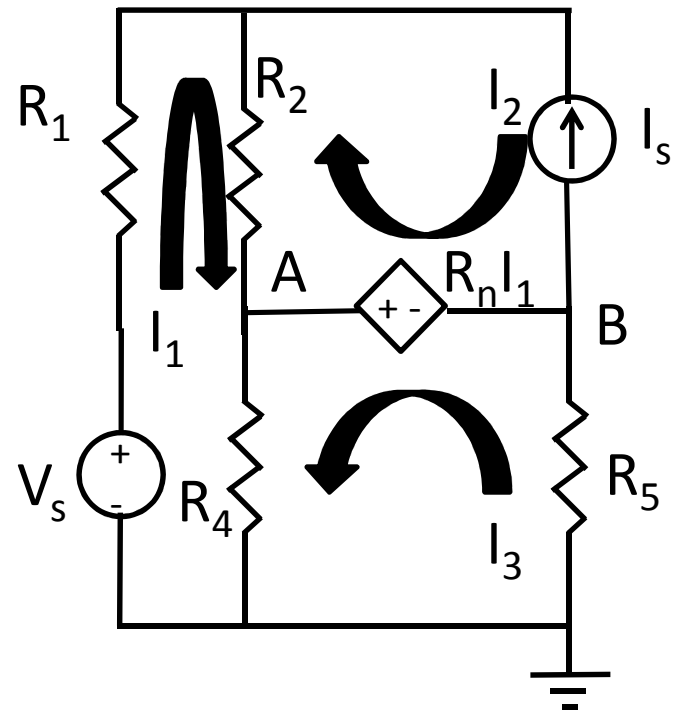



# Loop Analysis


- Rearranging as a matrix equation:

$$\begin{bmatrix} R_{124} & R_4 & 0 \\ R_2 + R_n & 0 & 1 \\ R_4 - R_n & R_4 + R_5 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_3 \\ v_1 \end{bmatrix} = \begin{bmatrix} V_s - R_2 I_s \\ -R_2 I_s \\ 0 \end{bmatrix}$$

# Loop Analysis

- Power delivered at each circuit element:
  - Resistors: can use  $P=I^2R$
  - Voltage sources: can use  $P=IV$
  - Current sources: use  $P=IV$
- Note that powers should sum to zero, due to energy conservation

# MATLAB Code

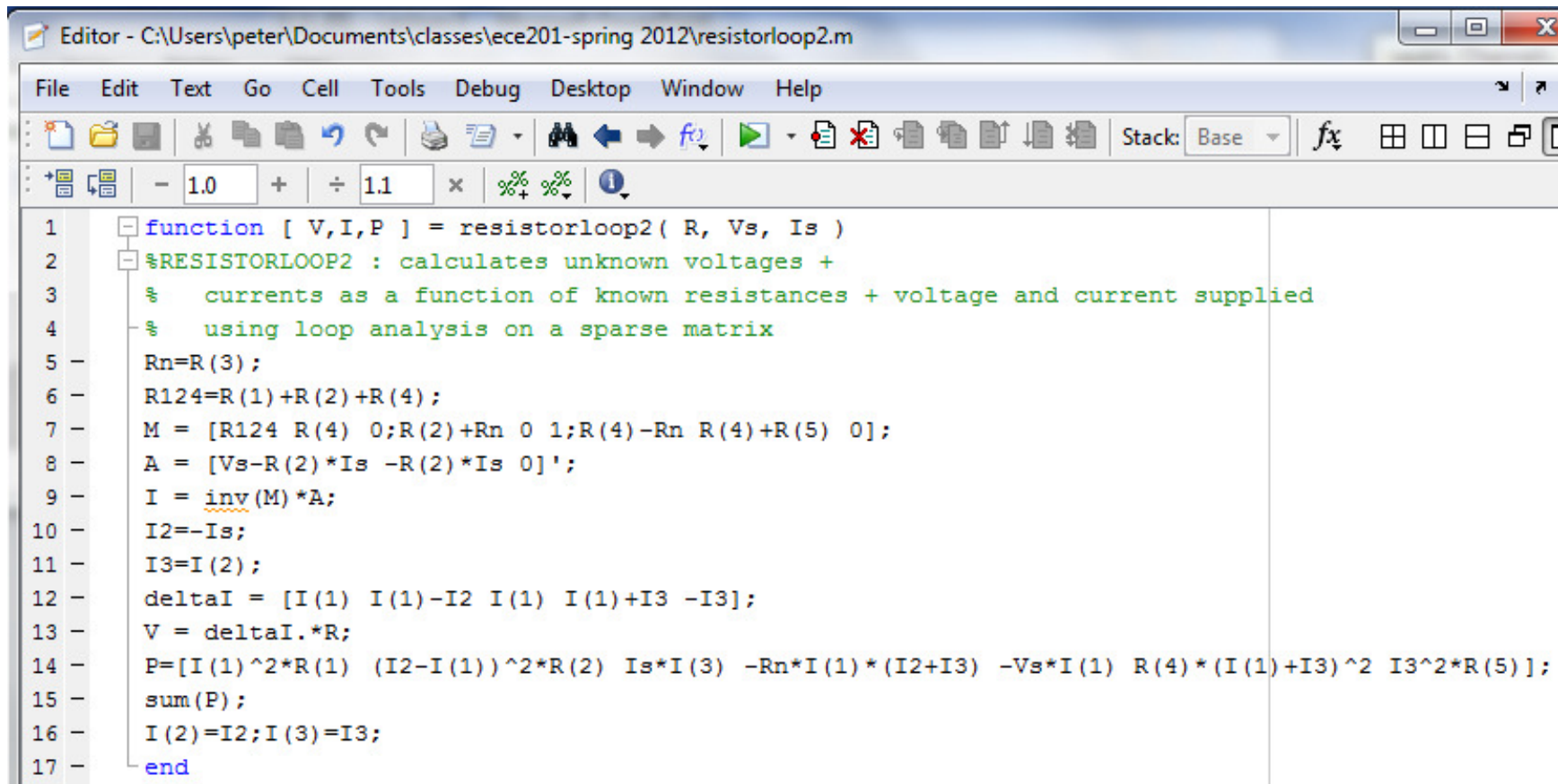A screenshot of the MATLAB Editor window. The title bar reads "Editor - C:\Users\peter\Documents\classes\ece201-spring 2012\resistorloop2.m". The menu bar includes File, Edit, Text, Go, Cell, Tools, Debug, Desktop, Window, and Help. The toolbar contains various icons for file operations, editing, and execution. Below the toolbar is a numeric keypad with values 1.0, 1.1, and mathematical operators. The main editor area displays the following MATLAB code:

```
1 function [ V,I,P ] = resistorloop2( R, Vs, Is )
2 %RESISTORLOOP2 : calculates unknown voltages +
3 %   currents as a function of known resistances + voltage and current supplied
4 %   using loop analysis on a sparse matrix
5 Rn=R(3);
6 R124=R(1)+R(2)+R(4);
7 M = [R124 R(4) 0;R(2)+Rn 0 1;R(4)-Rn R(4)+R(5) 0];
8 A = [Vs-R(2)*Is -R(2)*Is 0]';
9 I = inv(M)*A;
10 I2=-Is;
11 I3=I(2);
12 deltaI = [I(1) I(1)-I2 I(1) I(1)+I3 -I3];
13 V = deltaI.*R;
14 P=[I(1)^2*R(1) (I2-I(1))^2*R(2) Is*I(3) -Rn*I(1)*(I2+I3) -Vs*I(1) R(4)*(I(1)+I3)^2 I3^2*R(5)];
15 sum(P);
16 I(2)=I2;I(3)=I3;
17 end
```

# Calling MATLAB Code

```
>> R=10.0*rand(1,5);  
>> [V,I,P]=resistorloop2(R,10,-5)
```

V =

```
10.4154  -11.3549    6.8484   10.9395    4.0911
```

I =

```
3.0599  
5.0000  
-1.6037
```

P =

```
31.8699   22.0298  -22.5325  -23.2588  -30.5988   15.9293    6.5611
```

```
>> sum(P)
```

ans =



```
3.1974e-014
```

# Linearity Theorem



- For linear resistive circuits, output voltages and currents are a linear combination of independent sources, i.e.:

$$V_A = \sum_{k=1}^N [\alpha_k V_k + \beta_k I_k]$$
$$I_A = \sum_{k=1}^N [\alpha_k V_k + \beta_k I_k]$$



# Linearity Example: 3-Loop Circuit

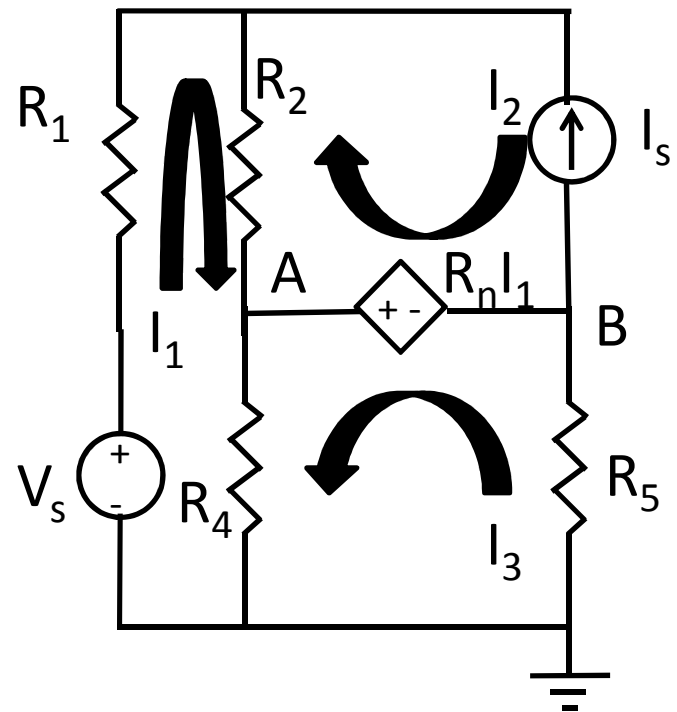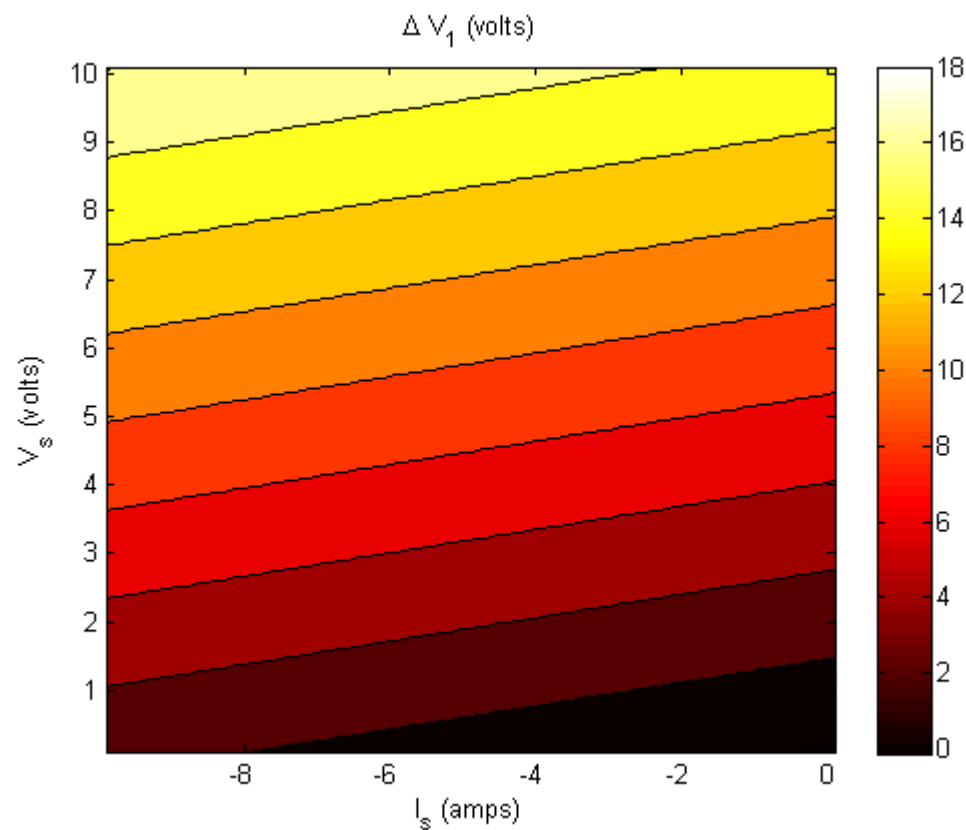

# Linearity Example: 3-Loop Circuit

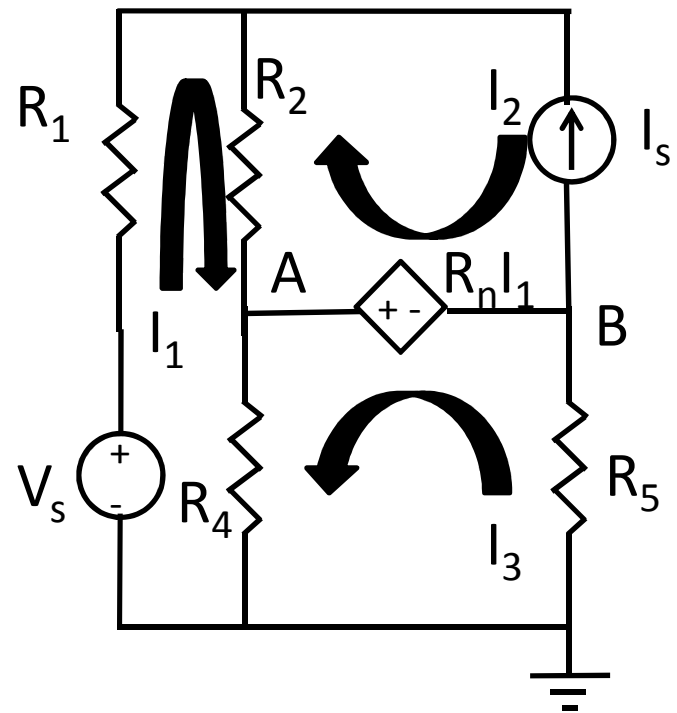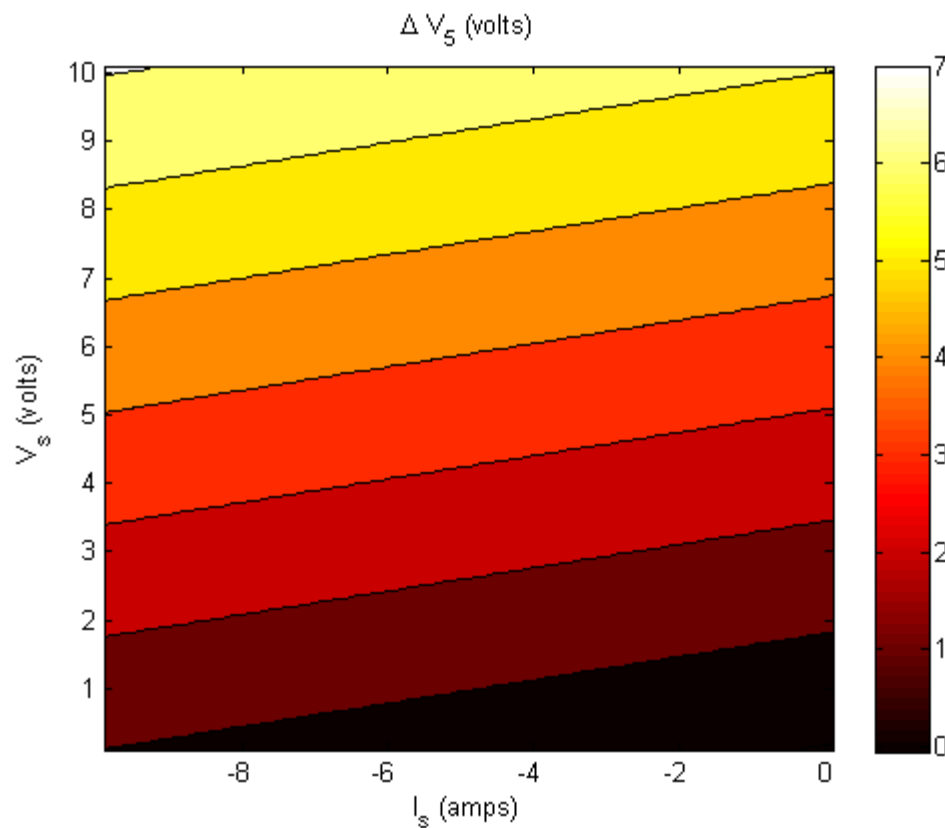

# Linearity Example: 3-Loop Circuit

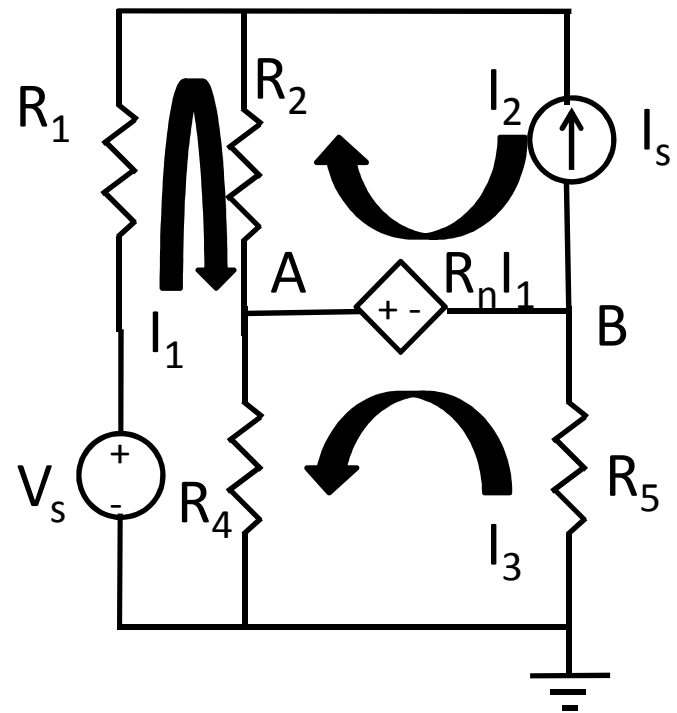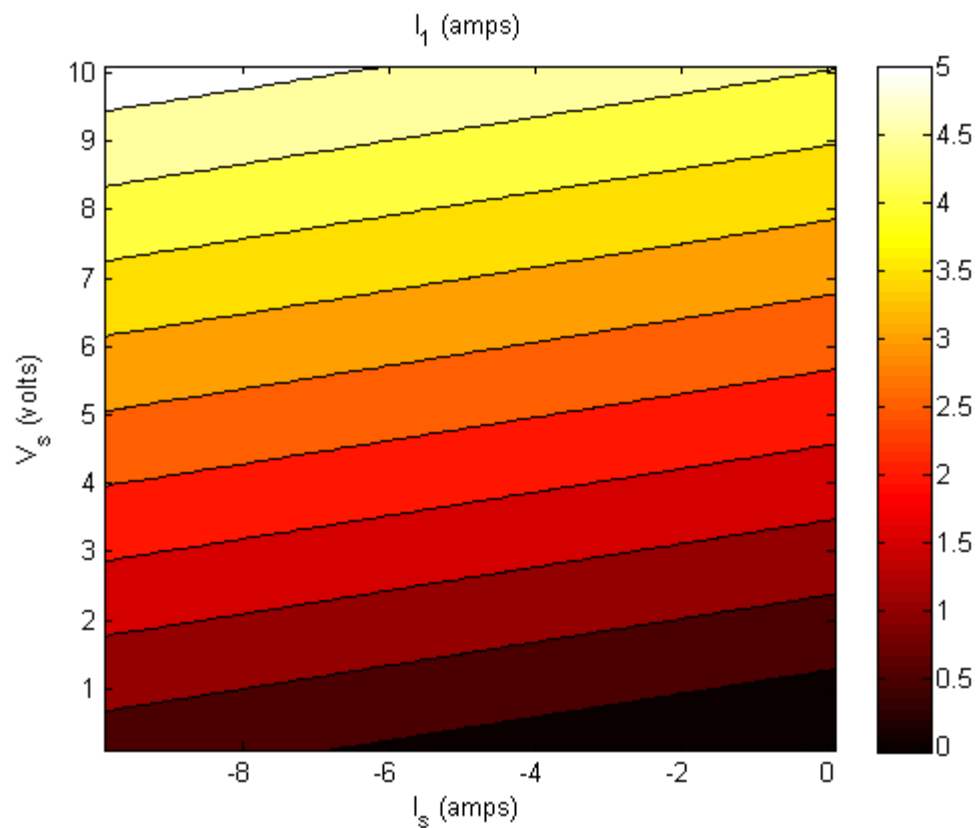



# Superposition Property

- Superposition property: total output of linear circuit is sum of contributions from each independent source
- Special case of linearity property
- Applies to current and voltage but not power (in DC circuits)

# Proportionality Property

- Proportionality property: multiplying independent source amplitude by  $\alpha$  changes corresponding output term by factor of  $\alpha$
- Again, applies to current and voltage but not power (in DC circuits)
- Will lead to some interesting tricks next time!

# Homework

- HW #8 due today by 4:30 pm in EE 325B
- HW #9 due Wednesday: DeCarlo & Lin, Chapter 3:
  - Problem 39
  - Problem 41
  - Problem 43