
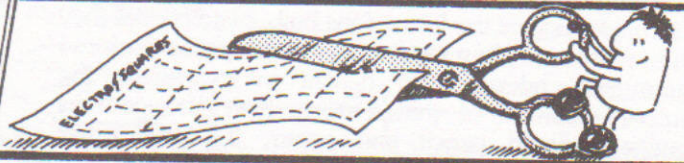


ELECTRO-SQUARES

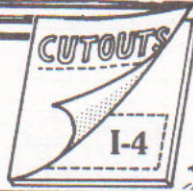
- 1** Find the paper called **ELECTRO-SQUARES**. Cut out each square along the dashed lines.




- 2** For each letter below:



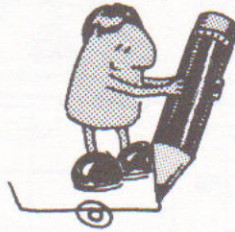Map the circuit with your **ELECTRO-SQUARES**.



Draw the circuit.

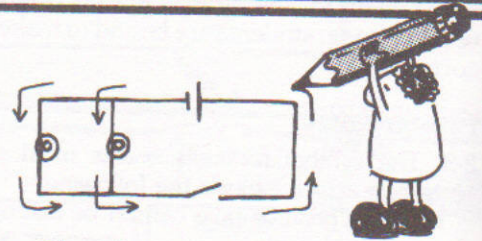

Show how electrons flow through the circuit.

- a.** 1 cell + 1 bulb + 1 switch:

Map
 Draw
 Show flow

- b.** 3 cells in series with 1 bulb + 1 switch:

Map
 Draw
 Show flow

- c.** 3 bulbs in parallel with 1 cell + 1 switch:

Map
 Draw
 Show flow

- d.** 2 cells in series + 2 bulbs in series + 1 switch:

Map
 Draw
 Show flow

- e.** 2 cells in parallel + 2 bulbs in parallel:

Map
 Draw
 Show flow

- f.** 1 bulb + 1 switch } in parallel with 1 bulb + 1 switch } 2 cells in series:

Map
 Draw
 Show flow

- g.** 1 cell }
1 bulb } in parallel:
1 switch }

Map
 Draw
 Show flow

- h.** 2 cells in opposition }
1 cell + 1 bulb } in parallel:
1 switch + 1 bulb }
1 switch + 1 bulb }

Map
 Draw
 Show flow

- 3** Paper clip your **ELECTRO-SQUARES** into one pile. You'll need to use them again.

